

ULTRA MODERN VIDEO CONTROL AT WOR-TV...N.Y.C.



### $\operatorname{\mathscr{Q}}_{\mathsf{UNNingham}\ldots\mathsf{the}}$ high mark in quality for over 33 years

As a PRODUCT of the vast engineering and manufacturing resources of the Radio Corporation of America. Cunningham tubes have consistently occupied the forefront in tube quality and performance. That is why RCA and Cunningham stand side-by-side as two great names in radio.

Cunningham tubes have enjoyed customer acceptance for over 33 years. Whether it's metal, miniature, or glass, there's a Cunningham type to meet practically every service requirement. Your Cunningham Distributor keeps complete stocks on hand to meet your immediate needs.

RCA LABORATORIES PRINCETON, N. J.

Behind every Cunningham tube is the engineering leadership





A QUALITY PRODUCT OF THE ADIO CORPORATION OF AMERICA



YOU BUILD this Transmitter Power Supply used in the basic experiments in RF and AF amplifiers, frequency



YOU SET UP trical signal" you produce). You

YOU MEASURE current. oltage (AC, DC and RF), resistance and impedance in cireuits with Electronic Multitester you build. Shows how basic transmitter circuits behave, needed to maintain sta-



-BUILD me it to determine frequency of operation, make other tests









WITHOUT COST UNDER G. I. BILL. MAIL COUPON.

### Course Is New! Different!

Mail coupon now for facts about my NEW, intensely practical course in Radio-relevision Communications. Let me send you FREE books. Read outlines of 78 les-son texts written for you by leading Comson texts written for you by reasons munications experts, edited by my practical staff. See the nine hig Kits of Parts I send that "bring to life" theory you learn. Read about the transmitter 1994 I send that "bring to life" theory you bearn. Read about the transmitter you tould and operate, about the Electronic Multitester you get. All equipment yours to keep. My BRAND NEW course in makes BOTH Theory and Practical Experience, with result-picting kits, in Rain-Television Communications. It's backed by N. R. 1.—the world's oldest and largest home study Radio school.

### Mail Coupon For Book FREE

Send today! See what my NEW rourse is like. Find out how I get you ready for a brighter future, better earnings, more security in Radio-Televison. Send coupon now in envelope or paste on penny pe NO OBLIGATION. NO SALESM NO OBLIGATION. NO SALESMAN WILL CALL! My books, sent to you FREE, tell the full story. J. E. SMITH, President, Dept. OBR. National Radio Institute, Washington 9, D. C.

### MAIL NOW-BOOK FREE

MEN STEPPED INTO GOOD JOBS. Only 19 Television Stations serve on the air 1947. Total vicers are more than 50 and experts say there will be 150 in a few months. 1900 within three years. That means thousands of seel-paid jobs for trained Operators and Technicians. Then add development of FM. Two-way Radio. Police, Marine, Avision and Micro-scave Eelay Radio. Tolink what all this means! New jobs, more jobs for beginners? Better jobs, better pay for experienced men.]

Are you a beginner who wants steady work in this growing field? My NEW course can help you get an FCC License and prepare for the job you want. Are you

Servicing Training

Also Offered by N. R. I.

MR. J. E. SMITH, President, Dept. OBR National Radio Institute, Washington 9, D. C.

Mail me FREE Catalog and Book about Radio and Tele-

Name			Age

Check if Veteran

Zone State Approved Under G. I. Bill



OLIVER READ, LIN.D., W9ETI

WM. A. STOCKLIN, B.S.

Technical Editor
H. S. RENNE, M.S.

RAY FRANK, W9JU

Contributing Editor
R. HERTZBERG, W2DJJ

Television Consultant MILTON S. KIVER

Short-Wave Editor

Editorial Assistants
I. M. CARROLL
E. V. HITZEL
P. B. HOEFER

Stoff Artist

Advertising Manager
L. L. OSTEN
Midwest Adv. Menager
JOHN A. RONAN, JR.

JOHN A. BONAN, JR.

Art Director
HERMAN R. BOLLIN



COVER PHOTO. Frank Gerufy, transmitfer engineer, and James Long, video engineer, at the studio controls of WOX-TV the New York area's newest video station (Kodachrome by Edward Ozern)

Chairman of the Board and Publisher WILLIAM B. ZIFF

President B. G. DAVIS

Secretary-Treasurer
ARTHUR T. PULLEN

Vice-Presidents

MICHAEL H. FROELICH Dir. Eastern Div.

H. J. MORGANEOTH Production Director

> H. G. STRONG Circulation Director

BRANCH OFFICES NEW YORK (1) Empire State Bldg., WI 7-0400

LOS ANGELES (14) 815 S. Mill St., Tucker 9213 Manager, WILLIAM L. PINNEY

### First in radio-television-electronics

Average Paid Circulation over 200,000

Radio Sees Tradomark Rog. U.S. Pat. Office No. 378427 € Trinstonen News Tradomark Rog. U.S. Pat. Office No. 51744 Radio & Tricvision News Tradomark Rog. U.S. Pat. Office No. 517025

### TELEVISION NEWS

### CONTENTS

### FEBRUARY, 1950

Processing Radio Transcriptions	J. Dale Healy	31
Crystal Diode Field Strength Meter	Robert C. Moses	35
Ultra-Modern WOR-TV Is 84th Television Station	Newland Smith	36
Test Equipment for Citizens Radio	Harold B. McKay	38
A Strain-Sensitive Phono Pickup	R. S. John	40
A Two-Band Piece of Wire		42
Modern Television Receivers (Part 22)	Milton S. Kiver	43
A Collapsible Speaker Cabinet	Michael Wolfe	47
Mountain Top TV City	Charles D. Perlee	48
Mac's Radio Service Shop	John T. Frye	50
Custom Video Has Built-In Booster	Clark E. Jackson	51
Electronically Controlled D.C. Load Maxim	ne G. Kaufman, W3OX7	54
3-Tube Amplifier for Variable Reluctance Pickup	Edwin W. Hill	57
A New Approach to Beam AntennasMajor C	harles E. Spitz, WIJHS	58
Build a Sweep Frequency Audio Oscillator	Glen Southworth	60
An Electronic Metronome	Albert H. Taylor	62
Instant Heating Devices	Norman L. Chalfin	64
Understanding Super-Modulation Jo	hn K. McCord. W1813	66
Receiver Servicing Without a Signal Generator	James Kauke	84

#### DEPARTMENTS

For the RecordThe Editor	8	Letters from Our Readers	102
Spot Radio News	16	AFCA News	110
Within the Industry	22	Manufacturers' Literature	114
Short-Wave K. R. Boord	56	MARS	126
What's New in Radio	79	New TV Products	132

Technical Books 151



COPYRIGHT 1950
ZIFF-DAVIS PUBLISHING COMPANY
180 North Wabash Ave., Chicago I, III.
VOLUME 43 • NUMBER 2



Subjective Company, 185 N. Wabash Ave. Chin. Se copies No. 10 Faminds \$4 did 12 Section. 84 doi: 12 Section. 84 doi: 12 Section. 10 British Systems.

RADIO & [LIAN\_SALES NEWS at published combine or the full flavor bulliagong company, 188 N. Walstah Ave. Chrimpi-1, ill. Schlerophyse Bern on the United whaters \$1.00 (12 courses arrange of her in Engage of her in Course, single course after its Mexico. South and Course \$1.00 (12 document of her in the Course of her in the Course of her address. A) commonwheat and advantage of her in the Course of her in the Course of the Course of the change 1. Ill. Entered as second class matter fields \$2.1 (144s, at the Post selber Chicago, Hillions, notice that Ad-March 2. (1971). Indeed as second class matter fields \$2.1 (144s, at the Post selber Chicago, Hillions, notice that Ad-March 2. (1971). Indeed as consideration contains the contraction of the Course of the

### Which Do You Want?



A New Car



**Happy Vacations** and Travel

**Get Your FCC Ticket** Jobs leading to \$3,000 to \$7,500 (Average Pay Reported by FCC Nationwide Survey) are opening up right now for

**FCC** Licensed

Radiomen.



How to Pass FCC COMMERCIAL RADIO OPERATOR

> License Exams

> > MONEY MAKING

FCC LICERSE

1

INFORMATION



Tells where to apply for and take PCC examina-tions, location of examining offices, scope of knowledge required, approved way to prepare for PCC examinations, positive method of checking your knowledge before taking the examinations.

Let me send you FREE the

Just fill out the coupon and mail it. I will send you, free of charge, a copy of "How to Pass FCC License Exams," plus a sample FCC-type Exam and the amazing new booklet, "Money Making FCC License Information." Edw. M. Guilford Vice President

### Add Technical Training to Your **Practical Experience & Get Your** MONEY MARING FCC LICENSE COMMERCIAL INFORMATION in a Few Short Weeks... It's EASY if you use CIRE Simplified Training

and Coaching AT HOME in SPARE TIME

Get your license easily and quickly and be ready for the jobs open to ticket holders which lead to \$3000 to \$7500 (average pay reported by FCC nation wide survey.) CIRE training is the only planned course of coaching and training that leads directly to an FCC license.

Your FCC ticket is always recognized in all radio fields as proof of your technical ability.

#### CIRE Job-Finding Service Brings Amazing Offers of Jobs!

"I am working at WRJM as transmitter engineer, and I received this position in response to one of the employment applications sent me upon completion of my course and the receiving of my Diploma. I received my ist class Radiotelephone License on March 2, 1949. I want to express my sincere appreciation to the staff of CRE."

"Have found and accepted a position at KWAD in Wadena, Minn. I am indebted to CIRE for I secured this position through the help of the CIRE Job Finding Service. I had six other offers from stations receiving my employment application and CIRE reference. I am sincerely under obligation to you."

SARPLE

FEE THE DAY

CLEVELAND INSTITUTE OF RADIO ELECTRONICS 4900 Euclid Bidg. Dask RN-14 Cleveland 3, Ohio Approved for Veteran Training under the "G.I. Bill of Rights"

#### Get This Amazing New Booklet

- 1. Tells of Thousands of Brand-New, Better Paying Radio Jobs Now Open to FCC License Holders.
- 2. Tells How We Guarantee to Train and Coach You Until You Get Your FCC License.
- 3. Tells How Our Amazing JOB-FIND-ING Service Helps You Get the Better Pay Job Our Training Entitles You to Hold.

### Send Coupon Now

CLEVELAND INSTITUTE OF RADIO ELECTRONICS Desk RN-14, 4900 Euclid Bidg., Cleveland 3, Ohio (Address to Desk No. to avoid delay)

I want to know how I can get my FCC ticket in a few short weeks by training at home in spare time. Send me your amazing new FREE booklet "Money Making FCC License Information," as well as a FREE sample FCC-type exam and FREE booklet, "Mow to Pass FCC License Examinations" (does not cover exam) for amateur License.

. Address . City

> Veterans check for enrollment information under G.I. Bill \_\_\_\_\_\_


# Good News FOR TV SERVICE MEN

"THE STANDARD BOOSTER" A new high gain TV preamplifier that assures your customers studio clear reception. This means plus profits for you by boosting your TV set sales in fringe areas. "The Standard Booster" features 2 knob control...continuous tuning, eliminates a switch from high to low channels... printed circuit trouble free operation.

"The Standard Booster" For Fringe Areas


Over 1,000,000 Standard Tuners Now In Use" Tomorrow's Market... Here Today
FOR TWO GREAT PRODUCTS
"THE STANDARD BOOSTER"
"THE STANDARD TUNER"

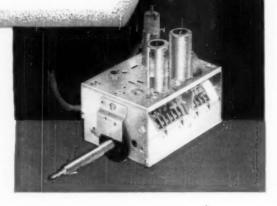"THE STANDARD TUNER" is nationally recognized as the accepted replacement tuner by the trade. Incorporated as original equipment in over a million TV sets produced by the majority of the outstanding manufacturers. This is the tuner for you. It gives higher sensitivity... quick interchanging of channel inductors ... adaptable to U.H.F. See your jobber for details.



Standard COIL PRODUCTS CO., INC.
CHICAGO LOS ANGELES BANGOR, MICHIGAN

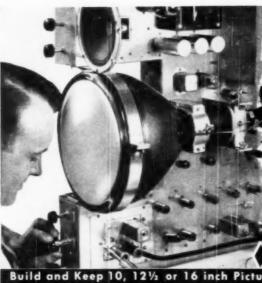Build your profits and expand your TV service business now with these two great "Standard" products. Write today for complete profit information, specifications and performance data.



Only D.T.I.

# LEFENSION

RADIO-ELECTRONICS

Laboratory Type
HOME TRAINING

HOME LABORA

You Learn by Reading

REGATIVELY CHARGED

Age

from D.T.I's MOD-

ERN LESSONS

PEATURE

Build and Keep 10, 12½ or 16 inch Picture Tube Quality TELEVISION RECEIVER as you prepare for a Profitable Future



Here is everything you need to prepare you at home for FASCINATING WORK, GOOD MONEY and a THRILLING FUTURE in one of America's most promising fields.

This includes the opportunity to build and keep the top quality Television Receiver shown above—with choice of a 10, 12½ or 16 inch picture tube that gives big, bright, sharp, steady pictures. Get the complete facts. This is an optional feature—available when you complete your training described below. See how D.T.L.'s wonderfully practical "BIG 5" method meets industry's needs. No previous experience needed. Mail coupon today!



16 Big Shipments of Parts — Plus Lessons

Work over 300 electronic experiments and projects from 16 big shipments of parts. This includes building and keeping all test equipment and radio set shown at left side of page. Modern easy-to-read lessons with handy fold-out diagrams simplifies your entire training.



D.T.I., alone, includes the modern, visual training aid... MOVIES to help you learn faster, easier at home. See electrons on the march and other fastinating "hidden action"—a remarkable home training advantage that speeds your progress.


#### EMPLOYMENT SERVICE

When you complete your training, our effective Employment Service helps you get started toward a real future in Televisian Radio Flectronics
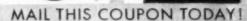
#### Modern Laboratories

If you prefer, you can get All your preparation in our new, Chicago train-

6 Tube Radio Receiver ing laboratories . . . one of the finest of its kind. Ample instructors . . . modern equipment. Write for details!



DeFOREST'S TRAINING, INC. 2533 North Ashland Avenue, Dept.RN-G-2 Chicago 14, Illinois.

Without obligation, give me complete facts showing how I may make my start in Television-Radio-Electronics.

Name

Street Apt.

City Zone State

### DeFOREST'S TRAINING, INC.

Chicago 14, Illinois A DeVry Institution





Heavy jobs and light jobs—the new 250watt Weller Soldering Gun speeds them all. Chisel-shaped RIGID-TIP provides more soldering area for faster heat transfer. New "over-and-under" terminal design gives bracing action to tip. Your Welfer Gun does delicate or heavy soldering with equal efficiency; compact and lightweight, it gets into the tightest spots.

Weller Guns actually pay for themselves in a few months. Fast 5 second heating means no time lost. Triggerswitch control means no current wasted —no need to unplug gun between jobs. Prefocused spotlight and longer length let you see the job and reach the job with ease. No other soldering tool offers so many time-and-money-saving features. Order your new 250-watt Weller Gun from your distributor today, or write for bulletin direct.

### SOLDERING GUIDE

Get your copy of "SOLDER-ING TIPS"—new fully illustrated 20 page booklet of practical soldering suggestions. Price 10c at your distributor's or order direct.



810 Packer Street, Easton, Pa.

### For the RECORD.

### WHY THE RUSH FOR COLOR TELEVISION?

SEEMS like every few hours someone calls to request information on the status of color television. "Should I wait until Spring so I can buy one with color?," "Which, in your opinion, is the best set for color television?," "I understand we are to have color soon and my present set will then be obsolete," and many similar statements.

The public, apparently impressed with news items read in its daily newspapers, is generally of the opinion that color television is "just around the corner." People forget, however, that they waited many years for our present monochrome (black and white) to emerge from "just around the corner."

Television, in its present form, has reached the stage where further improvements will be made largely at the transmitting end, rather than within the receivers. One of the greatest improvements will come from camera techniques. A majority of programs seen, especially remote pickups, suffer from the lack of picture quality, not from the equipment itself, but because of the careless use of monitors and other pickup techniques.

But these troubles will soon be ironed out and the public will then enjoy picture quality comparable to motion pictures. Then, and only then, will proper groundwork be laid for expanding into color video with its increased problems of register, tonal balance, and a host of other details that must be perfected before color will be acceptable. It took years of painstaking research and experiment to perfect what we now have and it will take an even greater period of time for color television to reach equal acceptance by the public.

It will take time to complete coax links—spreading like a giant web across the country—before the public can enjoy really worthwhile programs that originate from principal TV centers. Television set customers in remote areas soon tire of mediocre teletranscriptions and a steady diet of old movie films. They want the real thing. These folks certainly would prefer good monochrome now and would be content to wait for color.

TV technicians will have plenty of time to learn the intricacies of monochrome circuits before color emerges from its swaddling clothes, if we take time to perfect a good compatible system. That's good all around! In our opinion, color television will not reach the acceptance stage for many, many moons. The ballyhoo on color television, if continued, could even kill off that which the public now enjoys.

We are simply not ready for color! So why all the premature dreaming that we will soon be seeing stuff comparable to Technicolor movies—right in our own living room—within a few months? Who's kidding whom? Even newspapers owning and operating television stations, who should know better, treat color television as something ready for production as soon as the FCC decides on a system.

It is not that simple. We have seen several of the color television systems which are now being discussed at lengthy hearings in Washington, which in all probability will continue for some time to come, and we personally wouldn't want any one of the receivers in our own homes. It would take a staff of video experts to keep some of them operating—just for an evening.

Exaggerated claims of color television have done much to instill doubt in the minds of many potential video customers and even today many hesitate to invest in a television receiver simply because they have been led to believe that their sets would soon be obsolete. Some believe in the theory that color will be the ultimate in television. We doubt if that will ever be so. Perhaps it was a mistake on the part of the Industry to rush into the matter of color video. Wouldn't it have been better to have completely developed the huge market existing for black and white and to provide the masses with the best possible monochrome before even considering the addition or substitution of color?

Several of the systems under development do show promise. Unfortunately the better systems fall short of being compatible. It may be that a combination of systems can be devised, utilizing the best features of each, which will result in something really worth considering. Only time will tell. Television dealers and technicians can do a real service to the public by giving them the facts on the status of color television.

Yes, color television will be a reality in the future. However, let's stop telling the public "It's just around the corner," . . . . . . . O. R.

# There's Only ONE COMPLETE CATALOG that Brings You EVERYTHING IN RADIO, TELEVISION & ELECTRONICS

# IT'S YOUR FOR IT TODAY

### Get Radio's Leading Buying Guide

Here's the Buying Guide to everything in radio for everyone in radio! It's the one complete catalog, preferred in the field because it fills every TV, Radio, and Electronic supply need. It's packed with the world's largest selections of quality equipment at lowest moneysaving prices. See the latest in TV, AM and FM receivers; radio-phonos; new Sound Systems, P.A. equipment and high-fidelity sound components; recorders and accessories; full selections of newest Amateur receivers and station gear; test instruments; builders' kits; huge listings of parts, tubes, tools, books, diagrams.

ALLIED gives you every buying advantage: speedy delivery, expert personal help, lowest prices, assured satisfaction—plus the most liberal Time Payment plan in radio. Get the 1950 ALLIED Catalog—it will save you time and money. Send today for your free copy!

### ALLIED IS YOUR TELEVISION HEADQUARTERS



You keep up with TV when you depend on ALLIED!
Caunt on us far the latest releases and largest stacks
of picture tubes, campenent parts, antennas and
accessories—plus the latest in TV receivers, tunes
and kits. If it's anything in TV—we have it in stock! So
examember—for TV—it's ALLIED First!

### **ALLIED RADIO**

THE WORLD'S LARGEST RADIO SUPPLY HOUSE

Everything in Radio.TV and Electronics



### WORLD'S LARGEST STOCKS

Radio Parts Unlimited
Test Instruments—All Makes
Television & Home Radios
P. A. and Hi-Fi Equipment
Amateur Station Gear
Experimenters' Supplies

QUICK, EXPERT SERVICE

Send for Radio's Leading Buying Guide

	FREE
ALLIED RADIO CORP 833 W. Jackson Blvd.,	
Chicago 7, Illinois	-
Send FREE 196-	page 1950 ALLIED Catalog.
Name	
Address	T
City	7 6

### RADIO-ELECTRONIC Components by the Thousands!

### 6 OUTSTANDING VALUES FROM WELLS' FAMOUS STOCK

### WELLS TUBE DEPARTMENT

Brand new, standard make tubes by the thousands are ready for immediate delivery at the lowest prices in our history. Check this list for exceptional values.

### B-L Auto Radio Filterpac and Battery Eliminator

Replaces sterage battery for outo radio test bench or for soles domanstration. Supplies 10 amps D.C. tontinuous or 13 amps D.C. intermittant at 6 volts. Long life 8-L Selenium Rectifier. Brand new. 113 V. A. C. Save on our low price of only 522-50.



### 0-

### **Heavy Duty Blower**

Centrifugal type blower for cooling your transmitter or dark room. Adjustable air control. Capacity 100 CFM. 115 VAC. Price only \$12.95.

Junior Contribugal Blower with 25 CFM capacity - \$6.95.

### 5 Meter

Add an S meter to your receiver at low cos High grade 5 mil movement. 2 inch barre Only \$1.25.





#### Serve Amplifier

Beautiful 7 tube amplifier complete with 6 relays for serve system operation. Parts alone worth several times our low price. New in original packing—only \$11.95.



Perfectly built, silent running motor originally built for ART/13 tuner. 3900 RPM. 1/20 MP. Instructions for operating on 115 VAC. Makes a fine sewing machine motor. Priced very law at \$7.95.





### Circuit Breaker

25 Ampere circuit breaker protects your equipment in case of overload. Ideal for replacing household fuse boxes. Price only \$1.95.

TYPE PRICE EACH	TYPE PRICE EACH	TYPE FRICE EACH	TYPE PRICE EACH
0.x.6/7	6314(1	25D7	714AY 3.90
01.4	6157	30 .78	71511 9.79
145GT .65	6164	30 (VT-67: Walker	717A
1822 4.39	6BE6	23 (VT-13) Talker .75	
1823 7.50	0.4	14 .35	723AB 14.95
1842 5.25	60%	RK-74	721 A 3.75 723 A B 14.95 724 A 4.25
ICS/IT 68	60721 19.25	15 7 4	72431 4.26
IDMIT 95	6Ds	36	725A 9.95
1870T 1.96	6E5	37	726.8 17.45
1E70 1.99	676		736A 17.45 730A 10.95
1E7G 1.96	6G6G 30	38 .40 39 64	801
11.4		45 Spec 50	801 A
			5.25
1N5GT .75		ALLESS STREET	504 9.95
1N21 (Crystal Diads) .65	6J3GT	56 65	NO4 9.95 NOS 5.95
IN21A  Crystal Dodo: .95	6.56	70L7 1.05	807 1.25
1N21B Crystal Dode .95	6J7GT	72 1.75	NON 1.65
INE2 Crystal Diode .80	6,5×61	RKR-73 1.25	811 2.35
1N21 Crystal Dodg: .80	6K8GT	76	817 7.85
15/23A Crystal Diode: .85	61.7	77 \$0.55	814 3.75
1N27 (Crystal Drode) .85	6N7	VR-78	*15 2.89
1N24 Crystal Diode) .85	6R7G		579
	65.37 86.0E		
	68A7 \$0.65 68C7GT	FG-81A 3.95	
184 1294	6815 65	83V	830B 3.95 834 5.76
	6573		
	DOLLY AG	VIC-90	
2A3 1.05 2A785	60 17 CT		
	68 TOT 60 68 KTOT 60	10087 6-16	S41
2822 GL55s 3.78	68K7GT	FG-105 9.75 VR-105 .85	
2022 7193	@4.7GT	VR-105	
2026 .35		1 (-11)-5	
	68Q7GT	1168 1.20	861
A CANAL COLUMN NAME OF THE PARTY OF THE PART	20.57	11723	864
20.34	address.	VT-127 British 35 VT-127-A Triode 2.95	865 2.55
2J21A		VT-127-A Trade 2.85	1.30
	6V6GT	/ E-150	19.95
	93.90	VT-154 14.95	Smith 27.25
	7-7-11 Ballast 35	FG-172 19.75	1714 2.45
	784	200B 1.45	674 1.95
	7.67	205R 1.45 211 VT4C .60 215A 1.75	1.95
	7816		Six Photo Lube 1.00
	7C4/1203A	221.5 2.10	954
2334 13.85	71.6	231D 1.20	955
2.16× 12.86	787	268A 2.98	155 .50
	7117	304 1 11 5.73	957 .45
	7K7	304TL 1.75	9.50 .56
	71.7	307 A 4.29	591 NE-16
		1154	1005
	707	150H \$ 2.55	1784
	10 .45	354C 14.95	1201
3824 1.75 38Pt 3.75	10T1 Ballast	3714	1201A 704 1.05
	10Y		1616 1.25
3734 347	12A6 25 12A6/TT 25		1619
Account to the second second second	12A9/TT	1914 4.65	1624 1.25
38.29 4.95	12AH767 1.10	3954 4.96	1635
295	1208 50	MX408U	10.20
	12F3GT		1829
			1930 3.95
20177 2.35	121501	440.4	[16]8
10590	12.17171	450TH 17.95	1641 RK-6075
RFL-5 14.95 3.87 3.95			2.51
REL-5	12×17 .70		7197
3.427 3.95	175417 65	530 9.95	9011 2.25
3873	125117	531 12.95	witt 1.25
5814 3.95	128K7	532A/1B32 3.55	WICH 3.25
MT1 1.75 Mill 24.78	1751.71.77		8025 6.75
MRT 24.75	139437111	KT-610 7.45	
3.25		KU-610 7.45 HY-615 1.05	
5/1P1 4.95	12X+25-2-40-p.	700h 7.85	70.012
	Tongar 1.11 2.10	7.95	9000
13.45			9304
5/21 13.45 5/29 13.45	13-4 Hatlatt	700E1 7.95 702A 2.95	5006
	1436	703A 3.85	3x111A
0-4	15R 1.20	704A 1,75	111 446
6-7		7054 2.69	NEON BULBS
1113	TADA Ballast	705A 2.65 707A 17.50	NE-11 50.24
646	10%24 1.73	707B 19.50	
6.537	24A	1010	NE-16
144.7 .90	25.2901	704A \$ 4.95	NE-20
53.K5 .80	26 .65		NE-21
6.8166	27 .50	713A 1.55	NE-45

Distributors: Our standard distributor arrangement applies on these items.

### JUST OUT! CATALOG H500

Manufacturers, Distributors and Amateurs write for the brand new Wells Electronic Catalog H300, Full of tremendous values in highest quality components.



Order directly from this ad or through your local Parts Jobber.

320 N. LA SALLE ST., DEPT. R - 2, CHICAGO 10, ILL.



You receive complete standard equipment, including latest type High-Mu Tubes, for building various experi-mental and test units. You progress step by step until you build a com-plete Superheterodyne Receiver. It is yours to use and keep.



#### YOU RECEIVE THIS PROFESSIONAL MULTITESTER!

You will use this professional instrument to locate trouble or make delicate adjustments—at home—on service calls. You will be proud to own this valuable equipment. Complete with test leads.



SIGNAL GENERATOR You construct

Generator shown here, demon-rating Transitron strating

principles You in both and A.F. stages. You strangative type oscillators

### AUDIO OSCILLATOR:

An electronic device, which produces audio-

frequency sig-nals for modu-lating R.F. (radio frequency) carrier waves, testing A.F. (audio frequency) amplifiers, speakers, etc.



RECEIVER

Youbuild several T.R.F. Reof which, a 4-tube set, is shown

here. You learn construction, alignment, make receiver tests, and do trouble shooting.

### Get RADIO, TELEVISION and ELECTRONICS Master ALL Phases

Get Complete Training. You Receive and Keep All Tubes. Equipment, Parts and Lessons. No Extra Charges.

### GOOD PAY and Unlimited Opportunities in JOBS LIKE THESE:

Business of Your Own. Radio Manufac-Sales, Service. Broadcasting ing Television Manufacturing Telecasting. Sales, Service. Laboratories: Installa-tion, Maintenance of Electronic Equip-ment, Electrolysis, Call Systems, Garages, Auto Radio Sales, Service. Sound Systems and Telephone Companies; Oil Well rilling Companies; Engineering Theatre Sound Systems. Police and Drilling

> And scores of other good jobs in many related fields

### YOU CONDUCT MANY **EXPERIMENTS LIKE THESE!**

Checking action of condensers Experiments with AF and RF amplifiers Experiments with resonance Producing beat frequencies Calibrating oscillators

Experiments with diode, grid-bias, grid-leak and infinite impedance detectors Practical experience in receiver trouble

Application of visual tester in checking parts and circuits Experiments with audio oscillators

Advanced trouble-shooting and many, many others

### Complete Training by Practical Resident Trade School, Est. 1905

The same highly trained faculty, instruction materials and methods used here in our large, modern resident school, are adapted to your training in your own home. Shop Method Home Training has been proved by hundreds successful graduates

Both Resident and Home Study Courses Offered

You receive special labora-

tory experi-ment lessons

how to build

with your own hands various

experimental

units such as those shown at

left, and how

many tests.

to show yo

You will find all lessons easy to understand because they are illustrated throughout with clear diagrams and throughout with clear diagrams and step-by-step examples that you work out yourself. Every piece of the eqiup-ment and complete lesson material we send you is yours to keep and enjoy. including the multitester, experimental equipment, all parts of the Superheterodyne, tube manual, radio dictionary, and complete, modern Television texts. All parts are standard equipment.

### Shop Method Home Training . . . Earn While You Learn

With our practical resident Shop With our practical resident Shop Method Home Training, you study in your spare time. You receive Spare Time Work Lessons, which show you how to earn while you learn. Service neighbors' radios and TV receivers, appliance, etc. for extra movers and expliances, etc., for extra money and ex-perience. Many National students pay all or part of their training with spare

### DON'T DELAY! The Radio-Television Industry needs trained men NOW!

APPROVED VETERANS! Check causen below? For quick ection, mail coupon today and we'll rush you full information.



### NATIONAL SCHOOLS YOU LEARN BY DOING

										-							
L	0	5	At	40	G E	L	ES	3	7.	CAL	.IF		ES	Т.	15	205	ı
П	Г	П	ME	١.	ā	П	IT	N	10	w		1	-	AI	1	C	4

FIND OUT NOW MAIL	COUPON TODAY
National Schools, Dept. RN-2 4000 South Figueroa Street Los Angeles 37, California	Mail in envelope or paste on penny postal.
Send me your FREE book "Your the sample lesson of your course, man will call on me.	Future in Radio" and I understand no sales-
NAME	5.0 P

HAME	AGE	
DORESS		
TTY	ZONE STATE	
	Check here if Veteran of World War II	

February, 1956

### **Centralab Reports to**



### Service Engineers!

A successful serviceman spoke recently of a plan he uses to get each new year off to a fresh, profitable start. Here are some of the questions he asks himself. "1) Do the replacement parts I use give my customers trouble-free service? 2) Are these parts designed to help me do a good job quickly? 3) Are they packaged to save shelf space... to make accurate selection easy? 4) Am I getting the kind of service I want from my distributor?" If you can answer "Yes" to all these questions, it's very likely you use quality Centralab parts, too. If you can't, we're confident you'll find it profitable to ask your nearest Centralab distributor for all the facts. Call him today!




### Ask Your Distributor for These CRL Parts



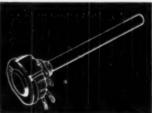
### TRIMMERS

CERAMIC TRIMMERS for padder application in RF and HF circuits. These trimmers are noted for their great mechanical strength and electrical stability; low power factor. Hold circuit drift to a minimum. Truly an indispensable "must," Ideal for amateur, experimental and industrial use.


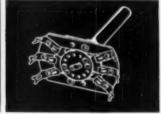
#### CONTROLS

MODEL "M" for voltage-divider, antenna shunt and "C" bias control, tone control, AF, grid control. MODEL "1" for all miniature applications; rated at 1'10 watt, actually smaller than a dime. MODEL "R", wire wound, for voltage divider, antenna shunt, "C" bias, AF grid or tone control circuits.



#### **SWITCHES**

ROTARY for band change, meter, intercom circuits; made in ceramic and phenolic models ROTARY SPRING RETURN for meter selection, intercom, phono-radio applications. MEDIUM DUTY for band changing in low power exciter-transmitters and receivers. LEVER ACTION for intercom, speaker, microphone and other applications.

### NEW G-E Gible-Play CARTRIDGE PLAYS ALL 3 SPEEDS



### Costs 25% less than Pickups it Replaces

A new General Electric "Triple Play" Cartridge that tracks any commercial record is now available to manufacturers, distributors, and dealers.

Simplicity is the key feature of this notable electronic advancement. Once installed in a tone arm, the cartridge will play all types of popular narrow groove and standard groove records without replacement or even a change in position?

#### ONLY ONE PRESSURE

The new cartridge retains the unsurpassed frequency response characteristics of the famous G-E Variable Reluctance unit and in addition, tracks the three types of records at 6 to 8 grams. Thus the pressure is constant regardless of the stylus you're using. The special design of the "Triple Play" permits precise adjustment of tone arm pressure. Weight changing and pressure compromise problems are eliminated. High compliance and low moving mass reduce record wear to a minimum.

#### TWO STYLI IN ONE CARTRIDGE

A single twist of a built-in knob turns either end of a dual stylus to playing position, A I-mil stylus, mounted at one end, plays 33½ and 45 rpm records, and a 3-mil stylus, at the opposite end, tracks standard 78 rpm records.

#### MANUFACTURERS NOTE LOW COST

Although it plays records that formerly required the use of two cartridges, the price of the "Triple Play" is 25% less than the price of two individual cartridges. It is adaptable to many types of tone arms and its use as an initial component will effectively reduce set manufacturing costs.

#### UNAFFECTED BY TEMPERATURE

The G-E "Triple Play" is unaffected by normal climatic changes in humidity and extreme variations in temperature. Needle talk and needle seratch are reduced to a minimum. Record reproduction—as always with G-E Cartridges—is superb. Mail coupon below for complete information.

You can put	your o	onfidence :	in_
GENERAL	<b>%</b>	ELECT	RIC

General Electric Company, Parts Section 920 Electronics Park, Syracuse, New York Send me full particulars on the new G-E "Triple Play" Carl	tridge.
NAME	
ADDRESS.	
CITYSTATE	

### Television Industry Adopts Another Rauland "First"!




1 The Rauland-developed aluminized tube—giving the most brilliant picture in Television.

2 The light-weight 12" metal tube – still available only from Rauland. And now...



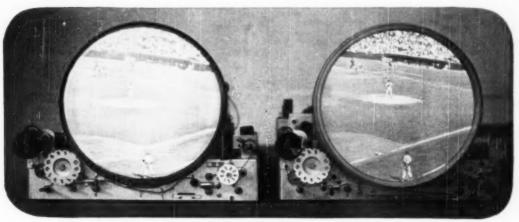THE SENSATIONAL NEW RAULAND LUXIDE SCREEN WITH ITS VISIBLY BETTER CONTRAST AND CLARITY



Luxide Screen (right) shows how improved contrast and clarity under high ambient light eliminates "washing out." (Standard tube at left.)

No single improvement in Television has won such quick and enthusiastic public acceptance as the Rauland Luxide Screen (black) picture tube—pioneered by Rauland from its conception to its present universal acceptance.

Rauland—first manufacturer of tubes of this type—received its initial production quantity of Luxide tube faces in mid-June, 1949. Sets featuring these new tubes were announced to the public in September. The public received them with such enthusiasm that the Television industry, almost without exception has already adopted this Raulanddeveloped idea and now offers it under a variety of names. The Rauland Luxide Screen improves picture quality by greatly reducing two former troubles—first, reflection of ambient light and second, halation within the tube face. The results to the viewer are a great reduction in apparent "blurring" and a much improved contrast and clarity, especially in lighted rooms. The improvement is so impressive that it has been given considerable editorial publicity.

Rauland is glad to have made another important contribution to the Television industry and the Television viewing public. The headline-making Luxide Screen is an additional example of Rauland's "PerfectionThrough Research,"

### THE RAULAND CORPORATION



Perfection Through Research



# For YOU!



### New Booklet to BUILD BETTER SERVICE BUSINESS

- Gives customers a new appreciation of your service facilities
- Helps you avoid "cutthroat" price competition

"Your Money's Worth in Good Radio and Television Service' the title of this new 16-page booklet now made available by the makers of Sprague Capacitors and Koolohm Resistors for distribution to your service customers and prospects under your own name!

Profusely illustrated, finely lithographed in two colors, the booklet will help you win customers. justify fair service prices and meet 'cut throat" competition that is springing up on all sides. It tells set owners about the complexities of today's radio and television equipment and about the extensive service facilities needed to keep receivers in first class working order.

In short, it is a book designed to win confidence for you by showing customers how complicated the work really is and by proving

to them exactly how and why good service work commands a fair price.



Sprague	Products	Company
	hall Stree	
Month A.	dame Ma	

City, Zone, State.

rush free sample of the new booklet Money's Worth in Good Radio and Tele-Service" and tell me how I can obtain anal copies for distribution to my service

	-
Address	_

from SPRAGUE Spot Radio News

Presenting latest information on the Radio Industry.

### By RADIO & TELEVISION NEWS! WASHINGTON EDITOR

COLOR TV. probably the most controversial subject since the KDKA days of broadcasting and certainly the seething topic of '49, ripped into the new year with quite a banner assignment direct from the seven men who are judging the future of green, red, and blue in video. The assignment, a field test, and all three who have color systems, RCA, CBS and CTI, were involved.

Colorcasting for a thirty-day period was ordered by the Commissioners to a representative assortment of receivers distributed among . . . "technical and non-technical persons who are not connected with the development of the system." The request, issued in the closing hours of the comparison tests, created quite a furore, since a representative assortment of receivers was just not available and only perhaps a wartime-type emergency production plan might, it was believed, produce the sets. And whatever models could be produced would be on a very limited basis, was the general consensus. The unfortunate interpretation of the test ruling by the general press, cited as a widescale public check of color TV, added to the general discomfort of everyone and brought sleepless nights to many a plant man who wondered just how they could race out all the sets required and at a sensible price. Many of the production experts agreed that the receivers would, in the main, be handmade types and certainly quite costly. Commenting on the latter point, a representative of one manufacturer predicted that the cost of about one hundred models which they expected to produce, would be in the neighborhood of a quarter of a million dollars. This spokesman declared that the sets would not be sold, but loaned out to a group of viewers.

As this column was being written, manufacturers were processing the test sets and shipping to locations which should produce the information sought by the FCC. Data that the Commission hoped to collect as a result of the test were expected to cover resolution or definition, brightness, contrast and flicker, registration, color fidelity and spurious images. Also to be explored during the tests were the desired-to-undesired signal ratios in a variety of combinations:

monochrome to color, color on color receiver to monochrome, color on color set to color, color on black and white receiver to monochrome and color in the black and white model to color. There were also to be reviewed signal-to-interference ratios. This study was expected to include tests where the undesired signals are continuous waves other than TV signals, such as oscillator radiation and diathermy interference. The FCC also asked that the tests should include representative carrier differences such as result from the use of standard intermediate frequencies, with particular attention being paid to critical carrier frequency differences. Results from susceptibility to various types of impulse and random noise were also to be reported, with emphasis on the troubles caused by auto ignition, and industrial and home-type electrical equipment.


Four classifications of receivers were described by the FCC as being representative for the tests: Black and white models, adapted to provide monochrome reception from color transmitters; converted or adapted receivers to provide color reception: new monochrome models capable of picking up black and white signals from colorcasts; and color receivers specially built for all color reception.


Observers have been asked to select a viewing distance, within four to twelve times the picture height, when the normal picture is free from interference, and base their reports on their reaction to fixed or variable viewing distances. Information on highlight brightness and contrast required in the room are also being compiled for the Commission, with specific data on the room lighting used during the tests. The FCC suggested that values of room illumination selected should be those representative of the lighting required by one or more persons when reading a newspaper

Not only have the present bands been selected for study, but the higher 470 to 890 region, too, the FCC hoping to be able to correlate the results on both of these bands for allocation purposes. Transmitter manufacturers are being asked to disclose powers available, frequency stability of visual and aural carriers, particularly
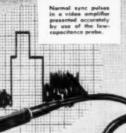
### Used by leading television manufacturers





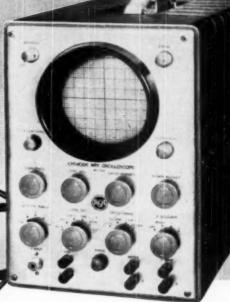

NOW - at \$249.50

### . . . the RCA WO-58A Television Oscilloscope has no equal

Unquestionably the finest instrument of its type, the WO-58A is a splendid investment for any service shop. Expressly designed for observation of voltages in TV receivers, this oscilloscope affords accurate presentation of sync pulses, deflection waveforms, and composite video signals. Defective waveforms can be traced step-by-step to their sources.

Peak-to-peak voltages of TV-receiver waveforms can be read at all times during operation. The frequency-compensated vertical range control is graduated in five voltage steps of 3-to-1 ratio which, together with a built-in calibrating voltage source, facilitates voltage measurements over any extended range. A crystal probe is supplied which can be connected to the kinescope socket of the receiver under test. When so used, it presents the same capacitance as the kinescope grid and, therefore, provides faithful reproduction of video-amplifier response curves.

The vertical amplifier of the WO-58A has a useful range from 1 cycle to 4 megacycles. Its characteristics of tilt, overshoot, and rise time are excellent. As a result of its unusual transient-response performance, the WO-58A provides accurate traces of sync pulses and other steep wave fronts. Supplied complete with crystal probe, direct probe, and low-capacitance probe. See your RCA Test Equipment Distributor today for full details.

AVAILABLE FROM YOUR RCA TEST EQUIPMENT DISTRIBUTOR



RADIO CORPORATION of AMERICA

TEST EQUIPMENT

HARRISON. N. J.



Here is the professional tape recorder selected by over 2400 critical users—radio stations, schools, recording studies and professionals. Portable dual coording studies and professionals. Portable dual coordinations. Frequency response 2.2 th 50 to 15,000 cps with less than 2°c harmonic distortion. Amplifier has low impedance make input with gain control, also high impedance input for radio timer, etc., Monitor Speaker with volume control. 3°c illuminated VU Meter. 10 watts power output with provision for external speaker, also 600 ohm line output terminal. Three position susted selects Record, and the selects of the provision for the used a public which the position such the used a public with the provision for the provis

96-205, PT6-JA Magnecorder, CASH PRICE

\$499.50

96-266 PTG-JAH Magnecorder with high speed forward CASH PRICE \$513.50

All other Magnecord units available from ALLIED on easy payments.

### ALLIED RADIO

	Jackson 7, Illin		Dept. 1-R-C	).	
Enter	my ord	ler for	Magnecor	der Mode	1
Dos	en Pay	ment e	nclosed	5.	
□ Sen	l comp	lete M	agnecorde	r literatus	10.
Name					
Addre	Miller.				
City			Zone	State	

the relative stability as it affects the intercarrier type receivers. Receiver makers were also involved in the higher band quiz, they were being asked to disclose the selectivity, sensitivity, oscillator stability, oscillator radiation and image and other spurious response characteristics of their models designed for the high channels.

The results of these tests are expected to become available at the second comparative test session, scheduled to begin just about the time this issue goes into the mailbag.

The first comparison studies, which apparently prompted the sensational decision to hold field tests, resulted in a barrage of explosive comments on the merits of the systems displayed.

An official spokesman for RCA declared that the images on their receivers were . . . "far brighter and truer in color fidelity than in earlier tests. Operation was stable and com-pletely free of flicker."

Dr. C. B. Jolliffe, executive vicepresident in charge of RCA Labs, said: "All proponents of the art should be impressed by this demonstration. . . . Experience has taught us that the whirling mechanical disk has no place in home television."

The Columbia camp was far from quiet with opinions. Said Adrian Murphy, CBS vice-prexy: "The color fidelity of the CBS system once again has been proved way out in front. The colors in the CBS picture were highly faithful to the original subject matter and were stable "

The enthusiasm for the color results was not shared by Dr. Allen B. Du-Mont who declared that neither system was adequate. In one, he said, the color changed every minute, and in the other the color fidelity was poor.

To many witnesses at the tests, the RCA system appeared to be more stable, while the CBS method afforded a more faithful picture. The black and white pictures from the standard monochrome set also appeared to many to have greater definition than black and white results on the color

The transmission procedures employed at the tests were unique in many ways. For instance, the studios of WNBW, the NBC station in the Wardman-Park Hotel, originated programs for feeding to the transmitters of not only WNBW, but WOIC the CBS station, and WTTG the DuMont setup. During the demonstrations RCA displayed transmission over a coax cable, the signal being fed into an eight-mile loop of cable

WASHINGTON lost its hold on the color wrangle for a few days, prior to the comparison test session, the scene shifting to London and BBC, where it had been reported color was in the offing.

The report stemmed from the trip Dr. Peter Goldmark had made to London at the invitation of the British Institute of Electrical Engineers to talk about and demonstrate his color

system, According to CBS representatives, a system paralleling Goldmark's setup was to be built for the BBC. with complete studio facilities being developed to accommodate colorcasting activities.

When informed of the report on BBC color work. Sir Noel Ashbridge, director of technical services for the British system, declared that . . . "no definite arrangements have been made for specific tests nor is any practical development in the immediate future envisaged." Sir Noel explained that "the only work in color televi ion by the BBC consists purely of research

Dr. Goldmark, commenting on the experimentation activities, said that he welcomed . "any experimentahe welcomed . . "any experimenta-tion by the BBC . . . and we are quite certain that its experiments with other systems in addition to ours will demonstrate the superiority of the CBS method."

experiments."

TV surrendered its headline spot on two occasions, during the close of '49. to two other substantial users of channels, the petroleum and taxicab industries.

Commissioner E. M. Webster provided the report on petroleum and radio in a talk before the Division of Transportation of the American Petroleum Institute during its annual meeting in Chicago. Reviewing the use of the airlanes by the oil drillers, the Commissioner described how radio was used by geophysical crews in connection with seismic, gravity meter. and magnetometer surveys, as well as by other divisions of the oil wellers covering such activities as off-shore operations in the Gulf of Mexico, communications during drilling and well operations, control and safety activities involved during the construction and operation of refineries, and vital contacts in the operation of natural gas, crude, and products pipe lines.

"In the pipe line field," said the Commissioner, "radio has proved to be most useful on the long-distance, cross-country lines where gas is traveling at high pressure and velocity, and where the problem of instantaneous communications for control purposes is most critical."

Tracing the history of marine telegraphy, which played so acute a role in the early days of radio and the ships which carried oil, the Commissioner went back to the days of WCC, the call letters of the pioneer station of the Marconi Wireless Telegraph Company of America at South Wellfleet, Mass. On the ocean side of the Cape at this site in 1903. Marconi had erected his famous transmitter building, located in the center of four 210foot lattice-work towers. In 1914, Marconi found it necessary to replace his early crude apparatus with modern equipment and a station was erected at Marion, where the Cape joins the mainland.

With the advent of World War I, (Continued on page 155)



Soon after you start training I send you my famous BUSINESS BUILDERS that show you how to make money in spare time doing interesting Radio jobs. Look at the useful you have to make money or while training with me (finisherated at left)—I send you these 8 big have of Radio you get while training with me (finisherated at left)—I send you these 8 big have of Radio you found not be a few and the start of the superhet radio at 16-ray given in the superhet radio at 16-ray given in the superhet radio at 16-ray given your 175 Inscinating experience while training. You will perform over 175 Inscinating experience while training. You will learn about Television—so that you will be qualified to step into this fast growing, profitable field. I also send you many valuable service manuals, diagrams and my book telling exactly how to set up your own Television and Radio shop. I wont you to larre all when my training—and that is why I arge you to dip and mall the coupon below for my two big PREE Radio tooks. I employ no salesmen—and nobody will call on you. The important thing is to set now and get the facts.



### HAVE A BUSINESS OF YOUR OWN

A profitable Radio and Television Service Shop may be started with little capital. I will show you how to get started and how to huild your small business. At left is justured one of my graduates, Mr. Merrit C. Sperry of Fairmont, Minnesota in his own shop, The way is also open for you to build a good SERVICE BUSINESS FOR YOURSELF

### ALL KITS ARE YOURS TO KEEP





### RADIO AND TELEVISION INDUSTRY BOOMING

You couldn't pick a better those to get into Radio-Tele-vision and Electronics. New Television stations are going on the air to serve every major city—hundreds of new AM and I'M Radio broadcasting stations are elso on the

THIS TRAINING AVAILABLE TO YOU UNDER THE G.I. BILL

My Training Includes:

Radio Servicing Television FM Frequency Modulation **Public Address** 

and High Frequency **Applications** 



SPRAYBERRY ACADEMY of RADIO, Dept. 25-F 111 North Canal St., Chicago 6, III.

Please rush my FREE copies of "How To Make Money in Radio-Television and Electronics" and "How To Read Radio Diagrams and Symbols."

Name		 	Ago
Address		 	

( ) Check here if you are a Veteran.



THE GREATEST CATALOG FROM LAFAYETTE IN 29 YEARS


164 large-size pages filled with Parts · Tools · Public Address

> High-Fidelity Components Radio & Television Sets and Chassis

Test Equipment . Ham Gear

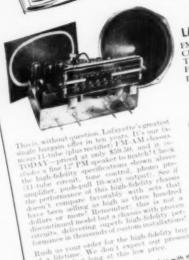**Record Changers** 

**Everything in Radio** and Television at the Lowest "Net" Prices!



SALE! LAFAYETTE'S FAMOUS FM · AM HIGH · FIDELITY

EM - AM HIGH - FIDELITY CHASSIS, 11 TUBES plus REC, TIFIER, Includes PRE-AMPLI, USER | TUBES | FIER for variable reluctance pickup.

PRICE NOW: \$5950

INCLUDING: MATCHED 12" PM SPEAKER! e Receives 88-108 MC FM band, 550 to 1700

- Receives 88-108 MC Fish bands, 550 to 1700 KC broadcast bands.
  Latest 11-tube circuit plus rectifier.
  Push-pull founds, power expens.
  Rated of 10 warts, understands.
  Rated of 10 warts, unde 105-125 volts, 60 cycles, AC only Chassi 105-125 volts, 60 cycles, Singing weight, 25 lbs Complete with thes, dial escatch con, two antennas and matching 12 speaker, \$20.50. e 12 PM speaker

Rush us your order for the high-fidelity buy of a lifetime. We don't expect our present supply to last long at this low price. NOTE: Order the above chassis together with the New Webster 3-speed variable reluctance NOTE: Order the above chassis together with the New Webster 3-speed variable reluctance catridge record-changer—and you have everything you need for a camplete high-fidelity radio-phano custom installation! Phono connector plug supplied at no extra charge when chass and record-changer are ordered together. radio-phono custom installation!

DON'T just take our word for it. Invest a penny postcard and send for your copy of the great new 1950 Lafayette Catalog. Then sit down with a pencil and paper and make a price comparison test yourself. Check the famousmake equipment, model for model, and see if Lafayette doesn't save you anywhere from a few pennies to a few dollars on most every item-

> And remember — Lafayette gives you the service of a national organization, with 2 great centrally-located mail order centers and 6 strategic outlets for personal shopping. That means you save more money on postage, and get the parts you need a couple of days sooner.

So if you're a service man, experimenter, ham, hi-fi bug, engineer, or set-builder-send for your new 1950 Lafayette Catalog now. It's one of the biggest things in America you can get

### wette

2 Great Mail Order Centers: NEW YORK: 100 Sixth Avenue, New York 13 CHICAGO: 901 W. Jackson Blvd., Chicago 7

ANNIVERSARY

6 Outlets for Shopping in Person

- NEW YORK: 100 Sixth Ave. and ATLANTA: 265 Peachfree St. 542 E. Fordham Road (Bronx)
  - BOSTON: 110 Federal St.
- . CHICAGO: 901 W. Jackson Blvd. . NEWARK: 24 Central Ave.

RUSH COUPON

LAFAYETT	E RADIO, DE	PT. R8-5	OVE
901 W. Ja	ckson Blvd.,	Chicago	7, HL.
or 100 Six	th Avenue, I	New York	13, N.Y.

- Check here for FREE 1950 Catalog
  Please don't check if you have already received your catalog:
- Please righ the Lampette FM-AM classis inclining speaker) at the reduced price of \$59.50. I enclose \$ in postal note, money arder or check, which includes slopping charges based on weight and note (Any surplus will be refunded).

lante														
ddress.														

---- PASTE COUPON ON PENNY POSTCARD----



Here is Television at its finest! . . . brought to you by Midwest, for 30 years a leader in the field of radio and elec-tronics. Immense 151-square-inch screen on new 16" metal-complete chassis as illustrated (not a kit, but a complete Television receiver ready to plug in and play) to place in your own cabinet. And you can buy Midwest Television at Low Factory Prices, with Low Down Payment and Long Easy Terms - and on 30 Days Trial!



FACTORY-

Not a KIT ... This is a Completely assembled Receiver

MIDWEST



Powerful new 1950 Series 16 and Series 12 AM-FM Radio n complete chassis. Also beautiful new Console models including the mag-nificent Symphony Grand Radio-Pho-nograph with latest FM circuit and new 3-Speed Automatic Record Player



THE MIDWEST FACTORY and SAVE!

Write in Name and Address (Please Print) on Coupon or 1c Postcard.

SEND

MIDWEST RADIO & TELEVISION CORP. Dept. X377, 909 Broadway, Cincinnati 2, Ohio

Please send me your new FREE 1950 Catalog.

ADDRESS.

ZONE STATE 



### Within the 8 19 INDUSTRY

DR. HARRY F. OLSON, Director of the Acoustical Research Laboratory of

RCA Laboratories, was recently awarded the first John H. Potts Memorial Award from the Audio Engineering Society.

Dr. Olson, a leading authority on acoustics, pioneered

in the research and development of directional microphones, including the velocity type. He was also responsible for the development of a large variety of loudspeakers, the first successful electronic phonograph pickup, and a radically different sound absorber.

He has been associated with RCA since 1928

HOWARD W. SAMS & CO., INC. has moved to its new plant located at 2201 East 46th Street, in Indianapolis. The new building has 30,000 square feet of space and houses all of the operations of the company which were formerly divided between four locations.

THE A A WIRE PRODUCTS COMPANY has announced that its offices are now located in its newly enlarged and modernized plant at 5401 S. Knox Avenue in Chicago. . . . BURLINGAME ASSOCIATES and its affiliate, BRUJAC ELECTRONICS CORPORATION, has moved to larger quarters at 103 Lafayette Street, New York 13, N. Y. THE ROBERT DOLLAR CO, has opened a new H-K Gammatron Tube Division at 947 Broadway in Redwood City, California. The new plant manufactures gammatron tubes for commercial radio transmitting, television transmitting, and allied uses. . . . Additional factory space, totaling 10,000 square feet, has been acquired by INSULINE CORPORATION OF AMERICA in Long Island City. The new space will increase the capacity of the firm's present four-story building at 3602 35th RAYTHEON MANUFACTUR-Avenue ING COMPANY has had to enlarge its Power Tube Division Plant at Waltham. Massachusetts in order to handle the increased demand for cathode-ray The new two-story addition tubes. will increase the floor space of the

000 square feet. RADIO ENGINEER-ING LABORATORIES has consolidated all of its operations into the company's main plant at 36-40 37th Street, Long Island City 1. New York. The general offices as well as the manufacturing facilities will be located at the same

Waltham plant to approximately 145,-

address.... MID-STATES WELDER MFG.
CO. has moved into its new offices and

factory building at 6025 S. Ashland Avenue in Chicago. . . GATES RADIO COMPANY of Quincy, Illinois has opened a new southeastern factory branch at 2700 Polk Avenue, Houston, Texas. . . MARS TELEVISION INC. of Long Island City, in an expansion move, has relocated its assembly plant in larger quarters at 112-33 Colonial Avenue, Corona, New York. The new plant will enable the company to double production.

RADIO MANUFACTURERS ASSOCIATION has set up a new industry committee composed of both RMA members and non-member companies to develop further plans for the educational "Town

Meetings" of television dealers.
A. T. Alexander of Motorola Inc., chairman of the RMA Service Committee, was named chairman of the new committee. Companies to be represented on the committee by executives of the sales, advertising, accounting, and service departments include Admiral, DuMont, Emerson, General Electric, Motorola, Philoo, RCA, Stromberg-Carlson, and Zenith, Chairman Stanley H. Manson of the RMA Advertising Committee will also serve on the committee.

Original plans for the television dealers' meetings proposed TV distributor-dealer meetings in 60 principal cities for the presentation of four 20-minute films on major subjects to assist dealers. The new committee will further study these plans with a view toward developing a more definite program to be underwritten by the set manufacturers in cooperation with distributors.

FRED W. PIPER has been named to head a new division at Starrett Television

Corporation. The new unit will provide the company's "Opticlear" television sets for various veteran, social, and educational organizations.

Mr. Piper will contact local posts

contact local posts of veteran organizations, as well as social and religious organizations, and will arrange to have sets provided for various social meetings and functions. He will work directly with Starrett dealers in the different communities in arranging for sets to be installed and operated during the meetings.

Mr. Piper has been associated with the radio industry in various capacities for over 25 years. He was formerly a member of the Amphon Corp. of



### TV Means Jobs—Good Paying Jobs—for Technically Trained Men



\* ENGINEERS



**OPERATORS** 



\* CAMERAMEN



**TECHNICIANS** 



INSTALLERS

### Here's How CREI Home Study Training Prepares You for a Better Job in TELEVISION



\* SERVICEMEN

TODAY THE CATHODE RAY TUBE can be the crystal ball that forecasts your future. Is the picture clear and bright-or is it fuzzy and

Are you going to learn now how to install and service all types of TV and FM receivers? There can be no doubt that TV is the important field for greater earnings: 83 stations on the air (many more authorized); two million new sets in 1949; twelve million predicted by 1953; practically every area in the nation soon to be in range of a TV sta-tion. Technicians with specialized TV-FM training will inevitably have the inside track installing and maintaining all these sets.

CREI offers just the specialized training you need. It's a streamlined course for the top third of the men in the field-thorough and complete. It gives practical answers to the technical problems you run into while servicing today's intricate TV and FM equipment. It is up to date, constantly revised to cover new developments as they are adopted by the industry.

Start your training now and apply your knowledge immediately. The profitable work, passed up yesterday because it was over your head, can be yours terday because it was over your tomorrow. Make this year the turning point in your TV career! Write today for complete FREE information. The cost is popular, the terms easy. (Veterans: CREI training is available under the G.I. Bill. For most veterans, July 25, 1951 is the deadline. ACT NOW!)

SAMPLE FREE "Television & FM Trouble Sheeting" devoted to live, "dollar - and - cents", practical practice based on day-to-day servicing problems. Read this interesting lesson! See for yourself how CREI training can help you. Mail coupon for sample lesson, free booklet and details

### THE THREE BASIC CREI COURSES:

- PRACTICAL RADIO ENGINEERING Fundamental course in all phases of radio-electronics
- PRACTICAL TELEVISION ENGINEERING
- Specialized training for professional radiomen
- TELEVISION AND FM SERVICING ALSO AVAILABLE IN RESIDENCE SCHOOL COURSES

### CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 292-8, 16th Street & Park Road, N. W. Washington 10, D. C.

Mem York (7) 170 Broadway . San Francisco (2) 760 Market St.



CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 292-8, 14th & Park Rd., N. W. Washington 10, D. C.

Gentlemen: Send me FREE SAMPLE LESSON and complete details of the TV and EM Servicing home study rourse. Also send brochere that explains the CREI self-improvement program and gives complete details and outline of course. I am attaching a brief resume of my experience, education and present position.

Check PRACTICAL TELEVISION ENGINEERING of PRACTICAL TELEVISION ENGINEERING Interest BROADCAST RADIO ENGINEERING Greatest BROADCAST RADIO ENGINEERING Interest BROADCAST RADIO ENGINEERING AM. FM. IV)

RADIO-ELECTRONICS IN INDUSTRY

I AM ENTITLED TO TRAINING UNDER GL. HILL.

NAME

AGE

ADDRESS

CITY ZONE STATE

SAMPLE LESSON SEND DETAILS ON RESIDENCE SCHOOL. Gestlemen: Send me FREE SAMPLE LESSON and complete details of the TV and FM Servicing home study course. Also send brochuse that explains the CBEI self-improvement program and gives complete details and outline of course. I am attaching a brief resume of my experience, education



FICE ON 610-A

### The complete TELEVISION

Generator

### SELF-CONTAINED MARKERS

makes your

RAPID

ACCURATE PROFITABLE

WITH THE HICKOK MODEL 610

you can

Align I F.

Align R.F.

Align Oscillators

Align Trap

Oscillator, Absorption, Crystal

V Cover all TV channels



Far over 39 years builders of the finest electrical and electronic test instruments

### THE HICKOK ELECTRICAL INSTRUMENT CO. 10524 DUPONT AVE. CLEVELAND 8, OHIO

ZONE

STATE

Please send me full details on the complete new HICKOK 600 series Television hest aquipment, including the brand-new linearity Pattern Generator.

HAME

STREET & NO.



FOR TODAY AND THE FUTURE

3. Crystal markers, any frequency, modulated or

Enables you to align any TV receives independent of any local station. This generator is complete, and will remain up-to-date for a long.

Thousands of the HICKOK Model 610 have been

in use by leading technicians for over a year.

ned markers

1. Complete frequency coverage

Variable, self-canta

4. Outstandingly stable.

6. Excellent attenuation

High output

lime to come

CITY

### RADIO ENGINEERING TELEVISION ELECTRONICS

Thorough training in all phases of raillo and etcotrations, upon to high subboard and notice college must called the established school operationing to Early training exclusively. Most of ever latteralistics and sources. Euroclineous Hostell, Appendix of section

VALPARAISO TECHNICAL INSTITUTE Dept. RD Valparaiso, Ind.



Thorough Training in All Technical Phases
APPROVED FOR VETERANS
WEEKLY RATES
BCA GRADUATES ARE IN DEMAND

RCA GRADUATES ARE IN DEMAND For Free Catalog write Dept. RN-50 6 Service of Radio Corporation of America RCA INSTITUTES, INC. 250 West 4th St., New York 14, N. Y.



America, United Radio Corp., Temple Radio Corp., and Howard Radio Corp. staffs.

H. P. BALDERSON, sales manager for Thermador Electrical Mfg. Company's transformer division, has been named chairman of the Los Angeles Council of the West Coast Electronics Manufacturers Association.

Serving with Mr. Balderson in 1950 are C. A. Swanson, manager of Standard Coil Products Co., Inc., as vice-chairman; and Fred W. Falck, Jr., general manager of Advance Electric and Relay Co., who was reelected to the post of secretary-treasurer.

The 1950 board of directors includes, in addition to the officers, Robert Newcomb, president of Newcomb Audio Products Co.; E. P. Gertsch, president of Gertsch Products, Inc.; Wilbur V. Phillips, personnel director of Hoffman Radio Corp.; and Richard G. Leitner, chief engineer for Lear of California, Inc.

DAVID T. SCHULTZ, vice-president and treasurer of Raytheon Manufacturing

Company since 1928, has been named to the board of directors of the company.

He joined Raytheon's predecessor company in 1927 as treasurer and has been associated

with Raytheon since its inception in 1928. Mr. Schultz is also a director of Metals & Controls Inc. and has served the radio industry in the capacities of director and vice-president of the Radio Manufacturers Association.

RICHARD F. DOOLEY, FRANK J. KAZDA, CY S. ROSSATE, and KENNETH D. TUR-NER have been appointed vice-presidents of real estate, purchasing, production, and engineering respectively by Admiral Corporation. The appointment of F. P. TAUGHER as manager of engineering for the Industrial Control Division has been announced by Westinghouse Electric Corporation. . . ROBERT J. MC DONALD has been named district sales manager for The Magnavox Company. He will headquarter in Philadelphia and cover eastern Pennsylvania, Southern New Jersey, and Delaware. . . LARRY F. HARDY is the new president of the Television and Radio Division of Philco Corporation. He will be in charge of all phases of the corporation's radio and TV business. FREDERICK D. OGILBY is the new vice-president in charge of sales for the same division . . . WESLEY L. WIL-SON has taken over as general sales manager of the Cathode-Ray Tube Division of Arcturus Electronics, Inc. of Newark ... JOHN D. SMALL is the new executive assistant to the president of Emerson Radio and Phono-

graph Corporation. JOHN A.
HICKEY has been named engineering
field adviser in the Raytheon Replace(Continued on page 128)

RADIO & TELEVISION NEWS

### HIAWATHA WAS A PIKER!



"Go out into the world," said Pops" "and don't come back 'till you're proved tops!"



The water test he passed with ease, Earning a feather was just a breeze...



Heat was applied to test his worth In "hat spots" he then won a berth...



The life test took a long, long time Though others quit — he kept his prime ...



His leads proved strong—his casing tough It did no harm to treat him rough!

His Pops was pleased when he came through We know you'll like the

Redskin, too!

### Sangamo's New Molded Paper Tubular Capacitor gives LONG LIFE under severe conditions!

The REDSKIN is easy to work with—on production line or on the bench—because the especially designed flexible leads resist breakage and can't pull out! It offers greater mechanical strength because of its plastic construction. It is molded under *low* pressure, assuring elements undamaged in fabrication, longer life and greater dependability. It is an 85°C tubular which offers assurance of long life under television and other severe operating conditions.

A trial of these better molded tubulars will convince you. See your jobber—if he can't supply you, write us.



\*Big Chief Sangama

### SANGAMO ELECTRIC COMPANY

SPRINGFIELD, ILLINOIS

In Canada: Sangamo Electric Company Limited, Leaside, Ont. February, 1950



N2014

## GREAT HOME BOOKS..




### LEARN BASIC RADIO-ELECTRONICS

COMPLETE BASIC RADIO-ELECTRONIC TRAINING for Beginners 36 Courses in One

No matter what part of Electronres-Ranto-Television work you plan to enter, a knowledge of basic fun-damentals is absolutely essential. Ghirardi's world-famous Ranto Ghirardi's world-famous Radio Physics Course book gives exactly the training you need—at a price you can afford to pay! If sent as monthly lessons, you'd regard it as a bargain at \$50 or more Instead, you buy it for only \$5—and many have finished it in only a few weeks.

Radio Physics Course starts at

the very beginning—with Basic Elec-tricity. Then it takes you step by step through the entire field of basic RABIO-ELECTRONICS and TELEVISION principles. You can understand it principles. You can understand a easily without previous radio train-ing Actually, this big book has given more beginners their start in Radio-Electronics than any other book or course. During the war it was more widely used for Signal was more widely used for Signal Corps and Navy basic training than any other book of its kind. Read it for 10 days at our risk! Order No. 1.

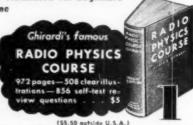

### Get a complete PROFESSIONAL RADIO SERVICE TRAINING

... at home without an instructor ... for only \$5



A. Ghirardi's giant, 1300-page BERN RABIO SERVICING gives a COMPLETE EDUCATION in truly profes-sional radio service work of the kind that can be your "Open Sesame! the real opportunities in Radio-Electronic servicing. Remember! The need is for Highly Trained men having a genuine knowledge of profes-sional equipment and techniques-

NOT "screw driver" mechanics. Read from the beginning, Mon-ERN RABIO SERVICING IS a complete servicing course from A to Z. Used

for reference, it is an invaluable refresher course on any type of work that puzzles you. Explains radio service test instruments—tells how to build your own. Shows how, when, why and where to use each one; how to make preliminary trou-ble checks and how to analyze circuits; how to repair or replace parts; how to make substitutions—and hundreds of other subjects including How to Start and Operate a Successful Service Business. Price \$5.
Use Coupon. Order Book No. 2.

### REPAIR RADIOS THIS FAST, EASY WAY!

This Big Handbook Shows Exactly How to Repair over 4,800 Radio Receiver Models

Ghirardi's Ranto Troubless morrows Hammook is a definite, dependable guide for diagnosing, locating and reparting the common troubles in almost experience and results and the second process of a living or work with them only occasionally, this big book will save yest time and money on four jobs out of five. Eliminates useless testing?

Simply look up the notes on the make and model of the raidic you want to fix. Chances are you'll find exactly the information you need. The Hamdbook tells what the trou-

ble be—what causes it—anul exactly how to repair it. It's the ideal book so repair it. It's the ideal book depending up their work—handling tough jobs in half the usual time—repairing low-priced sets rapidly and profitably.

Hundreds of additional pages contain valuable data on tubes, parts and equipment, graphs, diagrams, data and helpful service hints that day. Everything is carefully indexed so you can find what you want in a jiffy. Only 55. Use coupon, Order Hook No. 3.







### **MONEY - SAVING** COMBINATION OFFER

your servicing library More your servicing months record to the servicing months of the servicing mon money vaving price of only \$9.50 for the two (\$10.50 outside U.S.A.)



### Now! You'll Really Know

Don't let the escilloscope "stump" you! Learn to use it properly-and watch your efficiency and earnings

### MODERN OSCILLOSCOPES AND THEIR USES

by JACOS H. RUITER. Jr. of Allen B. DuMant Laboratories, 326 pages, 376 illustrations, Price \$6.00



Read ANY of them for 10 full days

### THAT MAKE IT EASY FOR YOU TO LEARN A GOOD PAYING TRADE

### The big book that MAKES AUTO RADIO REPAIR TWICE AS EASY!

Covers all auto radio types from the mid-1930's to the SJUST OUT! Present, including mobile F-M.

Here-written by a leading auto radio Here—written by a leading auto ratio repair expert—is everything needed to help the beginner or experienced service—convergence of the repair of the repair

#### Practical facts and methods on:

- e getting into the car radio business auto erecurs unterna installation terms of the ioudspeaker installations car set installations enceding interfer-ence enceding interfer-ence enceding procedure vibrator mainta-nance, etc. Use Coupon, Order Book No. 5 10-day Money-Back Guarantee

rachmon PRACTICAL TELEVISION SERVICING By J. R. Johnson and J. H. Newitt

(Outside U.S.A. \$4.50)



MODERN CAR RADIO By A. L. Hurlbut

Second edition, 702 pages 9 x 12, 222 ilias, over 500 circuit diagrams. Price \$7.50.

(Outside U.S.A. \$8.00)

### Learn ELECTRIC MOTOR REPAIR!



### ELECTRIC MOTOR REPAIR

By Robert Rosenberg

566 pages - 806 enaily Milit Dau-Book

(Outside U.S.A. \$5.50)

### Train for good pay in a field that isn't crowded IDEAL FOR RADIO MEN

There's big money in electric motor repail? The field isn't crowded—and Electric Moron Repails the book that will train you quickly for only \$5. Explairs every detail of motor trouble diagnostig, repair and rewinding. Covers all types of ac and de motors and generators in common that and Beritt systems. Quick reference guides show exactly how to handle specific jobs.

### SHOWS YOU HOW . . . EVERY STEP OF THE WAY

Based on what can be learned from Based on what can be learned from this big book alone, you can train quickly for this profitable field. The perfect book for beginners. Enexcelled for actual bench use. Every type in scork is demonstrated VISUALLY by more than you castly understood diagrams. MHII Duo-Book spiral binding divides book into two sections so that both text and retice from it. In days under our Money-Back Guarantee infer. Order Book No. 7 in compon.

### Get started NOW in TELEVISION SERVICING! \* Practical Servicing

New-Different-Down-to-Earth-Makes Television Work Easy to Understand

PRACTICAL TELEVISION SERVICING UNIT Our 10-day MONEY BACK GUARANTEE protects you absolutely. Order Book No. 6.

### FREQUENCY MODULATION

Fundamentals . Apparatus . Servicing By Nathan Marchand

448 pages, 6x9, over 300 illustrations \$5

(Outside U.S.A. \$5.50)

This new book by a well-known radio consultant makes it easy for you to understand FM radio clearly. Equally in portant, it explains exactly how to has deed it types of FM agylee work.

Bian theory, circuits, transmitters, reserves practical, easily understood manner—wells special emphasis on modern methods of installing, adjusting and repairing EM receivers. From M circuit



### How to Use an Oscilloscope!

MODERN OSCILLOSCOPES AND THEIR USES—shown on the opposits again right hown to earth in explaining the ourilloscope (cathode earthing rank) and showing exactly how to use it on specific AM-FM and showing exactly how to use it on specific AM-FM and the cathode and the cat



### OUR RISK

Dept. RN-20, Murray Hill Books, Inc., 232 Medison Ave., New York 16, N. Y

Enclosed find check or money neder for 8. for the backs checked below; or send C.O.D. (in U.S. 5, only) and I will pay posterior this amount plus postoge. In wither even, if uncutifactory, it is unfersional I may return backs after 10 days and you guarantee in before up processing the Control of the Contr


CIRCLE NUMBERS OF BOOKS YOU WANT TO RECEIVE

Book Number 1 2 3 4 5


Clock here for SPECIAL COMBINATION OFFER of only 49-58 1819-59 orbide U.S.A.: for both Chrant's MODERN RADIO SERV-UNDER HANDROOK Book No. 2: and Gorard's BADIO TROUBLESHOOTER'S HANDROOK Book No. 1:

Name Address

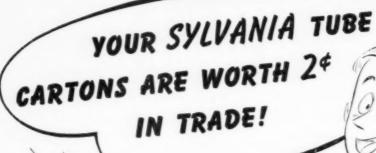City, Zone, State Please strite or print clearly



STITUTE STITUTE

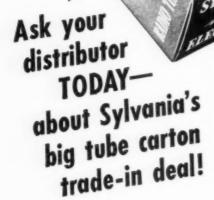

DURING FEBRUARY, MARCH AND APRIL YOUR EMPTY SYLVANIA CARTONS ARE WORTH 2¢ EACH AT YOUR DISTRIBUTOR'S when applied against the purchase of...

- . SYLVANIA ADVERTISING MATERIAL
- MORE SYLVANIA TUBES
- . SYLVANIA TEST EQUIPMENT

### SYLVANIA ELECTRIC

RADIO TUBES; CATHODE RAY TUBES; ELECTRONIC DEVICES; FLUORESCENT LAMPS, FIXTURES, WIRING DEVICES, SIGN TUBING; LIGHT BULBS; PHOTOLA APS





• Extra sensitivity for weak signal areas . . . extra performance for good Ham operation.


The newest thing in portables, just introduced by Hallicrafters. One r-f, two i-f stages. Range 540 kc to 31 Mc in 4 Bands. 8 tubes plus rectifier. AC, DC, or batteries.

Long-Wave S-72L, 175 kc, 12.3 Mc.....\$99.95

the hallicrafters co.

4401 W. Fifth Ave. . Chicago 24, III.

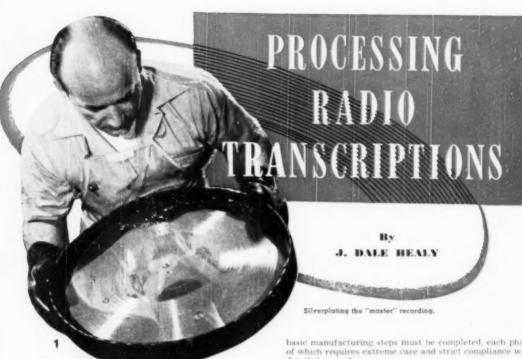Manufacturers of Precision Radio and Television Equipment



Most of your favorite radio programs are now coming to you transcribedhere is how the discs are processed.

HE processing and manufacturing steps necessary to produce a phonograph record or an electrical transscription are so fascinating and so little known outside a tight little industry, that this article should prove of great interest to even the casual reader.

The author has tried to capture in visual form what would be most difficult to describe in non-technical language, and hopes that the combination of words and pictures will give continuity and form to a most delicate series of operations

At the start, it should be pointed out that the tolerances permitted are fantastically small-so small in fact that no mechanical measuring equipment can record them

When dealing with the physical reproduction of a 10,000 cycle tone, the permissible variation is limited to perhaps only one millionth of an inch! This can be measured only by playing the groove and measuring the electrical output through the most critically balanced circuits

Measurements that in other industries would occupy the attention of laboratory technicians for hours, are made in minutes by use of specialized equipment. Hundreds of such measurements are made daily and plotted to indicate the over-all condition of the recording and processing departments. It is meticulous attention to minutiae that raises the quality of the transcription so far above the standards of three years ago, or even of the commercial phonograph of today.

The following sequence is used to maintain dimensional tolerances, frequency response, and fidelity

Before the final vinylite pressing is produced, thirty-six

basic manufacturing steps must be completed, each phase of which requires extreme care and strict compliance with detailed procedure.

The original, or "master" recording on lacquer, (the trade still refers to it as a "wax") has inscribed upon its surface minute sound modulations as picked up by the microphone from within the studio.

To make a number of copies of this original, the "master" recording is sent to a processing plant for the generation of metal parts which are an exact reproduction of the original "master" recording.

When the "master" recording is received at the processing plant, a code or serial number is assigned to it. This number is inscribed on the surface near the label area, and for all future reference identifies this particular recording.

Having been received and coded, it is sent to the matrix department where it receives visual inspection, and in some cases microscopic inspection, before being released to processing.


Once it is released to processing, it goes to a temperature controlled silvering room, where the operator, prior to silvering, cleans the surface with a detergent and copious rinses of distilled water.

The surface is then sensitized by the application of a stannous chloride solution. This application assures the proper adherence of the deposited silver to all the minute

detail of recorded groove and surface.

After sensitizing, the "master" is rinsed with distilled water and placed in a rubber tray. A chemical silver solution is now poured on the surface as shown in Fig. 1, and is rocked and agitated by the operator for approximately one minute during the precipitation of the silver solution. A film of metallic silver, "millionths" of an inch thick, is deposited on the surface of the "master" recording, thus making the surface a conductor of electric current. In its original state the surface was non-conducting and electrodeposition could not be accomplished.

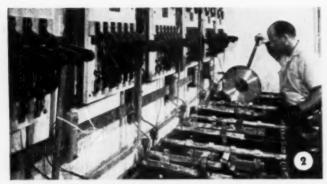Now that the "master" is silvered it can be placed in an acid copper plating tank to begin the first step in the generation of metal duplicate parts. See Fig. 2. The copper plating adheres to the thin film of silver and exactly conforms to every characteristic of the original master re-



The acid copper plating operation known as the copper preplate bath.




Stripping the metal "master" from the "master" recording.

Copper plating on a revolving hanger to insure even plating in a very active copper plating solution bath.




Centering to within .003 inch and center punching the "master."

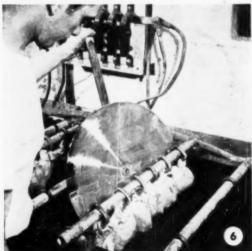
The nickel plating operation which forms a protective surface.



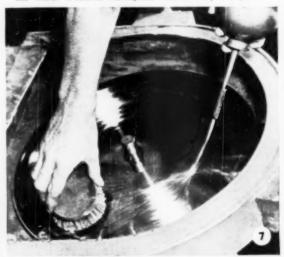The "master" is cleaned with naphtha while revolving on a spindle.



RADIO & TELEVISION NEWS

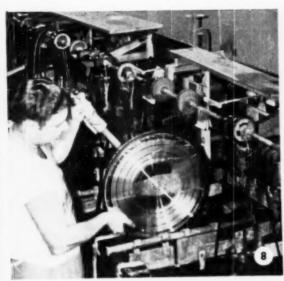

Metal "master," upon which a "mother" is formed, lowered in bath.

After approximately 8 hours of copper plating, a plate of .032" of copper has been deposited on the face of the silvered "master" recording. It now has enough strength so that it can be safely separated from the "master" recording without danger of bending or damage. Fig. 4 shows the metal "master" being separated from the "master" recording.

We now have the first of our electro-formed metal parts which is a true "negative" of the original recording. All of the infinite detail of the original sound pattern has been faithfully reproduced in a new medium—the metal "master."

The metal "master," after separation, goes to the finishing room where it is re-centered to within  $\pm$  .003". This operation is accomplished on a punch press by means of a dial indicator, as shown in Fig. 5.

Having been re-centered and punched, the metal "master" is electro-cleaned in preparation for a nickel facing plate that will form a protective film of nickel on its surface as shown in Fig. 6.

After nickel facing, the "master" is again cleaned by means of a spinning wheel and naphtha solution as shown in Fig. 7.


Our first metal part, the "master," has now been finished to the point where it is ready to serve as the original (negative) in another electro-forming cycle that will produce a second part, called the metal "mother."

In-order that copper can now be deposited upon the nickel surface of the "master," to form the next part a molecular film of oxide must be provided on the "master" that will allow the new copper to conform intimately to all detail and yet be free from bonding to the nickel surface.

This oxide film is developed chemically by the application of a dichromate solution to the surface of the "master" which makes the nickel passive. Now that the nickeled surface has been oxidized, the metal "master" is mounted on a plating hanger and immersed in the acid copper tank to begin the formative stage of the second metal part, the "mother," Fig. 8.

After approximately 10 hours of plating time, we have the first metal part, or "master," on the face of which has been electro-formed the second metal part—the "mother."

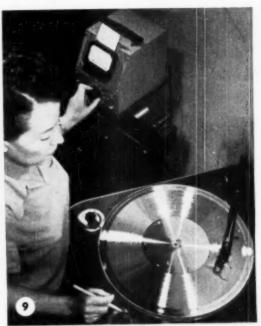Because the copper has formed around the edge of these plates it has to be filed away until a pry tool can be inserted at the edge to separate the two parts as was done with the original and metal "master" shown in Fig. 4.



Technician making sound test of the metal "mother" recording.



Craftsman repairing a defective groove on the metal "mother."

Having started this electro-forming cycle with the metal "master," which is our "negative," we have now formed the "mother" which is a "positive"; identical in all respects to the original "master" recording except that we now have a "positive" in copper instead of the "wax" or lacquer positive we started with.

The "mother," being a positive, can be played the same



The surface of the "stamper" being hardened by chrome plating.

"Stamper" is punched and sheared to fit die of the record press.



as could the original recording. And by playing it we can determine exactly the faithfulness with which we have reproduced the sounds picked up by the microphone—electrically transcribed to the "master" recording, and finally reproduced in copper metal.

The "mother" is not only checked for tone quality, but also for signal-to-noise ratio and distortion. This test is

shown in Fig. 9.

The term "mother" was no doubt applied to this second metal part because from it we can electro-form a number of "stamper" plates, which when mounted in the record press die, will produce mass quantities of vinylite pressings identical to the "mother" and the original "master" lacquer or "wax" recording.

If at any time in the handling of these metal parts they are unavoidably damaged, a skillful repairman with the proper tools and a basic knowledge of groove contour can repair the damage so that the untrained ear has difficulty in detecting the repair. A good example of the technique of repair is shown in Fig. 10.

The "mother," having passed sound inspection, is now nickeled and its surface prepared for the generation of the

third metal part, the "stamper."

The "stamper" is electro-formed upon the face of the "mother" by the same method used in making the "mother" from the "master."


After plating in the acid copper the "stamper" is separated from the "mother," as described before in the case of "master" and "mother," and is sent to the finishing room for proper dimensioning before being mounted into the record press die.

One operation of "stamper finishing" is the plating of a hard chromium film, Fig. 11, upon the face of the (Continued on page 108)

The heat and high pressure of the stamping machine form the transcription from either special plastic or shellac material.



BADIO & TELEVISION NEWS

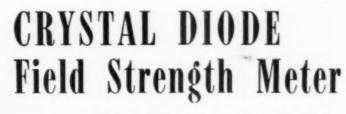

Design details of a compact unit having a range of 46 db. Crystal diodes obviate the need for a power supply or batteries.

Two views of the diode field strength meter showing compactness of unit. The meter is self-contained and requires no batteries. The anienna shown in the front view of meter is removable.

Rv

### ROBERT C. MOSES

Sylvania Electric Products Inc.

N THE development of an antenna system, one instrument above all others serves, when properly used, to give a true representation of the performance of the radiator. Particularly when applied to the design of a new antenna, a well-designed field strength meter will indicate when the optimum tuning adjustments and generally best performance have been achieved, and may also show directly the comparison of one system to another.

In the past, a great many types of field strength meters have been devised. One of the more widely used types consists of a vacuum-tube grid leak or bias detector with a suitably calibrated current meter in its plate circuit. This type of instrument is characterized by high sensitivity and an approximately logarithmic meter scale calibration, and in general is useful over a dynamic range of about 20 db. One problem, however, which is common to all types of vacuum tube field strength meters, is that of obtaining a suitable power source for the instrument. From the very nature of the device, portability and compactness are prime requirements, and since the instrument will, in general, be used remote from a source of a.c. power, batteries, with their many shortcomings, are inevitably required.

In order to overcome this inherent

disadvantage, several crystal diode field strength meter designs have recently made their appearance. While these effectively eliminate the need for batteries and lend themselves to the design of extremely compact instruments, in general the sensitivity of such instruments is quite low. This limitation may require a relatively long pickup antenna particularly at the lower frequencies, or the placement of the instrument quite close to the radiating system under measurement, where, it is generally conceded, the accuracy of the indication may not be all that is desired. This article describes a crystal diode field strength meter of extreme compactness, requiring no batteries, and whose sensitivity is considerably above that of other instruments of this type.

### **Circuit Description**


The circuit of the high-sensitivity crystal diode field strength meter is shown in Fig. 1. The r.f. detector and indicator portions of the instrument consist of paralleled pairs of type 1N34 germanium diodes together with condensers  $C_0$  and  $C_{\rm in}$ , and the meter,  $M_{\rm in}$ . The tuned input circuit  $C_{\rm in}$ - $L_{\rm in}$ , by virtue of its effective "Q" of approximately 30, provides a useful voltage step-up, (Continued on page 136)

Table 1. Winding data for various ranges.

RANGE	L	L <sub>1</sub>	C,
3.5-4 me.	32 t. closewound	14 t. closewound	120 mufd.
7-7.3 mc.	18 1., 3 4"	9 t. closewound	120 µµfd.
14-14.4 mc.	10 1 34"	6 t. closewound	82 µµfd.
27-30 mc.	6 t., 3 4"	3 t. closewound	68 µµfd.

All coils are wound with 224 enameled wire on ½" diameter slug-luned forms. The coupling coils, L., should be wound on loose fitting sleeves slipped over the forms so that accurate adjustment of the spacing between the coils may be made aft the unit is assembled. Such adjustment of the coupling is required in order to assure maximum transfer of energy through the input circuit. In practice, the coupling is set for maximum meter deflection with a steady signal applied to the antenna terminal through a resistor of the order of 20,000 ohms, and the frequency.

Fig. 1. Circuit diagram of the highly-sensitive crystal diode field strength meter.

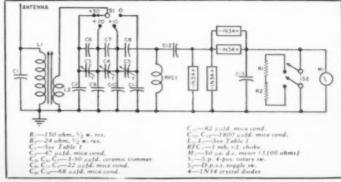

# ULTRA-MODERN WOR-TV Is 84th Television Station

New York's newest television station incorporates many interesting equipment and studio features.

### NEWLAND SMITH

WOR-TV Video Facilities Engr.

OR-TV, Channel 9, which has just gone on the air in New York, is the final station authorized for that area under present FCC v.h.f. allocations.


But WOR engineers have literally been in television ever since the new medium was first developed. They have kept abreast of the progress of the industry, watched new methods and equipment replace old. When WOR was granted a construction permit for WOR-TV, the engineering staff knew from their own experience, and from the good and bad experiences of engineers at other stations, exactly what camera pick-up and transmitting equipment would best enable them to build the most modern TV station in the area.

They chose their equipment from what they considered the best offered by the three leading manufacturers. This article will discuss the function and type of equipment used in each of three locations—the WOR-TV transmitter, studios, and mobile units.

A 760-foot, self-supporting tower holds WOR-TV's 50-foot transmitting antenna high in the air. The antenna is a six-bay superturnstile that radiates both audio and video carriers. The tower and antenna are located on the Palisades of New Jersey overlooking Manhattan, 240 feet above the Hudson River. Thus the combined height of the tower and antenna is 1050 feet above sea level.

Also located atop the tower is an FM antenna—a GE "doughnut" model, a special form of folded dipole. Because it is the belief of the station that both AM and FM radio will continue to co-exist with TV for some time to come, it was decided to integrate FM transmitting facilities with the TV installation. AM broadcasting facilities—without the problems of propagation affecting FM and TV—are satisfactorily supplied by WOR's existing

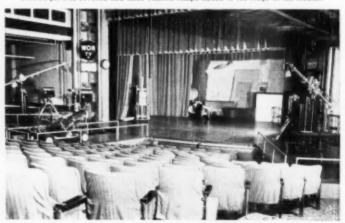WOR TV's audience studio theater. In adapting the theater for television use, the orchestra pit was covered and three camera ramps added to the stage at the theater.



WOR's television transmitting tower located in North Bergen, N. J. 760 feet high, the tower is the tallest structure in the state. It stands 1050 feet above the Hudson River on the Palisades. From the 50-toot antenna, WOR.TV began operation on a 20-hour a-week schedule on October 11th. telegasting on Channel 9.



Close up of transmitter control console (left) and video console (right, center). The turntoble in foreground belongs to sound desk. The video mixing desk operator faces the TV and audio tacks which line wall behind the console in right center. Instruments enable operators to set and maintain proper audio and video levels of the signals feeding into the transmitter unit.

A studio control room at the New Amsterdam Roof Theater with the temporary master control switching setup now being used.

TILLOS

AMPLINES

CAMBRA

INDA

TOMANA

transmitter in Carteret, New Jersey, FM and TV antennas are both equipped with heating devices to prevent formation of ice in the winter. This is important, since icing would change their transmission characteristics.

Located at the WOR-TV transmitter site, in addition to the television transmitter, are input video equipment for monitoring and handling incoming signals from the master control in the city, a microwave receiving terminal, and also a local source of video for generating the test pattern and transmitting sides.

The WOR-TV transmitter building has been designed for efficient operation. When seated at the transmitter control desk the operator on duty faces the transmitter unit, the racks of which line the walls at the right of the picture on this page. Both the sound desk and the camera control and mixer desks are easily available to him. Normally, however, the programs are originated elsewhere and routed to the transmitter via a master control point.

The master control was first located in WOR-TV studios in the New Amsterdam Roof Theater in New York. When studio facilities are completed in the Television Center at 67th Street in Manhattan, the master control will be located there.

The WOR-TV transmitter is a General Electric type TT6D rated at 5 kw. peak video power and 2.5 kw. aural power. Because of the present FCC 50 kw. e.r.p. (effective radiated power) limit, only 2.04 kw. is fed into the transmission lines.

The FM transmitter is a 10 kw. GE BT-4-B model. At this writing WOR-TV is originating its television programs from two studios and two associated control booths in the New Amsterdam Roof (Continued on page 148)



Interior view of power cubicle of FM transmitter showing rectifiers and transformers.

Passageway behind the FM and TV transmitter racks. Nearest racks house the television transmitter with diplexer mounted above. The other racks contain the FM transmitter. In the left foreground is the dummy antenna while above it are the dehydrators for automatically pressurising the transmission lines. Racks in background contain telephone terminal equipment (audio and video) and test and measuring equipment.



February, 1950

# TEST EQUIPMENT For Citizens Radio

Front panel view of the ascillater, wavemeter, and field strength meter. The aquipment is housed in a war surplus cabinet. The antenna is of the type used with APN-I altimeter.



### By HAROLD B. McKAY

Complete details on the design of a wavemeter and field strength meter for u.h.f. band, and a 460-470 mc. oscillator which can be used as a signal generator.

NE of the most important tools required in the testing of radio transmitters is a receiving device of good stability which is completely independent of the transmitter being tested.

For frequencies in the citizens band, 460 to 470 megacycles, there is no low-priced test equipment presently being manufactured. However, by using certain equipment which is still available as surplus, a useful wavemeter can be readily constructed.

This device will serve as an indication of transmitter frequency, field strength of the radiated signal, and as a crystal detector receiver for checking modulation quality.

The unit consists of a surplus butterfly condenser (300 to 1000 mc.), a diode crystal detector, and a microammeter.

Some of the surplus butterfly condensers are available with a crystal mounting and a bypass condenser built in the unit, which simplifies construction. In any event, a crystal of the IN21 or similar type may be readily connected as shown in the diagram.

The bypass condenser shown in the drawing may be any small value ceramic or mica unit. It is necessary to use this bypass condenser only if none is built into the butterfly condenser.

The butterfly condenser has an extremely wide tuning range. While this makes it unreliable for precise frequency measurements, it has the advantage of tuning to the second harmonic of the citizens frequency, which is an important consideration in transmitter adjustment.

The tuning unit is coupled to a dipole antenna by means of a short length of 52-ohm coaxial cable. A coaxial chassis-type connector mounted on the butterfly receives the cable. The lead from the coax connector to the condenser frame terminates in a small loop. Lot give slight coupling.

The antenna is the type used with the APN-1 altimeter. The large diameter of the radiating elements broadens its range. The stand-off supports hold the antenna at one-quarter wavelength from the cabinet. This is useful in field strength measurements, as it reinforces the signal uniformly and eliminates stray reflections from other objects when the antenna is held vertically.

The meter used in this model is a 0-50 microammeter though less sensitive instruments may be used with reduced range. Protective resistors are connected across the meter by means of a switch. Two resistors of about one-half of the resistance of the meter serve as shunts, when working close to a strong signal.

The "off" position of the switch places a short across the meter.

The leads to the meter may be extended to pin jacks on the front panel where headphones may be connected to monitor the signal.

The cabinet housing the device is

from a surplus transmitter tuning unit. It was chosen because of the two calibrated reduction-gear dials, which are the only parts of the original tuning unit used in this wavemeter.

To calibrate the wavemeter it is necessary to have a signal generator or transmitter, the signal from which can be received on the wavemeter. The frequency of the signal-generating device may be measured by Lecher lines, then the dial setting of the wavemeter noted. A calibration chart may be easily prepared in this manner for the wavemeter.

The wavemeter will not give sharp enough indications for frequency measurements as required by FCC, but is very useful for approximate adjustments.

In addition to its uses as a relative field strength meter, this device can also be placed near the transmitter during normal operation. It will function as an indication that the transmitter is on the air, and will indicate any large frequency drift which may occur.

### Oscillator for 160-170 mc.

A useful accessory which can be added to the wavemeter described is an oscillator whose fundamental range is within the citizens radio band.

Such an oscillator may be built around a Johnson miniature butterfly

condenser. Ultra-high-frequency oscillators are in general somewhat unstable, and extremely sensitive to stray capacity effects.

The coil-condenser combination used in this circuit has been found to be less sensitive to these effects, because of the small size of the oscillating elements. In this respect it has an advantage over the tuned-line circuits usually used at these frequencies.

If placed in a comparatively large cabinet enclosure, the oscillator will be completely immune to body capacity effects, and may be readily tuned and handled. However, it will be sensitive to changes in the dimensions of the enclosure and the device must be handled in a manner which will not cause the sides of the cabinet to bend.

Ordinarily, when used as a signal generator, no antenna will be required, as the cabinet itself will radiate. However, if an antenna is used, it should be connected by a coupling loop, L<sub>b</sub>, located at least an inch from the oscillator coil.

An antenna connected in this manner will not alter the frequency of the oscillator even if touched.

Considerable experimenting may be required in the construction of the oscillator in order to get the frequency to fall in the citizens band. The tuning range is very limited, covering only 8 to 10 megacycles.

This provides excellent bandspread for spotting exact frequencies in the band, but calls for a certain amount of trial and error in the construction of the tuned circuit.


In the model shown, the "coil," L<sub>n</sub> is a "V" shaped piece of 12 gauge silver-plated wire, ½ x5½ outside diameter. It was made by bending the wire around the tip of a pair of long-nosed pliers, then adjusting it to just fit the gap between the stator posts on the butterfly condenser.

The frequency of this assembly may be changed slightly by squeezing or expanding the "V." The shape of the wire, as well as its size, are not definite quantities. The shape and size of the cabinet, the proximity of wiring or brackets, the value of the grid condenser, and numerous intangibles will affect the frequency of the oscillator.

It may, therefore, be necessary to prepare several "V" and "U" shaped pieces of wire or copper strip with which to experiment. While a wide range of wire sizes may be used, No. 12 or 14 is best because it remains rigid. Silver plating is not necessary, but will increase efficiency.

In testing different sizes of loops, the wire should be shortened to raise the frequency and lengthened to lower it. Experiments may start with a wire about an inch long. This may be gradually trimmed down until the frequency falls in the required range.

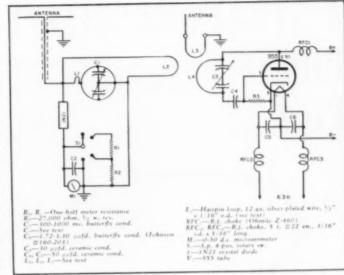Occasionally, as the loop is reduced, the circuit may fail to oscillate. For this reason, a 0-25 milliammeter should be kept in the plate supply



Circuit diagram of the wavemeter (left) and oscillator (right) test equipment.

lead while adjustments are being made. A reading of about 7 milliamperes indicates oscillation. Ten or higher means oscillations have ceased.

Should the oscillator fail, it may be necessary to change the value of the grid condenser. Past experiments have indicated that the final value may fall anywhere between 15 and 50 µµfd.

It will be noted that the circuit shown omits a connection to the condenser rotor, and has no plate circuit bypass condenser. This is intentional and the oscillator has been found to work best with the circuit shown. This simplifies construction and improves stability, as every condenser in the circuit affects the frequency.


In some cases failure of the oscillator to function may be caused by the r.f. chokes used in the plate and heater leads. If the oscillator failure can not be definitely traced to other causes, some experimentation with the chokes is indicated. Due to the many varying factors, the optimum size and number of turns will have to be determined by experiment. The values given will serve as a starter.

If this device is used in conjunction with the wavemeter, a pick-up loop,  $L_0$ , made of any piece of stiff wire, may be used to integrate the two units, so that one may be checked against the other.

The oscillator described may be operated from any power supply. However, leads to an external power supply may be sensitive to body-capacity effects unless bypassed effectively.

A better arrangement is a self-contained pack composed of two 67½ volt. Minimax batteries and five flashlight cells. Five cells are used because the voltage drop caused by the tube current brings the net voltage down to about six and one-half volts.

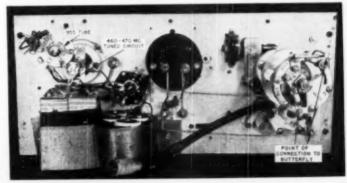Rear panel view showing how components are mounted direct to the panel.





HE search for quality and the natural, distortion-free reproduction of music and sound is a never-ending one. When it is made by way of phonograph records, present technical thinking puts its finger of suspicion on the ends of the chain, namely on the pickup and the speaker. The next most suspected link is the preamplifier. There is good reason to believe that amplifiers can be made to a high degree of perfection.

The function of the pickup is to take the mechanical energy supplied by the record, in conjunction with the turntable drive, and transform this energy pattern into an electrical energy image. Many a pitfall lies right at this point in the shape of the groove of the record, the record material, its linear speed under the needle. the shape of the needle tip together with its force on the record, the compliance of the pickup and in many other factors which have been discussed extensively in the technical literature. While much could be said about these things, they all add up to the degree of perfection with which the stylus is coupled dynamically to the groove. If we can assume, for the sake of making progress in our query. that this coupling is as perfect as possible, the picture broadens out to considerations of depth of cut, line spacing, and recording characteristic of the record-and inherent response characteristics of the pickup.


The different turnover points used in record cutting are well known. The amplitude of the groove swing below this point is constant, but it tapers to smaller excursions in the higher frequency range. The graphical representation of the cutting characteristic

above the turnover point is almost a straight line, or one rising toward the higher frequency. This rise or the emphasis in the treble is almost as familiar to the music quality fans as the knowledge of the turnover point.

which exhibits a linear characteristic.

The pickup that plays the record will be either a velocity or an amplitude type transducer. Crystal pickups are approximately amplitude types. The departure from true amplitude response is created by the damping and coupling schemes necessary in the mounting of the crystal in the cartridge. An additional departure from amplitude response is caused by the mechanical impedance of the stylus chuck and stylus itself. A velocity type dynamic or variable reluctance pickup falls off in bass response because of the reduced "velocity" in the

Fig. 1. The circuit used when the pickup is polarized with a battery.

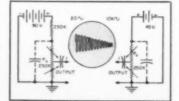

recording of bass tones. The response of this same type of pickup will also fall off in the treble because of the coil impedance increase with higher frequency-a varying impedance problem. A number of schemes have been employed in both types of pickups to improve the linearity of the type of response, some with considerable degrees of success but usually with reduced output. However, if the response of either type droops at either end of the frequency spectrum, a boost of some sort, obtained usually by an RC network, must be used to make the response flat and linear or shaped to fit a recording characteristic. The compensating network to correct a resonance is a similar problem but will not be discussed here.

The principal trouble with boosting is not easy to shape so that it perfectly corrects a non-linear output with which it works. The combination of this non-linear boost and a non-linear output seldom has a linear result. For this reason a boosted tone does not sound as good and true as a natural one. It can be considered a source of distortion. However, a poorly boosted low tone often seems to be very acceptable to a noncritical listener.

The pickup to be described here is an amplitude type of transducer with a comparatively high output level and a truly linear characteristic. If for the sake of experiment it is polarized by a battery, the response has been found to be uniform and undistorted to 20 cycles. This low frequency is easily obtained by running a Clarkstan 78 r.p.m., No. 1000 A, sweep frequency record at 33½ r.p.m. and observing the output on an oscilloscope. It will extend practically to 0 frequency, with rising output, if the mass of the cartridge and tone arm were to be increased, and a larger condenser used in the output.

The output of either circuit of Fig. 1 may be fed into a high gain amplifier if you want to listen. It is an uncorrected frequency response so the tone controls must be employed. Neither the scope nor the listening test will show any peaks or other evi-

dence of distortion.

The pickup offers a very clean signal to the preamplifier that ordinarily is used with it. This preamplifier uses a degenerative bass feedback which decreases the bass response to the "flatness" desirable. A small amount of treble boost may actually be used but great care should be exercised in the 10,000 cycle region. It is near that free ency that most of the steady hissing type of surface noise from the record appears. Any decided boost in that region is apt to add to the over-all background noise, but some can be used if it is desired, and the signal level is high enough above that of any background component or tube noise

It is common practice to turn a gain control up to a rather high level to have the music override the surface noise. There may be some justification for this practice where the high frequency output of the pickup is barely above the general noise level. When the treble output level of the pickup is high enough, a flat response to 10 000 cycles can be used on 78 r.p.m. records; and if the sound output level is moderate, the hearing characteristics of the ear will deceive one enough to eliminate all but a trace of surface noise. This moderate loudness level does need a relatively higher level bass for the natural fullness of the tone.

In reproducing music from records the operator and listeners should recognize the fact that the various 78 r.p.m. records can be just as different as people. There is a best way to play almost any record even if you can't find it! If one record when played sounds excellent and the next one far from it, don't be in too great a rush to condemn the record, the speaker, or some other component. The trouble may well include the operator. The people who know the most about the sound reproduction chain are the last to make a sweeping statement placing the blame on any one thing. Flat treble response may not be compatible with comfortable listening on some records.

A generally desirable output characteristic from the preamplifier is one having a steadily rising bass flare of about 6 db. starting at about 500 cy-

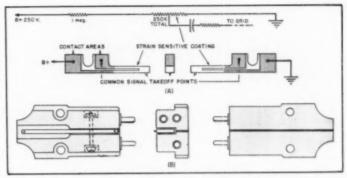


Fig. 2. (A) Active element with integral stylus. (B) Cartridge with strain sensitive element.

cles and extending to 40 cycles or lower, depending on the amount of turntable rumble that may be tolerated. No adjustment need be made for turnover point-response patterns will vary only a few db. for various recording characteristics. The rest of the range has a 1 or 2 db. drop to about 8000 cycles, where an additional tapering drop of about 2 db. to 10,000 cycles is introduced. The actual response may extend to over 15,000 cycles. This type of response with a complete absence of peaks retains the brilliance of the music with the least amount of surface noise. Surface noise is least noticeable when the response curve is smooth and free from peaks. The extended high frequency range adds much to the realism of violin overtones, triangles, and cymbal crashes. But no wishful thinking can make you hear these sounds if they are not actually recorded. The lift in the bass permits satisfactory playing of records at lower levels. It applies


Output	16 to 15 mv.
Resistance	250.000 ohms
Weight	8.3 qr.
Stylus Pressure	
(78 r.p.m.)	15-20 gr.
(33 r.p.m.)	6 gr.
Compliance	9x10-6 cm. dyne
Noise level	nil
Hum pickup	
Distortion	
Hangover	
Phase distortion	

Specifications on the strain sensitive pickup unit developed by Pfanstiehl.

an extra push to the speakers on low frequencies where they usually need help. The pickup will respond cleanly to well over 20,000 cycles when it is driven by an inverted recording head.

The active element of the pickup (Fig. 2A) being discussed is built up on a plastic rectangular cantilever beam, carrying the stylus near one end, and firmly held in the cartridge at the other end. The strain sensitive material, principally carbon, is coated (Continued on page 124)

Fig. 3. Preamplifier used with pickup. Switch S, enables the pickup to be used either double or single sided. S, selects the single or two stage output of the preamplifier.

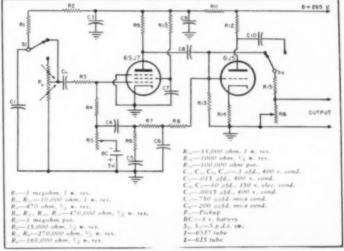



efficient multi-band antenna for the amateur.

N THIS era of multi-element rotary beams, stacked arrays, squashed cubicle quads, and other catch-named antennas, it may be re-assuring to realize anew that a single-wire antenna properly connected to a receiver or transmitter still works well. The degree of its performance depends greatly upon how efficiently it is connected.

Being a more than one-band opera-

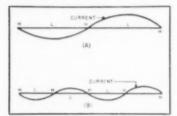


Fig. 1.

tor, the author some months ago dreamed and figured at considerable length on just how to feed a long, high-wire antenna so that it could be used on two or more harmonically-related bands, using a flat or untuned feed line, and still maintain efficient matching of feed line to both antenna and transmitter or receiver. One cold, early dawn the subconscious mind awakened the outer man, and several curves were hastily drawn, resulting in a very simple yet conclusive answer to how the problem could easily be resolved.

Perhaps at your amateur station location, you have some means of supporting in the clear a single piece of wire 68 feet long and would be interested in erecting in this available space a highly-efficient yet very simple antenna at but little cost. Or maybe you are starting from scratch and desire an effective sky-wire whose erection requires very little technical and structural knowhow and one that

is inexpensive to build. If you fall in either of these categories or simply would like to try something a little different in the way of an antenna, then the one described herein should interest you.

### Theory


A piece of wire 68 feet long and in the clear will resonate at approximately two half-wavelengths on 14.25 mc. and four half-wavelengths on 28.50 mc., according to the accepted antenna formula. The characteristic cloverleaf horizontal pattern of radiation makes such a piece of wire desirable as a general coverage radiator. If such an antenna were fed with a non-resonant line, and no electrical adjustments to it or the antenna were required when tuning up or changing operating bands, then you would have the most simple and convenient antenna conceivable.

Such an arrangement becomes a reality when thoughtful consideration is given to well-known fundamental electrical characteristics of long-wire antennas and non-resonant feed lines. Fig. 1A depicts the current distribution on a 68-foot piece of open end wire operating at 14.25 mc., and Fig. 1B shows the current distribution at 28.50 mc. In any antenna a multiple of a half-wave in length, as in Figs. 1A and 1B, the impedance of the wire reaches its lowest value at each current loop (point L) and its highest where the current almost equals zero (point H). Theory and practice establish the fact that at the end, or high impedance point, the value is approximately 3600 ohms, and at the center, or low impedance point, approximately 72 ohms. Fig. 2 shows the values of impedance of a resonant half-wavelength of wire plotted against physical length. It is to be noted that the curves cross one another at a common point which corresponds to 265 ohms impedance at a distance of 11 feet, 4 inches from one end.

Accordingly, the conclusion is reached that a single piece of antenna wire 68 feet long can be fed 11 feet, 4 inches from one end by a 265 ohm, non-resonant feed line and operated on both 14.25 mc. and 28.50 mc. with perfect transfer of energy to the system. Because height above the ground and proximity of nearby objects affect the electrical characteristics of any antenna to some degree, the common impedance value of 265 ohms in the described system can be considered as 300 ohms for all practical purposes, and the 11 foot, 4 inch dimension shall be considered as 11 feet, even.
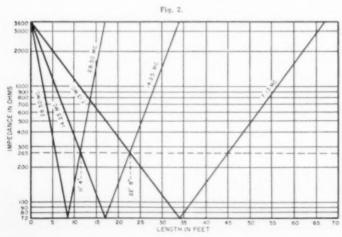
### Construction

On that basis, the author cut a 68foot piece of antenna wire 11 feet from one end and connected in series thereto a 300 ohm, twin-lead ribbon of random length, long enough to reach the operating position in the station. To provide a structurally and electrically sound means of making the connection of the feed line to the antenna, (Continued on page 70)





### Part 22. A continuation of the discussion on automatic frequency control systems used in television receivers.

AST month we investigated the operation of a sine-wave automatic frequency control system which utilized a reactance tube. Another approach to automatic frequency control of the horizontal sweep oscillator is the system shown in Fig. 1. A frequency discriminator, consisting of two diodes (V., and V.,), receives a saw-tooth voltage from the horizontal sweep system and sync pulses from the incoming signal. The two voltages are compared as to frequency and any existing difference produces either a positive or negative voltage at the grid of V. These changes are amplified and then transferred to the multivibrator whose frequency is changed accordingly.

In detail, the automatic horizontal frequency control network functions as follows: The incoming horizontal sync pulses are transferred by means of  $T_1$ to the two diodes,  $V_{\rm th}$  and  $V_{\rm th}$ , with the polarity as shown in Fig. 1. The top end of the secondary of  $T_1$  develops a positive pulse voltage and the bottom end a negative pulse. The positive pulse causes  $V_{ii}$  to conduct, and the negative pulse at the cathode of  $V_{\rm cs}$ causes this tube to conduct too. The current flowing through Via charges condenser Ci to approximately the peak value of the applied pulse while the current flowing through Vin charges C. The polarity of each voltage is indicated in Fig. 1. During the interval between pulses, each condenser discharges, the electrons moving from C, down through R, and R, to C, and from the other plate of C, through the secondary transformer winding back to C. The discharge is slow and the voltages developed across R, and R, prevent V, and V, respectively, from conducting until the arrival of the next pulse.

built by L. Poirier of Quebec.


Feeding into this same circuit is a saw-tooth voltage which is developed across C<sub>1</sub> from pulses which are applied to it from the secondary of the horizontal output transformer. The saw-tooth voltage possesses the same frequency as the horizontal sweep oscillator since the oscillator drives the

horizontal output amplifier. The saw-tooth voltage is applied in equal measure to each tube; this means that the plate of  $V_{10}$  and the cathode of  $V_{10}$  receive the same polarity saw-tooth voltage at the same time. Thus, at the discriminator, we have all the ingredients needed to check the operating frequency of the horizontal oscillator against the frequency of the incoming rulses.

The comparison of the two frequencies occurs only at the instant the syncpulses arrive, for it is only at this moment that V<sub>is</sub> and V<sub>is</sub> conduct and therefore are in a position to respond to the saw-tooth voltage. As in the previous a.f.c. circuit, three situations are possible.

First, if the syne pulses arrive at a time when the saw-tooth wave is passing through zero, then current will flow through V<sub>10</sub> and V<sub>10</sub>, recharging C<sub>1</sub> and C<sub>2</sub> for any voltage that they may have lost during the interval between pulses. This flow of current will remain within the branch of the circuit formed by the two tubes and the secondary of T<sub>1</sub>. No voltage will appear between point A and ground to

Fig. 1. A saw-tooth automatic frequency control system.

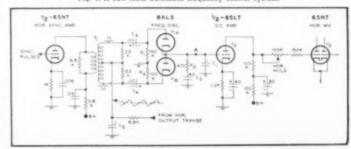

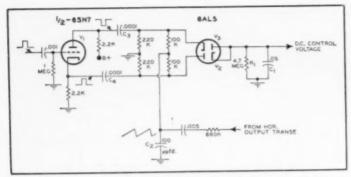


Fig. 2. A frequency discriminator that is widely used with saw-tooth a.f.c. systems.

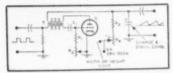


Fig. 3. The frequency of this sweep blocking oscillator is determined primarily by the values of components, C., R., and R.

affect the d.c. amplifier, V<sub>n</sub> and through this, the horizontal multivibrator. Actually this represents the desired condition since it indicates that the frequency of the sweep oscillator and the sync pulses are in step with each other.

The second situation arises when the sync pulses arrive and the saw-tooth voltage is positive at this moment. Under this condition  $V_{ii}$  will receive a positive pulse and a positive saw-tooth voltage.  $V_{ii}$  will conduct more strongly than usual, with current not only charging  $C_{ii}$  but also charging  $C_{ii}$  and  $C_{ii}$  since electrons are flowing from the region A through the cathode to plate of  $V_{ii}$ . This will establish a voltage at point A which is positive with respect to ground.

At the same moment that V<sub>is</sub> is conducting more strongly, conduction through V<sub>is</sub> is reduced because the positive saw-tooth voltage partially offsets the negative sync pulse applied to

the cathode of  $V_{iB}$ . Since the current flow through  $V_{iB}$  is reduced instead of increased as it is through  $V_{iB}$ , it cannot offset the positive voltage at point A. This potential, applied to the grid of  $V_{iB}$ , causes the current through  $V_{iB}$  to increase, driving the plate of this tube more negative. Since the grid of the horizontal multivibrator is connected to the plate of  $V_{iB}$  it, too, becomes more negative, thereby altering its frequency. In this instance, the change is toward a lower frequency.

The third situation occurs when the pulses arrive and the saw-tooth voltage is negative. Now, V<sub>n</sub> conducts more strongly than V<sub>ct</sub>, its current flowing not only into C<sub>n</sub> charging it, but also charging C<sub>n</sub> and C<sub>n</sub> since electrons will flow from cathode to plate of V<sub>in</sub>, producing an excess of electrons and so a negative voltage at A. This reduces the current flow through V<sub>i</sub> and acts to speed up or raise the frequency of the horizontal multivibrator.

Filter R<sub>0</sub>, C<sub>1</sub> and C<sub>2</sub> responds only to slow changes, thereby preventing fast acting noise pulses from affecting the operation of the multivibrator. A horizontal output amplifier receives the peaked deflection voltage from the multivibrator, amplifies it, and uses this voltage to drive a high-voltage rectifier (8016), and the horizontal deflection coils. A tuned circuit in the cathode leg of the multivibrator (not shown) is resonant to 15,750 cycles and

serves to further stabilize the operation of this unit at this frequency.

D.C. Control of Oscillator Frequency. In the first a.f.c. system discussed, the d.c. control voltage from the discriminator was applied to a reactance tube and this, in turn, varied the sweep oscillator frequency. In the present a.f.c. system, the d.c. control voltage developed by the sync discriminator is used directly to alter the frequency of the horizontal sweep oscillator. This direct method of frequency control is reacily adapted to multivibrators and blocking oscillators.

To understand what happens when the d.c. control voltage is applied directly to an oscillator, consider the operation of a blocking oscillator.

The length of time a blocking oscillator is cut off is determined primarily by the time constant of the grid circuit. See Fig. 3. When the grid resistor and condenser values are high, the charge accumulated across the grid condenser diminishes slowly and the tube is kept cut-off for a longer period of time. When the values of these components are low, the cut-off interval of the tube is shortened accordingly.


Now, if we raise the negative bias on the grid (by adding a negative voltage from some external source), then we can see that reaching the cut-off bias value of the tube, using the same grid resistors and condensers, will require a longer time than if no such negative voltage had been added to the circuit. And if the tube is kept cut off for a longer period of time, then obviously the frequency generated by this oscillator will be lower.

On the other hand, injecting a small positive voltage on the grid of the oscillator will decrease the total negative voltage developed here by the circuit operation and permit the tube to return to conduction sooner. The result: Generation of a higher frequency. It is precisely in this manner that the d.c. control voltage developed by this sync discriminator circuit varies the frequency of the sweep oscillator. While only the action of a blocking oscillator has been analyzed, the reasoning for a multivibrator is quite similar.

Circuit Variations. There are several variations of the foregoing sawtooth a.f.c. circuit that find extensive use in current television receivers. One of these is shown in Fig. 2. The incoming sync pulses are fed, in equal amplitude but opposite polarity, to two diodes, V, and V. The plate of V, receives a positive horizontal sync pulse at the same time that the cathode of V is receiving a negative sync pulse from Vi. Due to the polarity of these pulses, both diodes will conduct at this instant, with the current flowing around the circuit to charge the sync pulse coupling condensers. C, and C, The charge developed across each of these condensers will prevent  $V_i$  or  $V_i$ from conducting until the arrival of the next sync pulse.

In addition to the sync pulses,  $V_1$  and  $V_2$  also receive a saw-tooth voltage

Fig. 4. A variation of the automatic frequency control system shown in Fig. 2.

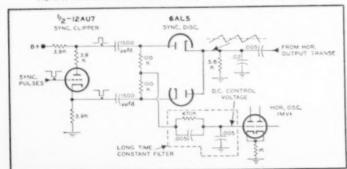

from the horizontal sweep amplifier. As in the previous system, the sawtooth wave will be going through zero at the time the sync pulses reach  $V_1$ and V, if the frequency of the horizontal sweep oscillator is properly synchronized to the incoming pulses. If a frequency difference exists, the sawtooth voltage will not be going through zero when the sync pulses arrive. If the saw-tooth voltage has some negative value at this instant, V, will conduct more strongly than V: and a negative resultant voltage will appear across  $C_1$  and  $R_2$ . (A negative sawtooth voltage favors  $V_1$  because this voltage is applied to the cathode of the tube.) The negative voltage across C. is then passed on to the following sweep oscillator, changing its point of operation and consequently, its frequency

By the same token, arrival of the sync pulses when the saw-tooth voltage is positive will cause  $V_1$  to conduct more strongly than  $V_n$  producing a resultant positive voltage across  $C_1$ . (A positive saw-tooth voltage favors  $V_1$  because it is being applied to the plate of this tube.) The effect on the sweep oscillator of the positive voltage across  $C_1$ , will be opposite to that produced by a negative voltage.

C, and R, form a fairly long timeconstant filter, permitting only the voltage variations due to differences between the frequency of the sync pulses and the saw-tooth voltage to develop here. Momentary voltage variations due to noise pulses are effectively suppressed.

The d.c. control voltage obtained from C, could be applied directly to the horizontal sweep oscillator and in some receivers, it is. On the other hand, a more sensitive arrangement is obtained when the d.c. control voltage is amplified before being applied to the horizontal oscillator.

Variations of this circuit, as used by such manufacturers as Bendix, Emerson, Garod, General Electric, Hallicrafters, Tele-King, United States Television, etc., consists primarily in the means of applying the saw-tooth voltage to the discriminator. The circuit shown in Fig. 2 represents one method; the circuit of Fig. 4 illustrates another approach. In either case, circuit operation is the same.

Troubleshooting Saw-Tooth A.F.C. Systems, Examination of the saw-

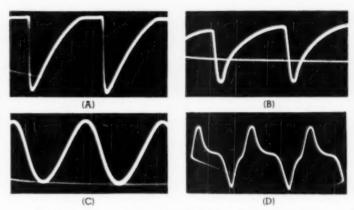


Fig. 5. Typical waveforms in the a.f.c. circuit of Fig. 6. (A) At pin 7 of  $V_1$  (30 volts); (B) At pin 5 of  $V_1$  (20 volts); (C) At control grid of  $V_1$  (52 volts); and (D) At the input of the horizontal discharge tube (80 volts). All voltages are peak-to-peak.

tooth a.f.c. system will reveal that it contains no controls other than the horizontal hold control. In this respect it is superior to the previous sine wave system where there existed two additional controls besides the horizontal hold potentiometer. Due to the simplicity of the circuit, failure of the system to operate properly can only mean a defective component. With the aid of an oscilloscope, the two pulse voltages and the saw-tooth voltage reaching the frequency discriminator diodes can be readily checked. To determine whether a d.c. control voltage is being developed at the output of the discriminator, connect a vacuum-tube voltmeter across the output, between point A and ground of Fig. 1. Set the meter to the lowest voltage scale pos-Now slowly rotate the horizontal hold control. If the saw-tooth voltage reaching the discriminator is being received properly, the meter needle will move back and forth. By the same token, switching the set to an unused channel (generally this is the next one on most sets) will cause the meter reading to decrease. In some sets the meter reading will decrease to zero: in other sets some small voltage will remain in this portion of the circuit. If either of these indications : (but not both) are absent, it indicates that the saw-tooth or pulse voltages are not reaching the discriminator

diodes. If both indications are lacking, the trouble exists in the diode circuit itself.

Where d.c. amplifiers are inserted between the discriminator and the horizontal oscillator, the foregoing voltage variations should be checked in the grid and plate circuits of the d.c. amplifier tube. The variations in the plate circuit should be greater than those observed in the grid circuit.

The hold-in range of the horizontal hold control, when the system is operating properly, is slightly less than that experienced with sets employing the sine wave a.f.c. system. In most sets, if the hold control can be varied through an arc of 90 degrees without forcing the circuit to lose sync, then the set is operating normally. In common with the previous sine wave system, the hold-in range is greater than the pull-in range. This is most noticeable when the set is first turned on.

A final servicing point regarding this particular circuit is the criticalness, in some designs, of the resistor values in the plate circuit of the d.c. amplifier. If these change to any appreciable extent, it may be impossible to bring the oscillator into sync. Check the values of these resistances against their marked or stated value.

Combination A.F.C. System. There is a horizontal a.L.c. system in use which combines both the saw-tooth and the

Fig. 6. A horizontal sweep system which utilizes a combination of saw-tooth and sine wave automatic frequency control. The phase relationships of this control circuit are shown in Fig. 7.


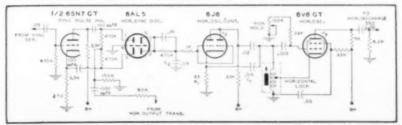


Fig. 7. Phase relationships in control circuit of Fig. 6.

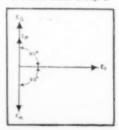

sine wave systems. This system is used in Admiral Model 30A1 sets. It consists of a horizontal sync discriminator, a reactance tube, and a Hartley oscillator. A long-time constant RC filter is inserted between the sync discriminator and the reactance tube to permit only the slow changes in sync pulse timing (if any) from altering the frequency of the Hartley oscillator.

The entire a.f.c. circuit, in detail, is shown in Fig. 6. The two diodes of the horizontal sync discriminator, V, are pulsed into conduction by a set of oppositely phased pulses received from the plate and cathode circuits of the preceding sync pulse amplifier. These same diodes also receive a saw-tooth voltage from the secondary of the horizontal output transformer. The circuit operation, thus far, is identical to the horizontal discriminator employed in the saw-tooth a.f.c. system. The amount of voltage developed across C: and its polarity will depend upon the phase relations between the saw-tooth voltage and the incoming sync pulses. This correcting voltage, for that is what it is, is applied to the horizontal oscillator control tube, Vz.

The triode reactance tube is connected across the tank circuit of the horizontal sweep oscillator, V.. At the same time, the series network of C, and R. is connected across this same resonant circuit, receiving the full 15,750 cycle voltage and consequently having a 15,750 cycle current flow through it. The value of  $C_{*}$  (0.015  $\mu$ fd.) is so chosen that it dominates the impedance of this network, thereby causing the current that flows through this series network to lead the applied a.c. voltage by nearly 90 degrees. This current flowing through R, produces a voltage here which also leads the tank circuit voltage by the same 90 degrees.

This voltage variation across the cathode resistor has the same effect on the tube current flow as a voltage on the grid of the same tube which is 180 degrees out-of-phase with the cathode voltage. This is characteristic of all conventionally operated tubes. A positive voltage, for example, applied to

the cathode will have the same effect as a negative voltage applied to the grid, because both will cause the tube current to decrease.

Perhaps the best way to visualize the phase relationships in the control circuit is to employ a vector diagram. This is done in Fig. 7. For reference, the voltage present across the sweep oscillator tank circuit is chosen. This is labelled E .. The voltage across the cathode E, leads this voltage by 90 degrees, as determined above. The grid voltage of the control tube,  $E_s$ , is 180 degrees out-of-phase with this cathode voltage. I, of the control tube is inphase with  $E_s$  and is indicated so. We note, then, that I, lags the sweep oscillator voltage by 90 degrees and since this current will pass through this tank circuit, it will cause V1 (from whence  $I_{\pi}$  comes) to appear as an inductance placed in parallel with the tank inductance. As the current through V, varies, due to changes in the voltage it receives from the sync discriminator, I, will vary, thereby varying the frequency of the horizontal sweep oscillator and forcing it to remain in step with the frequency of the incoming sync pulses.

Horizontal Oscillator Adjustment. If it is difficult to hold the picture in horizontal sync, the procedure for adjustment is as follows:

 Turn horizontal hold control (which is located at the front of the chassis) to the extreme counter-clockwise position.

Adjust the iron core of the horizontal tank circuit coil until the pattern falls out of synchronization.

Then turn this core until the pattern just falls back into synchronization.

4. Turn the horizontal hold control fully clockwise and turn the channel switch to the next highest channel. and then back to the original channel. The test pattern or image should return in synchronization. Should the pattern be broken up, slowly turn the horizontal hold control counter-clockwise until the picture just falls into sync. It should not be necessary to rotate


this countrol more than 25°, to obtain synchronization. If a greater percentage of rotation is necessary, trouble is indicated in this circuit. Typical waveforms present in this circuit, when the set is operating properly, are shown in Fig. 5.


Vertical A.F.C. System. For most normally operated television receivers, automatic frequency control of the vertical sweep oscillator is not required due to the presence of the long time-constant filter which invariably precedes this section of the receiver. However, when a set is to be operated in a fringe area, where the level of the signal is low, a.f.c. networks in the vertical system are sometimes employed. One such circuit is shown in Fig. 8. It is seen to be similar to the circuit of Figs. 1 or 2, with a saw-tooth voltage derived from the retrace pulses appearing at the plate of the vertical output amplifier, and incoming vertical sync pulses applied by the first tube. These two voltages are compared as to frequency in the 6AL5 sync discriminator. Any difference in frequency produces a voltage at point A which is amplified by a triode (12 of 12AU7) and then applied as a regulating voltage to the vertical blocking oscillator.

Throughout the circuit, the time constants of the various resistance-condenser networks have been length-ened considerably over their counterparts in the horizontal automatic frequency control circuits. The operating frequency of the vertical sweep system, 60 cycles, is approximately 262 times lower than the operating frequency of the horizontal sweep system and the time constants of the RC networks are increased by roughly the same factor.

One final word about this particular circuit (Fig. 8). The vertical output tube, a 6AQ5, is being used here as a triode. This lowers its plate resistance and permits it to act as a partial damper across the vertical deflection coils, reducing the ability of any shock-excited oscillations in the coils to exist for more than a cycle.

(To be continued)

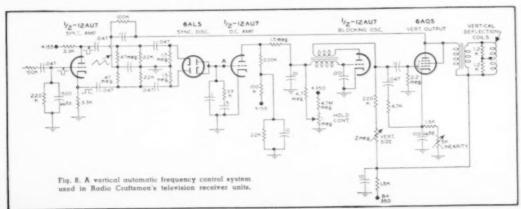

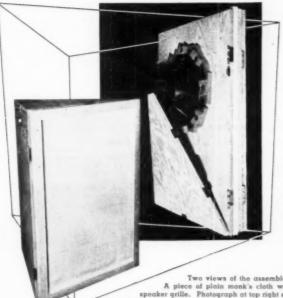

### A COLLAPSIBLE SPEAKER **CABINET**

MICHAEL WOLFE

Details for constructing a handy speaker housing which may be used as a portable unit with temporary p.a. installations.

Two views of the assembled baffle unit. A piece of plain monk's cloth was used as a speaker grille. Photograph at top right shows the unit collapsed and method for mounting speaker with gaskets.

NE of the basic characteristics of present-day moving cone loudspeakers is the necessity for some form of baffle arrangement to prevent the out-of-phase radiation from the rear of the loudspeaker from canceling the signal from the front. For the higher frequencies, this problem is not severe as a baffle of relatively small dimensions is usually sufficient, but for adequate low-frequency response a baffle or enclosure of considerable dimensions is often required.

To the operator of high quality pubaddress or sound reinforcement systems, the bulkiness of conventional speaker enclosures may represent a considerable problem from the standpoint of transportation. In many instances a compromise is made in the form of a small, open-backed enclosure slightly larger than the speaker. The low-frequency efficiency of such an arrangement is often very poor and often requires bass boost and treble cut to provide pleasing balance. For more critical applications the bass reflex enclosure is a common choice giving greatly increased low-frequency efficiency. In instances where high quality and high power are desired the corner radiator, which uses the walls of the room as portions of a folded horn, appears to be attaining increased popularity but suffers from the inherent limitation of spatial loca-

The collapsible baffle described in this article was developed primarily to fit the needs of a small orchestra playing many different engagements, often in private residences where adequate sound distribution in adjoining rooms


was desired. The problem was to build an enclosure capable of wide range reproduction and yet have it of sufficiently small dimensions to fit in an automobile trunk or rear seat. solution was to construct a baffle of fairly conventional design and provide for demountable sides, thus giving a substantial saving in volume during transportation or storage.

Dimensions of the baffle are given in Fig. 1. All sides are constructed from one-half inch, five-ply plywood to provide a fair amount of rigidity without too much weight. In the equipment shown, assembly is made through use of hinges with removable center pins. It requires the removal or insertion of eight pins to take down or assemble the unit, four pins at the front and four pins for the top, the two sides folding together. The design shown is for simple construction without need for special tools, however, the experienced woodworker with a shop at his disposal should have little difficulty in improving upon the construction. For instance, if beveled edges and inset hinges are used it is possible to have the cabinet fold together as one unit instead of three separate sections.

Although good results may be obtained by following the plans shown, many constructors may find it desirable to adapt the idea of a collapsible structure to their own particular requirements and as a result, a discus-

(Continued on page 146)

Fig. 1. Dimensions and layout of the collapsible speaker baffle. One-half inch. fiveply plywood is used throughout. All hinges have removable center pins. Side hinges should be mounted so that the center pins can be inserted from the top of the unit.

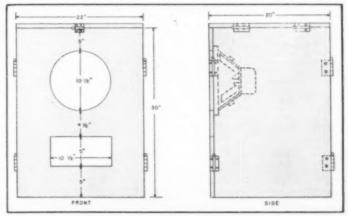

## Mountain Top TV CITY

By CHARLES D. PERLEE

California's Mt. Wilson, once famed as the home of the 100-inch telescope, is gaining an even wider reputation as a TV and FM transmitter site for Hollywood stations.



OUTHERN California's Mt. Wilson, long famed as the home of the 100-inch telescope, has lost some of its importance as an astronomical center with the installation of the 200-inch telescope at Palomar Mountain, also in Southern California. However, Mt. Wilson, almost 6000 feet high and close to the Southwest's center of population—Los Angeles, Pasadena, Glendale, etc.—is not playing second fiddle to Palomar even though Palomar is practically perfect for stargazing because of the clearer atmosphere.

With the advent of television, Mt. Wilson has become the world's largest center of video transmissions. Television programs originate in Hollywood but they are beamed to Mt. Wilson 18 miles away. By transmitting from Mt. Wilson it is estimated that the programs can reach 500 per-cent more listeners than could be served if the programs were beamed directly from Hollywood. The Mt. Wilson transmitters, located 5000 feet higher than Hollywood, telecast Milton Berle and other TV favorites onto screens in homes up to 100 miles away. This means a potential audience of 6,000 -000 in Hollywood's primary service area within the next decade.

As of October 1st the Los Angeles area's seven television stations were programming for an estimated 213,000 video screens in Los Angeles, and its neighboring cities.

Although the major emphasis has been placed on television transmissions from Mt. Wilson, other services are sharing this advantageous location. Both FM and mobile radio-telephone material is handled by these mountain top transmitters. At present there are six TV and several FM transmitters in operation at the "Mountain Top TV City," but 21 other sites have been leased or purchased, the FCC having approved a total of 27 licenses. Six other transmitters are now under construction at Mt. Wilson. In addition to the 27 licensees, 13 other television and/or FM broadcasters are jockeying for positions on this crowded mountain peak.

Earle C. Anthony, pioneer car dealer and long-time owner of station KFI, believes in the future of TV and FM broadcasting so wholeheartedly that he has purchased an entire mountain, Mt. Harvard, sister peak to Mt. Wilson, for his long-range expansion pro-

Mt. Wilson, once a quiet astronomical center and the goal of nature-loving hikers and motorists, is now a bustling "city." Buildings and antenna towers have sprung up all over the mountain top. Lumber-, cement-, and equipment-laden trucks make a steady roaring parade along the 30-mile route, of which famous Angeles Crest Highway is a part, from Los Angeles to Mt. Wilson.

The intricate "brains" of Television

City are housed in the huge rock building of the Pacific Telephone and Telegraph Company. Through this headquarters goes the cable from all of the stations in Hollywood. The building also houses the "eye" for the new mobile telephone system. Transmissions from automobiles operating in the vicinity of Los Angeles are picked up by a station located at Griffith Park Hills. From this point the message is beamed to Mt. Wilson and then to Mt. San Jacinto, the peak which overlooks Palm Springs, and from there to the home or office of the called party. Voices of motorists can now be heard exceptionally well on long distance calls and a decided improvement in transmission quality has been effected due to the high mountain beaming.

Mt. Wilson even with a Television City on top hasn't changed much. The score or more of new buildings are appropriate to the surroundings although the antenna towers, parabolic receivers, and radar-like transmitters do provide a startling contrast to the Ponderosa pines and big-cone spruces. The famous old Mt. Wilson Hotel still looks as it did 30 years ago, while nearby the six telescopes and sun towers of the Carnegie Institute's Observatory are still the scene of stellar discoveries and daily computations. The hotel's A. C. Childs gives his nightly astronomical lecture, although he now extends his remarks to include the newer wonders of TV and FM.

The peak's herd of 30 mule deer hasn't been frightened away by this new invasion of their domain and they and seven species of birds and a large congregation of gray squirrels are still getting their free meals of ginger snaps, fruit, and peanuts from visitors. This is one place where wild animals still have complete faith in humans and so far their faith hasn't been misplaced.

Mt. Wilson's human population is growing by leaps and bounds. There is often so much snow in this area that autos cannot traverse the slippery, precipitous roads. To eliminate this necessity, radio engineers and their families are now being housed right at the transmitter sites. It may be hard for Easterners to believe that Southern California can be the scene of devastating snowstorms but Mt. Wilson often receives as much as 30 inches of snow in a single storm. The TV people learned their lesson last winter when they didn't have engineers on duty 24 hours a day. A heavy storm hit the area, the snow piled up to over three feet, lightning struck and blew out the power system, and the

engineers were snowbound at the bottom of the mountain! Video screens and FM sets in hundreds of homes were blank while engineers were scrambling peakward with dogsleds, snowshoes, and skis. That situation won't arise again. Engineers now live right at the transmitters 24 hours a day,

Thus a new and specialized "city" is growing up, 6000 feet above sea level and within easy driving distance of Los Angeles and its tremendous television market potential.

-30-

Over-all view of "TV City." This concentration of transmitters means improved reception for set owners. A single antenna oriented in one direction covers all broadcasts.



Part of the telephone company's relay setup for mobile radiophone service. Messages are relayed from Griffith Park Hills to Mt. Wilson, thence to Mt. San Jacinto.

Two of the antennas on Mt. Wilson. TV unit (left) and FM tower (right) are each 199 feet high.



KNBH. NBC's Hollywood outlet shown during construction at Mt. Wilson. This \$150.000 station is now on the air daily.



Mt. Wilson's "younger set," children of resident radio engineers, pose beneath KTLA's giant parabolic TV receiving horns.

A close-up view of Mt. Wilson's "TV City" showing the seven TV and FM towers already installed. This number will even tually reach 27 when all of the stations licensed by the FCC for this area go on the air. Television stations KTTV, KNBH, KECA TV, KFLTV, KTLA, and KLAC are now transmitting regularly from Mt. Wilson. KTSL, which is now transmitting from Hollywood, will soon have facilities at Mt. Wilson location.



THE icy February wind carried little invitation to loiter in the great out-of-doors; and Mac, back from lunch, stepped right briskly through the door of his radio service He was greeted by Miss Perkins, the office girl, with an admonishing finger raised to her lips in what was definitely a "shushing" gesture. With the other hand she pointed dramatically to a crudely scrawled placard fastened with Scotch Tape to the closed door of the service department.

### QUIETI INVENTOR AT WORK!

Wondering what devilment his redheaded apprentice was up to now, Mac tiptoed across the room and soundlessly inched the door open. There at the bench sat Barney, his elbows planted on each side of a diagram-covered sheet of paper in front of him-Both of his bony hands were tightly clenching handfuls of his sorvel thatch, and his freckled face was screwed up in a look of agonized concentration. Upside down on the bench at his left was the chassis of the tube checker which had been removed from its case

"I hate to disturb you, Mr. Inven-Mac said softly; "but why is the tube checker lying there with its inner workings so immodestly exposed to the vulgar public gaze? Something the matter with it?

Barney slowly turned around to confront Mac with the glazed eyes of a sleepwalker. "Oh no," he said dreamily; "I was just looking to see- Say!" he suddenly exploded as his eyes focussed on Mac's face, "I've got it! I've

Yes, I rather suspected all along

that you had it," Mac said soothingly; "but we will keep it a secret between just us two. No one else need ever know. Most of the time you act perfectly normal-

"I mean I have just discovered a marvelous invention," Barney interrupted impatiently.

'A plastic coating on an all-day sucker to make it last two whole days, perhaps?" Mac hazarded.

Before replying Barney carefully shut the door of the service room and thrust a twisted bit of paper into the keyhole. Then he approached Mac and triumphantly announced in a hoarse conspiratorial whisper that could be heard out in the street: "A self-service tube checker!

"Oh no! Not that!" Mac cried in quick alarm. "We have enough trouble now patching up the sets that customers have tried to fix themselves without being forced to stand here helplessly and watch them burn out their own tubes.

"But that is just the point. My tube checker is foolproof.

"Even against the cute helpless little woman who simply can't understand why she can't get John's Other Wife when the bandswitch is in the short-wave position?" Mac challenged.
"Even against her," Barney boasted.

"This checker has no switches to throw. no dials to turn. All you do is take

that card into a slot in the checker. When the card is pushed clear in, a pilot lamp lights up behind the right socket. You simply put the tube into that socket and watch the meter hand to see if the tube is 'good,' 'bad,' or 'doubtful' "Sounds wonderful-too wonderful," Mac said skeptically. "How does it work, with atomic power?"

"Nope; the secret of the whole thing lies in several little holes punched in exactly the right places in the card. When this card is pushed home in the slot, several rows of spring-actuated 'fingers' rest against it. The holes in the card allow the rounded ends of certain of these fingers to drop into them. The movement of these fingers opens or closes contacts that do the same things you do on an ordinary checker by throwing switches and twisting

"Hm-m-m," Mac hm-m-m-ed, beginning to show some genuine interest. "How are you going to replace the variable resistors?"

"By using a multi-tapped resistor with the taps being connected to one row of the fingers," Barney answered promptly.

"But the wrong fingers will be dropping into the holes as the card is slid in or pulled out. Won't that cause trouble?"

"No, because only the very last thirty-second of an inch of travel of the inserted card turns the checker on. The instant you start to pull the card out the instrument is automatically turned

"Just think of the advantages!" Barney rushed on. "When the customer can test his own tubes, he will feel confident he is getting an honest check. You get his business without having to lese time checking his tubes. Keeping the checker up to date is as easy as pie. When a new tube comes out, all you need is a new card. The checker will be fine insurance against the mistakes that even servicemen make now and then in operating tube testers. Think what a boon it will be to busy clerks in radio stores. Why it will-

"Whoa there, Nelly! Slow down!" Mac commanded. Then he went on more gently: "Red, it could easily be that you have yourself a good idea there; but before you get too excited. try sleeping on it. Wait and see how it looks in the morning. Then, if it still looks good, go ahead. I'll help you all I can. But what ever started you on this inventing binge in the first

"You know old man Porter, the retired railroader who lives on Bethel Street?

"You mean old 'Packrat' Porter who boasts that he never throws anything

"The same! Well, he brought down a market-basket full of old tubes for me to test right after you left. There (Continued on page 105)

Fig. 1.



CUSTOM VIDEO Has Built-In BOOSTER

Details covering an interesting new high-performance set which features adjustable sensitivity.



### By CLARK E. JACKSON

HE trend in current television receiver design has been predominantly along the lines of streamlining in order to reduce the number of tubes in the receiver, a skimping and saving of component parts, reduction in chassis size and any other short cuts that would reduce manufacturing costs. As a result, the average purchaser of a television set is able to enjoy video programs at far less cost than a year or two back. However, there remains a very lush market for the aggressive television technician and dealer who gives equal attention to those who can afford and do demand something better than run-of-the-mill television. One answer to this demand can be found in a television chassis incorporating many features not found in conventional sets and designed especially for the discriminating cus-

By using finest quality components and by utilizing time-tested and proven circuits, in addition to many other special features, this set is ideally suited to custom installation and for use in fringe areas, due to its extreme sensitivity.

As a matter of fact the sensitivity of the set compares favorably with most television receivers that use separate high gain boosters, but instead of requiring two separate units the sensitivity is already incorporated within the circuitry of this new tuner.

Excellent reception is had even up to 125 miles from television transmitters. The circuit incorporates a remarkable new automatic gain control that operates instantaneously and eliminates all noticeable flutter caused by airplanes moving as fast as 300 miles per hour. It also is capable of eliminating disturbances, such as those resulting from wind-blown outdoor antenna systems and transmission lines, or from persons moving near indoor antennas.

Reference to the diagram discloses the extent to which the design has gone. Perfect interlacing and exceptionally sharp images (extremely important for the excellent picture obtainable on large kinescopes) is obtainable under all conditions of noise by an automatic phase control of both the vertical and horizontal synchronization. Vertical retrace lines are automatically removed by a special crase circuit, which operates even in the absence of a video signal.

The original design employed four-6AG5 video i.f. amplifier tubes. The new circuit employs the specially designed 6CB6 tube. This results in even better performance than was possible with the 6AG5's.

The exceptional ability to provide perfect interlacing is perhaps the most salient feature of this circuit. It means that pictures can be seen with clarity from any usable distance. It is not necessary to employ the old formula which requires the viewer to sit at a certain distance from the picture tube face. Perfect interlacing is the answer to flexible viewing distances.


A total of 25 usable tubes, plus 4 rectifiers are utilized in this circuit. A 6AG5 r.f. amplifier, 646 r.f. oscillator and mixer, four 6AG5 video i.f. amplifiers, 6AL5 video detector and d.c. restorer, 6AU6 video amplifier.

6AR5 amplifier, three 6AU6 sound i.f. amplifiers and limiters, 6AL5 FM discriminators, 12AU7 audio output, criminators, 12AU7 audio curput, 6AU6 keyed a.g.c., 12AU7 sync clipper and separator, 6AL5 vertical sync discriminator, 12AU7 vertical control and blocking oscillator, 6AQ5 vertical output, 6AL5 horizontal sync discriminator, 6AH6 horizontal automatic phase control 6AR5 horizontal oscillayor, 12AU7 horizontal discharge and vertical phase inverter, 6BG6G horizontal output. 1B3GT high voltage rectifier, 6W4GT horizontal damper, and in addition, three selenium rectifiers and the picture tube. Any of the conventional 16" tubes may be used, 16AP4 through 16GP4.

A cathode follower audio output of 500 ohms impedance permits connection to any remote system. This consolidation with existing audio equipment eliminates wasted expense of minimum performance systems, currently included in many TV sets. (See editorial, January 1950 Rabio & Television News.) Separate sound if, incorporates a double limiter and Foster-Seely discriminator for outstanding audio fidelity.

Experience has shown a definite need for separate audio systems in custom installations. In fact they are usually preferred by the customer. The selected output of 500 ohms permits accurate impedance matching to practically any high fidelity amplifier, having an input impedance of 500 ohms or more.

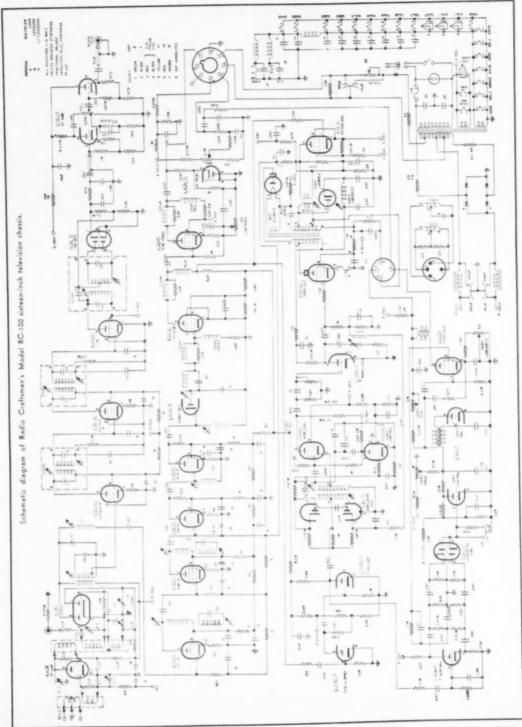Of particular interest, as will be noted by examining the photos, is the unique turret tuner design. Small cartridges, each containing essential coils, are easily slipped in and out of the turret. The tuner coil cartridges



furnished for 12 channels can be interchanged in any desired sequence for easier front panel selection, as well as being readily replaceable with u.h.f. cartridges when these channels are made available for television.

The set is capable of being tuned to receive all FM frequencies between 88 and 108 mc. by simply tuning the slugs which are a part of each cartridge. Full FM coverage is therefore possible and the technician should query his customer as to his interest in this feature.

Controls on the receiver are simplified and include only those which are essential to normal operation. They are: Off-On-Sound Volume, Contrast, Fine Tuning, 12 Channel Selector. Secondary controls are mounted conveniently for easy adjustment on the front apron of the chassis. They include horizontal hold, vertical linearity, focus, brilliance and vertical size.

The sensitivity of the video channel (measured on channel 6) is 25 microvolts or less for 1 volt at the detector. The noise figure is minus 12 db.


A new development, which adds a 10 db. video boost by shifting the position of the control knob, equals or betters the performance of external boosters. It does not in any way disturb audio reception.

The input circuit employs a 300 ohm balanced primary. Separately matched transformers for each channel are provided. This provides maximum transfer of voltage from the antenna system. The video i.f. is 26.1 mc, while the audio is 21.6 mc. The bandwidth of the video is 4 mc. and the audio 250 kc. Three volts of audio output are available at 500 ohms covering the range of 20-20,000 cycles per second, at less than 1% distortion. Power supplies provide 150 volts at 180 ma., 350 volts at 140 ma. and 13 kilovolts and 500 volts horizontal kickback.

As mentioned previously, the circuit is canable of extreme sensitivity and therefore ideally suited for fringe locations. This is made possible by five separate r.f. coils, including the individually matched 300 ohm input transformers for each of the 12 channels. Tracing the circuit shows that this is followed by six amplifying stages, to provide full four megacycle bandwidth, with negligible phase distortion. Phase controlled synchronization systems, unaffected by noise, control both the horizontal and vertical sweeps. Since the receiver is completely under the control of the instantaneous automatic gain control, itself immune to noise, further improvement is obtained in the synchronization because these circuits are always working at maximum efficiency.

The circuit, with simple additions, will handle the new 13" tubes.

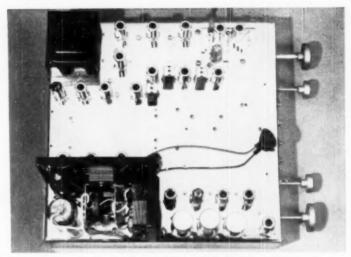One of the most unique features of the assembly is a remote tube mounting. The picture tube mount has been especially designed to make the picture tube assembly removable from




Top view of the RC-100 television chassis with the cathode-ray tube removed.

the receiver chassis for remote mounting. This is a particular advantage in custom installation. Five mounting screws hold the mount to the chassis. All connections to the picture tube are provided with plugs, so that extension cables can be made of the desired length and inserted in the appropriate sockets. Particular care should be taken with the high voltage extension. Use high tension wire capable of withstanding up to 15 kilovolts. The limiting factor in determining how far the tube can be removed from the chassis is the shunting capacity offered by the picture tube grid (green) lead. This lead should be run isolated from the cables and chassis and in general 6 to 8 feet will be found to be the maximum length permissible before highfrequency smearing results.

To achieve the very low heat dissipation necessary for mounting in confined areas, (wall installations, for example) a new selenium rectifier bridge circuit was developed. It permits the unusually low power consumption of 175 watts.

Many articles devoted to custom installation of television, radio, and audio have been published. The introduction of this new Radio Craftsmen RC-100 television receiver is certainly a step forward in the search for perfect television reception for a discriminating clientele.

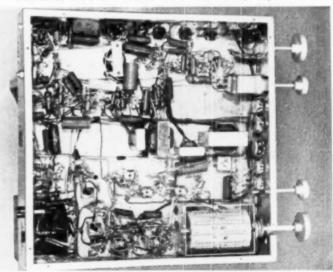Under-chassis view of receiver. Either a 16 or 19 inch kinescope may be used.





Panel view of home-built unit. Meters indicate both voltage across and the current through the load. A d.c. 50-watt resistor for direct current applications. Ideal for checking power supplies and the like.

FTEN times a good high wattage resistive load is needed around the work shop. The stocking of various values of these components would obviously be costly. Now the electronic d.c. load to be described will take care of this problem very nicely. Some of its applications are as follows:

 To check the regulation of power supplies.

 To determine the approximate value of a bleeder resistance.

As an example of its use, let us say that we wish to determine the resultant voltage of our power supply when it is delivering 120 ma. to a load. The value of resistance needed across the power supply becomes awkward to calculate, since we do not know what the final loaded down voltage will be. The usual procedure at this point is by guess and by golly; however, if we have the d.c. electronic load on hand,

the answer is simple. Merely connect its terminals to the power supply, turn the control clockwise to 120 ma., read the voltage and presto.


Reference to Fig. 1A readily shows the basic principle used in this electronic d.c. load. The bias control voltage varies the effective plate-to-cathode resistance of the tube, thus making it possible to vary the load presented to the voltage input.

In order to eliminate the bias battery, a full wave rectifier was incorporated as shown in Fig. 1B. To increase the power dissipation capabilities, four triode sections were paralleled as shown in Fig. 1C. Two 6AS7 tubes were used in this case; however, other types such as the 6L6G, 6Y6G, or the 829B would do as well. This circuit will handle a conservative 50

watts of dissipation. Fig. 2 is the final schematic diagram with its associated parts list. The additional filament transformer was needed to handle the current since the winding on the power transformer used was not quite heavy enough. The completed electronic power load is shown in the photographs. The chassis is a standard 7"x11"x2" box. On the left of the front panel is a 0-500 volt meter and on the right is a 0-500 ma. meter. In the center are the pilot light, toggle switch for the bias supply and tube filaments, along with the power control knob. The placement of components and the wiring is not critical. The rear view shows the line fuse, line receptacle, and the floating input terminals. This floating feature allows the unit to be used with either a positive or negative voltage source. It may be found more convenient to

CURRENT	VOLTAGE							
(ma.)	100 v.	200 v.	300 v.	400 v.	500 v.			
		Resist	ance in	ohms				
50	2000	4000	6000	8000	10000			
100	1000	2000	3000	4000	5000			
200	500	1000	1500	2000	2500			
300	333	666	1000	1333	1666			
400	150	500	750	1000	1250			
500	200	400	6.00	800	1000			

Table 1. Equivalent resistance chart.

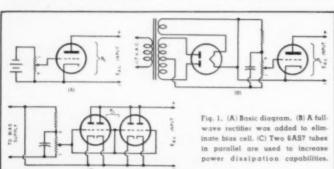

locate this terminal block on the front panel.

To stay within the safe power rating of the unit, reference should be made to Fig. 4 which shows the maximum amount of current that can be drawn at any given input voltage to the unit. This curve can be reproduced and secured to the front panel for ready reference. Temporary overloads can be tolerated if not left on for prolonged periods. Some drift in current will be noted as the 6AS7 plates heat

To save time in calculation, Fig. 3 is handy in that it shows the equivalent resistance of the power unit versus the current being drawn. Current values in the area below the dashed curve designate the region of rated power of the tubes and can be used as a precautionary boundary when taking readings.

### Applications

Checking regulated voltage power supplies becomes a pleasure rather than a task with the electronic load. In fact, the unit was designed for just that purpose. Such questions as how much current can be drawn from the regulated power supply and still have it hold its output voltage; and, what is the effect of a sudden change in the load on the supply voltage; can readily be determined. First, connect the power supply under test to the electronic load and note the voltage reading on the front panel meter. slowly increase the current through the electronic load with the bias control until the voltmeter gives a slight kick. The value of current, as read on the corresponding milliammeter, indicates the maximum current obtainable under regulating action.

Now to obtain an approximation of the effect of a transient load on the regulated power supply under observation, back down the control bias to about one-half of the maximum current just found in the above test on regulation. While watching the voltmeter, twist the control knob left and

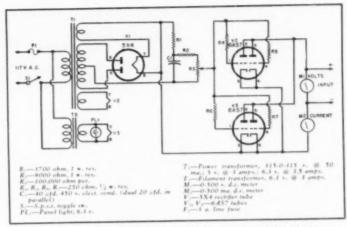


Fig. 2. Complete schematic diagram of electronically controlled d.c. load.

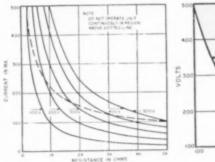


Fig. 3. Equivalent resistance value of load with given voltage and current readings.


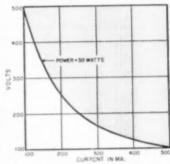


Fig. 4. Maximum current for any given voltage. Continuous overload is not advisable.

right rapidly. No change on the voltmeter indicates a favorable reaction on the part of the power supply.

For determining bleeder resistance values, connect the electronic load into the circuit as the unknown resistance and adjust the control knob until the required voltage is present on the voltmeter. Fig. 3 can then be used to find the resistance value needed and also the wattage requirement. Some spot equivalent resistances can be set up with the aid of the chart in Table 1.

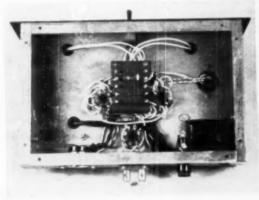Two views of completed test unit. Note particularly the neatness of all wiring and careful positioning of all components.





### International SHORT-WAVE

### Compiled by KENNETH R. BOORD

T IS a pleasure this month to dedicate the ISW DEPARTMENT to the Forces Broadcasting Service, Middle East. Our thanks for this material go to Leslie Knight, who is in charge of the station at HQ Forces Broadcasting Unit, MELF, Malta Garrison.

Mr. Knight informs me that the station is "still testing at the moment, and the object of these transmissions is to cover North Africa. The ultimate set-up in Malta will be three 7½ kw. transmitters—one for North Africa, one for Egypt and Cyprus, and one for Southern Europe.

"Our tests, as far as the coverage of North Africa is concerned, have not been as satisfactory as they might be. However, the Senior Technical Officer, Maurice Taylor, is ironing out the

troubles. "For this coverage we are using 4.782 and 7.270 on this schedule: 2330-0130, 4.782; 0430-1015, 7.270; 1200-1700, We shall, of course, be using other frequencies for the other shoots, but these have not yet been decided." (Note: More recently I have noted the Forces Broadcasting Service, Middle East, on 11.782 at 0100 with BBC news I suggest that DX-ers who fail to find the station on the frequencies listed by Mr. Knight try 11,782, 6,140, which are other channels or 4.965. tested. KRB)

It is recalled that the FBS brought many an hour's radio enjoyment in the days of World War II to members of the three British Services. Here

is the story of the development of FBS as related by Mr. Knight:

During the part of the War when servicemen were scattered in places outside the range of the BBC's domestic service, it was found that although the Overseas Short-Wave Service was good, it could not cope with the entertainment and educational needs of the serviceman. Items such

### COMING NEXT MONTH

"Around the Clock"

A table of English newscasts from shortwave stations throughout the world.

as local sports, local personalities, "What's On" features, and most important, request programs, were not being covered. And so it was from the consciousness of the serviceman's need that the FBS was inaugurated.

The very name itself is indicative of the thought that was behind it for, in weighing h up in the joint planning stage, it was realized that irrespective of who provided the required service, the result itself could be heard by everyone who cared to listen—soldiers, sailors, airmen, or civilians.

Under such conditions, it was considered wasteful for each service to provide its own organization. The British Army afforded the largest potential audience and so was made responsible for the organization, with the understanding that the other services

would undertake their share of the task.

Organization and maintenance of FBS was entrusted to the Army Welfare Service and a special place was found for broadcasting activities within the Army framework; the RAF made itself responsible for 25 percent of the manpower required. far as the Middle East was concerned, this activity was started in a tentative way. A Middle East Broadcasting Unit was formed and time was borrowed from the existing civilian or government broadcasting organizations that were in range of the troops. The headquarters of the Unit was based in Cairo, Egypt, under the command of Peter Hadden, who is remembered for his famous BBC series on 'Cairo Calling."

The "Forces Hour" was radiated from the Egyptian State Broadcasting Station in Cairo, the Palestine Broadcasting Service, Radio Lebanon, and later from Radio Baghdad.

About this time, E.N.S.A. inaugurated a special transcription service for use by these networks. These programs featured the most popular artists of the day.

The air time at the Service's disposal proved inadequate and soon plans were made for the installation of the Forces' own radio stations. The RAF helped a great deal by supplying lowpowered transmitters. The first fulltime Forces Broadcasting Station went on the air at Gaza. Palestine, followed by a second station in Beirut, Lebanon. Site for the Gaza station proved unsatisfactory and the transmitters and equipment were eventually moved to Jerusalem. About this time, an Army Signals Station, in Cairo, began broadcasting test transmissions as JCJC. Some time later, the Service took over the operation of JCJC and the station became known as the Forces Program from Cairo.

Due to the low power of these transmitters, a second station was necessary for troops in the Suez Canal Zone. So an installation was made at Kabri. An urgent demand came from (Continued on page 90)

(Continued on page 50).

(Note Unives otherwise indicated, all time is expressed in American EST; add 5 hours for GCT. News refers to hewsenside the Erailoh Language. In order to produce the American Continue of the Contin

This is one of the transmitters of "Radio New Zealand" at Titahi Bay, near Wellington.



### 3-TUBE AMPLIFIER For Variable

Reluctance Pickup

By EDWIN W. HILL. Chief Eng., Station WDHL

Features adjustable tone compensation and good fidelity at room level volume.

Designed for either crystal or VR pickup.

NALL, three-tube a.c.-d.c. audio amplifiers are, generally speaking, not very novel or new pieces of apparatus. However, here is a compact amplifier which differs from the usual run in that it uses only the three conventional tubes in a circuit not much more elaborate than the simplest and yet is suitable for use with a variable reluctance pickup without any further preamplification or outboard units of any kind. It can also be used with a crystal pickup, without modification, and it features adjustable equalization and good fidelity at adequate room-level volume.

This amplifier came into being as the result of a search for an inexpensive unit for reproduction of electrical transcriptions and records for audition and demonstration purposes. Since the playback outfit was intended to be carried by radio time salesmen to possible clients or sponsors, any saving in weight and space requirements was advantageous.

After considerable calculation and experimentation, a circuit was designed and constructed that met requirements in every respect. Besides being very satisfactory for its originally intended purpose, this amplifier can be used in the home record player, where only moderate audio power is desired, and it certainly brings down the cost of variable reluctance reproduction to a point where it compares favorably with that of the ordinary crystal pickup.

Only three tubes are used. One half of a 128L76T functions as a high gain first audio amplifier in cascade with the other half which works as a second audio amplifier, the output of which drives a 35L6GT power output tube. The rectifier is a 3525GT.

Construction of the amplifier is simple. A piece of aluminum, 5½ inches by 8 inches, was cut from a used acetate-coated transcription disc and folded 3 inches from one long edge to form a right-angle chassis. Steel, or other metal, could be used equally as well, but the aluminum from the

ompensation
erel rolume.

VR pickup.


Overall view of amplifier.
Chassis is made from an acetate coated transcription disc.

transcription disc has the advantage that, if care is taken not to mar it during working, the acetate coating makes a smooth, glossy and very attractive "ready-made" paint job for the completed chassis.

All of the parts fit into their places without undue crowding and no special shielding or wiring precautions are necessary, other than those which go to make up good construction practice, such as making all the grid connections as short as possible and keeping a.c. wiring away from the input circuit. The under-chassis layout is shown in the photograph on page 122.

The circuit is a straightforward one and, except for certain novel features like the combination VR-crystal input and the adjustable equalization, does not need a great deal of explanation. The input to the amplifier consists of a voltage divider. The lower (Continued on page 122)

Diagram of the three-tube amplifier for crystal or variable reluctance pickups.

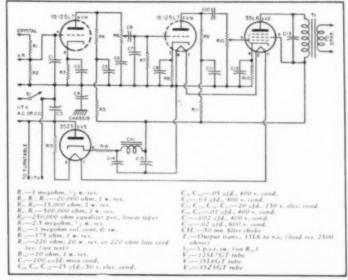

# A New Approach To BEAM ANTENNAS

By

Major CHARLES E. SPITZ, W7JHS

Obtain optimum performance over the entire band by tuning your beam to frequency from the ground.

HE amateur who erects a beam antenna is usually prepared for a lot of cut and try, and it takes it. Perhaps he copies or buys a commercial beam. The service technician buys a commercial beam for that FM or TV installation simply because he doesn't have time to fuss with it. The purpose of this article is not to deride the manufactured products. There are good assemblies available, but to illustrate the difficult nature of beam antenna installations and the fact that the process of tuning can be

Fig. 1. "Lazy H" antenna-feedlines go to X.

readily solved by the use of a simple method.

After experimenting for some time with the described system, the author has achieved results that more than came up to expectations, and possibilities seem to be unlimited.

Consider first a simple dipole and reflector. The radiator is usually cut for frequency and left at that length. Not so the reflector, however, as considerable adjusting must be done for either maximum forward gain, or front-to-back ratio at a particular frequency. Many surplus telephones have been pressed into service as a necessary aid.

It's a two-man job to adjust a receiving beam, and a three-man job for transmitting—someone has to carry the field-strength meter! If the antenna is out of reach when finally installed, as many are, a derrick is a mighty handy accessory. Most people tune on the ground and then just hope it stays that way when the antenna gets into position.

Look at Fig. 2. The classical method of adjustment is to slide small tubing ends into a larger diameter main piece, as in A. In B, tuning is accomplished by a small stub of a few inches and is the usual method for wire. It will be seen that the method in C is essentially that of B, in that the stub

L can be tuned remotely (in effect) if the reflector feedline is tuned from a position any number of half-waves longer.


Tuning a reflector with this system of parasitic excitation means there are standing waves on the reflector feedline; however, several experimental feedline lengths of fifty feet and beyond did not indicate excessive losses by virtue of increased lengths.

The antenna used in the tests, the results of which are shown in the graphs, consists of a radiator composed of four half-waves in-phase, two elements stacked above two, and is popularly known as the "Lazy H." A similar curtain was placed one quarter-wave behind. It will be noted that the feedlines between the upper and lower elements are not transposed, being phased by center feeding, and present a load impedance of about 70 ohms. The resultant broadband characteristic is easily seen in the graphs. For those who may be unfamiliar with the antenna, it is shown in Fig. 1.

Another advantage of remote reflector tuning is the fact that it may be tuned to any frequency, within reasonable limits, by simply turning a condenser dial at the equipment. This should be a major aid to the e.c.o. enthusiast, as well as valuable in conjunction with FM or TV channel selection.

Feedlines used in the tests were RG-11/U and RG-8/U coaxial cable with little differences noted. A field-strength meter and a folded dipole were set up 300 feet from the antenna, and with a remote meter at the operating position and the reflector tuned for maximum forward signal, the meter was set so that zero on the graph indicated a maximum signal with 100 watts of r.f. power. A Model MM2 "Micromatch" was used to monitor power level and to keep a check on standing-wave ratios. A condenser

Fig. 2. (A) and (B) are conventional beams. Tuning method described is shown in (C).

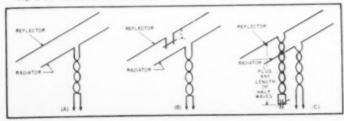

dial reading of 100 indicated 570 μμfd. (two sections of 285 in parallel) and zero for minimum capacity.

The graphs A, B, and C of Fig. 4 illustrate the field-strength and front-to-back ratios at all positions of condenser tuning at the frequencies of 28.5, 29 and 29.5 megacycles with a 55-foot coaxial feedline from the reflector. Accurate measurements were not possible beyond —26 db., and the —30 db. measurements were filled in by over-the-air reports.

Fig. 3 shows an example of the utility of reflector tuning. A check was made for the point of maximum front-to-back ratio every 100 kc. from 29.7 to 28.4 mc., and with the aid of the graph, tuning could be set at any time at the best position for the operating frequency in use.

As may be surmised, tuning the reflector affects the standing-wave ratio of the radiator feedline by changing the antenna impedance, and the effect is noted in Table 1; however, readings of forward gain indicated little field-strength loss for ratio orders of 2 to 1.

Coverages of the frequencies 27,150 to 28,500 kc. was accomplished by use of a fifty-foot feedline. Actually a fifty-foot feedline is used with a five-foot extension plugged in for the 28.4 to 29.7 mc. range, since it was felt that introducing such variables as tuned coils would unnecessarily com-

plicate the system. You may note that all discussions have referred to field-strength readings and wonder about receiving capabilities. It was noted that receiving checks in the amateur band were difficult to make due to fading, which would not occur in local FM or TV areas for such reception. An interesting application came to light, however, when the author was requested by KZ5AZ, who was visiting, to hook up with a Canal Zone station, so that he could talk to his wife. The antenna was swung in that general direction on a crowded weekend. W6 and W7 signals were pouring through by the hundreds, so as each signal was tuned in, the condenser was turned until the signal dipped or rose to indicate a southeastern signal. In that manner of DF-ing, five signals were quickly selected, three turning out to be Puerto Ricans, and two in the Canal Zone, one of which, KZ5CJ (a few houses from KZ5AZ's home QTH), was quickly raised and all in a matter of a few minutes!

The coaxial feedline to the balanced antenna proved poor in receiving discrimination. However a two-wire coaxial cable such as RG-22/U should improve receiving performance considerably, and in some installations molded parallel lines, provided impedances are matched, might be suitable.

The business of trimming the reflector feedline for a desired frequency and band may bother you; however, it is suggested that whatever feedline length seems readily available be tried. If the results are not satisfactory, then the feedline may be added

DIAL	1 0	10	20	30	40	50	60	70	80	90	100
SWR	1.3	1.25	1.1	1.02	1.09	1.1	1.11	1.15	1.15	1.17	1.17
	1,2						0	0	0	0	0
FS	2	2.5	.5	0	0	0			_		
FB	3.5	3	5	7	10.5	21.5	26.5	30	28	27.5	26

Table 1. Performance characteristics of the antenna described, measured at 28.5 mc.

to until the proper frequency is reached within tuning range. This is not so difficult as it might seem, as at high frequencies the transmission-line velocity factor is taken into account. With a factor of 0.66 for coaxial cable, on ten meters a half-wave becomes about ten feet, and any tuning range within that band could be covered within any portion of it as an added A larger tuning condenser length. than that used, in order to obtain a greater bandwidth, could not be employed, as at maximum capacity the impedance becomes so low as to be the equivalent of a short circuit. Double the capacity was tried and was of no value, simply making tuning at minimum capacity critical.

The value of reflector tuning may be questioned by some who wonder about the small forward gain changes indicated. It was mentioned that a broadband antenna was used in these checks which the curves bear out. A close spaced parasitic or Yagi antenna, being of a much higher Q should exhibit a distinct curve about the forward line. Where a broadband antenna is in use, tuning the reflector should be of value in reducing interference, BCI, or TVI, and for all reception, short-wave, amateur, FM, and it should increase external signal-to-noise ratios.

Some thought was given to the use of a phasing section between two elements or curtains of an array, and tests were made. The results were poor, however, since at the reflector the direct wave, when off frequency,

DIAL READING

1CI

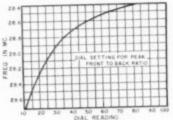



Fig. 3. Condenser settings for reflector tuning to give maximum front-to-back ratio.

exhibited a phase difference to the radiated wave, and unless the spacing between the elements was also variable, the bandwidth would be limited. This effect would be aggravated by a low transmission line velocity factor.

What about tuning all parasitic elements, such as directors, etc.? What about arrangements to steer radiation angles? The author has given some thought to these problems and is conducting further experiments. The sky seems to be the limit in tuning parasitic elements, and it surely seems that the manually-tuned beam is on the way out.

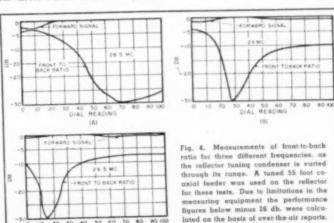Acknowledgement must be made here of the patience and valued assistance of Lynn Mutrix, W5OIX; Captain Bascom E. Tillotson, W5PDW; Chief Warrant Officer Chester B. Harmon, WOJG; Reynold E. Champagne, W4KQW; and the many others whose observations aided the work.





## Build A Sweep Frequency AUDIO OSCILLATOR



Over all view of the sweep frequency audio oscillator showing parts layout. The two r.f. oscillators are at opposite sides of the chassis, mixer in center.

THE sweep frequency signal generator is fast becoming an indispensable piece of test equipment for the alignment of FM and television receivers. When used in conjunction with an oscilloscope, this instrument is capable of giving a rapid and accurate analysis of the response curves of the receiver r.f. and i.f. circuits, saving much time over point-by-point checks with a manually operated signal generator.

Lesser known than its r.f. counterpart is the audio frequency sweep generator. Used in very much the same manner, it provides a means of rapidly showing the response curve of audio equipment on an oscilloscope screen. In practice a sweep varying from fifty cycles to above twenty thousand c.p.s. may be used to check deficiencies in high or low frequency response, the effects of tone controls, inductive circuits, inverse feedback, or any other factor that may affect the frequency response of the unit under test. Particularly useful in making response curves of electromechanical devices such as loudspeakers, microphones, phonograph pickups, and recording heads, the sweep frequency generator makes it possible to observe sharply peaked resonance points that might go unnoticed in a point-by-point frequency check.

There are several methods of approach to the problem of designing a satisfactory audio sweep frequency system. One commercial system uses a rotating disc upon which the varying audio tones are drawn. A photocell and slit arrangement is used as a

pickup to convert the varying light intensity into electrical energy. This piece of equipment has the advantages of stability and easy insertion of marker pulses but is usually limited to frequencies below ten thousand cycles, due to the electromechanical characteristics involved, and in addition requires an accurately drawn tone wheel.

A simple, easy-to-operate sweep generator may be built by the average constructor by using the beat frequency principle of generating an audio tone. This principle is used in a number of commercial signal generators and relies upon the fact that if two slightly varying radio frequencies are passed through a nonlinear detector the output of the detector will contain a frequency component equal to the difference between the two original frequencies. As it is a fairly easy matter to frequency-modulate one of the radio frequency oscillators by about twenty or thirty kilocycles, the resultant beat note may be rapidly swept back and forth throughout the audio range.

In the circuit illustrated, two 6J5 tubes are used as rf. generators, operating at approximately 250 kilocycles. A small variable condenser, capable of 360 degree rotation, is placed in the grid circuit of one of the oscillators and is driven at the rate of five to ten r.p.s. by a small, geared down, phonograph motor. A 6SA7 is

used as a detector and the audio component is recovered in the plate circuit.

The variable condenser used should be selected with special attention to the bearing fitting. A shaft which fits too loosely will cause erratic coverage, while too snug a fit may cause the condenser to "freeze." It would be desirable to use a condenser with ball bearings in this application. Occasionally such condensers may be found as surplus equipment.

Although not a very complex circuit, it is necessary to consider sevfactors in order to obtain good results. One of the most important of these is the tendency of the two r.f. oscillators to interact if any coupling exists between them. This results in distorted waveforms, especially at low frequencies, and in extreme cases a sudden cessation of audio oscillations at a few hundred cycles. This is caused by one oscillator "locking in" at the same frequency with the other. As a result, good shielding and adequate bypassing of stray r.f. is desirable.

A second factor, particularly relevant to a sweep frequency system, has to do with the low frequency limit of the sweep. If a sweep recurrence rate of sixty revolutions per second is used, the variable condenser will pass from minimum to maximum capacity in one one-hundred-twentieth of a second, a space of time long enough to permit


only a single cycle of a one-hundredtwenty cycle note, disregarding all other frequencies in the sweep. By lowering the sweep rate to about ten c.p.s. there will be a duration of about one-twentieth of a second in which presumably a twenty-cycle note could be traced. However as room must be left for higher frequencies the low frequency limit in a sweep extending to twenty-thousand c.p.s. will be approximately one hundred cycles.

A third factor, closely related to the one just mentioned, is that if the frequency variation is linear with the rotation of the variable condenser, the low frequencies from fifty to onethousand cycles will be crowded into one-twentieth of the space of the remaining spectrum from one-thousand to twenty-thousand. This makes the low frequency end difficult to observe and again imposes a limitation on low frequency response due to the fact that the period during which the low frequencies are being produced is so brief. To overcome this problem a special condenser arrangement is used. First, the variable condenser is specially cut so that only a slight variation in capacity occurs over a considerable portion of the rotation, thus extending the period during which low frequencies are produced Secondly, an air trimmer is placed in series with the variable condenser to provide a means of varying the sweep width from a few cycles to twentythousand cycles. This provision considerably increases the flexibility of the instrument by making it possible to sweep only a limited portion of any part of the audio spectrum.

The entire unit was constructed upon a 2" x 7" x 9" aluminum chassis and the layout arranged to give good separation between the two r.f. oscillators. Little difficulty was noticed from motor vibration but care should be taken that parts are rigidly mounted and non-microphonic tubes are used. A separate switch is used for the motor in order that the system may be used as a straight audio oscillator if required. If a variable condenser with an extension shaft is available a knob and calibrated dial may be added for extra convenience.

In operation one of the first steps is to observe the output characteristics of the sweep generator itself. This is easily done by connecting the output to an oscilloscope of known flat characteristics. Often the direct output from the 6SAT will suffer from high frequency attenuation, as illustrated in the scope photos, and it will be necessary to incorporate some form of equalization network such as shown in the schematic.

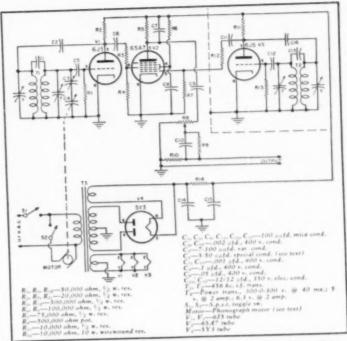As conventional 456 kc. i.f. transformers are used in the two oscillators, the built-in trimmer condensers may be used to zero beat the oscillators when the motor driven condenser is entirely open. For greater convenience, a small shaft-driven trimmer might be brought out on the front panel for this purpose. Although zero




Complete schematic diagram of the sweep frequency audio oscillator. Condenser  $C_i$  is used to vary the sweep width while condenser  $C_i$  is the specially cut motor driven unit.

beating may be done with the variable condenser motionless, it appears preferable to adjust the system with the motor running and while observing the pattern on the scope. In this manner the low frequency limit may be set so that a smooth pattern results without the distortion that may result from very low frequencies.

The frequency range covered will depend primarily upon the effective variation in capacity of the motor driven condenser. A variation of fifty micromicrofarads with the circuit shown should produce a frequency deviation of approximately thirty kilocycles and is a useful range for checking high frequency and ultrasonic peaks or dips in audio amplifiers. In testing limited range equipment, such as loudspeakers or electromechanical devices, a range of ten kilocycles or less is usually sufficient and a series (Continued on page 98)

Scope patterns taken with the aid of the sweep frequency oscillator. (A) A stationary sine wave output. (B) Unequalized output of the sweep generator. Due to faulty sweep synchronization, low frequencies appear at the right hand side of the picture. Gradual slope caused by the specially cut condenser is apparent when compared to the slope caused by the uncut side. (C) Equalized output of generator shows flat response with slight attenuation at low frequency end. (D) Output of audio amplifier feeding a loud-speaker load. Slight hum in high frequencies is caused by increase in speaker impedance not entirely corrected by inverse feedback. (E) Amplifier with controls set to boost bass. Poor sync makes low frequencies appear on right. (F) Amplifier with treble boost.

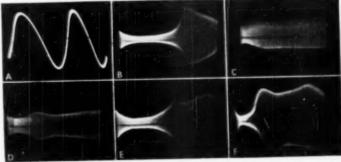

### An ELECTRONIC METRONOME



### Construction details covering an inexpensive yet accurate metronome for the serious music student.

HE familiar ticking metronome with its swinging wand which has accompanied the labors of music students for generations can now be replaced by a simple electronic circuit which has fewer moving parts and is not sensitive to position nor easily damaged by dropping.

Metronomes customarily are adjustable to beat from 40 to 208 times per minute. In addition, some, but not all, have a mechanism for accentuating every second, third, fourth, or sixth beat with a bell or a louder tick to indicate measures. A musician whom the author consulted stated that signatures with anything up to twelve beats per measure are sometimes encountered, although this is very rare. The electronic metronome can meet all of these requirements without additional complications.

### Circuits

Fig. 2 shows a very simple thyratron circuit which operates from the a.c. power line. One small thyratron is used to control the "tempo" function while a second operates the "measure" circuit. Fig. 3 is the circuit diagram of an a.c.-d.c. multivibrator circuit which provides the "tempo" function exclusively. A second multivibrator can, of course, be synchronized with the circuit of Fig. 3 to indicate "measure" in the same instrument.

The circuit of Fig. 2 operates in the following manner.

Tempo Section. When V, fires, C, is charged up very quickly to the plate voltage supply voltage minus the arc drop of the thyratron; in this case it charges to 142 volts. The brief surge of current causes the relay to give a smart click which resembles the tick

of an ordinary metronome. As soon as the voltage across the tube itself drops below the arc drop, the tube de-ionizes. C. now discharges through R..

Since the control grid of V, is biased about +50 volts with respect to "B—" the tube will again fire when the voltage on the condenser has dropped from 142 to about 50 volts. The voltage across the tube itself is approximately 100 volts at this point.

Measure Section. For delivering an accentuated beat or bell stroke at the beginning of each measure, the second thyratron, Vi, is used in a similar circuit whose ticking rate is synchronized at a submultiple of that of the "tempo" section. The combination of C. with R.R. differentiates the positive surge from the cathode of V, into a short, sharp tripping pulse which fires V somewhat earlier in each discharge of C, than would occur in unsynchronized operation. Variation of R causes the rate of the "measure" section to jump from one to another of the successive submultiples of the rate of the "tempo" section. There is no difficulty in indicating values up to 12 beats per meas-

The circuit of Fig. 3 operates like any multivibrator in that when  $V_z$  conducts,  $V_z$  is driven beyond cut-off and remains blocked until  $C_z$  has discharged sufficiently through  $R_z$  to unblock it. Then the current flips over,  $V_z$  is blocked, and  $V_z$  conducts a surge of current that lasts until  $C_z$  is discharged through  $R_z$  (in this application a much shorter time than the other phase). The relay clicks as in Fig. 2. A negative synchronizing pulse could be taken from the plate or screen of  $V_z$  and applied to the control grid of the tube corresponding to  $V_z$  in another

such multivibrator for "measure" indication. The screen rather than the plate of  $V_{\nu}$  is used for the multivibrator proper because, if the plate is used, a high audio or low r.f. oscillation takes place which blocks  $V_{\nu}$ .

The parts lists accompanying the diagrams of Figs. 2 and 3 show typical values used in the construction of these two types of electronic metronomes. The cost of such components at wholesale houses, including a cabinet for a "tempo" indicator only, is approximately \$8.00 at present prices. For an instrument incorporating both "tempo" and "measure" indication the cost would rise to approximately \$12.00. A little luck in finding suitable war surplus items would, of course, reduce the cost of building this instrument considerably.

The ticking sound produced by this sort of a metronome depends upon the relay used and also upon the way the relay is mounted. An objectionable tinny sound can result when the relay is mounted on a thin metal wall or when the relay used incorporates a coil spring which is used on the tongue of many such units. The coil spring can be quieted by the judicious use of a little petroleum jelly.

The design equation for the RC circuit of Fig. 2 is:

$$t = RC \log \left[ \frac{(E-a) \cdot (n-1)}{E + (n-1) \cdot (u+e)} \right]$$

Where: t = period in seconds or time between ticks

E = plate supply voltage a = thyratron arc drop while conducting

= control ratio of the thyratron

u = minus the intercept on the grid volts axis of the projected straight portion of the control characteristic curve for the thyratron

e= grid bias In Fig. 2, when using 2D21 tubes, the various values are as follows: E= 150 volts, a= 8 volts, u= 250, u= 1.3 volts, and e= 50 volts. The design equation for Fig. 3 is:

$$t = RC \log \left( \frac{E_w - E_v}{E_w - E_v} \right)$$

Where:  $E = \text{grid voltage of } V_1 \text{ with respect to "B-"}$ 

 $E_e$  = plate potential of  $V_e$  at zero bias with load  $R_e$ minus plate supply voltage

E = cut-off bias for V<sub>b</sub>
E = zero in Fig. 3, but might advantageously be positive.

The values of  $E_0$  and  $E_1$  are approximate and should be measured dynamically with an oscilloscope. RC is  $R.C_0$ 

In Fig. 2 it is necessary to choose the value of  $C_1$  large enough to click the relay with the available plate supply voltage and adjust the fixed and variable parts of R, to cover the desired range of "tempo" or "measure" indication. If a relay which requires too large a condenser to click it is used R, may be so low for the fastest rates that the thyratron will not de-ionize. Higher plate voltage permits the same energy storage in a smaller condenser.

To provide a linear rate scale on the "tempo" dial, a linear variation of conductance, i.e. a hyperbolic variation of  $R_n$ , would be necessary. However, a logarithmic scale is preferable, thus a resistance vs. rotation curve, such as Centrulab Curve 6, can be used. In any case it takes a large dial or scale to carry all of the numerals usually put on metroromes.

The positive grid bias in Fig. 2 is important in that it minimizes the effect of tube variations. Positive bias for  $V_1$  would be desirable in Fig. 3 if the tube selected for  $V_1$  is one requiring but a few volts bias for cut-off.

Although types 2050 and 2D21 thyratrons have given no trouble in the circuit of Fig. 2 when the heater center tap is returned to "B-," the rated heater-to-cathode potential is, in this instance, momentarily exceeded at each tick. It is, therefore, preferable to use a separate heater winding, tied to the cathode, for each tube. Alternatively, a circuit could be constructed with RC in the plate circuit, both cathodes at "B-," and R, and R, returned to a negative bias. This would require the use of an additional rectifier which would, in most cases, cost as much as a second transformer winding.

It will be necessary to calibrate the electronic metronome in individual steps if the instrument is constructed of ordinary stock components. R. of Fig. 2 can be equipped with a pointer knob and a celluloid-covered paper scale with a metal rim. This scale should be large enough to accommodate all of the usual metronome figures carried on such a dial. The quickest way to get a few calibration points is to compare the ticks of the instrument with the second-ticks transmitted by WWV. It is desirable to extend the range of R. slightly beyond the usual metronome range in order that points at 30, 60, 120, 180, and 240 per minute

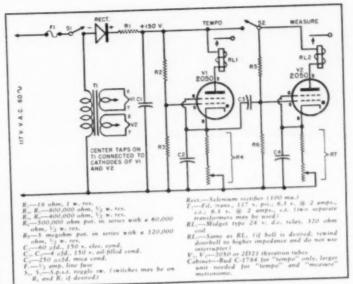


Fig. 2. Diagram of electronic metronome which provides tempo and measure indication.

may be obtained. Some users consider these points sufficient and are content to interpolate intermediate points. A metronome now under construction for a blind piano teacher has various numbers of screw heads placed opposite the pointer position at these WWV points which can be felt to read the tempo.

The "measure" section needs no calibration. After "tempo" has been set as desired, the "measure" knob is merely turned until the bell or reinforced beat is heard at the correct number of beats


apart.

If fine calibration is required, a counter such as the Cenco No. 72506, can be operated by the "tempo" relay contacts and used with a stopwatch.

Large variations in line voltage appear to have no effect on the rate of the instrument shown in Fig. 2. The circuit of Fig. 3 was not tested for the effects of line voltage variation. The calibration of the metronome of Fig. 2 was stable in several hours of operation and with several different thyratrons. Longer tests have not been made. High absolute precision is not considered necessary in a metronome, however, if the grid of V, in Fig. 2 is led to a potentiometer inserted between R<sub>1</sub> and R<sub>2</sub>, any user can easily reset the instrument so that it will beat with WWV or the ticks of a clock.

It is very important that R<sub>z</sub> and R<sub>z</sub> have nearly identical temperature coefficients and be located close together and away from a heat source. A carbon resistor over the tube for R<sub>z</sub> caused severe warm-up drift and had to be replaced by a better unit placed in a cooler location.

Fig. 3. Circuit diagram of the a.c. d.c. metronome which gives tempo indication only.

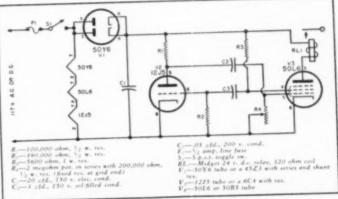

# INSTANT ILATING DEVICES By NORMAN L. CHALFIN Crystal Devices Co. THERE are several types of electronic equipment that should be designed to operate instanta-

Fig. 1. Child's phonograph with carbon pickup. Lifting arm places unit in operation.

### Description of several different circuits suitable for equipment requiring instantaneous operation.

abandon the instrument before it starts full operation and thus the unit

R=27 ohm, ½ w. ret.

R=1200 ohm, 3 w. wrow.ound ret.

R, R, R, =150 ohm, ½ w. ret.

Cy=200 ifd., 150 v. elec. cond.

Cy=C=100 ifd., 150 v. elec. cond.

M=Phono motor

Rect.=75 ohm v.e. PM speaker

Spkr.=45 ohm v.e. PM speaker

L=Double-butten carbon pickup (Astanic)

A phonograph or radio designed for a child's use is one type of equipment

which should function immediately as soon as the small fry turns it on. Any prolonged warm-up period will prob-

ably mean that the youngster will

neously

Fig. 2. Circuit diagram of the carbon pickup phonograph made especially for children.

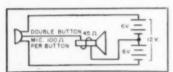


Fig. 3. Amplifier to be used with double button carbon microphone covered in text.

will keep running for some time unattended.

Another type of equipment which

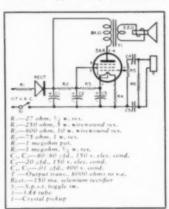


Fig. 4. Circuit diagram of phonograph unit employing quick-heating vacuum tubes.

and other business establishments, and the telephone amplifier. With most standard circuits these instruments must be on throughout the working day no matter how infrequently they may be used. While power consumption on such units is relatively small, over a period of time the cost of continuous operation can become a sizable item, especially if a large number of these instruments are in use. The author estimates that approximately 70 per-cent of such power costs can be saved through the use of instant heating devices. In addition, substantial savings can be effected on maintenance and replacement parts when such devices are used intermittently. rather than continuously.

must operate at once if it is to be of any practical value is the intercom-


municating systems found in offices

The convenience of having a home radio receiver operate instantaneously is generally conceded by most house-holders, especially if they have missed time signals or brief news reports during a warm-up period.

Commercially available components now make possible the construction of instant heating apparatus which is both economical in operation and in initial cost. This writer's experience has been that the quick-heating tubes and selenium rectifiers commonly used in such devices are as rugged as some of the separately-heated cathode types, if not more so.

For any electronic apparatus one of the first things to be considered is sources of power. In instant heating devices the filament-type tubes such as the 80 or 523 can be used as "B" supply rectifiers. Filaments of other

Fig. 5. Three representative quick-heating power supplies for various applications.

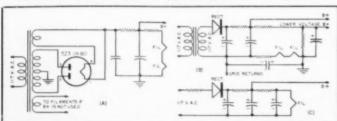

tubes used in the apparatus can be supplied through a series string with a dropping resistance from the "B" supply. Where hum is not a critical factor, suitable filament transformers could be used. For a.c.-d.c. operated apparatus (the so-called transformerless units) the selenium rectifier is definitely indicated. In such a case where filament-type tubes are used the only practical filament source is from the "B" supply through a suitable dropping resistance. In this instance, of course, the rectifier rating must take into consideration the filament current in addition to the plate currents of the other tubes. Several representative power supply arrangements are illustrated in Fig. 5.

The filament-type tubes that can be used in instant heating apparatus have characteristics which closely parallel their separately-heated cathode counterparts. A representative list of comparable types is given in Table 1 (Page 88). Consideration will be given to vacuum tube instant heating devices a little later in this article.

One of the most often encountered units incorporating instant heating features without the use of vacuum tubes is a child's phonograph. This instrument operates from the power line, uses no vacuum tubes, and delivers a substantial output from the loudspeaker. The primary element in this phonograph is a double-button carbon pickup made by Astatic. The circuit of the carbon pickup record reproducer is shown in Fig. 2. The unique bridge circuit employed is the subject of patent applications prepared by the author. The selenium rectifier, which requires no warm-up period, delivers d.c. directly from an a.c. power line. Through a dropping resistance, 12 volts of button current, tapped at 6 volts, is supplied. The rest of the connections can be readily determined from the diagram.

When a variable resistance device, such as the carbon microphone or pickup, is employed, the optimum output conditions are obtained when the load is one-third of the quiescent button resistance. For this reason a 66%

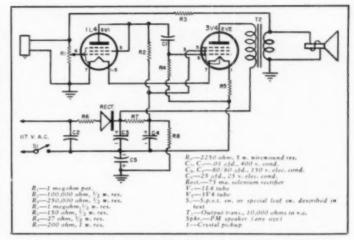


Fig. 6. Circuit diagram of a two-tube, quick-heating phonograph amplifier unit.

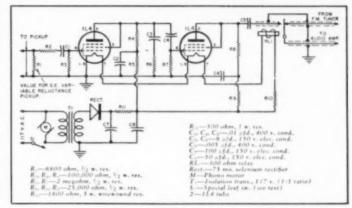



Fig. 7. Schematic of a self-switching, quick-heating phonograph preamplifier.


ohm impedance speaker would be desirable. Since a 45 ohm voice coil impedance was the closest thing available in a speaker such a unit was incorporated in the phonograph. (Continued on page 88)

Fig. 8, Bottom view of FM tuner with preamp added. Isolation transformer is to left of filter block (upper flange) while rectifier strip can be seen on the left wall of the chassis.



Fig. 9. The two-tube phono preamp assembled on a General Electric FM tuner chassis from which the power supply has been removed. Unit to the left of tuner is the power amplifier.

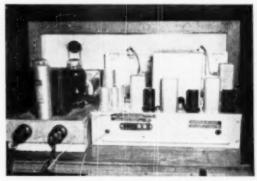

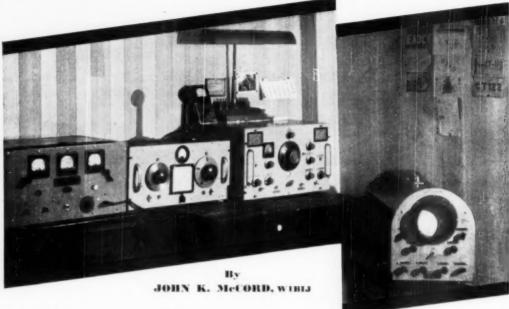

## Understanding SUPER-MODULATION

Super-modulated amateur station designed and built by W1BII. (Left to right) Supermodulated final amplifier using 807%, the v.f.o. and driver, 15-tube superhet for ham bands, and the 12-tube Panadaptor used in the signal comparison tests at the station.

mands maximum r.f. grid drive. By

preference less drive is left for the r.f.

tube grid and its output drops, sup-

pressing the carrier. At "D" the p.m.

tube's power cycle is ending and the

NEW method of amplitude modulation has appeared recently. It is simple and efficient and readily adapted to amateur use. In building a low-power transmitter using the "super-modulation" principles and getting it on the air, several major differences, compared to regular AM methods, were noticed. This article will explain in practical "ham" language what happens in a supermodulated rig that makes it so different from conventional AM transmitters. A step-by-step tuning method and panoramic comparison with other systems will also be covered. Fig. 2 is the home station final using 807 tubes in super-modulation.

For a basic understanding of supermodulation operation see Fig. 1. The unfamiliar tank circuit is electrically the same but redrawn to simplify an understanding of the action. The r.f. tube functions as a regular class "C" amplifer. The p.m. or r.f. modulator tube, being biased about four times cut-off, doesn't go to work until you speak into the microphone to modulate. The r.f. tube makes the carrier and the p.m. tube puts your voice on it by adding r.f. power to the common tank at an audio rate.

Fig. 4 shows the super-modulation

How it works, tuning instructions, and a comparison with other modulation methods, as seen on a Panadaptor.

output waveform and its separate components drawn on a common time base. As the p.m. tube's fixed grid bias is series-fed through the modulation transformer secondary, and the r.f. tube bias is in shunt to the transformer center tap (see Fig. 2), the first audio voltage cycle from the modulation transformer secondary being a.c., alternately adds and subtracts from the fixed bias supply voltage. As a result both the r.f. and p.m. tube outputs increase and decrease accordingly. At time instant "A" in Fig. 4. an unmodulated carrier from the r.f. tube is shown. At "B," the start of the first positive audio alternation increases the r.f. carrier slightly to provide a cushion for the coming p.m. tube operation. At "C" the full peak of the positive audio alternation has cancelled out the p.m. tube's fixed bias and driven the grid positive resulting in a very large amount of power released. At this point the p.m. tube de-

r.f. tube's carrier rises as a result of returned grid r.f. drive and provides the final cushioning. At "E" the negative audio alternation adds to the p.m. tube's fixed bias and the p.m. grid is momentarily about eight times cut-off. Through the modulation transformer center tap this same negative voltage adds to the r.f. tube's fixed bias and decreases its output, forming the negative or valley portion of the output waveform. This completes one cycle of audio voltage from the modulator and this is repeated for each succeeding cycle. This method of AM modulation has the following advantages. The positive waveform peaks can be extended to a point only limited by the p.m. tube's plate saturation point and the r.f. carrier can be suppressed at the same time. Using regular AM methods, extending the positive peaks

beyond the 100% modulation level

<sup>\*</sup> Taylor, R. E. "The Taylor Super-Medula tion" Principle, "RADIO & TELEVISION NEWS Sept. and Oct. 1548

would result in a clipped carrier. With super-modulation the r.f. tube supplies some carrier at all times and fills in between modulation peaks, preventing carrier clipping regardless of how high we extend the positive peaks, and it's the peaks that carry the voice intelligence.

Regarding power supply requirements, two plate supplies are not needed. The r.f. and p.m. tubes do not draw maximum plate current at the same time, so any supply adequate for a single tube will be OK. Grid bias can be supplied either by batteries or a separate supply. I tap mine off of the driver power supply bleeder. The r.f. tube can operate with grid-leak bias, but the p.m. tube must have a fixed supply and a means of varying the bias voltage over a small range. Tuning the super-modulated transmitter is quite different from usual procedure and the method is given step-by-step below. It is assumed bugs and parasitics have been eliminated from your super-modulated final and enough r.f. drive is available for a single tube. Both finals do not require maximum drive at the same time. Start with final plate voltage off.

1. Vary the r.f. grid drive and grid bias voltage until the r.f. tube grid draws ½ normal drive and the p.m. grid is zero or just starting to draw current. This balance is important. Run the r.f. tube cool and let the p.m.

tube do the work.

2. Closely couple a dummy antenna to the final tank and switch on plate voltage. The r.f. tube should load normally like a c.w. rig with the key down. Reduce grid drive rather than antenna coupling to decrease loading. The amount of coupling affects the tank impedance into which the p.m. tube works.

Keep the r.f. tube running cool at about half c.w. rating, but enough to prevent carrier clipping during modulation. An oscilloscope check will show

the right point.

3. Now apply modulation while increasing the audio gain. The p.m. tube grid and plate current should both kick upward to high values. The r.f. tube grid and plate current should show a downward movement, indicating carrier suppression. My 807 p.m. tube shows plate current peaks of 80 to 100 ma. and over. As the meter indicates an average value, the true peak current is about twice that shown.

 Disconnect the dummy antenna and load the regular antenna to approximately the same tuning values.

The oscilloscope pattern of Fig. 3 shows how the r.f. tube drive should be adjusted to prevent carrier clipping and still retain high modulation peaks. The vertical scope plates were directly link-coupled to the final tank which was loaded with the dummy antenna. WARNING—If scope is left coupled to tank when using antenna, r.f. may be fed to the power lines or the connecting leads may radiate, causing TVI, etc., so check this point carefully.

Checks have been made using a 5-inch Panadaptor to compare supermodulation waveforms with other signals on the air. The human ear is quite unreliable, even though we all use it for this purpose. Being logarithmic in function and having poor retaining qualities we shelved it along with the average receiver "S" meter and found the Panadaptor to be a decided improvement. Using this visual method small changes in both carrier and modulation could be seen. A change in amount of modulation not noticed by the ear can make a real difference in signal-to-noise ratio at a distant receiving location. It can mean the difference between being readable and not readable. The Panadaptor shows this difference. Fig. 5 is a mock-up waveform showing method used to determine relative signal characteristics with the panoramic image.

An average regular-method AM signal on the air appears as shown in Fig. 6. Notice that the modulation peaks extend just to twice the carrier height without modulation, and recede to the zero base line. This represents 100% modulation. Extending the peaks higher would also make the bottom


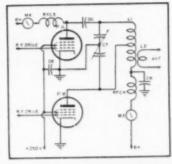


Fig. 1. The r.f. tube plate is shunt-fed and the p.m. plate series-fed to allow use of separate plate current meters. For a diagram of complete unit and an identification of parts see the schematic shown in Fig. 2.

peaks go lower which they can't do without hitting the zero base line and clipping the carrier. Fig. 7 shows a super-modulated signal of about the same power or pip height. Notice the positive peaks extended to three times the unmodulated carrier level, yet the carrier is a long way from being

Fig. 2. Circuit diagram and parts list for the super-modulation final amplifier and modulater.

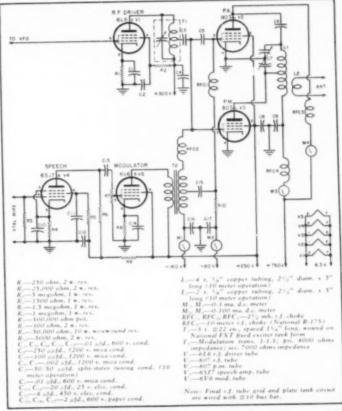

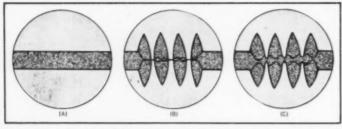


Fig. 3. How r.f. tube drive should be adjusted to prevent carrier clipping yet retain high modulation peaks. (A) Carrier only, (B) overmodulation with clipping, (C) under 100% modulation.

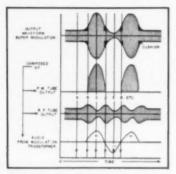


Fig. 4. Graph showing the super-modulated output waveform and its separate components, drawn on a common time base.

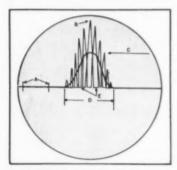


Fig. 5. Panadaptor image showing method for determining relative carrier strength, percent modulation, and bandwidth. Point "A" is 10 kc. marker. "B" voice peak, "C" carrier level, "D" bandwidth, and "E" carrier clipped showing overmodulation. This signal is overmodulated as shown by flattening at "E."

clipped. The carrier has even been suppressed to minimize heterodyne tendencies with other carriers. This is still amplitude modulation, but with greatly extended positive peaks. Fig. 8 is an average NBFM signal with narrow deviation, and no splatter when received on an AM receiver. amount of voice power is small and even using a discriminator for correct reception results in low audio content because of the small deviation allowable. Wide-band commercial FM staof course, are very efficient. NBFM has many advantages, but voice efficiency is low. It is evident that super-modulation delivers far more "talk-power," as Mr. Taylor calls it, than any of the other types of signals shown. Perhaps some day we may report a received signal as: "Fine business OM or coming in 10 db. over 9 on my Panadaptor. Your modulation is about 80% and your bandwidth is 8 kc." This report would give the operator real information.

While operating a super-modulated transmitter some major differences were noted compared to the operation of a conventional plate-modulated AM rig.

 Using regular AM methods the final r.f. plate meter should not vary with modulation. With super-modulation it should, and does, vary. In fact, they vary, both the r.f. and p.m. tube plate milliammeters. If they don't, you are not modulating.


2. When receiving a regular method AM signal the "S" meter indicates carrier strength. A strong movement of the needle with modulation could indicate overmodulation. With supermodulation a large needle movement is normal, indicating extended positive signal peaks. On one transmission check with super-modulation the "S" meter read S-9 with the carrier only and reached 15 db, over on peaks. "S" meters are relative indicators only and should not be depended upon for accurate measurements.

3. In modulating the usual plate-modulated AM transmitter, an audio power equal to 50% of the r.f. final stage power is required of the modulation. With super-modulation the modulating power is r.f., not audio, and is supplied by the p.m. tube. A comparatively small amount of audio power is sufficient to trigger the p.m. tube into releasing its power into the common final tank circuit.

When receiving super-modulated signals on a conventional receiver equipped with a.v.c. the background noise will tend to rise during periods of reduced carrier. This action will cause no difficulty in the majority of cases unless the carrier suppression is severe. In any event, the turning off of the a.v.c. will result in a much more readable signal when this occurs. It is advisable to try both ways.

I have heard super-modulation referred to as a form of pulse modulation and unlawful for amateurs. Super is definitely amplitude modulation. The word "pulse" could just as readily describe the driving power to a pair of class "B" modulators. One works as much on a pulse basis as the other. Super has been referred to as a form of low-level grid modulation, perhaps as a result of a hasty glance at the schematic diagram. Because the modulation is added to the carrier in the final transmitter stage, this insures its being high level. Although audio is applied to the tube grids, the p.m. tube is not a class "C" amplifier making a constant carrier as would be found in The p.m. grid modulation systems. tube is actually an r.f. modulator and can be thought of as taking the place of the usual class "B" modulators used in regular-method AM transmitters. In conclusion, super-modulation represents real efficiency. The p.m. or modulator tube is dead until you speak. Then it releases r.f. power at an audio rate only half of the time, on the positive audio voltage alternations. On the negative alternations it is cooling. Expensive audio transformers are not required. It's still cheaper to obtain say 100 watts of r.f. power than the same amount of audio power. -30-

Fig. 6. (A) Unmodulated regular method AM carrier only. (B) Same signal 100% modulated, as seen on Panadaptor screen. Fig. 7. (A) Carrier only, super-modulated signal. (B) Fully modulated "super" as seen on Panadaptor. Notice extended positive peaks and suppressed carrier (lower peak). Fig. 8. (A) NBFM signal without modulation. (B) Same signal modulated ± 3 kc. Notice dead spot at "C."

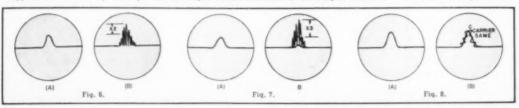

### IF IT'S NEW ...

KEN-RAD DEALERS HAVE IT!

JOU'RE in the driver's seat as radio-TV You're in the ariver a sould sell Ken-Rad tubes. Backed by General Electric's vast research and development facilities, Ken-Rad engineers provide you at all times with outstanding new designs. You can service latemodel receivers in your neighborhood knowing that the Ken-Rad complete line of tubes. TV-picture, metal, glass, and miniature, includes the advanced types to be found in new circuits . . . like the pace-setting gated-beam 6BN6 shown here (heater 6.3 v, 300 mg), or its 12BN6 companion (heater 12.6 v, 150 mg). ... Get the service business that goes to the dealer who has the new types—who handles Ken-Rad tubes! It's new and profitable business, and builds prestige for your shop. . Phone or write your Ken-Rad distributor today!

### HOT THIS MONTH!

Here's a clear-all-wires news item! Ken-Rad 1950 advertising help is ready and on its way to you via your distributor. There are sales-getting small ads for newspaper use-postcard mailers that pull-spot announcements for your local radio station. Add these to the fine Ken-Rad displays and other promotions, and you as an alert Ken-Rad dealer have "what it takes" to profit from the active tube market in your area.



### 6BN6 MINIATURE

Typical Operating Conditions, TV Application

Plate supply voltage Plate load resistance Accelerator voltage Cathode resistance Minimum signal voltage g action Audio putput voltage

175 . .22 megohms 145 to 400 ohms

> 1.25 V RMS 12.5 . RMS

KEN-RAD Radio

PRODUCT OF GENERAL ELECTRIC COMP

Schenectady 5, New York

The gated-beam 68N6 does three tubes' work. It functions as a limiter, discriminator, and audio-amplifler in new TV and FM receivers. You'll be servicing sets soon with 6BN6's in their circuits, and replacements will be in order. Make sure you have this essential new miniature when you need it ... and other up-to-theminute tube types . . . by stocking the Ken-Rad brandl



WIDEST SELECTION . BEST VALUE . HIGHEST QUALITY

### SINGLE UNIT TWEETERS

MODELS 4409 409 600
CYCLE TWEETERS: Become
mended for highest quality
reproduction systems requirting a law crossover frequency. Cabra shaped horn
results in perfect wide angle
distribution. Frequency resonne 600 to 15,000 cycles.
Model 4408 handles 6 watts
and 4409 25 watts.



MODEL 4407 ADAPTER MOUNTS 4401 TWEFFER ITS ANY 12° CONE UNIT. Converts any 12° cone proposer in a superior of the superior of



MODEL 4401—2000 CYCLE
TWEETER: An economical 6
was a committed to the committed of the comm



### DUAL TWEETERS



MODEL 4402, MODEL 4404 reproducts 5,000 cycle. Crand duties 5,000 cycle. Crand class 6,000 cycle

### CROSSOVER NETWORKS



MODEL 4405 HIGH PASS FILTER: An effective and economical unit for preventing laws reaching the tweeter unit. Cantains high frequency control to balance highs and laws. Cutoff frequency 2000 cycles.



MODEL 4410, 4420 LC CROSSOVER NETWORK: Genuine LC frequency did ers for segregating highs and laws. Not to be confused with ardinary high-pass filters. Crossover frequencies Model 4410, 2000 cycles. Madel 4420, 2000 cycles. Attenuator controls included and wired.

Write today for illustrated literature



### A Two-Band Wire

(Continued from page 42)

a simple connector made out of lucite was devised and used as shown in Fig. 3. The antenna was thus assembled, hoisted in the clear about 30 feet above ground and placed in use.

The same principle is applied if the antenna is being constructed for 7.13 mc. and 14.25 mc. operation. For such, however, the "300 ohm common point" is to be noted in Fig. 2 as 22 feet from one end, and the feed line must be connected accordingly. Ten and twenty meters at 11 feet, or twenty and forty meters at 22 feet—take your choice; it can't be both combinations with a single connection.

Upon installation of this antenna at the writer's station, it was noted that regardless of which of the two bands the antenna was used on, the finoi stage of the transmitter did not detune from minimum plate current state when the antenna was connected to it, thus indicating an excellent impedance match throughout the entire antenna system. In addition, the system loaded very readily as demonstrated by the required loose coupling of the two-turn pickup loop at the final stage of the transmitter.

With a Class B modulated phone transmitter operating at not more than 150 watts input, no trouble has been experienced by the writer and others in working out satisfactorily on the 7, 14, and 28 mc. bands, even during the most congested hours. Sur-

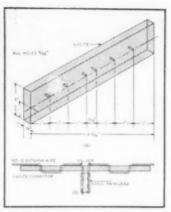


Fig. 3. Method of lacing wire through connector and attaching 300 ohm line.

prisingly enough, the antenna seems to be not at all critical as to tuning anywhere within these bands.

With the use of a non-resonant feed line as indicated and the absence of standing waves as borne out by test, maximum efficiency in the transfer of energy from the transmitter to the antenna is achieved, and broadcast interference is kept to a minimum. These desirable factors alone should appeal to any amateur, new or experienced, and make construction of this simple antenna system a next-weekend must.

The author's address is 2062 Eudora Street, Denver 7, Colorado. -50-

### QUALITY LOSS IN TAPE AND WIRE RECORDERS DUE TO METALLIC DUST By MATTHEW MANDL

OFTEN tape and wire recorders suddenly develop severe distortion, in conjunction with low output and poor erase qualities. In most instances this trouble is due to an accumulation of metallic dust which has rubbed off the tape or wire as it slides over the surfaces of the recording-crase heads. New reels of tape and new spools of wire are the worst offenders, though prolonged replay or re-recording of older tapes will also result in clogging of the recording and erase heads.

An excellent method for cleaning the tape recorder heads is to use a pipe cleaner or a toothpick with cotton wrapped around its tip. Either of these is dipped into carbon tetrachloride or acctone; then applied to both the recorder and crase heads, repeating with another pipe cleaner or cotton tip if the first one shows evidence of picking up considerable dust residue. Finish with a dry pipe cleaner, or allow the cleaner fluid time to evaporate before running the tape over the heads again. Sometimes the heads need cleaning after only one or two new reels have been run through.

In the case of the wire recorders, the aperture through which the thin wire runs on the recording head is too small to clean properly with a pipe cleaner or cotton-tipped toothpick. A thin piece of string or cotton thread can be used, again dipped in acetone.

Tape recorder heads need more frequent cleaning than wire recorders, because the recording compound on the tape rubs off more easily than metallic dust from wire. Occasionally the heads may clog so much that even acctone cleans it only with great difficulty. This occurs after long use without cleaning, and in this case it may be necessary to scrape off the cakes of recording dust which have adhered to the heads. A thin plastic aligning stick may be used for this purpose, or any other hard. pointed, non-metallic rod. A metal screwdriver or pin is not recommended because it will scratch the surfaces over which the tape rides. A scored and rough surface aggravates the trouble, for the heads will pick up more of the tape coating than before.

Pipe cleaner can be used effectively to clean clogged recording and erase heads.



RADIO & TELEVISION NEWS

# Study | Features

### Heathkits QUALITY **EQUIPMENT KITS**



### MODERN STYLING

Heathkits have brought a new conception of beauty to laboratories and service benthes.

Many organizations have standardized on Heathkits to make their shops.

The penels are produced in grey and maroon and the modern streamline cluminum headles give the instruments a pleasant, professional appearance. There is no waste space or folkeeffort to appear large in Meathkits—space on service benches is at a premium and the size of Heathkit instruments is kept as small as is consistent with good angineering design.



### COMPLETE KITS

When you receive your Heathkit, you are assured of every necessary part for the proper operation of the

Strument. Boustrie cobinet, handles, two-color panels, all tubes, test leads where they are a necessary part of the instrument, quality rubber line cords and plugs, rubber feet for cords and plugs, rubber feet for cord instrument, all scales and diels ready printed and calibrated. Every Meath, kit is 110V 60 cy, power fransfarmer operated by a husky transformer especially designed for the job.

### BEST OF PARTS

You will find many fomous nomes on the parts in your Meathkit. Mellary switches and filter condensers, Chricogo Transformer Corporation and Electrical Assembly Transformers, Centralable Patentioneters, Belleville Patentioneters, Editorial Patentioneters, C. E. E. State Condensers, Control Patentioners, C. E. State Condensers, Control Patentioners, C. E. State Condensers, Eby binding post and many other quality parts. The finest of parts are used to assure long trouble-free service from Heathkits.



### PRECISION PARTS

Wherever required, the finest quality 1% ceramic resistors are supplied. These require no aging and do not shift. No matching of runnan resistors is required. You amid do not shift. No matching of common resisters is required. You find in Heathkit the some quality voltage divider resistors as in the The transformer, are designed especially for the Newthit unit. The scape transformer has two electrosteric shields to prevent inferenction of AC fields.

These transformers are built by several of the finest transformer componers in the United States.





### LARGE EASILY READ CALIBRATIONS

No charts or calculations are necessary to use any Neothkit properly. All scales are simply and plainly marked.

The operator instantly knows the proper use of the instrument and can proceed confidently. No multiplication is required as each scale is calibrated independently of the others.



### COMPLETE INSTRUCTION MANUALS

Everyone is pleased at the thorough instructions covering the assembly of each Heathkit instrument. Every detail of the assembly is covered, together with sections on the use of the instrument and trauble shooting instructions in case of difficulty. Actual photos of the assembled instrument enable fast and accurate assembly, clear schemister and patients and actually assembled instrument enable fast and accurate assembly, clear schemister and patients and actually assemble to a complete the writing to be completed quickly. Everyone is pleased at the thor-



Heathkit chassis are precision punched to fit the quality parts supplied. The grey crackle aluminum cabinet and the two-colar panels are die punched to assure proper fitting.

Many builders have written marveling at the ease with which assembly can be accomplished.

can be accomplished.
The chassis are specially engineered for easy assembly and wiring — there are no small, tight corners which cannot be reached—the ends of the chassis are left apen in order that installation of parts and soldering can be done with both hands.



### IDEAL FOR SCHOOLS

ifeathkits have been adapted as stendard equipment of many of the largest universities and calleges. The low cost plus the fact that the students learn by actual assembly make them ideal training mediums. Munny high schools and small tolleges are finding that they too can have a madern physics and electronics laboratory by using Healthkits. Some of the largest technical Some of the largest technical contents as the best macns, of securing the necessary equipment to start their own shops.



EXPORT DEPT. 13 East 40th St. NEW YORK CITY (16) CABLE ARLAS - NY

The HEA COMPA ... BENTON HARBOR 15, MICHIGAN



### Heathkits ARE LABORATORY ENGINEERED . . .

### The NEW V-4 Heathkit VACUUM TUBE VOLTMETER KIT

### Features Accessory probes (extra) extend ranges to 10,000 Valts and 100 Megacycles. Uses 1% precision ceramic divider resistors. Medern push-pull electronic voltmeter.

- Meter scale 17% longer than average

- Meter score 1770 longer man areas 419" meter Modern streamline 200 up meter. New modern streamline styling. Burn-out proof meter circuit. 24 Complete ranges. Isolated probe for dynamic testing. Most beautiful VTVM in America.

circuit.

Electronic AC circuit. No current drawing rectifiers.

Shorterproof plastic meter face. • Most beoutiful VIVM in America.

The new Heathkit Model V-l Vacuum Tube Volumerer has dozens of improvements. A new modern streamlined 200 micromapree meter has Alnico V magnet for fast, accurate readings. The new electronic AC voltmeer circuit incorporates an entire new balance control which eliminates contact potential and provides greater accuracy. New simplified wirches for quicker assembly. New snap hattery mounting is on the classis for easy replacement.

The Heathkit VTVM is the only kit giving all 16-3007, 0-1000V and can be extended to 18-000V and 0-10,000V DC with accessory probe at slight extra core Electronic chammerer has six ranges measuring resistance accurately from 1 ohn to one billion ohms. Meter pointer can be offered to report of the probe is isolated for dynamic measurements. Has db scale for making gain and other audio measurements.

The DC probe is source for dynamic measurements and step-by-step instructions for easy audio measurements.

The new instruction manual features pictorial diagrams and step-by-step instructions for easy assembly. The Heathkit VTVM is complete with every part — 110V transformer operated with test leads, tubes, light aluminum cabinet for portability, grant 4½% 200 microamp meter and complete instruction manual.

Order now and enjoy it this entire season. Shipping weight 8 lbs., Model V-4



THE FINEST VTVM KIT AVAILABLE FOR THIS PRICE.

Accessory: 10,000V high voltage probe, No. 310, \$4.50. Accessory: RF crystal diode probe kit extends RF range to 100 Mc., No. 309, \$6.50.


### New Heathkit HANDITESTER KIT
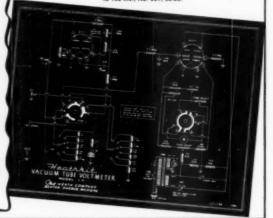
### Features

- Beautiful streamline Bakelite
- AC and DC ranges to 5,000
- Valts.
  1% Precision ceramic resistors.
  Convenient thumb type adjust
  - 400 Microampere meter
- 400 Microampere meter
   mevoment.
   Quality Bradley AC rectifier.
   Multipliying type ohms ranges.
   All the convenient ranges 10-30-300-1,000-5,000 Veits.
   Earge quality 3" built-in meter.

• Surge questry 2" built-in meter. A precision portable volt-ohm-mili-ammeter. An ideal instrument for memory, hobbysist, etc., experi-menters, hobbysist, etc., experi-menters, hobbysist, etc., experi-menters, hobbysist, etc., and meeter movement. Twelve complete ranges, precision dividers for accuracy. Easily assembled from com-plete instructions and pictorial dia-grams. An hour of assembly saves one-half the cost. Order today, Model M-1. Shipping wgt., 2 lbs.





EXPORT DEPT 13 East 40th St. NEW YORK CITY (16) CABLE ARLAB - N.Y.

... BENTON HARBOR 15,

MICHIGAN



# TEST INSTRUMENT KITS



Heathkit PUSH-PULL EXTENDED RANGE 5" OSCILLOSCOPE KIT Features

- The first truly selevision oscilloscape.
  Tremendous sensitivity. D& Volt RMS per inch defloction.
  Fush-pull vertical and herizontal amplifiers.
  Useful frequency range to 2½ Megacycles.
  Extended sweep range 15 cycles to 70,000 cycles.
  New television type multivibrators sweep generator.
  New magnetic allay shield included.
  Still the amazing price of \$39.50.

• Still the amening price of \$39.50.
The new 1950 Push Pull 5" Oscilloscope has features that seem impossible in a \$39.50 oscilloscope. Think of it — push-pull vertical and horizonal amplifiers with remendous sensitivity only vix one-hundredths of a voli required for full inch of deflection. The weak impulses of relevation can be besitted to full size on the free-inch streen. Faces was couldn't see before. Amazing frequency improved push-pull amplifiers. Only Heathkit Oscilloscopes have the frequency range required for elevation. New type multi-whrator sweep generator with more than twice the frequency range. I5 cycles or \$0,000 cycles will actually synchronize with 250,000 cycle siznal. Dual positioning controls will move trace over anistection of the screen for observation of any part. New magnetic alloy CR tube shield protects the instrument from outside fields. All the same high quality parts, cased electrostatically shielded power transformer, aluminum cabinet, all tubes and parts. New instruction manual now has complete step-by-step pittorials for castest assembly. Shipping weight, 25 lbs. Model O-5.

# Heathkit ELECTRONIC SWITCH KIT

DOUBLE THE UTILITY OF ANY SCOPE

An electronic switch used with any oscilloscope provides two separately controllable traces on the screen. Each trace is controlled independently and the position of the traces may be varied. The input and output traces of an amplifier may be observed one above the other or one directly over the other illustrating perfectly any change occuring in the amplifier. Distortion-phase shift and other defects show up instantly, 110V 60 cycle transformer operated. Uses 5 tubes (1 6X5, 2 6SN7's. 2 6SI7's). Has indivdual gain controls, positioning control and coarse and fine switching rate controls. The cabinet and panel match all other Heathkits. Every part supplied including detailed instructions for assembly and use. Shipping weight 11 lbs. Model S-1



EXPORT DEPT. 13 East 40th St. NEW YORK CITY (16) CABLE ARLAS - N.Y


# Heathkits

### New 1950 VERNIER TUNING RE Heathkit SIGNAL GENERATOR KIT Features

- New 5-to-1 ratio vernier tuning for ease and accuracy.
- New external madulation switch use it for fidelity twitch -
- · Covers 150 Kc. to 34 Mc on
- 400 cycle audio available for audio testing.
- Most modern type R.F. oscillator.
- New precision coils for greater output.

Convers 150 Kc to 34 Mc on fundamentals and collibrated strong hearmonics to 102 Mc.

The most popular signal generator kir has been vasily improved — the experience of thousands combined to give you the best Check the features in this fine generator and consider the low price \$19.50. A best buy for any shop, yet inexpensive enough for thousands combined to give you the best Check the features in this fine generator and consider the low price \$19.50. A best buy for any shop, yet inexpensive enough for the second of the construction of the construction as variable audio signal. Internal with the make fidelity checks on receivers by inserting a variable audio signal. Internal with the construction of the construction of the construction of the construction. The generator is \$10.00 to \$1

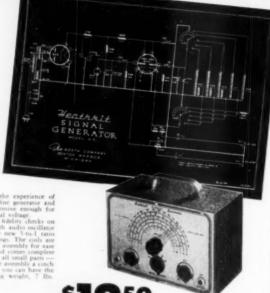

# Heathkit

### SINE AND SQUARE WAVE AUDIO GENERATOR KIT

Experimenters and servicemen working with a square wave for the first time invariably wonder why it was not introduced before. The characteristics of an amplifier can be determined in seconds compared to several hours of tections plotting using older methods. Mage by stage, amplifier testing is as easy as signal tracting. The low distortion less than 176: and linear output (± one db) make this Heathlett equal or superior to factory bull equipment selling for three or four times its price. The circuit is the popular RC, tuning circuit using a four gang variable condenser. Three ranges 20-200, 200-200, 2,000-20,000 cycles are provided by selector switch. Either sine or quare waves instantly available at slide switch. All components are of highest quality, cased 1 10V. 60 cycle power transformer. Mallory FP. fitter condensers. 5 tubes, calibrated two-color panel, grey crackle aluminum cabinet. The detailed instructions Shipmake assembly an interesting and instructive few hours. Shipmake assembly an interesting and instructive few hours. Shipping weight, 12 lbs. Model G-2

Nothing ELSE TO BUY

EXPORT DEPT 13 East 40th St. NEW YORK CITY (16) CABLE ARLAS - N Y

... BENTON HARBOR 15. MICHIGAN

# TO USE THE Best **F WORKMANSHI**



# Heathkit TUBE CHECKER KIT

Features

- Has gear driven roller chart.
- Has lever switching for speed
- Complete range of filament valtages.
- 5. Uses latest type lever switches.
- Uses beautiful shatterproof full view meter.
- Large size 11" x 14" x 4" camplete
- 9. Checks new 9 pin miniatures

9. Checks new 9 pin miniatures.

Check the features and you will tealize that this Heathkit has all the features you want. Speed, simplicity, beauty, protection against obsolescence. The most modern type of tester — measures each element — beautiful Bad-Good scale, high quality meter — the best of parts — rugaed oversite 110V. 60 cycle power transformer — finest of Mallory switches — Centralshotontrols — quality wood cabinet — complete set of sockets for all type tubes including blank spare for future rypes — fast action gear driven roller chart uses brass gears to quickly locate and set up any type tube. Simplified switching cuts necessary time to minimum and saves valuable service time. Short and open element check. No matter what arrangement of tube elements, the Heathkir flexible switching arrangement easily handles it. Order your Heathkir Tube Checker today. See for yourself that Heath again saves you two-thirds and yet retains all the quality — this tube checker will pay for itself in a few weeks — better build it now.


Complete with detailed instructions, all parts, cabinet, roller chart, ready to wire up and operate. Shipping weight, 12 lbs. Model TC-L.

Only \$2

#### Heathkit BATTERY ELIMINATOR KIT

Now a bench 6 Volt power supply kit for all auto radio testing. Supplies 5 - 7½. Volts at 10 Amperes continuous or 15 Amperes intermittent. A well filtered rugged power supply, uses beavy duty selenium rectifier, choke input filter with 4.000 MPD of electrolytic filter. 0 - 15 Volt meter indicates output. Output variable in eight steps. Excellent for demonstrating auto radios. Ideal for servicing—can be lowered to find stickly vibrators or stepped up to equivalent of generator overload—easily constructed in less than two boars. Competers in server respect. Shipping sext. 19 Dec. two hours. Complete in every respect. Shipping wgt., 19 lbs. Model BE-1

nothing ELSE TO BUY

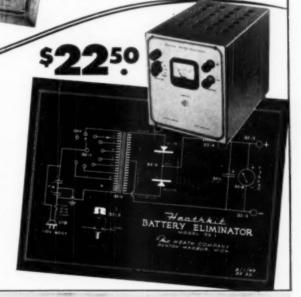

EXPORT DEPT 13 East 40th St. NEW YORK CITY (16) CABLE ARLAB - N.Y.

COMP ... BENTON HARBOR 15.



# Heathkits ELIMINATE

#### Heathkit TELEVISION ALIGNMENT GENERATOR KIT

Everything you want in a television alignment generator. A wide band sweep generator covering all TV frequencies 0 to 46 — 54 to 100 — 174 to 220 Megacycles, a marker indicator covering 19 to 42 Megacycles, do not seen in the calibrated sweep width 0-50 Mc. — mechanical dirent inductive sweep. Husky 110V, with 1000 to 1 tange — high output on all tracempos aromators with 10,000 to 1 tange — high output on all tracempos aromators with 10,000 to 1 tange — wenier diven main calibrated dial with over 45 inches of calibration — vernier driven main calibrated dial with over 45 inches of calibration — vernier driven calibrated indicator marker tuning. Large grey crackle cabinet 16½" x 10½" x 7-3/16". Phase control for single trace adjustment. Uses three high frequency triodes plus 5½ rectifier — split stator tuning condensers for greater efficiency and accuracy at high frequencies — this Heathiki is complete and adequate for every alignment need and is supplied with every part—cabinet, calibrated pand, all coils and condensers wound, calibrated and adjusted, tubes, transformer, test leads — every part with instruction manual for assembly and oue Actually three instruments in one — TV sweep generator — TV AM generator and TV marker indicator.



HEALTRIL IMPEDANCE BRIDGE

New Heathkit MPEDANCE BRIDGE

A LABORATORY INSTRUMENT NOW WITHIN THE PRICE RANGE OF ALL

Measures inductance from 10 microheneis to 100 henries capaci-tance from 00001 MFD, to 100 MFD. Resistance from 01 ohms to 10 megohms. Dissipation factor from .001 to 1. "Q" from 1 to 1000.

Ideal for schools, laboratories, service shops, serious experi-

to 1000. Ideal for schools, laboratories, service shops, serious experimentees.

An impedance bridge for everyone — the most useful instrument of all, which heretofore has been out of the price range of serious experimenters and service shops. Now at the lowest price possible. All highest quality parts. General Radio main calibrated control. General Radio 1000 cycle hummer. Mallors ceramic switches with 6th degree indexing — 200 microamp zero center with the serious experiments of the processional type binding posts with standard 54." centers. Beautiful birth cabinet: Directly calibrated "Q" and dissipation factor scales. Ready calibrated expective and industrance standards of Silver Mica. accurate to 15. of 1% and with dissipation factors of less than 50 parts in one million. Provisions on panel for external generator and detector. Measure all your unknowns the way laboratories do — with a bridge for accuracy and speed.

Internal 6 Volt battery for resistance and hummer operation. Circuit utilizes Wheastone, Hay and Maxwell circuits for different measurements. Supplied complete with every quality part — all calibrations completed and instruction manual for assembly and use. Deliveries are limited.

EXPORT DEPT 13 East 40th St. YORK CITY (16) CABLE ARLAS-N.Y.

24

COMPA ... BENTON HARBOR 15. MICHIGAN

# DIFFICULT METAL FABRICATION.

# NEW Heathkit SIGNAL TRACER AND UNIVERSAL TEST SPEAKER KIT

The popular Heathkit Signal Tracer has now been combined with a universal test speaker at no increase in price. The same high quality tracer follows signal from antenna to speaker, locates intermittents, defective parts quicker, saves valuable service time, gives greater income per service hour. Works equally well on broadcast, FM or TV receivers. The test speaker has assortment of switching ranges to match push-pull or single output impedance. Also tests microphones, pickups, PA systems, comes complete cabinet, 110V. 60 cycle power transformer, tubes, test probe - all parts and detailed instructions for assembly and use. Shipping Wt., 8 lbs. Model T-2.

Nothing ELSE TO BUY

Heathkit

# CONDENSER CHECKER KIT


Features

- Power factor scale
   Measures resistance
   Measures leakage
   Checks paper-mica-electrolytics
- Bridge type circuit
   Magic eye indicator
   110V. transformer e
   All scales on panel

Checks all types of condensers, paper-mica-electrolytic ceramic over a range of .00001 MFD, to 1000 MFD, All on readable scales that are read direct from the panel. NO CHARTS OR MULTIPLIERS NECESSARY. A condenser checker anyone can read without a college education. A leakage test and polarizing voltage for 20 to 500 volts provided. Measures power factor of electrolytics between 0% and 50%. 110V. 60 cycle transformer operated complete with rectifier and magic eye tubes, cabinet, calibrated panel, test leads and all other parts. Clear detailed instruction for assembly and use. Why guess at the quality and capacity of a condenser when you can know for less than a twenty dollar bill Shipping weight, 7 lbs. Model C-2.

EXPORT DEPT. 3 East 40th St. NEW YORK CITY (16) CABLE: ARLAB - N Y.

... BENTON HARBOR 15,

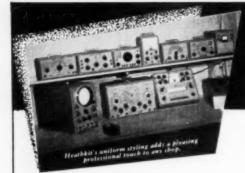

# Heathkits PROVIDE **PROFESSIONA** LABORATORY APPEARANCE

New Heathkit BROADCAST AND 3 BAND SUPERHETERODYNE RECEIVER KIT

BROADCAST MODEL BR-1 550 to 1600 Kc.



Two new Heathkit Superheterodynes featuring the best of design and material. Beautiful six inch slide rule dials — 110 V, 60 cy. AC power transformer operated-metal cased filters-quality output transformers, dual iron core metal can IF transformers -motor and phono pickup jack. Each kit is complete with all parts and detailed instruction booklet. Pictorial diagrams and step-by-step instructions make assembly quick and easy.

3 BAND MODEL AR-1 550 Kc. to 20 Mc.



Ideal AC operated superheterodyne receiver for home use or teplacement in comole cabinet. Comes complete with attractive metal panel for advinct mounting Modern circuit use 12KS conserver, 128H7 input IF stage, 12CS output IF stage and first audio 12A6 beam power output stage, 5Y5 recriber. Excellent sensitivity for distant reception with selectivity which effectively

The husky 110 V. cased power transformer is conservatively rated for long life The illuminated vix inch slide rule dal is accurately calcilibrated for long life-tion. Enjoy the pleasure of assembling your own fine home receiver. Has tone, volume, tuning and phonor-rable controls. Chassis size 24% x 3" x 1215". Comes repliere with all parts including quality output transformer to 3.4 ohm work; oil, tolles, instruction manual, etc. (less speaker). Shipping We, 10 lbs. No. B&. 1 Receiver \$19.50.

No. 335 Communications Type Table Model Metal Cabinet No. 320 High Quality 5" PM Speaker for above

Enjoy the thrill of world wide short wave reception with this fine new AC operated Heathkit 3 band superheterodyne — amazing sensitivity 15 microvolt or better on all bands. Continuous coverage 550 Kc. to over 20 Mc Easy to build with complete step-by-step instructions and pictorial diagram. Attractive accurately calibrated via tinch slide rule dual for easy tuning. Six tubes with one dual purpose tube gives seven tube performance. Beam power output tube gives over 3 warts output.

Heathkit PUSH-PULL HIGH FIDELITY AMPLIFIER KIT



\$12.50

Build this high fidelity push-pull amplifier and save two thirds the cost - has two pre amplifier stages, phase inverter stage and push-pull beam power output stage. Comes complete with six tubes-quality output transformer (to 3-4 ohm voice coil) tone and volume controls-varnish impregnated cased J10V. power transformer and de-tailed instruction manual and all small parts. Six watt output with output flat within 11/2 db between 50 and 15000 cycles. Build this amplifier now and enjoy it for years. Shipping Wt. 7 lbs. Model A-4 12" PM Speaker for above \$6.95

ORDER BLANK						
ORDER BLANK						
		24	R .		-	183

HEATH CO. BENTON HARBOR MICHIGAN	FROM	SHIP VI —Parcel Po —Express —Freight —Best Way
Quan	DESCRIPTION	Price Tot

PLEASE SHIP COD ... POSTAGE ENCLOSED FOR POUNDS

EXPORT DEPT. 13 East 40th St NEW YORK CITY (16) CABLE ARLAB - N. Y

COMPAN ... BENTON HARBOR 15. MICHIGAN

# What's New in Radio

For additional information on any of the items described herein, readers are asked to write direct to the manufacturer. By mentioning RADIO & TELEVISION NEWS, the page, and the issue number, delay will be avoided.

#### CONVERTER LINE

A new line of d.c. to a.c. converters has been announced by Cornell-Dubilier Electric Corporation of South Plainfield, New Jersey. These "Powercons" have been de-

These "Powercons" have been designed for use with radio or television



equipment and are filtered for clear reception. They are capable of starting under full load without the necessity of starting the converter first and then applying the load. Several of the 32 and 110 volt models include the company's "Phantomswitch" circuit for automatic starting and stopping when the a.c. load switch is operated.

A dozen different models of converters are available ranging from units capable of operating from a 6 volt battery source to units capable of converting 110 volt d.c. to operate television receivers in d.c. urban areas. Complete data and further information are available from the company.

#### FILM SYNCHRONIZER

The Amplifier Corp. of America, 398-2 Broadway, New York 13, New York, has developed a simple and efficient system for synchronizing a mag-



netic tape recorded script with any automatic slide projector without the use of tone signals or push-buttons.

A high-fidelity "Twin-Trax" dual-

channel tape recorder is used as the recording and playback medium. At pre-set intervals, a pulse is sent to the projector, activating the projector's tripping mechanism. A pair of leads from the recorder to the projector is the only electrical or mechanical connection required.

The script is recorded in the normal manner on sound recording tape. At each point in the script where the slide is to be changed, a 2" long, 1s" wide strip of special self-adhering copper foil is placed on the back, or uncoated side, of the recording tape. As the recording tape passes a laminated switch on the recorder during playback, the copper foil shorts out a section of the switch which activates a relay to send the tripping pulse to the projector.

Full details and operating specifications on this film synchronizer are available from the company's Audio-Visual Division.

#### S.W. CONVERTER

A new auto radio short-wave converter that makes reception possible



on all makes and models of autoradios has just been announced by Phileo International Corporation of 50 Broadway, New York 4, New York.

The short-wave converter, Model SW-4940, features six push-buttons that provide for the instantaneous selection of 49 meter, 31 meter, 25 meter, 19 meter, 16 meter, and standard broadcast bands.

The unit mounts compactly under the dashboard. It uses two miniature tubes and has a fixed-tuned r.f. stage.

#### TAPE RECORDER

National Recorder Co. of 7120 Melrose Avenue, Los Angeles 46, California has developed a new tape recorder which provides two hours of recording time (at 7.5 inches per second) instead of the customary one hour's recording. The unit operates on a new patented principle which eliminates the rewinding of tape before playback.

Instead of using the conventional 14 inch tape, the new recorder uses a 1 CITY STATE.

# These Men are Getting PRACTICAL TRAINING



# IN RADIO-

TELEVISION SETS
RADIO RECEIVERS
F.M. RECEIVERS
IN THE GREAT COYNE

Big opportunities are waiting for men who know the practiced and technical end of Kadho and Telecision. That's what you get at COVNE—besides practical Shop Training in F.M., Electronics and other branches of the gator field. Recommer, Feltoday, and Radio is one of the biggest.

#### NOT "HOME STUDY" COURSES

All Coyne Training is given in our mamouth Chicago training shops. We do not teach by mail. Von train on actual equipment, under friendly instructors. Previous experience unnecessary. Hundreds of firms employ Coyne trained mea.

# OLDEST, LARGEST, BEST EQUIPPED SCHOOL OF ITS KIND IN AMERICA

Come to the Great Shops of Coyne in Chicago. Established 1899—now in our 51st Year, Fully approved for G.L training. Finance plan for nonveterans.

#### MAIL COUPON FOR FREE BOOK

Send today for lag new neck packed with large pictures taken in Coyne Shapa No obligation. No salesman will call, Get the facts now!

COYNE 9, W. Cooke, Press.

ELECTRICAL, RADIO & TELEVISION SCHOOL.
500 9. Peuline Bt., Dept., 39-18.
(Diamois Cheeges 12, Blamois



į	B. W. COOKE, Pres. COYNE Electrical, Radio & Television Schoose S. Paulina Street, Dept. 26-18, Chicago 12, I	o E
E	Send FREE BOOK and full details on Bad Television Course.	200
ľ	NAME	
	ADDRESS	

February, 1950



JUST PUBLISHED - Ask your Stancor distributor or write for your free copy of the New STANCOR TV COMPONENTS REPLACEMENT GUIDE, Bulletin 338C. Lists Stancar replacement components for two-hundred and fifteen models and chassis made by forty-three leading receiver manufacturers.

20176 used in model 630TS Deflection Yoke, Stancor Part Number DY-1. Exact duplicate of RCA type 201D1. For use with direct viewing kinescopes such as 7DP4 and 10BP4.

Focus Coil. Stancor Part Number FC-10. Exact Duplicate of RCA type 202D1. For use with magnetifocused kinescopes such as RCA type 10RP4.

Vertical Blacking - Oscillator

Transformer, Stancor Part Num-ber A-8121. Exact duplicate of RCA type 208T2. For general

of 60 cps required to drive grids of vertical discharge tubes.

Plate and Filament Transformer. Stancor Part Number P-8156. Exact duplicate of RCA type

Herizontal Deflection Output and HV Transformer. Stancor Part Number A-8117. Exact duplicate of RCA type 211T1. For use with ing kine es, such as types 7DP4 and 10BP4.

For complete specifications and ces of these and other Stancor TV replacement components, see your Stancor distributor or write tape two inches in width. The wide tape allows the recording of twelve tracks per inch instead of one per quarter inch. This feature utilizes the maximum amount of tape possible while cutting waste tape surface to a minimum. Upon reaching the end of the tape, the recording head drops



down one track and the tape reverses, giving continuous recording in the op-posite direction. The time cycle for this operation is 1/60th second.

#### "ELECTRONIC BLACKBOARD"

As an aid in teaching television and electronics courses, Television Equipment Corporation of 238 William Street, New York 7, New York has an-nounced a new "Electronic Blackboard."

The new T-602 projection oscilloscope delivers pictures either 18 x 24



inches for small groups or 8 x 10 feet for larger audiences. The light-gathering power of its Bausch & Lomb refractive optical system is said to provide the largest, brightest cathoderay tube display now commercially available.

Particular new features including functional centering controls, improved calibration circuit, driven and recurrent sweeps, line frequency deflection and phasing, as well as novel brightening and Z-axis intensity circuits increase the basic usefulness of the T-602

#### REPLACEMENT CONTROLS

A packaged set of specially designed parts, tradenamed "Concentrikit" is being marketed by International Resistance Co. of 401 N. Broad Street, Philadelphia 8, Pa.

From this kit, radio technicians are enabled to assemble a variety of concentrics to meet over an estimated 90 per-cent of their replacement require-

(Continued on page 118)

for Television Catalog 337

#### STANDARD TRANSFORMER CORPORATION

3584 ELSTON AVENUE

CHICAGO 18, ILLINOIS

FOR BARGAINS IN Receivers, Transmitters, Amplifiers, Television Sets, Batteries, Instruc-Read RADIO & TELEVISION NEWS CLASSIFIED COLUMNS

### HAMMOND ORGANS WANTED

Any Model - Any Condition

Box 492, % RADIO & TELEVISION NEWS

> 185 N. Wabash Ave. Chicago 1, III.

#### SUB-MINIATURE Printed Electronic Circuits

on ceramics, glass electron tubes, plastics and paper bases from your Special attention given to small orders. All service and cor respondence held strictly confidential.

Write for full details and our latest bulletins on printed circuit components and assemblies available from

PLASTICS & ELECTRONICS COMPANY P.O. Box 38, Station J Suffalo 8, New York



ULAR S110.00 VALUE ON SALE AT MCGEE FOR A World's Finest Radio Value for Custom Installation

nown being at \$33.21, or the at \$12.95, with your 8-56



HALLICRAFTERS 8.59 S-TUBE FM-AM CUSTOM **CHASSIS** 

Pre-amplifier for \$-56 and \$-59 \$3.95



#### FM-AM RADIO-PHONO COMBINATION Sale Price \$59.95

**Build Your Own Radio Station** Ministure



Our Leader Changer Scoop \$11.95, 2 for \$22.95



212 x 11" Plays 10" A super duper value sup price \$12.08. 2 for

#### SALE ON RECORDING WIRE

ST. GEORGE WIRE RECORDER MECHANISM \$22.95

WIRE RECORDER CONVER

#### COMPLETE RADIO AND AMPLIFIER KITS BEST QUALITY AND PRICES DETROLA-SCOOP

#### 6-TUBE AC 2 BAND RADIO KIT \$9.95 BIGGEST RADIO KIT VALUE IN U. S. BUILD A RADIO WITH MATCHED "DETROLA" PARTS

#### New 3-Way PORTABLE RADIO KIT ONLY \$9.95



#### GAROD PERSONAL PORTABLE KIT

McGEE'S NEW FM-AM-PA KIT \$39.95



1 P.A. system, a recording amplifier, or for a high fidelity T.V. size, 15(g. 8.71 g. 8.12); ready morehold. Everything furnished ubes: 0.465, 0.987 V. 2-0.146, 0.470, 0.100, 0.000, 2-12ATT, 2-0.06 socious or ends wired cools and swhether, to make this sixt easier section is ready sixed cools and swhether, to make this sixt easier section of the cools of the cools

#### 6-TUBE AC-DC KIT \$11.95 5-TUBE MODEL \$9.95



### SOLAR F.P.

النب	W. S. T.	COI	AD	. SAL	E
405-307		v. FP cond	1	121	5.29
	Mrs 150	v. FP cond		8.2	.29
MO	SH4 150	v FP cond	- 1	W57.75	.29
901-40		v FP cond	1	8.3	.39
30-50	1500y 2				
		100 109	2.5	2×2	49
80-80	3818 150	V			-39
20.20		40-40-25v	2.7	8.45	39
		v 10 23v		83	49
25.23	3574 200	v FP cond		2.3"	.39
40	2504 250	v 20 23v	- 1 -	942"	1.9
50	300v. 4			4	
340		20 254	1	A714"	.49
100 A 1 A 100	SECRETARY.	e 20 25e		8.7	39
20		w 20 25w	î.	×215	39
40-10		e 20 25v	Ť.	8216°	.49
8		w FP cond	- 1		29
			÷	42"	29
10		w FP cond	1	×2"	-34
1.6			- 6		.34
24		r PP cond.			
.349		s FF cond		× 1	39
293	MITS ADD				
		25 v	1		3.9
		n FF cond	- 1	43"	.34
		re FP count	- 1	4219"	.49
15-15	MANA 455	W 20 25W	1	431	.59
20-111	MIG 850	W 25 25W	1	8.3	5.0
30-15	10 Mid 4				



# ALUMINUM TUBULAR-ELECTRO-

12c Order 100 AGO VOLT BY-PASSES



3-SPEED RECORD PLAYER KIT \$16.95

12 WATT PORTABLE AMP KIT \$12.95

> 6-110 VOLT POWER SUPPLY KIT, \$14.95

Sic arm, with 3 walt L-82

McGEE RADIO COMPANY

TELEPHONE VICTOR 9045. WRITE FOR FLYER 1422 GRAND AVE., KANSAS CITY, MISSOURI

#### McGEE'S FEB. SPECIAL - 20 VIDEO COILS AND SARKES TUNER \$1495



TELEVISION VIDEO COIL KIT-20 MATCHED COILS FOR PICTURE AND SEPARATE \$795 SOUND I. F.

nd TV cultiv video and smind IV. Medice Scorp price \$1.65. Twice

KR5 for IV seeds and to 16 of 10 order for the control of the cultivation of the







10" TV CABINET \$595 Stock No. RY-10



FARNSWORTH Partially Built-Up CHASSIS Stock No. GYZ-60

Buy Both RY-10 Cabinet and GVZ Chassis for \$7.95



T.V. BOOSTER-REGENCY-\$17.61 ANCHOR-\$22.05 Regency 08-213 low and high band television booster. Dual Regency 08-213 low and high band television booster. On the takes with true core push pull RF amplification. For either 3 of 300 down inputs. With booster off. Ant. is commerced direct to receiver. Weight 3 lbs. Not. . \$17.61



#### TELEVISION ANTENNAS-ON SALE

felexision Artennas, Rest prices. Top quality, R's Motice for T.V. Corneal Model RT-6441, as pictured with 6 foot mast, bracket and foot muuti, Realisis set \$6.75, insideal attenues for slacking, on the above automa-score as slaver actions to the mast. Not. \$4.05. Stork No. 87-52. No. 

WIRE RECORDER



# MUSICAL P.A.



P. A. SYSTEM \$69.95

NATIONALLY FAMOUS 15-INCH CUSTOM CHASSIS WITH PICTURE TUBE

Regularly \$250.00 McGEE'S SCOOP PRICE



Pocus Coil 202D1, 247 ohms DC re-sistance, for 10 or 12" picture tube, SAVE ON T. V. PICTURE TUBES



for 100 34c each

Popular G.T. Cartoned and Branded STANDARD BRAND TUBES HYVAC Guaranteed 39cia

HYVAC 49c BRACKET 6AKS 68G6 6J6

STANDARD BRAND 59C Every Day Numbers 59C 12SA7GT 12SK7GT 50L4GT

6L6GA-\$1.09 each, 10 for \$10.00 en Electric Type 15cH, a super heavy (1.6; lasts twice as lone—plugs in for \$1.95 vach; 10 for \$17.95.

V.R. CART. \$2.95

C.F. RPS010, with permanent needle \$2.95 warm to be for \$2.495. Rit of parts to build GSC7 type preampli-ter, \$2.49 extrs.

MAGNIFIER Stock No. HA-22 FOR 7-10-12 INCH TUBES

REGULAR \$25.00 TELEVISION

McGEE RADIO COMPANY With under. Bal. Sent C.O.D. With Under Description of the United Processing Control of the United Processing Co

# McGEE OFFERS YOU THE BEST SPEAKER VALUES IN THE WORLD

**ALUMINUM VOICE COIL** 

REPLACEMENT SPEAKERS-FACTORY PRICES

McGee's Aluminum Voice Coil Double X Jine. Mc-Gee offers you our Double X line of replacement P.M. Speakers. Made by a pioneer of the aluminum voice coil speakers. All of the Double X speakers have Almico V magnets. All aluminum voice coils with RMA standard 3.2 ohm impedance. Why pay twice as much for a replacement speaker? McGee buys them by the carload and sells them for half price. Every speaker is unconditionally guaranteed.

MODEL CU-13X 12-INCH "COAXIAL" WIDE RANGE SPEAKER \$ 195

\* Regular \$32.50 List On Sale at McGees for



MODEL P15-8

15-INCH "COAXIAL" WIDE RANGE SPEAKER \* NEW 1950 MODEL

\$62.50 List \$ \* Regular On Sale at McGees for

"IT WOOFS AS IT TWEETS"

20-20,000 CPS. Wide Range Base and Treble Boost, Amp. Kit \$29<sup>95</sup>





KIT \$9.95

VM-406





ANOTHER RED HOT

617.95 15-Inch 50 Watt WIDE RANGE SPEAKER 20 TO 12,000 CPS.

15 INCH JUKE BOX P.M. ONLY \$9.95



HIGH FIDELITY

Only

OUTPUT TRANS. 20 20,000 CPS aly .....\$6.95

BEST VALUE IN U.S.A.

12-Inch 25 Watt WIDE BANGE SPEAKER 35 TO 12,500 CPS. \$9.95

40 WATT OUTPUT

"CAPEHART" \$795

SALE MAGNAVOY 12" P.M. \$4.95



\$19.00

50-Watt 12" Super Heavy Duty P.M. \$13.95

NOW YOU CAN WIRE A COMMERCIAL QUALITY AMP. 20-WATT

RADIO SERVICE MEN



AMP. KIT

30-WATT AMP. KIT \$19.95 MAKES AN AMP, WORTH \$40.00

#### 12-WATT MUSICAL AMP KIT Only \$12.95





plastic front 12-C. net \$1.68,

JUKE BOX OPERATORS SPECIAL




McGEE RADIO COMPANY

TELEPHONE VICTOR 9045. Write for Fiver 1422 GRAND AVE., KANSAS CITY, MISSOURI


\$13.95

# WHAT IS YOUR PROBLEM?

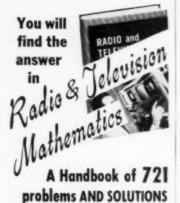

Save time and trouble. Arranged under radio and electronic headings and completely indexed for quick reference, these problems give you step-by-step solutions to every problem components arising in work on receivers, power supposed to the second series of the second second series of the second second series of the second s

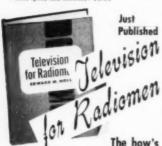Good practice for your FCC exams. This book shows you how to solve every problem requiring mathematics in the FCC STUDY GUIDE for licenses of all classes. You will find no better handbook for practice in solving problems with ease, speed and accuracy. \$6.00



# AND WHY'S in the practical terms of operation & servicing

This book explains the theory as well as the techniques of television construction, operation, and servicing in the clearest, most practical terms. It gives the radioman all the basic information he needs to meet the increasing demand for skilled television technicians. It shows how and uby all modern equipment operates; includes all the essential mathematics and especially good material on antennas, \$7.00

#### SEE THEM FREE

The Mi	acmillan Co., 60 Fifth Ave., New York 11
below.	send me a copy of the books checked I agree to remit in full or return the within ten days without further obligation.
8	Radio & Television Mathematics, \$6.00 Television for Radiamon, \$7.00
Signed	

# Receiver Servicing Without A Signal Generator

By JAMES KAUKE

A calibrated superhet plus a volt-ohmmeter is all that is required to handle occasional receiver service jobs.

N A rural or small-town locality, anyone whose neighbors know him to be a radio engineer is apt to be called upon for occasional receiver servicing. Where the volume of this work does not justify the expense of special instruments or a shelf full of service manuals, he can put his basic knowledge to work and get along with a volt-ohmmeter and a stable and accurately calibrated superheterodyne receiver which he may already own.

Many superheterodyne communications receivers make satisfactory substitutes for a signal generator, provided the operator knows the relationship of the local oscillator frequency to the tuning frequency for the receiver in question. To couple to the receiver local oscillator at high impedance, it is necessary only to thrust an insulated wire end into the appropriate coil can through the trimmer hole. The calibration of the receiver does not appear to be shifted by this, and the loosely-coupled signal is usually adequate for aligning the i.f. and r.f. tuning of receivers. A more elegant, though still inexpensive, way is to put into the communications receiver (author used a Navy RAX-1) a miniature tube connected as a cathode follower, loosely coupled to the receiver oscillator and feeding a concentric line connection. A 6C4 has about 400 ohms output impedance as a cathode follower, and the losses in a short line connected to it would not be serious; a 6J6 with both sides parallel (90 ohms) would actually match some lines.

Care should be taken that the heat from the additional tube does not affect any frequency-determining components of the receiver. If a true standard signal generator is desired, delivering known outputs at low impedance, a simple vacuum-tube voltmeter and a calibrated attenuator can be added at the end of the line. These parts, separable from the receiver, do not interfere with its normal use as a receiver.

The frequency range over which a signal can be obtained from the local oscillator of a superheterodyne receiver depends upon the receiver tuning range, the intermediate frequency, and whether the local oscillator operates above or below the incoming signal frequency. Table 1 shows the ranges of several receivers, band by band.

It will be seen that the RAX-1 (Unit

Table 1. Ranges of various superhets suitable for delivering signals to a receiver.

TYPE RECEIVER AND LF. FREQ.	TUNING RANGE	LOCAL OSC. (LO.)	REMARKS
RAX-1 Unit 1, 160 kc. Lf.	200-300 kc. 300-500 kc. 500-900 kc. 900-1500 kc.	360-460 kc. 460-660 kc. 660-1060 kc. 740-1340 kc.	LO above signal LO above signal LO above signal LO below signal
BAX-1 Unit 2, 915 kc. r.f.	1500-2400 kc. 2400-3800 kc. 3800-6000 kc. 6000-9000 kc.	2415-3315 ke. 3315-4715 kc. 4715-6915 kc. 5085-8085 kc.	LD above simil above simil to below simil
RAX-1 Unu 3, 2275 kc-1.f.		9.275-12,275 mc. 12.275-15.275 mc. 15.275-19.775 mc. 19.775-24,775 mc. 24,775-29.275 mc.	LO above signal on all bands in this unit.
BC-45) B 85 kc 11.	200-500 ke.	285-585 kc.	LO, above signal
BC 946-B 239 km LL	500-1500 km	739-1739 km	LO above signal
BC348.P 915 kc. Lt.	200 500 km 1.5-8.5 mm 8.5-6 mm 6.9.5 mm 9.5-13.5 mm 13.5-18 mm	1115-1415 km 2415-4415 km 4415-6915 km 6915-10415 km 6915-10415 km 12585-17085 km	above simil above simil above simil below simil below simil

YOU BUILD 'EM "

IN ONE EVENING THEY LAST A LIFETIME!

SAVE 50% WITH L

LABORATORY PRECISION

#### SENSATIONAL NEW EICO Model 360-K TV-FM SWEEP SIGNAL GENERATOR

FACTORY WISED AND TESTED
Model 360. Heady to use Sween Supplies \$39.95





#### NEW! MODEL 320-K SIGNAL GENERATOR

tide TV marker frequences. Highly stable Harties oscillator has range of 150 k. to 102 mc, with fundamentals to 24 mc. Colpits and conditions of the pure AOO cycle sine wave voltage for modulation. Use audio oscillator simplies to test distortion in audio occuliance with the condition of the co

FACTORY-WIRED AND TESTED \$29.95



#### VERSATILE MULTI-SIGNAL TRACER

Model 145-K. (figh gain—high frequency. Self-contained text speaker permits and the signal tracing of RF. for closed tracing with NTVM. Response in self-over 200 sec. 3-role transmitting pasel. 110-125 V. AC. Sizes 10°×"s 2°-z. Comes complete with tubes and during probe in lat

#### NEW EICO PUSH-PULL WIDE RANGE HIGH-

SENSITIVITY TV Model 425-K

ALL-NEW laboratory precision scope has Push-Pull deflection and .05 to .1 volts per not sensitivity. Wide range, flat from 6 rps to 500 åc, with full gain setting, useful to .2; nor. Wide-tange, multi-behavior, sweep section to plates of CRT available at rear of abnet. Z axis intensity medulation feature included. Size Styl-s17\*13\* high. Complete with 3-65878, 2-d37, and 58P1 CRT.

FACTORY BUILT OSCILLOSCOPE \$69.95



#### HIGH PRECISION VACUUM TUBE VOLTMETER Model 221-K

Tope in workbench versatility—15 different rouges? AC and BC rouges; 0.5-10-140-500.7

2 shus to 1000 megs in 5 steps. New features include Zero Center for TV discriminator alignment, 2-6 Meg. BC inpud impediance. Actually, and the step of the control of the co

FACTORY WIRED AND TESTED Medel 221. Name, but completely \$49.95



#### **DELUXE SIGNAL** GENERATOR

MODEL 315

band-spread vernier tuning for FM. AM, and TV. Voltage reg-ulator. Write for \$59.95 full details.

\$14.95

ASSEMBLED READY TO USE tory Rugged, built \$17.95



Model HVP-1 HIGH VOLTAGE PROBE

SEE THEM-TRY THEM-YOUR LOCAL JOBBER!

EICO Instruments and Kite are on display at your local

Prices Higher on West Coast

#### HIGH FREQUENCY RF PROBE

raid meters with the head plyson the MI FORM 1 53.78 to head plyson the MI FORM 1 53.78 to head plyson to the MI FORM 1 54.78 to head plyson to the Model PTGK same as above, but for accilionation to the Models PTG or FTG aimilar to show that factors are 55.78 topy sixed, ready to operate. Each 57.50

#### EASY-TO-FOLLOW SCHEMATIC & PICTORIAL DIAGRAMS

Come complete with every EtCG in strument K.t. Eart kill fully quaran-ters! In operate perfectly when as sention according to our simple in

EXCLUSIVE LIFE TIME REPAIR
SERVICE: For a minimal charge, we
sail repair and service year EICO in

ELECTRONIC INSTRUMENT CO., INC. 276 Newport Street, Brooklyn 12, N. Y.

### SAVE S ON SUN SURPLUS AND STANDARD SPECIALS!

### REPLACEMENT PARTS FOR SERVICEMEN

SPEAKERS	PHONO ARMS
4" PM\$1.85 5" PM1.95 615" PM2.49 6"x9" PM with	American Model 1J with CR1A 3.5 volt High out- put cartridge \$1.65
transformer \$2.89 8" PM 2.95 10" PM 3.95 12" 1000-ohm	Astatic SL-8 with L-26A cartridge \$1.89
field 6,95	Astatic D-9 with
15" 5500-ohm field 19,95	L-26A cartridge \$1.89

#### **Condensers for TV Replacement**

	1.005-5000 v. mica
.001-10,000 v59	\$0.39 . 4 for \$1.25
.0005-6000 v49	

POTENTIOMETERS,			
Assorted	.10	for	\$1.90

AMPLIFIER, 20 watts, Mike and Phono inputs, P.P. 6L6's Regal. Regular \$65.00 Reduced to \$24.95

RECORD CHANGERS, Single speed, various types, removed from new consoles, values up to \$65.00. \$14.95

### TEST EQUIPMENT

#### Clearance of Display Models!

RGP Electronic Multitester, VTVM, Model 668 Reg. \$77.50 Only	644.50
REINER, Laboratory VTVM, Measures R.F. up to 700 MC Model 451,	
Reg \$165.00 Only	99.50
RCP, Pocket Signal Generator: Model 710 AM—Reg. \$17.95. Unly Model 720 FM—Reg. \$19.95. Unly	
RCP, Pocket Multitester, 5000 ohm per volt, Model 499A, Reg. \$24.50 - Reduced to	17.50
RCP, Standard Signal Generator Model 705A, Reg. \$49.50—Reduced to	35.00
General Electric YTW1 Tube Tester - ites \$49.50 - Reduced to	37.50
Approved Electronics A-200 Signal Generator, Reg. \$47.50 - Reduced to	24.95
Ferret Model 728 TV-FM Sweep Gen- erator with Built-in variable market.	

Reg \$165.00—Reduced to 115.50
Speco, Capohmist Condenser and Resistor Substitution Box, Reg \$16.95
Reduced to 11.9
Industrial Instruments, Wheatstone

Bridge, No.2, Reg. \$125.00—Reduced to 94.50 Decade Box DR-50, Reg. \$65.00— Reduced to 49.56

Western Ohmmeter, los range 0-10/1000 ohns in leather vase, Model 689-IF. Reg. \$25.30—Reduced to. 14.95

TERMS All items F.O.B., Washington, D. C. All orders \$40.00 or less, cash with order, balance C.O.D. Foreign orders cash with order, balance C.O.D. Foreign orders cash with



I. F. of "B"				 	 	252 kc.
Nominal dial reading of "B"				 	 	900-1100 kc. (seldom accurate)
						. 1252 kc. (picked up by "A")
Signal frequency required	*			 * 4	 * *	1000 kc.
						1160 kc. (if "A" is RAX-1)
Tune "A" to		*				761 kc. (if "A" is BC-946-B)
	_	-	_	 _	 	

Table 2

Nominal dial reading of "B"							
Local oscillator of "B" picked up by "A" at			× ×				1082 kc.
"B" picks up local oscillator of "A" with RAX	I tuner	d to		 			1150 kc.
Or BC-946-B tuned to							751 kc.
Actual signal frequency							
Intermediate frequency of "B" is therefore .					*		92 kc.

Table 3

 or the BC-453-B plus the BC-946-B, would appear the best for delivering signals to align ordinary broadcast receivers. Doubtless there are numerous others which would be as good.
 BC-344-D, BC-433G, ARB, DZ-1, or the DZ-2 would also be of use for the number.

An accurately-calibrated receiver was specified as a signal source. Actually, many operations require only a moderately close calibration. The calibration can be checked if necessary and a curve drawn by tuning in stations of known frequency. A list of these is available from the Superintendent of Documents, GPO, Washington, D. C. A calibration of the receiver is equivalent to a calibration of the local oscillator, provided the intermediate frequency is accurately known. If another receiver is available as a detector, the local oscillator can be calibrated directly by zero beating against stations of known frequency.

In aligning typical receivers, call the receiver being used as a signal source "A," and the receiver under test "B." In cases where the i.f. for "B" is available directly from the oscillator of "A," for example, where "B" has 456 kc. i.f. and "A" is the RAX-1 (Unit 1) or BC-453-B as shown in Table 1, the RAX-1 would be set to 296 kc. to deliver a 456 kc. signal; the BC-453-B would be set to 371 kc.

In cases where i.f. for "B" is not available directly from oscillator of "A." usually where "B" has a very low i.f., or where "A" does not tune below i.f. or where "A" does not tune below the broadcast band or has an i.f. above its lowest tuning range, a signal of the necessary frequency can be produced in the mixer of "B" as follows: Tune "B" to some convenient setting and pick up its local oscillator on "A." Note the frequency. Set receiver "A" to deliver from its local oscillator a

signal which differs from the local oscillator frequency of "B" by the required intermediate frequency of "B," and feed to antenna input or mixer grid of "B." The intermediate frequency is then developed in the mixer of "B," if it is functioning properly, just as in normal reception. Table 2 shows the readings at various signal stages.

Without a service manual, the intermediate frequency of "B" may not be known unless it is stamped on the transformers. It may be determined by picking up the local oscillator of "B" with "A" and then ascertaining what setting of "A" gives a signal from the local oscillator of "A" which is picked up by "B." The tuning of "B" must not be changed during this test. Coupling should be loose. Naturally, if the i.f. trimmers of "B" are misadjusted very much, this measurement may be in error, but the trimmers may subsequently be reset to a different i.f. if the receiver can not be made to track (see Table 3).

The dial reading of "B," which in broadcast receivers is seldom accurate, plays no role in this measurement. Table 4 shows r.f. alignment and typical settings for the upper and lower ends of the broadcast band.

Since these signals are not modulated, it is desirable to connect a high-resistance d.c. voltmeter to the a.v.c. circuit of "B" as a tuning indicator. In the absence of this, one must tune by the carrier hiss. Overcoupled i.f. transformers can be adjusted symmetrically by detuning "A" 5 kc. each way and watching the voltmeter.

One of the first tests on a dead receiver having normal d.e. voltages should be an attempt to pick up its local oscillator on "A." Ordinary superheterodyne receivers can often be picked up at considerable distances.

Table 4

DESIRED SIGNAL	RECEIVER "A"	RECEIVER "A" SETTING
1340 kc.	RAX-1	1500 kc.
1500 kc.	BC-946-B	1261 kc.
550 kc.	RAX-1	- 390 kc.
550 kc.	BC-453-B	465 kc.

# DON'T MISS THESE IMPORTANT ARTICLES IN THE MARCH ISSUE

The Antenna Research Laboratory

The Batwing FM Receiving Antenna

Simulating TV Interference Patterns

The Mini-Rack Transmitter

An Effective Sync "Lock-in" Circuit

A TVI Filter for Coaxial Transmission Lines

Elimination of Radio Interference By Off-Frequency Inversion

Many Other Important Articles

RESERVE YOUR COPY AT YOUR NEWSDEALER OR USE SUBSCRIPTION CARD IN THIS ISSUE



CHICAGO, ILLINOIS



# NEW KITS TELEKITS NOW 4995

#### Jobbers: Write for Confidential Price Information

NEW TELEKITS 10-B \$69.95 7-B \$49.95 Less Tubes



Sparkling new Telekit 10:8 has 52-inch stress. Brand new congact lay-out has video tobe mounted on chassis. Big illustrated see the follow startfactor hook guides you tree to follow startfactor hook spark to the see through easy assembly. No spark to the seed of television is required. All you specified to the seed of the startfactor of seed of seed of the seed of

Write for catalog listing 10-8 and 7-8 Telekits New 7-8 Telekit for 7-inch tube, \$49.95, 7-8 cabi net, \$15.95 and \$24.50.

TELEKIT BOOSTER 12.95



This Telekit booster will bring in TV signals bright and clear in the fringe areas. Has a 20 times boost ar all TV channels, NOT A KIT. Completely assembled

13 CHAN-NEL TUNER 12.95



This compact front end has a stage of RF for extra distance. Made to conform with Telekit or any TV as having a video 19, of 23,75 Mc. Complete with tubes, pre-wired, pre-assembled. Only four connections to make.

Write for catalog of Telekit antennus, booster

TELEKIT
ELECTRO-TECHNICAL INDUSTRIES

#### Instant Heating Devices

(Continued from page 65)

Another feature of this child's phonograph is the operating switch in the playback arm rest. When the arm is in the rest a pin in the unit is forced against a leaf switch which is thus held open by the weight of the arm. When the arm is lifted off of the rest, the leaf switch closes the power circuit to the motor and the button current rectifier simultaneously, thus placing both in instant operation. By this means shut-off is assured since the child must put the arm back in the rest to stop the operation of the turntable.

Another tubeless device is the amplifier shown diagramatically in Fig. 3. A carbon button microphone and a loudspeaker combined with a source of button current will deliver an unbelievable amount of power when connected as shown in the diagram of Fig. 3.

Among the instant heating vacuum tube units is a record player which was housed in the same cabinet as the carbon pickup phonograph discussed previously. The circuit diagram of this record player is shown in Fig. 4. This instrument uses a 3A4 power output pentode and a selenium rectifier. The output of a high output crystal pickup (about 3 to 3.5 volts) will drive this tube sufficiently to give a sound output loud enough to satisfy a child. The tone quality of the unit is excellent. This device also uses the

arm rest power control switch described before.

A two-tube version of this amplifier with negative feedback and other refinements is shown in Fig. 6. This device uses tubes requiring a lower filament current which means that the rectifier used in this connection can have a lower rating than the one required for the circuit of Fig. 4.

One very interesting device that has been built along instant heating lines is the automatic switchover preamplifier for the low output magnetic reluctance types and other phonograph cartridges. The photographs of Figs. 8 and 9 show one of these systems built into a General Electric FM tuner. By referring to the circuit diagram of Fig. 7 it can be seen that this preamplifier is straightforward with the exception of the two filament-type pentodes which are wired as triodes. A relay is wired into the filament string which is supplied from the selenium rectifier. It is, in part, the filament dropping resistance. In this set-up the isolation transformer primary is wired to the record changer's starting switch so that the instant the record player is turned on the amplifier will be in operation and the relay energized. The relay can then switch the amplifler input connection from the FM tuner output to the phonograph pickup preamplifier output. When the last record has been played and the record changer shuts off, the preamplifier ceases operation, de-energizing the relay and returning the FM output connection to the amplifier input.

Table 1. Filamentary tube types equivalent to heater-cathode types. The equivalence is based on the use of the tube type rather than on its specific characteristics.

TUBE	FILAI	MENT	HEATER-CATHODE		
	1.4 v.	2.0 v.	6.3 v.	12.6 v.	
DIODE DETECTORS One Diode Two diodes	1 <b>A</b> 3		SH6. SALS	12H6	
POWER AMPLIFIERS Triodes High Mu Medium Mu Eeam Power Power Pentode	Twin 1G6GT 3A5* 1O5GT 3Q5GT* 1T5GT 3L74* 3A4*, 1A5, 1C5, 1LA4, 1LB4, 1S4, 3S4*, 3Q4*, 3V4*	Twin 1J6G	Twin 6J6 6N7, 6N7G 6AQ5, 6V6, 6V6GT 6AK6, 6G6G	Twin 12AX7 12AUT High-volt 61 types 70L7, SOL6, SOBS, 25L6, etc. High-volt 61 types 43, 25A6, etc.	
CONVERTER & MIXERS Pentagrid	1A7, 1LA6, 1LC6, 1RS	1C6, 1C7G, 1A6, 1D7G	6A7, 6SA7, 6BE6, 7Q7	12SA7, 12BE6, 14Q7	
VOLTAGE AMPLIFIERS Triode Triode-Pentode-Diode Triode-Double-Diode	ILES, 1G4G IDSGT, SASGT	1H4 1B5 25S 1H6G	6C4, 6C5, 6J5, 6L6, 7A4, 76 No equivalent 6R7, 7E6, 6SR7, 6SQ7	12JS, 14A4 No equivalent 14E6, 12SR7, 12SQ7	
Pentodes Sharp Cut-off	1LC5, 1LN5, 1L4, 1U4, 1N5GT	1ESGP, 1B4	6AU6, 6J7, 6W7G, 7C7, 7L7, 7V7	12AW6, 12SJ7, 14C7, 12J7GT	
Pentodes — Remote Cut-off	IPSG, 1T4	IDSGP, 1A4P	6BA6, 6D6, 6K7, 6SK7 6S7, 6SS7, 7A7, 7B7	12BA6, 12SK7, 14A7, 12F7, 14H7	
Pentode One Diode Pentode Two Diodes	185, 1U5, 1LD5	1F6, 1F7G	6B7, 6B8, 7E7, 7R7	12C8, 14R7	

# NIAGARA SLASHES



	ALL	BKWIND MEM	-SIANUAK	DEMANUS	10		
Type Price	Type Price	Type Price	Type Price	Type Price	Tope Price	Type Price	Type Price
1822	10 NET 7.100	800	8014A 24.95	0A2 Log		GNT7 NN	TIES NN
1B23 5.45	101	801A	8016 1.10	0A3/VE7598	GARG FR	68V7 88	1105 SS
	10SPEC69	NO2 4.25	8020 7.95	0A1G .01	6AD7G 1.28	6U5 G5	1107 88
1B25A 4.95	10BP4	803 3.15	8026 12.95	0B3/VR90, 01	GAPGG IN	SUGGT72	118.7 88
1827 4.95	100 P4 29 50	200.0	BR 2.50	0C3 VE105 IN		61.76 34	1117 38
	12DP8 . 11.95	807	BH 4.95	0D3/VB150 51	C. C. C	6V6 186	0.60%
1R39 1.95	12FP7 14.95	808	CIA 4.95	014 88	6.145	STREET TORY	140761
1B38 31.50	12612 1295	809 2.50	CIB 4.95	0Z4 56	6385 21	6W 7G88	1447 1.00
1B40 1.95	12HP7 12.05	810	CNB 12.95	0210 0130	GARG	GX4 IN	11/2 2014
1B59 12.95	12KP4 49.50	811 2.00	CGA 7.58	61A	GALS Jul	18.501000	1407 56
1B60 1.95	12LP4 49.50	01.5 m + x x x	CEQ72 . 1.95	1A3 1.13	GA1.7GT. LOG	6776 88	1187 1.00
1N21 60	15E 50	812H 6.90	CK100508	IAIP Die	6496 58	6276 1.15	0.035.7 1.000
1P23 1.95	E.O.O		CK1006 . 60	1A3GT 18	CAQTOT. NR	6ZY5G AIR	14X7 1.00i
2AP1 1.50	2304 49	815 1.25	CN 1000 . 2.10	146	6AR566	7.14/XXL 38	14X4 SN
204 1.18	35T 4.93	816 1.19	EF50 35	1A76T	6A87G 4.95	7.5.5	818
2021	458PEC .	826	ELIC 4.95	1836T 1.49	SATS	7.56	1978 1.56
26.55	53A 21.95	N'29/A/B	EL3C 4.95	1B1 1.18	6116 58	7A7 20	22 1.28
2026A18	75TL	830 2.95	F123A 12.50 F128A 10.00	1B GT L06	6AV646	1.60	2546 1.06
2034 2.98	Report of the con-	N308 4.95	F660 110.00	ICSOT	C 10 C C C C C C C C C C C C C C C C C C	7A17 1,00	25.1/10 1.06
2043 9.50	14016 7 20	GONA GIAN	FG17 2.70	16.6	- FE-247	1AG7	25ACSOT 1.16
2014 1.75	101F 4.95	4474.9	BYCHTA SUBS	1C1G 306	CBG2	7.10788	25L66-F50
2046 7.50	1148 1.25	836 90	FG32 5.95	1106P 96	GES NR	7184	25% 5 L.16
2051 6.50	120 5.95	837 1	FG33 8.95	1D76 88	0R8G 1.28	785 75	252518
	121A 2.05	838	FG81A	108T91	CRAG Al	7166	25Z6GT 48
2E22 LTS	2034 16.95	811	FG95 9.95		GREG 50	78772	26
2E24 4.95 2E25A 4.25	2058 4.50	843 845/W 1.00	FG105 9.30 FG172A 13.75	11676 1.36		70 4/1003A 30	2807 11
2E23A . 4.25 2E26 . 3.95	205F 4.50	819A H 69.50	FG235 59 50	11/3671	GRJG	26.2	30 36
	211 10	834 H 69.30	FG2388 160.00	196 1.36	604 21	706 .72	31 86
2321A 10.75	218 12.50	NG109	GL146 . 9.75	1876 L.56	605 10	767 38	3290
2426 1 11.11	021A 1.40	861 35.00	GL473 .	16.16.T68	6056T10	7E5/E20E .0G	32L7GT . 96
2327 13.25	2311) 1.0	864 130	GL502A 1.98 GL530 49.50	16.66.T68	60'600	7 P/G AR	33, 68
2430 19.95 2431 8.95	2190 1.10	865 8664 99	GL559 . 5.35	IHSGT 53	66.7 1.28	107 68	35/51 56
2,832	250R 19.50	Neidalk 1.19	GL673 I1.50	I EDGG Noti	elfici in	108 1.06	353366
19.85	2524 4.95	872A 1.30	GL697 . 65.00	HGGT SG	6188866 M.	10:7/1232 L.66	3583 (63
2436 75.00	2593 4.95	874	HF100 . 3.95	ILIGAT SS	67.5 1.06	747 1.06	SNESGT . AS
2437 12.95	262A B 3. 0	876 1.15	HF210 17.95	11.A128	6E6 1.06		3584 18
2148 21.50	274B 1.00 275A 7.95	NN1 1.19	HF300 17.50	ILAG SS	GENGT dii	71.7	3573
	282A B 9.95	NN.5	HK254 19.95	11.B4	GF361	7N766	35Z16T - 43
24B51 4.95	283 4 10 95	SHOR 110.60	HV18 12.95	1LC5 38	CFGGT66	197 58	35Z5GT . 39
2J54B 24.36	286A 10.9a	891 110 60	HY615 -20 HYE1148 -35	H.C6 566	617 St	787 1.06	36 39
28.23 21.95	290 \$ 1.95	903F1 115.00	KU23 15.00	11.E3 88	414 1914	757 1.00	36 37
2K23 24.95	291A 4.95	905	KUG10 9.50	11.6.5 88	6 HG 46	717 88	300/11201
28.08 . 2 s.16.5	3004 3.95	907 11.95	MI.101 75.00	11.11161	citically fill	TAT/XXEM 308	41 51
	3014 6.95	913 6.95	MX tost 19	11.N5	6.75	28.6	42 48
30023 4.95	301B 5.9.	917, 1.50	F#23 L33 E100 3.15	1P56.T 166	815GT18	7Z4 56	15 51
3B24 1.98	304TH 3.50	922 1.00	R200 3 7.95	105GT	6.56	12456	4523 56
	307A 4.95	9/23	K1130 : 12.93	112.4 (124	GIZGT	1236	45Z56.T48
3B26 1.50	3104 7.95	925 1.40	n.E.L.3G	(R508	6.186 L.28	CTAGGT 18	\$40 (68
5B28 5.95	3154 6.95	9314 2.00	RK20A 7.50	184 38	646.5GT	12A7	47 GH 49 RR
3BP1 2.50		0.754.75	KK22 4.95	174 56	GKGGT	12 ARGT 58	19 NR 10 1.56
5C23 2.25 3C24 35	327A 2.50 338A 3.15	93461 . 1.50	RK31 2.50	PERGE TH	68.7 IN	12AL5	50A5
3630	348A 5.95	950	KB33 25	16.4	CRS TH	12AT6	5085 51
3031 0.00	350A B 2.75	954 10	HK31	16.572	CKSGT TR	12AT7 1.16	SOLGGT . At
3CP1 1.10	354C D 19.95	955	RK30 1.75	243	x1E5G 1.00	12ALG	SOVEGT . SE
3DP1-A. 3.95	357B 490	956 18	EK51 3.95	2A1G 1.06	61.6 1.16	12AU778	56
3EPI 2.50 3E29 4.95	368As 4.93 371A B 50	958A 18	RK59 1.75	235 68	61.66 MI	128.06	07 97
2FP2 L75	3744 2.50	959 35	EKG079	286 38		F2C8	586 418
3GP1 4.95	393A 5.50	966A99	EK62 1.98	2A7 HH	61.7 1.16	toFaGT . at	59
3JP7 7.95	394A 3.a0	972A 2.95	RK63 12.95	28788	6866 1.56	8 12 8 6 6 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	701.7GT . 1.16
4-65A 14.50 t-125A 27.50	399A 2.50 400A 3.25	975A 14.95	KK65 24.95	2V3G 308	6N7	1242G . 26	71A66
4-250A . 37.50	401A 1.95	1613 15	EK73 63	384	GP5GT	1247GT80	76 38
4A1	403A B 1.75	1614 1.33	RX21 3.10	345	6066 1.06	12K2GT	77 43
4/41.10	417A 0.50	1616 56	RX120 8.73	3A8GT 1.98	607	12K8 38	79 14
	434A 7.15	1619 15	T20 1.50	206 . 34	MARKET - P	12K8GT	MAR.
4E27 4J26 110.00	4468 . 1.85	1620 4.95	T21 1.70	3LF4 1.28	GRIGT	1207GT - 18	81 1.76
5AP1 1.85	4501H 24.95	1622 1.75	T200 10.95	304	CB7	128 A 7GT	Nº2
5AP4 1.NO	450TL	1621 1.05	Taite 1.50	BURGT	6876 NIL	12867	M3 31
58P1 1.35	464A 9.50	1625	TZ40 2.95	25.5 80	6886T . 1.06	128F5	83V 88
5BP4 2.50 56'22 49.50	527 · · · · 6.00	1626 4.95	UH50 5.95 UN20075	5A74	68A7GT . 43	128F5GT, 56	84/6Z462
5CP1 1.50	532A 4.95	1629 4.90	V200 6.95	5846Y 1.00	08B7Y	128F7GT. 36	85
5CP1A 9.95	631F1 4.95	1631 1.33	VK75	OTI SE	6196.7	125427	MOSe V
5D21 29.95	70 1 1 10 10	16333	VR78	51 10 56	ONDITOT	12807	1171.7GT, 1.78
MFP7 1.25	701A 2.50	163479	V RCHO	51 tG SH	68F5 . 18	128J7 18	117M7GT 1.56
56P1 5.50 58P4 9.95	203A 2.50	1636 3.50	VR94 1.49	SWIGT66	GSF7 . ST	12857GT 18 12857 56	117N7GT. 1.36
5423 100.00	706AY 18.50	1641 45	VK150	5X10 58	6867	1288.76T. 3d	11773 56
5429 12.50	70 X X 18.50	1612	VT127A . 2.00	AVSOT So	68H7 18	1281.76T. AR	117Z1GT. 1.16
54P2 0.50	70GGV 49.50	1614 1.49	VEIII 50	5116 18	6847 56	12857GT. 51	117Zect ma
5LP1 11.95	707A B 14.00	1645 1.98	WL160 11.95	5Z318	dSJ7GT . 50	12897 18	FM-1000, 1.28
5MP1 4.95 5NP1 1.98	708 \ 710A 2.95	1649 1.25	WL168 . 6-75 WL532A . 1.75	5Z4 1.8 6A3 1.28	GSK7GT	128Q76T. 18	UX120 . L38
GAFGG BR	713A 1.00	1851 95	W L562 150.00	6A3 1.28 6A6 88	GSL7GT . 54	12867GT. 15	E 5.200 1.28
6021 21.95	214AY . 1.75	1852 1.06	WL616 85.00	GAT SIN	GSN7GT . 61	1273 18	19091 29
6F4 5.95	715A B . 0.75	1853 LOG	Z225 1.95	GAR TR	6807 43	1233 .98	
644 4.95 78P1 4.95	7156 22.50 717A	2050 85	ZB120 . 6,95 ZB3200 150.00	6 ASGT .80 6 AB5/6 N5 .88	68Q7GT . 43	14A7/12B7 (08	3001 30
7887 8.50	7200Y 34.95	2051 10	ZP477/	6AB7 1853 .78	GNEGGT . Se	88. 1177	9005 1.90
7023 75.00	221A B . IAB	5514 4.95	12DP8 14.95	6AC5GT 1.16	688738	EEEG AIN	9006
2C24 80.00	723 4 11 7.95						
7025 90.00	721A B 0.70	5562 10.00				-	

Miagara Radio Supply Corp.

Dopt. N-20 160 Greenwich Street, New York 6, N.

### SPELLMAN HIGH VOLTAGE POWER SUPPLIES

#### SPELLMAN REGULATED 40 KV RF POWER SUPPLY

Regulations of 1/10 of 1% at 1 mil. load. Available in voltage outputs 15-20 KV, 20-25 KV 25-30 KV, 30-55 KV, 35-40 KV Ripple contenses than 15° at maximum voltage. Regulatio maintained within the limits 95 to 125 volt 0 cycles AC

THRE COMPLEMENT. Regulators: 1

Oscillators: 3-614



#### 30 KV RF POWER SUPPLY

For TV and Experimental Work Width 111/2 Height 121

s variable from 15 KV to 30 KV through the front panel. The high voltage uses control and voltage tap variable fro for use with 5TP4 Projection Kinesco. 115 volts AC—60 cycles. Utilizes 6 tub \$99.50

#### HIGH VOLTAGE COILS \$ 3.25 7.75 FILAMENT TRANSFORMER for 1B3 Rectifier Tube for use in 200 KC RF Power Supply 906

#### SCHMIDT CORRECTING LENS

eplace your 15°x20° correcting lens with a new 3'x4'
as for GIANT pictures only \$30,00

SPELLMAN TELEV

OF POWER SUPPLIES FROM BOKY TO 130KY

40 KV RF POWER SUPPLY



Dimensions: Length 1414", Width 1114 Height 1214"

Voltage Output: 40 KV Price \$114.50 complete. Specify desired

HIGH VOLTAGE TELEVISION CAPACITORS Specifications: Joffers Type SKC Conneitors

abarrenament sames			
Typo	Capacity	Operating Voltage	Net Price
SKC 10-10.	1000 mm.5d	10.000	45 en.
10-20	500	20:000	84 ea.
10-30	300	30.000	2.10 eu.
SEC 20-10	1600 mmfd	10.000	2.52 es.
20-20	1200	20.000	3.36 ea.
20-30	600	30:000	4.17 no.
SKC 30-10	3200 mmfd	10,000	4.17 cm
30-20	2500	20,000	5.01 ea.
30-30	1,200 ~	30.000	5.85 en.

CENTRALAB "HI-VO-KAPS" Coramic Capacitors TV1-502-500 mmfd. at 20 KV

#### International Short-Wave

-30-

In the photograph of the bottom

(Kotron strip) can be seen

view of the FM tuner with the preamplifier assembly (Fig. 8) the recti-

mounted on the front chassis wall.

The isolation (power) transformer

and the filter condenser block are

mounted on the wall of the chassis near the drive flywheel. The top view (Fig. 9) shows the positioning of the

components in the space originally

occupied by the tuner's power supply which was subsequently removed. The

amplifier, with a pair of 6A3's in the

output and a Thordarson "Tru-Fideloutput transformer, is shown at

Although the units mentioned in

this article represent only a few of

the uses for instant heating devices,

many additional applications are fea-The well-known and widely-

marketed battery operated tuners and

receivers are familiar to most readers

and so were not considered in this dis-

cussion. More complex instruments

and apparatus are, fundamentally, simply adaptations and extensions of

the elements already described and

most readers will quickly recognize the additional possibilities inherent in

instant heating devices.

the left of the tuner.

sible

(Continued from page 56)

the G.O.C. Troops South Iraq. asking for the installation of yet another station at Beara. This not only catered to British troops but to Indian troops as well. Regular transmissions of Indian music and Indian announcements were given.

FBS radiated for some 1412 hours a day-starting at 6:30 a.m. and with only a short break 8:30-10:00 a.m.continued to 11:00 p.m.

Servicemen took an active part in these programs. Quiz and magazine programs became extremely popular. The best received of all was always the request program-under the title. "Ask for Another."

It was decided in 1946 to move the headquarters of the organization from Egypt to Palestine where it remained until the evacuation of British troops from Palestine. Two m.w. transmitters were used-one in Jerusalem and the other in Haifa. A 712 kw. s.w. transmitter covered the whole of the Middle East.

Mr. Knight comments: "It was during the time of the trouble in Palestine that it was found how invaluable a Service of this kind could be. Special orders from the G.O.C. to his troops were given over the network. Hourly announcements entitled 'Operation Reetle' were broadcast in which items of interest and warning were given to the servicemen. When the decision was made known that the British were going to surrender the Palestine Mandate and conditions were unsatisfactory, the decision was made to move to Malta.

DEPT. A, 130 WEST 24th STREET, NEW YORK 11, N.

TELEVISION KIT featuring AGC

(Keyed automatic gain control)



for 10" or 12" KINESCOPES

Four-stage video IF--4Mc band width. Completely assembled ... ready to wire. Factory tested parts of finest make. Trouble-free wiring diagrams permit wiring in a week-end.

Complete with all tubes, less Kinescope \$11995 At your distributor, or write Dept

TECH-MASTER PRODUCTS CO 443-445 Broadway, New York 13, N

Acre leading engineers and tech sicians have built Tech-Master for the



WITH A GREENLES BADIO CHASSIS PUNCH

· Make smooth, true holes quickly this easy way. Just turn GREENLEE punch with an ordinary wrench and have an accurately-sized opening for plugs, sockets, and other receptacles. No reaming or filing. A GREENLEE Punch for each of these sizes: 10": 16"; 16"; 16"; 1"; 1\6"; 1\6"; 1\6"; 1\6"; 1\6"; 1\6"; 1\6"; 1\6"; 21, \* Also GREENLEE Knockout Punches and Cutters for conduit and meter holes up to 314". Get facts now. Write Greenlee Tool Co., 1882 Columbia Avenue, Rockford, Illinois,



# When Mickey and Felix were our leading "TV" stars...

Those celebrated "movie actors"—
Mickey Mouse and Felix the Cat—were
pioneer helpers in television research


No. 1 in a Series Tracing the High Points in Television History

Photos from the historical collection of RCA

 Strange though it seems, two toys had much to do with television as you now enjoy it! As "stand-ins" during television's early days, Mickey Mouse and Felix the Cat helped RCA scientists and engineers gather priceless information.

Choice of this pair was no accident. Their crisply modelled black-and-white bodies were an ideal target for primitive television cameras. The sharp contrast they provided was easy to observe on experimental kinescopes.

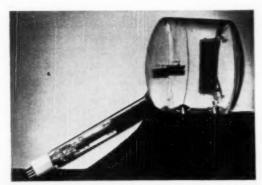Would living actors have done as well? No, for what RCA scientists were studying – as they trained their cameras on the two toys—was the effect of changes and improvements in instruments and telecasting techniques. With living actors it could never have been absolutely certain that an improve-



The iconoscope, electronic "eye" of telectision, invented by Dr. V. K. Zworykin, of RCA Laboratories.



Felix the Cat and Mickey Mouse were, during television's experimental period, the most frequently televised actors on the air. Using them as "stand-ins," RCA engineers gathered basic data on instruments and techniques.

ment in the televised image came from an improvement in equipment and techniques—or from some unnoticed change in an actor's appearance, clothing, make-up. Mickey and Felix provided a "constant," an unchanging target which led to more exact information about television...

Problem after problem was met by RCA scientists, with the results you now enjoy daily. For example: In the "Twenties" and early "Thirties," there were still people who argued for mechanical methods of producing a television image, despite the obvious drawbacks of moving parts in cameras and receivers. Then Dr. V. K. Zworykin, now of RCA Laboratories, perfected the iconoscope, to give television cameras an allelectronic "eye"—without a single moving part to go wrong, Today, this same all-electronic principle is used in the RCA Image Orthicon camera, the supersensitive instrument which televises action in the dimmest light!

Also developed at about this time, again by Dr. Zworykin, was the kinescope. It is the face of this tube which is the "screen" of your home television receiver, and on its fluorescent coating an electron "gun"—shooting out thousands of impulses a second—creates sharp, clear pictures in motion. Those who may have seen NBC's first experimental telecasts will remember the coarseness of the image produced. Contrast that with the brilliant, "live" image produced by the 525-line "screen" on present RCA Victor television receivers!

Credit RCA scientists and engineers for the many basic developments and improvements which have made television an important part of your daily life. But don't forget Mickey Mouse and Felix. They helped, too!



Radio Corporation of America
WORLD LEADER IN RADIO—FIRST IN TELEVISION

February, 1950

Advertisemen

91



quantities are limited so get in your order

NATIONALLY FAMOUS! 15 In. (130 Sq. In. Picture)

T V CHASSIS \$259.50

THIS IS NOT A KIT!

agreed not to mention the name you've seen it Notionally Advertised a name you respect for "know how" if quality. You get the identical Chassis for a notion of a second of the name of th

Mount it in a cabinet of your own choosing —in a wall—in any location that meets your own requirements.

130 sq. in. picture on a 15" direct view vube. All channel selector switch provides instant tuning. Fine tuning control on front

\$9000

panel. 8" electro-dynamic speaker provides rich tone.

Supplied mounted on reinforce pagenese metamese on reinforces wood frome ready to be slipped in cobinet, well installations etc. Dimensions 1915-in high 23-in wide, 21/4-in deep Footors wised and tested, complete with 19 tubes, plus 3 recthiers and 15DP4 Dumont picture tube. For 110-120 V 60 cycle AC Shipping Wt. 80 lbs.

Quantities are limited—all orders subject to prior sale. Order Now!

No. 39A18X

\$169.95

"The evacuation was a superhuman task. It involved the movement of approximately 1000 tons of valuable and irreplaceable technical equipment and more than 250,000 phonograph records. Stores and equipment had to be moved through openly hostile country against the will of two well-armed and determined partisan armies—each badly in need of such equipment for their own propaganda purposes; each willing to go to any lengths to persuade the British Army to abandon it, and each jealous and suspicious of the other's designs upon it. "The main transmitter was located

next to the headquarters of the Syrian Liberation Army - a well-organized and well-equipped band of about brigade strength - and the dismantling and evacuation of the whole unit had to be carried out under their very noses. At times, as the evacuation convoys moved slowly down along the deep valleys and gorges of the Palestine landscape, with heights on either side liable to be concealing the apparatus of a determined ambush, many a member of FBS wished he could remember more of the lessons on Bren guns and fieldcraft that he had learned in his earlier and more active days. FBS had its casualties-one man was killed, four others were badly injured. But somehow-by road, by rail, and by sea-everything went out and all that now remains as a reminder of FBS in Palestine are the two 400-foot aerial masts on Belt Jala, a hill overlooking Jerusalem itself.

With the demobilization and natural rundown of the Service staff, the need for economy became more apparent. The installation in Malta will consist of medium-power shortwave stations. It is proposed to have transmissions beamed in an eastern and southern direction. The eastern beam is intended to take in Cyprus and Egypt and the southern beam to take Tripolitania and Cyrenaica, and therefore the whole of the Eastern Mediterranean. In Commands and Districts where the number of troops justify it, relay stations will be installed. All stores and equipment have arrived in Malta and the FBS staff is most grateful to Army Movements for their assistance. Only a small number of phonograph records were broken and a few cases of equipment were lost."

The various persons who have been guiding the fortunes of the organization through the past eventful years have arrived in Malta. With Mr. Knight, who is Chief Broadcasting Officer and formerly of the BBC, came Captain J. C. Butler, K.O.Y.L.I., the Chief Administrative Officer, whose main problems deal with the organization of the FBS network; Maurice Taylor, again of the BBC, who is Chief Technical Officer and whose days are filled with the establishment of the technical equipment throughout the various stations; S. T. Moffett, Chief Programs Officer, who apart from handling the program side of the Network.

hallicrafters S-59 8-TUBE CUSTOM FM-AM CHASSIS



High fidelity Receives broadcast 540 to 1700 kc and FM 88 to 108 mc. Excelmarches most speakers. Limited quantity still available. Order Now! With ar without speaker. Complete description on page 137 in our catalog. No. 501. Write us. If you do not have this catalog.

WILL BUY

ELECTRONIC PARTS &

COMPONENTS, WIRE, ETC.

QUANTITIES

GOULD GREEN

252 Greenwich St., New York 7, New York

34A19-Hellicrefters \$32.95



parts and complete instructions included conversion, works on 110V AC or 12V battery by a flick of a switch.

INNE DIATE MALIVERY ON ALL MAN, ORDERS.

CINEX, INC., 165 W. 46th St., N. Y. 19, N. Y., Dopt.


RADIO AMATEUR NEWCOMER

Ideal for those just getting started for interested) in radio. You need no other book to get your license and get on the air. How-to-BY THE EDITORS OF "RADIO HANDBOOK


AT YOUR DEALER - On mail orders from us. \$1.10 postpord. Add soles tex in Colifornia.

EDITORS AND ENGINEERS, LIG. 1902 KENWOOD ROAD . SANTA BARBARA, CALIF.

# RADIO & TELEVISION'S GREATEST BOOKS!

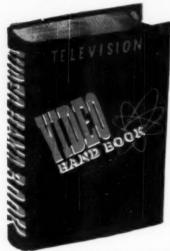

Make every operation easier . . . get all information in condensed. easy to read form in the RADIO DATA and the VIDEO HANDBOOK! These books give you all facts, data and techniques for engineers, technicians, students. They provide complete reference, text, charts, data and thousands of pictures: drawings, photographs, diagrams, schematics, sketches, etc. Complete set of test patterns illustrated in the Video Hand Book. All text and charts in easyto-understand, non-mathematical style. These books are best sellers in the radio and television field. The first printings of 30,000 are sold out . . . second printings are going fast! Make sure you get your copies now . . . order both, you'll profit by the valuable information they contain!

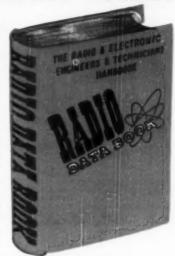

GET THESE BOOKS AT YOUR FAVORITE DEALER! IF HE CANNOT SUPPLY YOU, ORDER DIRECT, USING COUPON BELOW

#### THE VIDEO HANDBOOK

How Television Works, Basic . . . through advanced.
How to Design and Engineer Television.
How to Troubleshoot and Repair Television, Safety procedures.
How to Select and Install a Television Antenna.
How to Create a Television Show.
How to Suld an Operating Television Receiver, Complete Instructions.
How to Select a Television Receiver.

The VIDEO HANDBOOK is designed to give you the practical—answers to all your questions on television—the complete, detailed procedures on all phases of television work—step-by-step explanations for everyday problems. This book provides the ready information to make your television education

The Volte marks and interesting reading—it is an investment in prove for freedom.

Mondsomely bound in DuPent Febrikoid ... ever 900 pages ... 14 sections ... quer 800 illustrations—photographs, charts, diagrams, schematics.

Section 1. Templom Ross, Present K Fature, Sestion 2. Fundamentals of licetronic Februarian Status. Section 4. The Talescope Receiver betton & Television Assessing Section 4. The Talescope Receivers betton 6. Februarian Status 5 certain 4. The Talescope Section 5. Discription of Mostern Template Februarian Section 5. Certaing and Februarian Section 5. Section 1. Section 1



February, 1950

ORDER BOTH ... SAVE MONEY! the RADIO DATA BOOK and the

VIDEO HANDBOOK COMBINED IN HANDSOME SLIP CASE THE RADIO and TELEVISION LIBRARY COMPLETE ONLY....\$9.00

### THE RADIO DATA BOOK

Plan every operation in radio and electronics with the Radio Duta Book.

This new radio bible will be your lifelong tool..., you will use it svery day, on
the board, at the bench, in the field Use it for engineering, construction, troublesshooting and testing. The RADIO DATA ROOK will be your invaluable aid in
design, experiment and in layout. It will help make your production better,
faster and easier. In any and every operation in radio and electronics, you will
use the RADIO DATA ROOK:

The BADIO DATA BOOK is a work of complete authority, prepared by eu The BADIG DATA BOOK is a work of complete authority, prepared by engineers with many years of practical experience. They have been assisted by the Boland & Boyce staff of editors skilled in preparing electronics manuals for the U.S. Signal Corps for many years. These men have worked for exercise gathering material for this book. ... all the knowledge of radio principles and peration. ... all the statistics ... all the newsed evelopments in electronics ... every possible angle and detail. Eighteen months were spent digesting this material into the most consist, the clearest, and the most revoluble form. The cesult is this invaluable manual ... The BADIO DATA BOOK better you use this book for general reference, for scientific instruction, or for education, one thing is vertain—the practical help, the dady usefulness you will derive from it will prove to be worth many, many times its astonishingly lose price.

Section 1: PUNDAMENTALS (consists introduction to electronic Section 1: FIRSCAMENTA'S (Complete inhologous to inhology, corrent yields theory, volume folias, rotale, yours, AM, FM, TV, and all inhologous engapments', Sociolo 2: BASIC CRCURTS Section 3: TEST (QUIMNIN), Section 4: TESTING, MIASSIRFAIS and AUSTRINGS Section 5: ANTENNAS, Section 6: RECORDING Section 7: SOUND 3: STATIMS Section 8: CHARTS, GRAPHS, CURVES, Section 9: CODES, SYMBOUS, STATIMSROS, Section 10, 59 TESTIED CIRCUITS, Section 11: DICTICHARMY, Section 12: UNB CHARTS.

The Boyce-Roche Book Co. handles ALL Radio and Electronic books, Immediate shipment, Send stamp for FREE Catalogue.

#### MAIL THIS COUPON TODAY

	BOYCE-ROCHE BOOK CO., MONTCLAIR, N. J.	
i	Send me the books listed below. RN-2	
	□ RADIO DATA BOOK \$5 □ VIDEO HAND BOOK \$5 □ RADIO & TV LIBRARY \$9	
	<ul> <li>□ I will pay postman for books plus few cents postage on delivery.</li> <li>□ I enclose payment. Send books postpaid.</li> </ul>	
	NAME	
	Address	
	CityZone	
	State	



# OF TONE...

It is possible to most rigid requirements and tolerances of a "mechanical ear"... amplifiers that show perfect laboratory measurements, BUT may, despite their mechanical and technical perfection fall short of providing enjoyable "Istening-quality."

When you buy a phonograph amplifier you buy one thing . . listening quality. That elusive characteristic which, after all, is any amplifier's prime reason for being.

Newcomb amplifiers must not only measure up to the highest standards electrically ... but in addition are subjected to critical

"listening quality" tests by trained experts.
That is why Newcomb amplifiers provide more real listening pleasure.



Insist upon hearing a Newcomb. Compare the listening quality of Model KXLP30 from the standpoint of enoughnet with that of any other amplifier. Your ear will readily hear the pure natural quality and true character of each deep bass note. Now, listen to the clear, undistorted, brillant, high tones with their remarkable freedom from surface noise made possible by Newcomb's exclusive Macia, Rep. Kson, A comparison will convince you that Newcomb Sound is without question the closest you can get to "Live Music" quality.



Dept. F. 6824 Lexington Avenue, Hollywood 38, Colif.

is known to Middle East listeners through his sports commentaries and features from Palestine and Egypt.

Mr. Knight concludes: "With these senior members of the organization are the rank and file, some of whom have seen long and arduous service in many corners of the Middle East, and others newer arrivals who are being trained in the tortuous ways of radio. And so, with this slow but steady accumulation of material and personnel, it is hoped that before long, with the cooperation of Malta Forces, the headquarters of the Forces Broadcasting Service will once again be in regular operation while 'out-stations' in Kabrit, Cyprus, Tripoli, Benghazi, and East Africa continue to provide radio entertainment for the servicemen under the familiar callsign . "This is your Forces Broadcasting Service . . ." . . .

#### Radio Indonesia

At the time this was compiled, Paul Dilg, California, had just received confirmation from M. P. Breedveld, Head of the Technical Department, Stichting Radio Omroep in Overgangstijd, Hoofkantoor, Batavia-C, Koningsplein Zuid 17, Batavia, Java, N.E.I., that the 6.045 outlet of Radio Indonesia in Batavia is the new 100 kw. transmitter.

Mr. Breedveld said: "Your reception report of the 100 kw. transmitter YDF on 6.045 is the second report I have received since experimental transmissions on this frequency started. . It was quite interesting to learn that you had a very strong signal in California, as radiation is not especially beamed in the direction of the West Coast of U.S.A. The target-area of the transmissions of 0400-1000 is South East Asia, and an antenna of rather unusual form is used. The radiation pattern shows a main lobe in the direction of Sumatra and Malacca, several small lobes to Borneo and Philippines, and a second main lobe over Java, Celebes, and New Guinea. It may be the power of the latter that reached California.

"The preliminary program schedule reads: 0400-0600 Indonesian, parallel YDE, 11.770, the latter beamed to Celebes (and so to California): 0600-0700 English, parallel YDC, 15.150, the latter beamed to Australia; 0700-1000 Dutch. We soon will add French at 1000-1100; you heard the November 7 test of this program.

"Within a few weeks, transmissions beamed to India, Middle East, and Europe will start on 11.795 at 1115-1530 in Arabic. English, French and Dutch, under the callsign YDF-3.

"The British Far Eastern Broadcasting Service at Singapore moved from 6.770 to 6.045 on October 30, just a day before YDF started its transmissions. I hope the heterodyne will soon end, as their regular frequency is 6.075; the interference is very bad here since the program times are nearly the same."

Mr. Breedveld indicated that it is



George Nordh, regular contributor to the ISW Department, shown at his Listening Post in his home in Sweden.

probable that the new 100 kw. Batavia outlet later will be used to beam programs to the United States around 2200-0100.

He also informed Dilg that Radio Indonesia is in charge of all broad-casting stations in Indonesia now except the stations at Jogjakarta of Radio Republic Indonesia but that the two organizations were to be merged shortly.

At the time this was compiled, YDF, 6.045, was fairly good level on the West Coast, according to Dilg and Balbi; here in the East it had bad QRM from BFEBS, Singapore.

#### Radio Club Notes

Norway - The Norwegian DX-Listeners League was founded May 3, 1948, by J. K. Bjoernseth, who has been an ardent radio fan for 15 years. NDXLL now has 25 members; while this may not seem impressive, it must be remembered that DX-listening on s.w. is a comparatively new hobby in Norway, and the League is the first radio organization of its kind in that country. The club publication is called "Night and Day," issued monthly. Address for those who are interested in further information is Norwegian DX-Listeners League, c/o J. K. Bjoernseth, Sorgen-frigata 10A, Oslo, Norway (Norge), (Halvorsen, S.W. Editor, Radio Teknikk, Oslo, Norway)

#### This Month's Schedules

Anglo-Egyptian Sudan—Radio Omdurman, 9,747, noted in Georgia 1400-1430 with Arabic program. (Fargo)

Argentina—Widely reported is LRT, 11.840. Tecuman; all Spanish; gives slogan (in Spanish) of "LRT, Radio Independencia, a new Argentina wave to all America." (Mesquita e Sousa, Portugal) Relays news in Spanish from Radio Belgrano 1700, continues with own program to 2300. (ISWC, London)

Australia—Recent changes to Radio Australia schedules include—1500-1630, VLB2, 9.65, and VLC11, 15.22; 1500-1635, VLA4, 11.85; 1643-1815, VLB11, 15.16, and VLC11, 15.22 (this one beamed by long-path to the East Coast of North America); 1700-1815, VLG6, 15.23 (to Europe and British Isles); and 1710-1815, VLA10, 17.84 (to



VI	BRA	TOR	SPEC	HALS	1
Brand !	New!	OFIL	Conta	aner-	Some
Arry new	e alwi	No.			57.50
14. 24. Any are	28.	115 ×	olts.		
Each.	980;	2 for	\$1.80;	10 fo	58.58

	TRANSFORMERS! 115V 60 Cyc. Inpt. Plate & Filament Xformers
All	80ms & 360vet 55 ma. 3 x 5v 3A, 6.3 vet 1A, 6.3 vet 0.3A Cad HiVms \$4.95 900v 30ms, 2x2 5v 2s Ced HiVms \$3.98
5V 2a Cut HiV):	v/100ms. 2x6.5v 1A. \$2.96 3v/1.9s. Also Topts 6
TATTO ACTION DW R. D.	\$1.98, 10 to \$16.98

Plate Transfermers Thomas or 150000 Plate .0154 Cad . 20000 10000 20010000 10 ma our 660000 10000	4	95 50 98
Filament Transfermers, O-beet 2-5 Acts 3 Sect 13a, Cod 10 Vision 26.57 C 5 Acts 3 Sect 13a, Cod 10 Vision 26.57 C 5 Acts 3 World for 0 12A acts 12 Front 1 25 Acts 40 HAVIng O-beet 12 Acts 40 HAVIng	4 1 3 1	29 95 95 49 29 69 39 98

#### MODULATION AND AUDIO XFORMERS

SOT ST-PPSOT - RF 2000 ohm Load	
PERCENT AT AS 29 RCAS SOURS 2000 ORDER	
According USN minit or 900 to 300 or	
60 shina 500Watts	12.95
UTAH 12W UnivOsited 5000 Any	
Tube Acy Votce Coil.	1.39
WI sutput 300W PPS0/4090/an/VC	
HITT	12.98
UTC TAM-11 LineAutoformer 30W	2.96
UTC 0-14 "supper" 50: 1 Mile or	
Line To Getd 200 ohms In La	
Meg. \$13 1 let. Only \$3.98; 10	



#### METER and SHUNT

Nean Bulbs NE2 1144 for \$3.98 NE16 991 25 NE16 991 35 NE16 991 34 NE16 NE20 07	Mazda Pilet Lites 44thox10 50.50 49thox10 60 55thox10 50 64 Each 07 86 / 74 / 3W 18 100W / 20V 225
Tungar Bulbs 103.407 52.49 203.072 2.95 180.084 3.49 190.08 2.95 280.841 2.50	291Bes 10 .36 511 28V .15 513 28V .15 323 2V .19 84Varia 86 6W 120V .15 Weighs C7

#### SOLDER LUGS

	All	Purpose-	-teran	IN PROPER	
Meter	Luga	min or A	4 A	overted.	
RADIO		= n hole		1000 for	\$2.49
		100 for	27c	1000 for	\$2.49
RADIO	Lugs	E S hole	111	16" lg.	
		100 for	31c;	1000 for	52.90

### KITS

	30 for 5	1.50
Controls,50ohmTo2Megs	10 for	2.00
Resinture, Up&   W. to 2 Maga	100 for	2.50
Vitreous WW Resistors	20 for	1.00
Sockets Assid 8.7.5.4F	25 for	2.49
Botary Switches Assid.	& for	1.75
G&P Tubet are. Availd.	50 for	1.49
Cail Forms, The d Sm. HF	50 tur	1.00
Iron Core Shapknerew.	50 tor	1.00
Elastic Stop Nuts, Austd.	50 1-	1.00
Krossa Asadd - a descri-	25 for	1.25
Spurgbetti Sherving, Assid	75 H. for	00.4
FERROLLOW Cridays, Asold.	2.50 From	1.00
Fusca Assid CF&Book	300 for	1.95
Grassimeta, Rubber Austd.	LOG THE	1.00
Rescators, 2W Appld	100 for	3.50
Tor-Pont Lags, Auch	25 for	.35

# "TAB" THAT'S

# COLLINS ART-13 SPEECH AMPLIFIER Distance or Carbon Mike of Tube. Less Tubes, Kit, AME W. (Califfied Kit,

100	SAME W.CLIPPER KIT	
BLOW	ERS-Cool That Tubel	
	40 CFM 28vandr \$ 3.45	ř
TA	70 CFM 115V40009 4-45	ė
	100 CFM Livardy 8.95	į.
11 10	110vac 18v to	ė
Common Co	250 (FM & 28 115	į
10 M	vac After 11.95	
	100 CFM linvacde 7.90	
_	180 CFM 113varde 10.94	r

CATHODE	RAY TUBES
PART S A.MS	S1.00 \$18.00
2.521 4.75	51.07 18.00
133P1 2.89	5 MP5 2.89
BPIA 7.98	7807 4.65
30P1 2.69	7011 12.95
SCP1-81 . 3.49	7107 8.9
30P1 1.87	
118F1 2.75	10809 . 19.7
3FP7 98	
3GP1 0.55	12007 . 12.4
14P7 3.49	120P1 49.9
	12GP7 12.8 12JP4 34.7
	12KP4 34.7
	121.04 34.0
5CP7 7.50	12004 49.9
5FF5 6.49	10314 95.0
5FF7 1.26	902 3.7
DEP14 18.95	905 3.6
51(1") 4.95	010/SAPL 4.7
AJF2 11.75	910 89.9
51.17 18.00	014 49.0
C'Ray Tubes Vis	Railway Expres

	Corps					
BASS	749 6.4	150,737	I toly	Potesia	Volt	31
四条 775	Lightsto	inUng	41714			3.5
DADO	150 Vato	WY BIL	CIRCO S	800		75
	13V W	alkw-T	alby			21
HAZIN	10319 V	Walks	A.Tall	12		- 9.1.4
ISA(219)	150 77 1	Villaria	TAA	OID		1.2
ELA-AVI	00 1 15	Burs 4	(CERN)			
	900.4571	LAN				91
DASI	67 to V	Strong Man				7.6
AATES	on for a	1.53				9.27.5
	90 60 4	A	180		W 6.	9.1.0

# METER BUYS Famous Mfrs.

SPECIAL	1	985c
100-0-100 & 0-200us		0.5
DuniMyt Cross-Lambia	-	10
director	5.2	.95
	5.4	98
O. I. 25 ma. 13. an. Min. Disper Mir.	53	49
0-50ms, 2ha Amery Delut	28	98
0-S0ms, 25g Amere Delur 0-S0ms, 3 Gen. Elev.	5.3.	98
0-3000umbes, 4" s.T.L. ". Wicker's.	5.9	.98
O-IA, 114 Weights O-2A, 214 GF & Weights	\$ X.	69
O-2A. Dita DE & Watshe.	3	49
O-15A, 21, Hort O-30A, 21, SmintWittesWatghe	2	95
O-30A. 21a ShuntWillias Watghs	- 2	9.8
		49
0120A. 21g W.ExtShoot Wire A		
0-300A 3 Less Shunt When	- 3	.08
O-ROOM 3" Lean Shamt When	- 4	49
30-0-308, 25a Westers 20 126 Wester	- 4	98
\$0-0-50A, 1 Int. Shunt. Witte.	4.	.00
60-0-60A, 215", W.ExtStond, Wha		.98
Water	- 2	900
120-0-120A, 21g W ExtShunk, WECk		0.60
& Water		240
DC VOLTMETERS		
0-30V, 214 An B'Cel 1	1 2	22
0-28V, 215 GE Ext. Resistor 0-108V, 315 1mg basic Ext. Resistor		22
Weston B Cad	600	-
Acceptus II. Cad		. 94
DE METERS	-	-
-10+600, 315" Sq. Watghs B Cod		

Water	3.98
120-0-120A, 21g W ExtShunk, WECo	
O-30V, 21g An B'cel \$ 0-2KV, 21g GE Ext. Resistor 0-10KV, 31g 1 ma hasic Fat. Resistor	2.49
Weston B Csd	10.99
OR METERS	
-10+608, 315 Sq. Watghs B Cod .1	99.98
BF METERS	
0-120Ma. He WESTON JAN Accy	12.95
O. TOOMS, ILL WESTIN IAN Appr	
to 65 Mc's B'cod	12.95
0-1 Amp. 3 Triplett Mi-Freq. Int.	53.95
Couple 0-9A, 212 Wetghs U.S., 23 cs to	54.00
0-9A, 212 Weight USN, 25 cy to	
Q-8V. 31g Western	22.40
	00.40
O-15V. INTIA Western	
0-150V. 215 Watgh Sampson GE 25	54.92
to 125 eye	
0-150V, 3" Sq Wetghe.	\$4.98



1200								3.3	ö
SPE	CIA	L!	MB	126	Rac	lio	Con	spas:	5
								mi Se	
Lines	W.	Sold	An	1- 1	ena	Tub	er. 9	8.95	8

# BASIC PHOTOFLASH KIT Complete Pur Supply with crosters, lamp, data. etc. 115 VAC

Complete Per Supply with coders, lamp, data, etc. 115VAC Studio Kil Air Corps 1169	629	95
set 115VAC or Batt = 2 Lamps	53	95
NEW incides  PFlash Replacement Colors 1500 or	24	916
1169 AN Set. Each	80.	98
PHOTOFLASH CONDENSE	RS	

25md 330me 1800mde 187. 16md nolwar 2800mde 187. 16md nolwar 2800mde 187. 16mm PAN film 65AP camera, 54 rolls  8.*V 9*Siash Per Kif Ideal 1800V Disc 115VACING Outpe 1900V Abn 282.5V 2Aca Wodg 46Vus per Bidl PUS 22-25md, not	5.49
282.5V.2Aca Wodg/46Vine	
See Finsh Unders & Data Flash W.Flush Lamp 82	Wate-
"SUNFLASK" SPECIAL! 100 300W-Sec lept Non-Darke Shock Mid 100,000 Flashes IntChaptle 5804X Data: \$1 100W-Sec \$1 X-600 Air Corps Lamp \$1	0.98

Electr	olytic	Con	denser	Spe	ial	511
感的	15 mf 50 mf 30-15- 40 mf 25v 30mf 25v 10 mf	350 10 m 250v dc 430v& dcFP	5vac (de: pp (-250mds & 20 m 2520 ml	7 5 5 8 4	for for for for	9.6c
7		FL-5	Range 6 s Out 10 for CW h & Di	e Ven	te F	ilter

****	SUPER	WIDE	RANGE
20000	HIG	H FIDE	LITY
	AMP	LIFLER	KIT
Harmonie Dia	r cycles.	And Wa	Allen Man
put only at o	Acres War	output	Ware
WILL ANY MI	he. Pica:	op on Ro	YH. AL
Electronic siz	age for o	or willy	GE Pick
or, otc. Vari			
& HI-Freq. To			
bulancing Ca			
6846 29 4	other sta	gree Plan	A.O. Pw
& partly But	in the me	A Chan	sis, Las
Only of Xing.			294 OI
SPECIAL.			824.30
10 Walt Hi-F			
balanting I			
Harrison' cir	reutt.	isstile t	in 1 Mi
Chatmat Afron	(C)	ports.	

-	BAND PASS FI	Courd and
M. E.	S for	52.25
W	Ove. 1024	\$1.95 \$4.50
0.0	LINE FILT	
0.0		CDC \$1.28 de 110VAC \$1.96

-	ter 0.15 to 1000   red Cont duty	94.50
Solar Elim-0-9 New	tat. Sommy SouvDC	25nV AC 89.90
	ARC-5 SPECIA	

ACCES.	Tubes In				9	Be
BC458 (5	961457 3 to 756	N. N.	extr.	AN		40
BC455 Reve	(FLC+10), T	Mich	A. NO	989		

MEM TELEVISION	N COMPONENT	\$!
HIV Horiz & Deft Out 21175 For 15-16" Pic	tpt Xformer Son B	CA
Width Control Sim 20	1184.	19kc
Forus Coil Sim 202D:	2	9.60
UTARRIIS BEDO XIME	H Sid	1940
UTC MRSS2 VBOXYMP	H SId	\$9c
TV YEAR SPECIAL		4.9
Focus Coll Magn Kines	scps 82	.98
ERIE HIV Coder 500	mmf lokv	19c
JEFFERS Coder 500m	umf 20KV	590
IonTrapMagnetHCA20	101	9.0kc
RCA HIV Doff X from 211	71 54	-198
V OutptXfmr%lmBcA2	0472 52	.69
IZ or 12th Tube Pic	ture Frame Mask .	96.9
TWINES TV LOOSSENS	while I con Ft \$4.	. 1, 0
TV TWINES TACKER	52	-16

21	cherry broduce	10 400			94
63	Crystal	Diode	Specials	11	1
100	Type	Each	Z for	10	
ij	1834	83c	51.64		.94



#### PRECISION RESISTORS-

Over 21/2 Million in Stock

	1.62	664	1913	5500	20500
	182.4	669	1914		21500
					22000
					22500
					22990
T.		733			23000
	225	740		6125	23150
9.	2 90	750	1922	6.1.40	23321
	235	800	1924		23400
	240	806	1.926		23900
13	248	0.50			24000
15				6500	24600 25000
					25200
					25400
	271	0.0			25631
				7500	26000
		9.76			2650
				TTET	26600
	299	1030	2150	79.00	27000
	300	1056	2160	7930	27504
	310	1067	2180	7950	25000
36	311.5	2100	2187	8000	26434
25	320	0333	25.62	8094	26900
	325	1150	2200		28000
					2899
(8)	140	1162	2300		30000
					30000
					3150
				9445	32/00
	375				3300
	180	1 100		9710	3500
	169	1322	2925	9600	3700
	390	1350	2600		3614
	400	1355	2629	9902	38500
	410		2615	10000	3800
		1.488			4000
					4200
	426 m				4300
				10930	4500
			2900	1.0000	4700
					4750
				11500	4800
.78	460	1650	3163	11680	4666
	470	1670	3259	12000	4900
0.2	475	1640	3290	12500	5000
	476	ETEG	3333	12600	5200
	480		3384	1.3000	5500
					5600
	500			13500	5706
			5700		5633
			2750		6143
					6200
			4010	14400	6400
		1884		14500	6500
	540	1695	4220	14550	6660
10	586	1896	4200	14600	6665
16	600	1097	4300	15000	6750
15	612	1696	4314	16000	6600
5.7	629	1899	4440	16500	7000
30	633	1900	4444	16600	7200
0	640				7350
0.20	641	1.605	4720	1.7500	7500
5					6000
					6200
					8400
					8500
					8600
		1910	9.2 19		2000
0	680		5270	20000	9330
5	GRE	1012	5100		95.00
190					
	2207 1 5 35 5 45 1 38 5225 5 7 7 4 6 015570150800700000	2 2 2 2 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0	2 2 20 0 4 607 2 1 4 6 7 7 1 1 1 2 1 2 2 1 1 1 1 1 1 1 1 1 1 1	2 2 200	2 2 200

679				
Loy Size	Atsove.	Each 2%c	Ton for	\$1.98
000000	175000	240000	153500	5.70000
0.00000	1.60000	245000	175000	575000
115000	180600	250000	360000	600000
LEGGET	165000	265000	400000	620000
20000	1.000.00	268000	402000	650000
0.25000	1,90000	270000	420000	65.6000
DODDE	198000	275000	422000	660000
135000	200000	294000	425000	690000
140000	201000	300000	45.0000	Emman
141000	205000	EGFSGG	458000	FIGRO
45000	210000	311000	470000	750000
147000	215000	314000	478000	TO DEGG
150000	220000	316000	5.00000	ROOGGG
155000	225000	125000	520000	B13000
00000	229000	330000	521.000	650000
165000	230000	330000	525000	900000
1.66750	219900	333500	541000	9.10000
167900	218900	150000	\$50000	950000
00500				
Any Size	Above,	Each 35c	Ten for	52.90

661	E-SEAR.								
ny.	8166	A	bove.	Black	3.9c	Ven	fine.	5.0	90
				WEG	OHNES				
	10.5	SPI	0 2		3.9	6	- 10	-	as.
1.	10.0	6	2	9	4	- 6	6	- 9	.00
25	10.0		2.	7.5	4.23	6	. 2	1.0	
25	1.	75	2	80	4.25	70		5.5	55
3	31		2.	455	4.5	20	5	8.40	
3.5	10.7	90	- 3		4.7		.62	0.20	63
39	2		3.	. 3	8	77	74	1.1	
4	2.	8.8		9	5.5	- 0		1.3	80
8	2.	2:	3.	4.73	6	- 8	60.	1.9	
87	2.3	25	3.	7.5	6.3	- 6	.9		
mw.		-	harrie.	Simole.	T.Out:	Ten	Cor	80	-



a n	TWO for	\$1.	49
HOLTZER-	Sciency Typ	100	
n Magnet, 27g	fres. I I B V		.980

The Anguest 2's (fig. 118 Votes 148 Votes 148

THAT'S THAT'S A BUY A BU

Write for Your FREE
"TABOGRAM" \$3 Min.
Order F.Q.B. N.Y.C.
Add Shpg. Charges and
25% Deposit
PHONE: WOrth 2-7230



to-tube variation bugaboo by using the same stricter set of test tolerances and more rigid TV tubes leading set manufacturers use -Raytheon Quality Television Tubes. The wealth of experience Raytheon gained in the development and manufacture of tubes for video iceman. amplifiers in Radar applications, is proving invaluable in the production of high efficiency tubes for modern TV receivers. Raytheon instantly recognized that the normal industry test tolerances of many tubes being used in video applications were not close enough for perfect perform-

Television servicemen minimize their tube- ance in today's television receivers. A new, quality standards were introduced with the result that Raytheon Quality TV Tubes save many a headache for manufacturer and serv-

> Save time and trouble - save money safeguard customer goodwill - standardize on Raytheon Quality Television Tubes.

> > RAYTHEON CATHODE RAY TUBES come in all the most popular types. For peak video performance, specify Raytheon Television Picture Tubes as well as all other Raytheon Television Type Tubes.

RAYTHEON MANUFACTURING COMPANY

#### ...... KEEPING PACE with SOUND. SERVICE and AMATEUR NEEDS





NEW! Model "B" Supplies 1 to 20 Amperes 6 Volts DC, Continuous Duty

USES

Electro

ELECTRO PRODUCTS LABORATORIES, INC., 4509 N. Ravenswood Ave., Chicago 40, Ml.

South America). VLC11 is sending a much better signal to Eastern North America than did VLA4 on 11.85.

VLX, 4.897, Perth, heard irregularly: news 0600: VLX2 replaced by VLX. (Balbi, Calif.) Heard in West Virginia fairly well mornings to after 0800: BBC news relay 0800.

Austria - ISWC, London, says the "Blue Danube Network" at Salzburg, U. S. Zone, is now on 9.490 at 0000-1700 but that announces 9.533,

Azores-CS9MB, 11.090, Ponta Delgada, heard on winter schedule 1500-1600: all-Portuguese, news in that language 1530; many popular recordings.

Brazil-This country is now on Summer Time. It will be observed each year between December 1-April 30, during which period the time will be one hour ahead of normal time; the Eastern part of Brazil will be three hours ahead of EST, and the Western part (Manaus, Cuiaba) will be two hours ahead of EST. This measure resulted from a general shortage of electricity in the whole country. It is the first time since 1931 that "summer time" has been used in Brazil. Brazilian radio schedules are affected accordingly. (Levan, Brazil)
PRL-8, 11.72, Rio de Janeiro, heard

in Australia 0430, good signal in music and news in Portuguese. (Sanderson) ZYC-9, 15.370, Rio de Janeiro, heard in Newfoundland 1600-2130. (Peddle)

British Guiana-Cox. Delaware, gives schedule for ZFY, 5.984, Georgetown, as 0545-0745, 0945-1145, 1445-

Bulgaria - Radio Sofia, 7.671, now has news 1630; has bad QRM and is seldom entirely readable. (Alcock, Ky.)

Cameroons - FIA6, 9.145V, heard 1430-1530 daily in Newfoundland. (Peddle) Heard in Pennsylvania 1455-1519 sign-off. (Starry) I have heard this one lately too after 1500 but with severe QRM.

Canada - CHNX, 6.130, Halifax, Nova Scotia, is scheduled 0800-2315; QRA is P. O. Box 400, Halifax, Nova Scotia, Canada. (Cox, Delaware) VE9AI, 9.540, Edmonton, Alberta, nice signal in news 2400; at 0015 has detailed weather report for entire Northwestern end of North American Continent, then popular recordings. (Hankins, Pa.) Noted very weak in Oklahoma 0900-0920. (Pierce) CKFX, 6.080, Vancouver, British Columbia, heard a recent Sunday signing off 0305; had cowboy music 0245-0300, news 0300-0305: this is a privately-owned station, 100 watts; fair signal but had shrill noise. CBNX, 5.970, St. John's, Newfoundland, noted Sunday with news 1400-1405, then "Sunday Screnade." (Cox, Delaware)

Canary Islands - Tenerife, 7518, heard in Alabama well 1700-1800; signs with Spanish National Anthem; all-Spanish with Latin-type music. (Ha-

Cape Verde Islands-ISWC, London, reports CR4AA, Praia, on a new chan-(Continued on page 139)

RADIO & TELEVISION NEWS

# Order your **TELLIO** Test Instrument Kits NOW

# SAVE UP TO 50%

by building your own precision laboratory test instruments! Easy to build in one evening —They last a lifetime







#### SIGNAL GENERATOR

Model No. 320-8. An invaluable test unit for eervice, laboratory and school use. Highly stable
Hartley oscillator has range of 150 ke to 102 me with
fundamentals to 34 mc. Ideal for quick alignment
of FM-AM receivers; provides TV marker frequencies. Also supplies 400-cycle audio output
from a Colpitto oscillator, Audio resultator voltgar can be used for testing distortion in audio
equipment, bridge measurements, etc. Complete
knobs, wire, shielded cable, instruction, disgrams, and operating manual. Size: 10 x 8 x 4½."
For 110-120 volts, 60 cycle AC. Shpg. wt.,
10 lbs.

# VACUUM TUBE VOLTMETER

Model No. 221-K. An easy to-build, sensitive VTVM formaking measurements in high resistance circuits. 15 different ranges, with DC imput resistance of 25 megohns. 4½" meter is protected against burnout. Includes zero center for alignment of FM and TV discriminators. Double-triode balanced bridge circuit assures top stability. Ranges: AC-DC volts. 0-5-10-100-500-1000; resource 0-1000 ohns and 0-1-10-100-000 megohns. With tubes, all parts, portable case, etched panel, wire, instructions, diagrams and operating manual. Size: 6 x 9½ x 5". For 110-120 volts, 60 cycle AC. Shpg. wt., 10 lbs.

83-132, Only

523,95 83-152, Only

#### **NEW 5-INCH OSCILLOSCOPE**

Medel No. 425-K. A sensational scope with all new features at smazing law price! With Push-Pull deflection! A precision instrument for TV. FM and AM alignment. Extra sensitive. 95 to 1: volts per inch. Wide range, flat from 5 cps to 500 kc, useful to 2½ me. Wide range sweep circuit from 15 cps to 15,090 cps. Direct connection to plates of CR tube available at rear of cabinet. Complete with tubes (3-6SN7, 2-64)5, 5RP1, 2-5V3 rect., portable case, etched panel, all parts and knobs, wire, instructions, diagrams and operating manual. Size 83°, x 133°, x 13° deep. For 110-120 volts. 90 cycle AC. Shpr. wt., 30 lbs. \$39.95 83-155, Only



**VOLT-OHM-MILLIAMMETER** 

Model No. 513-K. A pocket size re-liable VOM. 3" meter. Germanium crystal for AC. Ranges. DC v., 0.5-50-250-500-2500; AC and out-put v. 0.10-100-500-1000; DC current, 0.1-10-100 ms, 0.1-10 amps: res. 0.500-100,000 ohms, 0.1 meg; decibels, —8 to 455. Complete kit, ready to assemble. Shpg. wt., 3½ lbs. 514.95

SWEEP SIGNAL GENERATOR

Model No. 360-K. For visual alignment at TVa FM frequencies between 500 kc and 128 mc.
For use with any scope. Sweep width variable
from 0.30 mc. Crystal marker with variable
from 0.30 mc. Crystal marker with variable
amplitude. Provision for injection of external
marker. Phasing control. Vernier dial calibrated
in frequencies. Complete with tubes (2-6C4,
1-12AUT, 6X5GTrect.), all parts,
shielded cable, portable case,
panel, wire, instructions and operating manual. Less crystal.
Size: 10 x 8 x 6'4," For 110-120
Size: 10 x 8 x 6'4," For 110-120
Less Complete with tubes (2-6C4,
1-6C4,
1



Complete with Easy-To-Follow

Diograms and Asstructions

WE STOCK ALL EICO EQUIPMENT

Model 145-K Multi-Signal Tracer. 83-158. Only...... \$18.95 Model P-75K High-Frequency Probe Kit. 83-156. Only. 3.75
Model P-75K High-Frequency Probe Kit. 83-156. Only. 3.75 Model P-76K H-F Probe Kit. 83-137. Only..... Model HVP-1 High Voltage Probe 83-160. Only..... 6.95

(All Prices Net F. O. S. Chicago)

REE SEND FOR YOUR 196-PAGE 1950 ALLIED CATALOG Radio's Leading Buying Guide

Get the only complete Radio Buying Guide in the field—the one book that fills all of your Radio, Television and Electronic supply needs! Get every buying advantage at ALLIED-world's largest stacks of quality equipment at lowest money-saving prices -speedy, expert shipment, personal attention, complete satisfaction on every order. Get your FREE ALLIED Catalog today!



ALLIED RADIO CORP., Dep 833 W. Jackson Blvd., Chic	
Ship the following E1CO equipme	nt:
Enclosed \$   Full Payr   Part Payr   Send FREE 196-Page ALLIEL	nent (Balance C O.D.)
Name	
Address	
City Zo	ne State


# TYPE "DP" SERIES

#### for Rack & Panel



Type DPD - Pin and Socket

# CONNECTORS

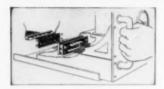





DPD with

Sacket



This type series of Cannon Electric Connectors contains a wide range and many variations of rack and panel connectors for radio equipment, quick-disconnect and instrument applications. For engineering data, write for DP Bulletin; brief data are included in the C48 Catalog

Cannon Electric also manufactures signal equipment for hospitals, industrial plants, schools, institutions and many other electrical specialties such as con-duit fittings, D.C. Solenoids, fire alarm relays, cable terminals, indicator, pathway and pilot lights, etc., etc.

Address Cannon Electric Development Co., Division of Cannon Manufacturing Corporation, 336 Humboldt Street, Los Angeles 31, Calif. Canadia offices and plant: Teronto, Ontario. World export. Frazar & Hansen. San Francisco.



#### Audio Oscillator

(Continued from page 61)

trimmer may be used to narrow the range. If wider deviations are wanted a larger capacity variable condenser may be used or the frequency of the two r.f. oscillators increased by removing the 100 µµfd. condensers from across the coils. However this last procedure tends to reduce the stability of the circuit.

As shown in the scope photos, two traces are produced by the variable condenser, causing the sweep to vary from a low to a high frequency and back again. In judging frequency response from the scope, only one of the traces should be considered as the other is merely a reversed image. This has the occasional advantage, however, that while one of the traces will have an expanded low frequency end, the other trace will have an expanded portion at the high frequency end. The experimentally inclined constructor may find it practical to use a mechanical contact on the rotating shaft of variable condenser to provide blanking during one of the traces. This, may be done by insulating half of the shaft with tape or other material and running a lead from a wiping contact to the oscillator output, thus shorting the output during one half revolution of the condenser. This will allow the scope sweep frequency to be doubled or the speed of rotation halved. A similar method would be to use the contact to provide a negative voltage to blank the scope trace, thus avoiding the appearance of a straight line through the center of the pattern. Marker pulses might be produced in a like manner, but it is usually simpler to draw them on a transparent screen covering the cathode-ray tube. The lowest frequency will be at one side of the screen and the highest at the other. The condenser may be rotated manually to any position and the frequency checked by Lissajous figures or other means and


a mark made on the screen according to the degree of rotation. Zero degrees will be at one end, 45 degrees onequarter of the way across, 90 degrees one-half way across, 135 degrees three-quarters and so on.

As suggested in the first part of the article, applications of a piece of test equipment of this nature are quite numerous. Besides presenting easily decipherable information regarding frequency response characteristics of audio equipment, the unit makes possible the observation of transient and harmonic distortions as noticeable in the oscilloscope patterns. Variations in which the width of the trace is unchanged but a displacement up or down occurs, indicate second harmonic distortion. Extra brilliance at the outside edges of the trace indicate flat topping and so on.

Response curves of amplifiers, tone controls, and resonant circuits, as well as a host of other pieces of equipment, are easily and rapidly traced, making this an ideal piece of equipment for an assembly line or a repair bench. If wished, a diode rectifier and filter may be used in conjunction with the unit to trace graphical response curves on the oscilloscope screen. In this case the output of the equipment under test is rectified and the resulting d.c. voltage applied directly to the vertical deflection plates of the oscil-This makes a somewhat loscope. neater, though limited, form of presentation and the screen may be calibrated horizontally in frequency and vertically in decibels.

Tape or wire recorders may be easily checked with this instrument and a permanent recording kept for future use. In testing phonograph pickups it is, however, recommended that a commercial sweep frequency record such as produced by Clarkstan be used. Similarly, in testing disc recording heads it is important to have a playback pickup of known flat characteristics. In checking loudspeakers or microphones it is worth while to realize that room acoustics can apprecia-

View of the disassembled variable condenser showing detail of the specially cut taper. If more convenient, the stator may be cut in a similar manner instead. The condenser used was similar to the Bud "MC" midgets but any small condenser capable of 360 degree rotation might be used. Aluminum plates may be cut to shape with a fine-blade coping saw or rotated out of position one at a time and cut with shears. If care is taken in cutting it is not necessary to cisassemble the condenser to cut the plates to shape.

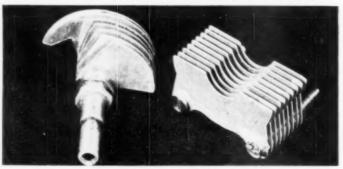



Above is the Bell System's new "musical keyboard." Insert shows the digits of telephone numbers in musical notation, just as they are sent across country.

# Playing a tune for a telephone number

Before you talk over some of the new Bell System long distance circuits, your operator presses keys like those snown above, one for each digit in the number of the telephone you are calling. Each key sends out a pair of tones, literally setting the number to music.

In the community you are calling, these tones activate the dial telephone system, to give you the number you want. It is as though the operator reached clear across the country and dialed the number for you. This system, one of the newest developments of Bell Telephone Laboratories, is already in use on hundreds of long distance lines radiating from Chicago, Cleveland, New York, Oakland and Philadelphia, and between a number of other communities.

It will be extended steadily in other parts of the country—a growing example of the way Bell Telephone Laboratories are ever finding new ways to give you better, faster telephone service.

#### BELL TELEPHONE LABORATORIES

Exploring and inventing, devising and perfecting, for continued improvements and economies in telephone service





More than a catalog, it centains installa-tion and servicing data of invaluable interest to every Serviceman, Also FREE for the asking ... IFD Cat-alog of Radio Accessories, No. 438.

Write for FREE JFD Catalog of TV

Accessories No. TV100



bly affect the results, though not to as great a degree as in point-by-point checks, and a variety of tests in various positions is desirable. This, however, is not much of a problem due to the rapidity of the check.

Other possibilities include use as a form of panoramic wave analyzer through consecutive zero-beating of fundamental and harmonics of a continuous wave and as an audio fre-

quency noise generator.

The unit described in this article is inexpensive and easy to build and has greatly increased usefulness compared to a conventional audio oscillator. An equalized output of approximately two volts is obtained from the unit shown and should be adequate for most applications. The flexibility of the system can be increased however by the addition of a power output stage. Push-pull is recommended to provide good low frequency response with minimum distortion. In any test run it is usually desirable to check the output of the sweep generator first to insure proper operation into the load used.

In conclusion, the constructor should find himself well repaid for the moderate cost in parts and time in adding this versatile unit to his test equipment.

-30-

#### SERVICING TIP

S. L. Chertok, sales promotion man-ager for Sprague Products Company, has forwarded a worthwhile serveing suggestion received from Richard Wiseman of Tomaso's Incorporated of

One of the most pressing problems in servicing television receivers nification of a frequent difficulty in servicing compact a.c.-d.e. "hot-box" table radios. How do you locate a defective condenser or other part which is defective only when it is heated up during actual operation?

Removing the receiver from its cabinet for test won't work since the extra ventilation does away with the damag-

ing temperature rise.
Mr. Wiseman's solution is practical and ingenious. He simply uses a home type hair-dryer to blow a stream of very warm air on the suspected part. This simulates the "in cabinet" condition quite quickly.




# STAY ON THE AIR an ONAN Electric Plant




When storms, floods, or fires interrupt electricity and force you off the air, you lose listeners and income. Guard against assure vital public service during emergencies by installing an Onan Electric Plant. Onan Standby Electric plants serve many network and private stations. Automatic models to 35,000 watts.

PORTABLE ELECTRIC PLANTS FOR MOBILE RADIO USES Supply A.C. power for broad-Supply A.C., power for broad-casting at scene of events. Can be carried by hand or in trunk of car. Weigh as little as 80 pounds. A.C. models 350 to 35,000 watts.

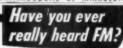Write for FREE Folder D. W. ONAN & SONS INC. 4804 Royalston



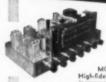

MODEL RJ-20 High-fidelity FM-AM Tuner incorporating tens controls

#### To truly enjoy FM . . .

and the unmarred brilliance Armstrong-circuit FM alone makes possible — you need the performance of the RJ-20. The man who knows radio knows nothing less will give equal performance.

Music is flawless, noise-free every instrument sounds true . . . speech is clear, with astonishing "presence". Tuning is precise and

#### And for better AM . . .

Superior performance with maximum tonal quality. Wide-range tone control to suit your taste; 20 db, treble and bass boost.

Also available: RJ-12A FM-AM tuner with friple funed IF transformers in AM, RV-10 FM tuner only, All with same Armstrong

Free Bulletin RN-150 gives performance curves and data on these high-fidelity





USED TEST and COMMUNICATION EQUIPMENT NOW for BRAND NEW COM-MUNICATION RECEIVERS, TEST INSTRUMENTS, TELEVISION SETS TV CUSTOM CHASSIS!

EASY TERMS ON YOUR NEW EQUIP-MENT PURCHASES

**Headquarters** for big-name brands of Communication Equipment and Test Instruments, Skyrider and National TV.

We specialize in Reconditioned. "Good-as-new" Test Instruments and Communication Receivers. Get our extra liberal offer on your old, unwanted equipment.

All Prices F. S. St. Leais .

**Phone CHestnut** 1125

CATALOG

COLLINS 75A-1 RECEIVER

Shpor. wt. 93 lbs. ing with a Walter Ashe

Surprise" Trade in deal What have you to trade? Only \$37500



Amazing RADIOSON

NOW ONLY



COAXIAL CABLE (RG-8/U)

\$ 5.00 100 feet

**1125 PINE** 

Did we say Big Trades? Brother, until you have sampled our special brand of bargain, you haven't lived! A "SUR-PRISE" Allowance on your used (factory-built) Test or Communication equipment will put you next to a cashsaving deal you never thought possible! Simply



what you have to trade, Indicate your preference in new equipment. Back will come your big "Surprise" offer. So climb on the band wagon. Join with thousands who have discovered that there just isn't anything to equal a Walter Ashe "SURPRISE" Trade in Allowance, Don't delay. Get your deal working today. Use handy coupon, write, wire, phone or come in.

WALTER ASHE RADIO CO. 1125 Pine St., St. Louis 1, 8	to.		RN 50 2
Rush Special "Surprise" To	rade in offer	r on my	
	nied equi	ponent)	
Ship today type Al	model No. N/AMQ-1	new equip Radiosand	ment desired) at price quoted.
Enter my order in (feet)		Cable at a	price quoted.
Send new Free 1950 Catalo	16.		
NAME ADDRESS			
CITY	75774	NE	STATE

# BARGAIN COLUMN

\$9.95

7	Round & Square 0-15 Mil DC Round 0-1 Amp DC Round 0-150 Amp AC	Each
3".	Round & Square 0-15 Mil 18. Round 0-1 Amp DC Round 0-150 Amp AC Hound 0-50 Amp AC Bound 0-50 Amp AC	\$3.45
Z**	Hound 6-1 Mil.	\$2.25
100000000000000000000000000000000000000	GENERAL ELECTRIC ME Hound 0-2 Amp RF Hound 0-15c Ac & Bc Square 0-15 Mil Bc. Round 0-30 Mil Dc. Round 10-30 Mil Dc.	\$2,25 2,50 3,45 3,95
	MISCELLANEOUS MET	ERS
3" 3" 2"	Round 6 % Mil DC Triplett Reund 100-0-100 Mil DC W.E. Round 1 Mil McClintoc Round 6 % Amp RF Simpson	\$2.25 3.45 3.45

WESTINGHOUSE METERS

#### TRANSMITTER-RECEIVER

portable lab 0-15V DC with han-



450 MC-15 TUBES, Brand New

Here is what you get: COMPLETE \$15.95



BATTERY

EVEREADY AIR CELL \$1.39

pt Delivery—25°s deposit D. order. Shipped F.O.B. Write Dept. RN-2

MICHAEL STAHL, INC. 39 VESEY ST.

New York 7, N. Y.

#### A GOOD IDEA

HEREWITH submit an idea that may be worthy of publication. At any rate, I have had considerable success with it and would like to pass

"Many amplifier builders have encountered ground loops in their amplifiers with their attendant headaches. It is difficult in an elaborate system to run many ground wires to one point in a low level stage. To overcome this, before mounting components, I insert a sheet of insulation paper in the bottom of the chassis, exactly the same size as the chassis. I then drill through it and mount all components. Now, instead of ground wires, I paint all my grounds on this sheet with regular silver paint used in printed circuits. When connections are to be made I cut oat a tab, lift it up, paint with silver (very heavy), squeeze a lug on to it, and solder my wire.

"If the selected spot for a one point ground is not satisfactory, it is easily moved to another. I have been unable to create a ground loop with this method even when trying to do so as a

> James G. Meyers Audio Consultant New York, N. Y. . .

#### FORGOTTEN MEN

JUST finished reading the editorial in your September issue. It congealed some ideas and thoughts I have had on the subject for some I feel compelled to write these thoughts with the hope that you will publish them in order to get adverse reactions from service technicians in places not now served by television.
"We grant that TV is growing by

leaps and bounds. We grant that it will continue to grow. However, when you state that because the FCC is planning to add 42 new video channels to the u.h.f. band, which will mean over 1700 additional TV stations in remote areas, then I believe that you are taking too much for granted.

"I feel many will agree with me that the main problem in the extension of television to remote areas is economic, rather than technical. With the cost of a TV transmitter and associated equipment running from \$200,000 up, plus the cost of coax cable extensions running into fancy figures per mile, just how, from an economic standpoint, could we expect thousands of small, isolated communities to ever have television serviceunless, of course, there is a technical solution to the problem.

"Remember further that a TV station in a community not served by coax, that is, not on a network, will run out of program material worth looking at in something around two days. There just isn't the local talent for such a thing. Possibly Hollywood will become interested to the point of putting out films for such service only, but that also is questionable, as they would run into terrific objections from local theater owners. Remember also that the few local merchants who advertise would have to be liberal indeed in their advertising appropriations to support such a setup. There is also the question of just what volume of sales could be expected if purchasers knew that the only station they could receive would be the one local station. There would be no choice of programs, but just a 'take it or leave it' setup.

"There has already been a channel allocated to this city (Ironwood, Mich.) but so far I see no mad rush to start construction of a station, and for obvious reasons. Some way or another the investor must get his money back.

"In connection with your line of thinking, I would like to make another statement of fact. It seems to me, and to many other radio dealers with whom I have talked, that the manufacturers are going just a bit whacky on this television thing. In fact, they are going so cuckoo that they have all but forgotten that they have a dealer organization outside of the big television centers. This organization holds four major franchises. They are Zenith, Philco, Admiral, and Capchart. We have had console combination radios on order with all of them for nearly two months. The store is almost clean of console combinations. yet, to date, we have received just two 1950 combination consoles. Evidently these four companies, along with too many others, are devoting all their facilities to the manufacture of television receivers.

"We dealers in isolated communities (of which there are thousands) understand why they are doing it, but we wonder just what is going to happen to their dealer organizations which cost them so much to build up. What are we supposed to live on while they all get in the mad scramble in an attempt to capture the television market? Such a victory is bound to be short-lived at the best. Who pays our rent and what should we tell customers who want radio combinations?

"Can't you and these manufacturers see that there is still a market for harnesses and horseshoes, even in this age of the horseless carriage.

'Don't get me wrong. We are for television. It is a great thing. How-

WO 4-2882



#### "LITTLE DEVIL" RESISTORS

For quick, easy identification, resistance and wattage are clearly marked on every one of these tiny, rugged insulated composition resistors. In three sizes -1/2, 1, and 2-watt and all RMA resistances. Tolerance ± 5 and ± 10%.

#### CLOSE CONTROL RHEOSTATS

Available in 10 sizes from 25 to 1000 watts, Ohmite rheostats can be relied on for close control and long life. Ceramic and metal construction. Windings are locked in place by vitreous enamel, and the metal-

graphite brush provides unsurpassed



R. F. PLATE CHOKES
"Frequency-rated" for easy selection and top performance. Single-layer wound on low power factor steatite or molded plastic cores. Wire is held rigidly in place, insulated, and protected by a moistureproof coating. Seven stock sizes from 3 to 520 mc. Two units rated 600 ma; all others 1000 ma.

# OHMITE DEPENDABI



"BROWN DEVIL" RESISTORS

Wire-wound, vitreous enameled Brown Devils provide utmost de-

pendability in a size small enough to fit most installations. Easily mounted by 11/2" tinned wire leads. Three sizes: 5, 10, and 20 watts. Tolerance ±10%.

#### MOLDED COMPOSITION POTENTIOMETER

It's quiet! This Type AB Potentiometer has a resistance unit that's solid-molded. As a result, the naise level aften becames less with use. Has a 2-watt rating, good safety factor,



Write for your copy of Ohmite Catalog

"LITTLE DEVIL" RESISTOR ASSORTMENT

Packed in this attractive. all-plastic cabinet are 125 carefully selected "Little Devils" (either 15 or 1 watt) in the 40 values you

use most often. The assortment costs you only the regular price of the resistors, nothing extra for cabinet.

OHMITE MANUFACTURING CO. 4883 Flournoy St., Chicago 44, Illinois



RHEOSTATS . RESISTORS . TAP SWITCHES . CHOKES . ATTENUATORS



# Easy on the Ears.

#### TELEX Monoset\*-Under Chin Headset

Stethoscope design of the Telex Monoset eliminates tiresome pressure instrument swings lightly under the chin. Wear it for hours without fatigue!



Weighing only 16 oz., Earset's flat plastic frame slips onto the ear, holds the sensitive receiver securely in place. User's other ear is always free for phone calls or conversation.



# TELEX Twinset\*—Nothing Need

Lightest twin-receiver headset made-weighs only 1.6 oz. Adjust to any head. Flexible, slips into pocket.

Write for Colorful FREE Specifications Folder Today!



DEPT. H-20-2, TELEX PARK MINNEAPOLIS, MINNESOTA

In Canada, Atlas Radio Corp., Toronto



ARC-5 RECEIVERS: 6-9-1 Mes 5.95 52-1.6 Mes., Broad-cast. En. 19.95 cast Ea 1.5-3 Mes. Ideal for 12.95 sed, excel cond i Mcs. Ea 59.95 5.3 Mcs., less cover. Ea 3-7 Mcs., less cover. Ea APN-1 ALTIMETER-TRANSCEIVER: Operates approx. 420 Mes. FM designed to give accurate beight above ground. Unit can be revamped for the 420 Mes. ham: or foundation for eitzen's hand Contains. 2-955, 2-9601, 5-128H7, 2-128H7. A dyname vibrating capacitant for producing an FM signal, many other useful parts. (Makes excel unit for FM or TV sweep generator.) Excel cond. \$3.95 FL-8 FILTERS, the lazy Oler. Ea. OIL FILLED CONDENSERS: NEW 2.29 2.50 V-WILLARD WET CELL BATTERIES: 12 FOOT COLLAPSIBLE BRASS ANTENNA: W. E. HANDSET, TYPE TS-7, push but EC733D RECEIVER & R89 ARNS Localizes \$4.95

ran Scope). With schematic and 100 kes, crystal Hooked up to 110 V. Each ABOVE INDICATOR & RECEIVER POWER

RECEIVER POWER SUPPLY. BOTH FOR ... 535.50 METERS! LOOK! METERS!

ROCKS Within 12 | Ke of ur specs in the ham 40, 20, 11, 10, 6, 2 meter bands Ea.

10, 0, 2 meter bands Ea.

NEW TUBES! NOT SURPLUS!

Month of Feb. ONLY!

50.63 384
1.09 636
4.49 12AT7 NEW SURPLUS TUBES! Month of Feb. ONLY!

Rush Orders to:

#### COLUMBIA ELECTRONIC SALES

522 South San Pedro Street LOS ANGELES 13, CALIFORNIA ever, careful thought tells us that we would like to use atomic energy to run our automobiles as well, but we just will have to wait, and, in the meantime we are hoping the filling stations don't close.

"All we dealers and service technicians ask is a reasonable chance to do a good job in our field without too many impediments and blows below the belt."

L. W. Van Slyck Northern Electric Co. Ironwood, Mich.

PHONE VS. C.W.

\*\*A CCORDING to the National Bu-reau of Standards, a radiophone signal must be 14 db. stronger than a c.w. signal to maintain the same readability, thus db. = 10 log power ratio,  $14 = 10 \log x$ ,  $1.4 = \log x$ , and therefore x = 25.2.

"From this it can be seen that if I am speaking to someone on c.w., running 40 watts, if I want to switch to phone and still maintain the same readability, I must increase the power to 1000 watts (100% modulation).

"It seems to me that this is reason enough for the respect given to c.w. by the Government and consequently

for the code test. "Phone is fine for communications under good conditions, but when things get bad, c.w. gets through as proven by the log equation. Another point is selectivity. I have an excellent com-

munications receiver. On phone the best selectivity obtainable is 1 kc.

More would destroy readability. On c.w., with a good audio filter. I can get 50 cycles. This means that for every phone signal. I could fit 20 c.w. signals. "I operate phone often. For ragchewing I think it is better than c.w.

But credit must be given where it is

David L. Wiesen, W2WHB New York, N. Y.

-30-

#### SPEED CHASSIS CLEANING

A Nordinary electric household sweep-er with a suction attachment (see Fig. 1, will pull the bulk of dust and dirt from a radio chassis.

Car radios in particular pick up a lot of road dust which should be removed when they are serviced.



#### Mae's Service Shop

(Continued from page 50)

were exactly thirty-nine of them, and most were of the old-fashioned slowheating type that take forever and a day to warm up. Boy! did he have some oldies in that mess! He got real annoyed because there were a couple I could not test. They seemed to have the filament leads brought out to pins on the sides.

"Old Kellogg tubes!" Mac exclaimed in the tone of fond reminiscence that a man usually reserves for speaking of an old flame. "He must have had some

"By the time I waded through that basket. I decided there ought to be an easier way. That is when I started inventing

"Well, they always say that if you want to find out the best and easiest way of doing something, just put a lazy man at the job," Mac gently jibed; "but what did you find out about that new customer's radio?"

"That's it playing there on the end of the bench. A 50L6 was out. She says that in the last two months she has put in three 35Z5's, and this makes the second 50L6. Yet most of the time the radio plays OK. Once in a while, though, she says it will kind of die away for a few seconds and then come back. She noticed, too, that when this happens the dial lamp flickers. Probably the 50L6 filament was intermittent for a while before it went clear dead. The set sounds perfectly all right now."

"Sounds logical except for one thing." Mac said with a frown. "That \*does not account for so many tubes going out in such a short time especially the same kind of tubes."

He picked up a little rubber hammer such as doctors use to test muscular reflexes and struck each of the tubes sharply from several different angles. When he struck the 12SK7, the radio developed a sudden hum that slowly died away-along with the music. At the same time the dial lamp and the filaments of the 50L6 and the 35Z5 grew much brighter. A second sharp rap on top of the 12SK7 returned the dial lamp to normal brilliance, and a few seconds later music started coming again from the speaker.

That 12SK7 cathode is shorting out to the heater," Mac said in answer to the mute question of Barney's arched eyebrows.

"That explains the hum," Barney agreed; "but what causes the filaments of the glass tubes to brighten up?"

Before answering, Mac sketched the diagram of Fig. 1 on the blackboard at the end of the bench.

"As you know, the tube filaments are all in series. Notice that the 12SK7 is in the middle of the string. In this set, the 12SK7 cathode goes directly to the chassis, as does one side of the line. When the filament of the 12SK7 shorts to the cathode, it is just the

# NOW - - - TWO GREAT



# RADIO HANDBOOKS

11TH EDITION: the standard work on practical and theoretical aspects of all radio communication, both amateur and commercial.

12TH EDITION: detailed constructional information on a wealth of radio communication equipment; all brundnew; none from prior editions.

Both these top-notch books should be in the hands of every person interested in radio communication. There is little overlap in coverage; each is a perfect companion volume to the other.

#### TWELFTH EDITION CHAPTER HEADINGS

#### ELEVENTH EDITION CHAPTER HEADINGS

#### TWELFTH EDITION EQUIPMENT DESCRIPTIONS

#### ELEVENTH EDITION EQUIPMENT DESCRIPTIONS

EITHER EDITION


AT YOUR DEALER

By Mail from Us: \$3.25 in U.S.A. (plus any tax); elsewhere, \$3.50

Editors and Engineers ( 1818 VINWOOD BORD Santa Barbara Chinomia



# TV Money Savers!

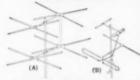

#### A STACKED CONICAL TV ARRAY

High gais, all band, TV array at amazingly low cost. Direct coupling to 72, 180 or 300 or mine with minimum loss. All dural construction. Less mest. Shpg. wt. 14 lbs. Cat. No. CC852A. Single. As above, but with 10-foot mast. 17 lbs. Cat. No. CC852. Single. 51195.

#### B HI-LO DIPOLE AND REFLECTOR

B meta broke and hards easy to in stall, trouble-free and highly efficient Corrosion resistant 8 foot seed mark Adjustable mounting base and bracket. All elements secuely locked. Dipole and reflection of hard seed to be seen as the seed of the seed Separate orientation for each bay. Sparate orientation for each bay. Sparate orientation for each bay.

### TUBES Con't mention name; top.

1B3GT \$1.40,6B6GG \$1.90,6AK\$ \$0.99 6AG\$ 1.00,616 1.10112N7GT 7.9 6AL\$ 79,6SN7GT 79,6AG7 1.28 6AU6 79,6K6GT 65,6V6GT 79 6BA6 75,5U4G 60,6SR7 55

# Federal's K-111 300 ohm shielded transmission line

Fine quality, 20 guage twin-lead, 1000 1 1/2 ft, \$11.25; 100 ft, \$1.25; per foot...... 1



LOUD SPEAKERS



#### RADIONIC EQUIPMENT CORPORATION

Tribune Theater Entrance
170CC Nassau Street :: New York 7, N.Y.
WOrth 2-0421 :: Open daily 9 to 6-Sat. 9 to 5



same as though you placed a jumper from point 'X' to point 'Y.' Instead of the line current going through all of the filaments, it just goes through the 50L6 and the 35Z5. As the short first occurs, it causes a hum to be fed through to the speaker; but as the filament of the bypassed 12SQ7 cools down, both the hum and the music die away.

"Ordinarily, this short is brought about by the expansion of the hot 12SK7 cathode and filament. It is probably close to the 50L6 end of the filament; so this allows the remainder of the 12SK7 filament to cool down after the short has happened. The contraction that accompanies this cooling relieves the short. That is why she said the set would die away and then come back by itself."

"And I suppose the extra current that goes through the glass tubes when the short happens is what accounts for their short life. Get it? 'short happens' 'short life!'."

"Yes, I get it," Mac said, holding his nose, "and it ought to be buried. You had better go outside and air off a while after that pun."

"You'll be sorry you talked to me like that when I am wallowing in the government lettuce I will get for my invention." Barney warned.

"Yes, and you will be sorry if I catch you forgetting to check all the tubes carefully for shorts in an a.c.-d.c. receiver that seems to be exceptionally hard on filaments," Mac countered as he replaced the 12SK7 with a new tube from the bin.

#### -30-

#### CANADA'S MORALE-BUILDING BROADCAST STATIONS

By R. V. PARRETT, VETTG

OF INTEREST to readers of RADIO & TELEVISION NEWS are the low-powered broadcasting stations maintained by personnel of the Canadian Army and the Royal Canadian Air Force throughout Canada's vast northland.

These stations are licensed by the

These stations are licensed by the Canadian Broadcasting Corporation for the entertainment of the service personnel who maintain the northern outposts and any civilians within range of the transmitters. Most stations are built and staffed by the post's personnel. They operate on powers ranging from 25 to 100 watts.

Programs are mostly recorded, with a sprinkling of Armed Forces transcriptions left over from the war days. Everyone going "outside" on leave or furlough is expected to bring back a couple of records.

Typical of the stations is CFSJ at the R.C.A.F. station at Fort St. John, B.C. The station is licensed for 30 watts and operates on 1600 kc. The "studio" is built into one corner of the airport control tower and is operated by the staff on duty in the tower. The transmitter which was originally housed in the tower had to be moved to a remote location to escape induction in the airport control circuits.

The station was promoted by Flying Officer Gillian and built by Leading Aircraftsman J. Crawford of the Air

Radio station CFWH is a busy northern outlet maintained by the Canadian Army at Whitehorse. Y.T. Transmitter and studio are in an old army harracks on the Alaska Highway.





The CFSJ "studio" located in the disport control tower at Fort St. John. B.C. At the mike of "The Tower Broadcasting System" is Flying Officer K. S. Bateman of the R.C.A.F.

Force. Other station staff members contributed to the establishment of the station. The 30 watts is rather optimistic, they report.

Probably the most active station in the morth is CFWH at Whitcherse, Yukon Territory. It is operated by the Canadian Army under Capt. C. J. A. Hamilton and technician Carp. Jack Spall of the Royal Canadian Signals. The whole military and civilian population of the busy northern town cooperate to keep the station on the air seven days a week.

A recent quiz show over CFWH netted 8730 which was used to buy muchneeded recordings and transcriptions for the station. The old AFRS transcriptions had been worn down to the felt on the turutables!

To provide the northern stations with program service the Canadian Army has located a 5000 watt short-wave transmitter at Edmonton, Alberta with the call VED. Programs are beamed to the Northwest Territories and picked up by CHAK, Aklavic; CFNW, Norman Wells; CFHR, Hay River; CFYT, Dawson Gity; and CFWH, Whitehorse. VED operates on 8265 ke. from 7 a.m. until midnight (MST) relaying the programs of CBX.

MONEY BACK GUARANTEE— We believe units offered for sale by mall occupant on the design, calibration and value of all items advertised by us and unhesitatingly offer all merchandise subject to a return for credit or refund. You, the customer, are the sole judge as to value of the item or items you have purchased.

The New Model TV-20 A COMBINATION 20.000 OMMS PER MULTI-METER

#### and TELEVISION KILOVOLTMETER



S D. C. CURPENT RANGES: 0-50 Microamperes 0-5, 50 500 Mills

4 RESISTANCE BANGES: 0-2 000 20,000

THE NEW MODEL TV-10



The New Model 200 AM and FM

#### SIGNAL GENERATOR



MODULATING FRE

\* ATTENUATION:

#### The New Model TV-30 TELEVISION SIGNAL GENERATOR



and FRONT ENDS without the use of an ascillascope,

SPECIFICATIONS

18- 32 Me.

plete with shielded re-axial seed and all operating in-

THE NEW MODEL 670



A Combination VOLT-OHM-MILLI-AMMETER plus CAPACITY RE-ACTANCE, INDUCTANCE and DECIBEL MEASUREMENTS.

O.C. VOLUSE: 0 TO TOTATE OF THE TOTAL OF THE Ohms to 3 Megohns, INDUCTANCE: 1.75 to 70 Henries; 35 to 8,000 Henries.

DECIBELS: -10 to +18, +18 to +38,

# MODEL 770 VOLT-OHM MILLIAMMETER



D.C. CURRENT HANGES: 0-7% 15-75/ RESISTANCE RANGES: 0-500 ogms. 0-1

\$1390

20% DEPOSIT REQUIRED ON ALL C. O. D. ORDERS

GENERAL ELECTRONIC DISTRIBUTING CO. DEPT. RN-2, 98 PARK PLACE, **NEW YORK 7.** 

# Sharp, Clear Television Reception at 100 MILES AND OVER

Out in the "fringe" areas and beyand is where you really need "signal strength" to get good pictures. That means high gain and sharp beaming with minimum interference. With a Workshop Series 2A Antenna you get maximum signal strength . . . and brilliant, noise-free reception. A Workshop Antenna is your assurance of clearest pictures.

LIST PRICES

Channels 2 to 6 Channels 7 to 13 \$52.00 43.50

Write for Television Antenna Catalog

#### WORKSHOP ANTENNA **FEATURES**

HIGH GAIN - 5 to 11 db. over a conventional dipole

SHARP DIRECTIONAL PAT-TERN - narrow "beam" in both horizontal and vertical planes.

HIGH SIGNAL - TO - NOISE RATIO - to eliminate inter

SINGLE CHANNEL SELECTIV-ITY - single, tuned array for each channel.

FRINGE AREA RECEPTION exceptional signal strength --- even beyond 100 miles.

RUGGED CONSTRUCTION -1/2-inch duraluminum eleme strong, weatherproof assembly, CLEANCUT APPEARANCE -



### WORKSHOP ASSOCIATES, Inc.

# Gederated Announces ...

# SENSATIONAL REDUCTION ON RCA BATTERY VOLTOHMYST

TYPE WV-65A

NOW \$3950 Was \$87.50

Now Federated makes it possible for you to own world-renowned RCA's push-pull VTVM for \$48 less than you would have paid only a short time ago! This battery Volt-Ohmyst measures voltage, current and resistance and operates on a self-contained power supply. You'll find it's useful beyond all expectation for radio, television, lab and service work.

Please include 25 % deposit with order Balance C.O.D. Dept. 28-8



A-C Voltmeter Ohmmeter 1115 HAMRTON ST.



Bix Ranges 0/A Input Hose-tance Sensitivity (max

D-C Ammeter Six Ranges 0/3/10/30/100/300 milliamp and 0/10 amp

for full scale deflect

#### Transcriptions

(Continued from page 34)

"stamper" so that it can resist the abrasive effect of the pressing material from which the final product is formed.

The "stamper" is punched and sheared to size. Fig. 12, and is finally checked by the Quality Control department as to dimensions, before being issued to the press department.

The information compiled by Quality



"master" and "mother" for future use.

Control on these "stampers" is posted on three sigma control charts so that the production department can know daily whether or not the processing facilities are producing parts that fall within predetermined control limits for quality and tolerance.

The "master" and "mother," having produced the "stamper" plate, are routed to Production Control, where they are numerically filed by the code number originally assigned to the master recording upon receipt from the recording studio, Fig. 14. Here they re-

The transcription as it comes from the die of record stamping machine.



RADIO & TELEVISION NEWS

Dighy 4-3050



Visual inspection of each transcription.

main, the property of the customer, until his further need for production on this number.

The date of receipt of the "stamper" by Production Control is noted on its code card and the "stamper" is immediately sent to the press department with labels and a production order. The code card shows the production control clerk that production on this number was promised for immediate delivery. The press department receives the "stamper" plate and the job is routed to the first available press.

The "stamper," having been mounted in the record die, is ready to make the first impression, Figs. 13 and 15. This first pressing will be sent to Sound Check where it is played completely before an order to continue production can be given.

As production continues, the pressings arrive at the visual checking point and are checked for any flaws that would affect the play of the record or detract from its appearance, as in Fig. 16.

When the production of this order has arrived complete in the shipping department, the shipping clerk checks his shipping instructions and prepares the necessary shipping labels, waybills, etc. required to get these units of production to their required destination in the time originally specified by the customer.

The quality and engineering standard to which these electrical transcriptions must be produced for proper presentation over the air have been set by the National Association of Broadcasters. Their interest in keeping standards abreast of technological advancements has assured the listening public of high quality transcribed shows.



# Build Your Career! Become an **ELECTRICAL ENGINEER**

# Major in Electronics

# B. S. Degree in 36 Months

THE Electrical Engineering course offered by this non-profit, 47-year-old Technical Institute and College is world famous.

Save a valuable year by gaining your major in Electronics and a Bachelor of Science degree in 36 months of year-round study.

Follow an industry-guided program which is constantly attend to current developments. It presents a solid program in the basic sciences . . . . chemistry, physics, mathematics, economics and electrical engineering subjects . . . plus 19 technical specialty courses in Engineering Electronics, including four courses in electronic design.

You are invited to request helpful guidance literature which illustrates how your electronic interests can be the foundation of a worthwhile career.

Over 35,000 alumni and 1,555 students • Faculty of 85 specialists • Train in modern, well-equipped shops.





# AN EXPANDING INDUSTRY

Electronics is of tremendous, growing importance to industrial applications—high frequency heating, power system course, air conditioning, printing, webling and many others. And husiness leaders predict television will be among America's top ten industries by 1931. Persare now to lecome an Electrical Engineer, with a specialized, practical hackground to capitalize on all those fast growing opportunities.

# in one year of study, become an ELECTRONIC TECHNICIAN

This certificate is yours at the end of 12 months of study in the Electrical Engineering

# Prepare Here for a Coreer in RADIO AND TELEVISION

In 18 months you can become a Radio-Television Technician, ready for positions in receiver and transmitter testing, servicing, sales, supervision and production. Because of this school's concepts curriculum, the Bachelor of Science degree in Electrical Engineering t Electronics Major'i may be carried in 24 additional.



WRITE today for the helpful 48-page pictorial bulletin, "Your Career"; and the 110page 1950 catalog.

# SCHOOL OF ENGINEERING

A Special Preparatory Program is offered for students who wish to review basic subjects or who require additional background.

Ozcar Werwath

Military, Practical or Academic training will be evaluated for advanced credit.

Next Terms Open
APRIL 3 . . . JULY 3

	KEE SCHO				ires, Wis
Without Your C	obligation,	send []	48-page gr 1950	picturial Catalog.	bulletin I an
interesto	in				course
NAME				A	E
ADDRE	SS	* ( ( ) * * * )	*******		
	eteran of			STATE.	

-----



FREE!

MERIT TV

"REPL" GUIDE

# JAN. 1950 ISSUE

400 MODELS MOST COMPLETE UP-TO-DATE LISTING

Get this easy-to-use, timesaving guide to exact replacements for all popular television receivers. Simplifies servicing, cuts repairbench time. Write us today for your free copy!

WATCH FOR Merit's future issues of the TV "Repl" Guide

USE MERIT TVI

TV Supe Muchal Company (N)
Parasts Maching Oscillators,
Variest Outputs, Paras Californa
Deflection Yakes, Flybechs



4437 NORTH CLARK ST., CHICAGO 40, ILL.

# AFCA SOCIATION NEWS

This Association is a patriotic non-profit organization, with chapters in most of the larger cities, dedicated to developing and maintaining efficient personnel, commissioned, enlisted, civilian, for the supply fincluding design and development), installation, main-tenance, and operation of communications and electronic equipment for Army, Navy, and Air Force and their supporting civilian activities. It publishes a maga-zine "SIGNALS" at its national at its national headquarters in Washington. Every American interested in any way in communications is eligible and invited to join. Dues are \$5.00 per year. Application should be submitted to the secretary at 1624 Eye St., N. W., Washington 6, D. C., who will furnish details upon request.

# DIRECTORS' MEETING

The Board of Directors met in New York on December 7th. It was decided to appoint a special committee to re-examine the alms and purposes of the Association and the means to implement them. Col. J. D. O'Connell, President of the Fort Monmouth Chapter, presented a description of plans for the fourth annual meeting at Fort Monmouth May 13th. These plans in-

clude several spectacular "firsts" and promise to make the meeting the best so far held.

### AFCA CHAPTER NOTES

# Augusta-Camp Gordon

The sixth meeting of the chapter was held on November 16th at the Camp Gordon Officers' Club. Plans for a membership drive were approved and a nominating committee was appointed to handle business in connection with the annual election of officers at the next meeting.

At the close of the business meeting chapter members adjourned to the Unit Training Group Area of Camp Gordon where they inspected an Army Mobile Communications Center.

#### Chicago

The Chicago Chapter held its December meeting at the Bell & Howell Company's Lincolnwood plant on the evening of December 7th.

Chapter President Oliver Read presided at the meeting. Malcolm G. Townsley, Bell & Howell vice-president in charge of engineering, welcomed the group.

After dinner Charles E. Phillimore, vice-president in charge of manufacturing, briefly described production operations centering about the completely air conditioned 220,000 square

Bell & Howell staff discusses operation of microfilm equipment at the December meeting of the Armed Forces Communications Association in Chicago with Chapter President Oliver Read (right). Those taking part in the discussion are (left to right) S. E. Plattner, C. E. Phillimore, E. E. Strauss, P. M. Thomas. and M. G. Townsley.



BADIO & TELEVISION NEWS

# SELENIUM RECTIFIERS

- and -ELECTRONIC COMPONENTS

### THREE PHASE FULL WAVE BRIDGE RECTIFIERS

	BEIDGE RECITIES	
finput 0-234VAC		0-250*VDC
Type No.	Corrent	Price
3813-1	LAMP	\$ 22.66
3813-2	2 AMP	32.00
3813-4	4 AMP.	56.00
31:13-6	6 AMP	81.50
31-13-10	10 AMP	105.00
31 F 1 B 32 - 5 KL	D. T. A. T. E. E.	130.00

#### CENTER TAPPED RECTIFIERS SINGLE PHASE FULL WAVE

Input 10-0-10VAC		0-8°VDC
Type No.	Current	Price
C1-10	10 AMP	\$6.95
C1-20	20 AMP	10.95
C1-30	30 ANTE	14.95
C1-40	40 AMP.	17.95
C1-50	50 AMP	20.95

# RECTIFIER MOUNTING BRACKETS

For Types Et	through	156	and		
Type C1			\$6	.35	per set
FOR TVINES BILL				.70	DIET HEE
For Types 3B			1.	.05	per set

# SINGLE PHASE FULL WAVE BRIDGE RECTIFIERS

0-18VAC		0-12°VDC
Type No.	Current	Price
B1-250	250 MA.	\$0.98
Fr1-500	5683 NEA	1.95
B1-1	3 .4,769 8*	2.49
B1-1X5	1.5 A34P	2.95
B1-3X5	3.5 AND	4.50
B1-5	5 AMP	5.95
B1-10	10 ANSP	9.95
B1-20	20 AMP	15.95
B1-30	30 A MT	24.95
B1-60	40 A M P	27.95
B1-50	50 AMP	32.95

Input 0-36VAC		Output 0-26°V DC
Type No.	Current	Price
Bi2-150	150 MA.	\$6.98
B2-250	250 MA	1.25
B12-300	200 MA	1.50
B2-2	2 AMP	4.95
B2-3X5	S.5 AMP	6.95
152-5	5 AMP	9.95
132-10	10 AMP.	15.95
B2-20	20 AMP.	27.95
R2-30	30 AMP	36.95
B2-40	40 ANIP	44.95

toput 8-115VAC		Output e-9e-VDC
Type No.	Current	Price
B6-250	250 MA.	\$2.95
E16-600	600 N.A.	5.95
B6-750	750 MA.	6.95
Fi6-1X5	1.5 AMP.	10.95
B6-3X5	3.5 AMP.	18.95
B6-5	B AND	24.98
B6-10	10 AMP.	36.95
B6-15	15 A 31P	54.95

# CUSTOM DC POWER SUPPLIES

# RECTIFIER CAPACITORS

CF-14	3000	MED	12VDC	\$1.69
CF-15	6000	METE	12VINC	2.93
CF-I	1000	METE	15V DC	98
CF-2	2000	MED	LSV DC	1.69
CF-20	2500	MED	L5VIN:	1.95
CF-3	1000	MFD	25VDC	1.25
CF-R	2X3500	MED	25VDC	8.45
CF-5	1500	MED	30V DC	2.49
CF-6	\$000	MPD	30V Dr.	3.29
CF-7	3000	MEIN	35VDC	3.2%
CF-8	1.00	MPD	SOV DC	9%
C D-118	500	MESS		1.45
CF-16	2000	MFD	SOVING	3.25
C. FZ.I	1200	MED	90V DC	8.25
C-B-10	200	MED	150VDC	1.69
CF-10	500	MED	200VDC	5.25
CF-12	125	MED	350V DC	2.49

Mounting clamps for above capacitors. . 15c ca

# RECTIFIER TRANSFORMERS

Type No.	Volte	Amps.	Shoe We	
		ve cee fine.	SHIPE WE.	Price
XF15-12	15	12	7 Ib=	\$ 3.95
TXF36-2	36	2	6 Ibs	3.95
TX136-5	36	.5	8 lbs	4.95
TXF36-10	36	10	12 ths.	7.95
TXF36-15	36	1.5	20 Pbs.	11.95
TX F36-20	335	20	30 Ibs.	17.95
XFC18-14	ISVCI	1.6	Itt Ibec	5. 9.5

All TXF Types are Tapped to Deliver 32, 34, 36 Volts, XFC Type is Tapped to Deliver 16, 17, 18 Volts Center Tapped.

# RECTIFIER CHOKES

Type No.	Mr.	Amps.	De Bes.	Price
HY5	.02	5	25	\$8.25
REYSA	028	.5	20	8.95
BEY 10	02	10	.30	9.95
DIVION.	.014	10	0.6	7.95
HY15	015	15	-30	83.98
BIY20A	.007	20	82	12.98
Type A-	low res	istance et	okes are	specially
suited to	circuits	PRODUITING.	excellent	WOIS MADE

# ADDITIONAL SELENIUM RECTIFIER TYPES AND GENERAL INFORMATION MAY BE FOUND IN OUR CATALOG No. 719

# VACUUM CAPACITORS

12 Mmfd	20 Kv	\$4.98
50 Mmfd	33 Kv	4.95
50 Mmfd	32 KV	5.95
Overall length 6	i. diameter	22.0
terminal diameter	" " struct wit.	2 Ibs

# EDISON THERMO TIME DELAY RELAY

Heater voltage 115 V Norm open SPST con-tacts 15-30 sec delay. Contact rating 115 V 3.4, 440 V 2.8. Suc 25, 2514 dism. Standard 4-prong tube base. Ea. 98C

# OIL CONDENSERS

5 Mfd. 400VDI Telephone Type	50	20
2X I Mid 600VDC Bathtub		39
6 Mfd 600VDC w mtg clamp		79
8 Mfd 660VAC /2000VDC w/brkts		50
15-15 Mfd. 8000VDC Voltage Doublet	9	
Type 26F381 w brats	3	9.5

# KLIXON 40 SECOND DELAY SWITCH

Heater operates on 115 VAC or DC Contact DFST—one pair rated at 30 A., 115 V. or 20 A 220 V. Auxiliary contacts for lighter loads \$2.49

# PILOT LIGHT ASSEMBLIES



Each.

A trent type, panel mounting, amber jewel only. Sunfield rim centrals -713M-181(6117\* Basellet and aliminum construction, Built replaceable from from panel. For single contact bayonet builts, up to T-34<sub>3</sub> size. Differential 2-1<sub>3</sub>° overall length, 1, danneter, 1, panel mide hole. Indicated the control of the control of

# G-R VARIAC

Type 100 R 2 KVA, Input: 110 or 220 V.A. C. 60 CPS, Output: 0-220 or 0-270 Volts. Brand new—limited quantity. Shpg Wt 36 ibs \$39.50

# ATTENTION !!!

Eulletin No. 713, listing various government and commercial surplus items, is new available upon request.

# DC POWER SUPPLY

Limited quentity-Gov't Surplus



Output: 2.5/24/28. seh mounting Overall dimen-shpg wt 30 lbs \$36.00

# DIEHL MOTOR



Noiseless ball - bearings heavy cast construct \$4.50

# RECTIFIER KIT No. 612-10

6 and 12 VDC at 10 Amps. This unit will deliver unfiltered direct our or operation of motors, dynamotors, solen-icetroplating, battery charging and sin

enipment.
The two output voltages can be used simultaneously, and can be varied above and below their nominal ranges.
Complete with schematic diagram. \$15.95 and instructions. Show wt., 12 lbs. \$15.95.

# FILTER KITS FOR No. 612-10

I section choke input, 10% ripple. \$9.64 19.28

PANEL METERS
Attractive, rugged, and reasonably priced. Moving varie soletand type with accuracy within 5% in Ampere Dec.
Ampere Dec.
Any range. Any range \$2.49 each

Minimum order \$3.00. No C.O.D.'s Add 10% for Prepaid Parcel Post and Handling. Terms: Net 10 days in the presence of approved credit.

All prices subject to change without natice. Prices and delivery F.O.B. our NYC Warehouse.

All merchandise subject to prior sale.

# WESTERN . **ELECTRIC BLOWER**

\$13.95

# DIEHL BLOWER



rocco type, displaces 100 C F.M. 115 VAC. 60 sps. Mosture and fungus resistant. Flange diameter 4. Overall size 7 5 25 13. Removed from equipment Tested \$9.95

Adjustable right angle aluminum extension tube to fit flange ..... 98c

# WESTINGHOUSE AIRCRAFT MOTOR

Brand new 24 VIC or AC reversible on both 1.50 ff P. 4800 HCM continuous daty Length of leads 18° Dimensions 315, 23 M° 43 M° 43 M° 43 M° 43 M° 44 M° 45 M°




# OPAD - GREEN + COMPANY +

71 Warren St. New York 7, N. Y.

Phone: Blekman 3-7385-6
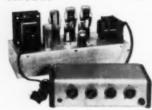
# Add ONE & COLUME TO YOUR ELEVISION **BROOK High Quality AUDIO AMPLIFIER**

ALL TRIODES Attractive small remote control console for maximum convenience in operation and installation



For you who revel in fine music and abhor distortion over radio, television, phonograph-the BROOK alltriode high quality AUDIO AMPLIFIER has been developed, after years of intensive engineering research. Now you can have "live" music in your own home clean . . . clear . . . bright music through any good speaker. The use of triodes in all stages-together with Brook designed transformers-means amplification at its level best. For REALISM in critical music reproducts hear this finest of amplifiers at your Brook Dealer's NOW

ALL TRIODES

Madel 12,43-10 watts

# FOR BEST RESULTS - BROOK GIVES

- . Extremely High Volume Without Any Loss of Quality
- · Brilliant, Clear Tone
- · Separate Controls Stepped for Bass and Treble · Minimum Distortion

· Reduces Listening Fatigue Write JODA' for FREE Technical Bulletin and Detailed Distortion Analysis



BROOK ELECTRONICS. Inc. Dept RB-0,34 De Hart Place, Elizabeth, N.J.



foot main building at the Lincolnwood

Edward E. Strauss, project engineer, gave an illustrated talk on the Bell & Howell combat recording camera, followed by a demonstration by Stewart E. Plattner, microfilm products engineer, of automatic microfilm equipment.

A technicolor film of "Operations Crossroads," the Bikini tests, was shown with additional explanation by Lt. Col. Perry M. Thomas, Bell & Howell director of sales training, who was second in command of photographic activities for the Air Force observations at Bikini. The program con-cluded with an illustrated talk on atomic fission by Lt. Col. Thomas.

Some 200 members and guests, including a considerable number from the University of Illinois, attended the November 17th meeting of the De-catur Chapter. The principal speaker was Col. A. M. Shearer, Chief, Procurement and Distribution Division, Office of the Chief Signal Officer.

#### Fort Monmouth

The chapter held its first fall dinnermeeting on November 16th. The two hundred members attending heard K. E. Gould of Bell Laboratories, New York, discuss the subject of coaxial cables as applied to communications and television.

A varied musical and legerdemain show directed and supervised by Lt. V. T. Hall of the Special Services School, aided by the Fort Monmouth Glee Club, rounded out a festive evening. Among those present were Mai. Gen. F. H. Lanahan, Commanding General of Fort Monmouth; Maj. Gen. J. O. Mauborgne and Brig. Gen. Harry Reichelderfer, Harry B. Haines, prominent newspaper publisher of Paterson, N. J., was special guest of the evening. Col. J. D. O'Connell. chapter president, acted as toastmaster at the dinner. Lt. Col. W. R. Herrlein, vice-president, and Col. W. L. Seibert, board director, were in charge of arrangements.

# New York

The 1949 annual meeting of the New York Chapter took place on December 14th at the 71st Regiment Armory. Following dinner and business meeting, an extremely interesting demonstration of "Radar in Navigation" was presented by John E. Ganley, General Service Engineer of the New York Telephone Company.

# San Francisco

Henry E. Austin, district manager of RCA Communications, Inc., has been selected to head the chapter for the coming year. Plans are now under way for increased chapter activities.

# Southern California

New chapter officers were recently elected as follows: president-A. C Hohmann, Deputy Chief of Police of Los Angeles; vice-presidents: Loyd C. Sigmon of Station KMPC, Kenneth B. Lambert of Metro-Goldwyn-Mayer Pictures, and Col. S. W. Sheely; secretary-treasurer: R. F. Walz of Walkirt Co., Culver City.

The November meeting was devoted to a discussion of the military weather services by Col. T. R. Gillenwaters who was active in the AAF Weather Service during the war. The subject of the December meeting was "Sonar and Telemetering" presented by an official of Bendix Aviation.

# Chapter of the Year Contest

Figures on the annual chapter contest, which ends April 30th, show that Fort Monmouth, headed by Col. J. D. O'Connell, has forged into first place as a result of its very successful membership drive in November. The Chicago Chapter, with Oliver Read as its president, is running a close second because of its splendid meetings and other activities.

# New York University

Current officers of the NYU student chapter are as follows: president-William A. Bocchino; vice-presidents Gilbert Ben-Haroche and Robert D. Hawkins; secretary-treasurer-Robert E. Buckley.

### University of Alabama

The University of Alabama joined the roll of AFCA student chapters in November. The chapter was organized through the efforts of Lt. Col. R. A. Dutton, Asst. PMS&T, who reported that there has been considerable interest in the Association since its ROTC award at the university last spring. -30-

# USING OLD TV BOOSTERS

By JOHN R. DONNELLY, W3LVH

THERE are a lot of old television boosters on the market that can be put to good use by hams who have TVI. Most of these boosters have tunedgrid, tuned-plate, and make very good r. f. amplifiers.


I am using an old Maryland booster that tunes from Channel I to 6. With a new 1N34 crystal and a meter I can locate my harmonics on Channels 2 through 6. This gadget also indicates any r. f. that may be present in a. c.

This unit can be kept in operation at all times, to keep a check on harmonics that might develop.

A pair of phones can be used in place of the meter to monitor. I have my harmonic finder antenna located in the yard about 25 feet from the shack

As the circuit Fig. 1 indicates, this is an easy way to whip one of the tougher problems in ham operation.

Fig. 1. Diagram of booster conversion.

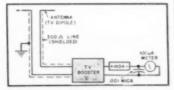

# RIDER BOOKS

# Get BETTER and BETTER and BETTER! And these 3 NEW Books are our REST!

They are in keeping with the high RIDER standards. They're "tops" in the field...containing more factual information, more practical data...more clearly presented than anywhere else. RUSH your order now...you can't afford to be without them!

# More Than Valuable...INDISPENSABLE! THE THEORY AND PRACTICE OF 30-1000 MC RECEIVING ANTENNAS

by Arnold B. Bailey

This book is a rare combination of theory and practice that: 1.... Clearly explains and feaches 2.....Can be used as a daily work reference An ovistanding book, the like of which has never before been written. And since the artisant has reverbed to the mathematics of antenna problems into graphs, there is no service to the mathematics of antenna problems into graphs, there are the put a good use by all. Reflexing world-wide knowledge of Johnson art, it clears and tables—it are to be put a good use by all. Reflexing world-wide knowledge of Johnson art, it clears are to be a seminated to the conformance of every type to Johnson art, it clears are to be a seminated to be a seminated to the conformance of every type for the conformance of every type of the understanding of the conformance of every type for the conformance of every type of the understanding of the conformance of every type for the conformance of every type of the understanding of the conformance of every type of the understanding of the theory to be a second to the conformance of every type of the conformance of every type of the conformance of the three types of the conformance of every type of the conformance of the three types of the conformance of the three types of the conformance of the three types of the conformance of the types of the types

To be released in March. Order your copy TODAY! 

# RADIO OPERATOR'S LICENSE Q AND A MANUAL

by Milton Kaufman

that book is a most complete and comprehensive meathers are subject and should grave as thought provided as a quitter of the control of the c 60s pages, 193 explanatory and active opera \$600

The New CATHODE-RAY

TUBE AT WORK

by RIDER et al

We pay Postage If You Remit With Order, Slight Postage Charge on C.O.D.'s.

theory of velocity as a grand should submitted the service of the first of the firs
COUPON! FAST DELIVERY! PUBLISHER, INC.

Please send me the following EIDER Books:	
Theory and Practice of 30-1000Mc Receiving Antennas	\$4.50
Cathode Ray Tube At Work	\$9.00
Radia Operator's License Q & A Manual	\$6.00
Tetal	\$
NAME	
ADDRESS	
CITYZONESTATE	

☐ Check Enclosed ☐ Maney-Order Enclosed ☐ Send C.O.D. ------------------

# At last—a built-in booster!



# ... brings 'em in out of the snow



FRINGE AREAS

now can enjoy excellent reception without cumbersome,

costly external boosters! Craftsmen Television alone gives you a built-in booster that literally brings a picture right out of the "snow"—gives a 10 db. video boost simply by shifting a knob! Unparalleled performance, and it will not interfere with audio reception.

HI-FIDELITY SOUND available through cothode-follower audio output. And RC-100 television—engineered from the mounting bolls up for big picture operation—is twice as sensitive as before! Automatic phase control of both vertical and harizontal synchronization guarantees perfect interlace. Keyed AGC, too, Will accommodate UHF channels.

COMPLETE THE PICTURE with Craftsmen high fidelity audio—RC-8 FM-AM tuner featuring automatic frequency control that entirely eliminates drift, and RC-2 high fidelity amplifier.



Write for information—or send 50¢ for instructions and schematics.

Dept. D, 1617 S. Michigan Ave., Chicago 16, III.

# Manufacturers' Literature

Readers are asked to write directly to the manufacturer for the literature, By mentioning RADIO & TELEVISION NEWS, the issue and page, and cerclosing the proper amount, when indicated, delay will be prevented.

# MANAGEMENT LITERATURE

A check list of publications covering seven management fields has been issued by American Management Association of 330 West 42nd Street, New York, New York.

This complete bibliography includes a listing of the Association's publications during the past 18 years on such management subjects as personnel and industrial relations, insurance, marketing, office management, production, finance, and packaging.

Entitled "Progress in 7 Fields of Management," this bibliography is available on request from Association headquarters.

# COMMUTATOR BOOKLET

Ideal Industries, Inc. of Sycamore, Illinois has prepared an elaborate 40-page booklet entitled "Commutator and Slip Ring Maintenance" which has been described as a handbook of procedures and methods.

The booklet is divided into four main sections dealing with "Trouble and How to Correct It," "Brushes," "General Maintenance Procedures," and a condensed listing and description of the company's maintenance products.

For details on how to secure a copy of this handy booklet write direct to the company at the above address.

# TRIAD TRANSFORMERS

Triad Transformer Manufacturing Company of 2254 Sepulveda Blvd., Los Angeles 64, California has issued a new catalogue covering its line of geophysical transformers.

Known as "Geoformers," these transformers are completely described, illustrated, and priced in this new 4page publication. In requesting copies ask for Catalogue CP-49.

# WALDOM CATALOGUE

A catalogue listing replacement cone assemblies for both postwar and prewar models has just been issued by Waldom Electronics, Inc., 911 North Larrabee Street, Chicago, Illinois.

It covers cone assemblies for every set from Admiral to Zenith. The information includes part number, set model number, o.d. of cone, and pertinent dimensions consisting of o.d. of speaker, i.d. of voice coil, depth of cone, type of spider, etc.

# RECTANGULAR TV BULB

Details on American Structural Products Company's new rectangular television bulb are given clearly and simply in the new 4-page booklet just released for video tube and set manufacturers.

Rotated photographs and dimensional drawings are shown on the back cover of the bulletin, copies of which may be obtained from the Sales Promotion Dept., American Structural Products Company, Toledo 1, Obio.

### PRECISION CATALOGUE

A new catalogue covering the company's complete line of steel office, factory, and shop equipment has just been issued by *Precision Equipment Co.*, 3708 N. Milwaukee Ave., Chicago 41. Illinois.

Of particular interest to the radio service technician and radio manufacturer are parts cabinets, storage cabinets, shelf and shop boxes, and various other units for storing radio parts inventories or replacement components.

Copies of this 12-page catalogue are free of charge.

# HERMETIC SEALS

A new 16-page catalogue on hermetic seals has been announced by Hermetic Seal Products Compuny of 37 South 6th Street, Newark 7, New Jersey.

The catalogue, covering both standard and custom designed hermetic seals, illustrates the company's exclusive multi-point plugs and multi-headers, high voltage terminals, and solutions to miniaturization, high altitude, and high ambient temperature problems.

Photographs are included for the different general kinds of seals, and engineering drawings give the details of specific alternative designs. Seals for various applications by manufacturers and users of relays, filters, transformers, condensers, etc., are also described and illustrated.

# CROSSOVER NETWORK DATA

Racon Electric Company, Inc. of 52
East 19th Street, New York 3, New
York has prepared a 4-page booklet
which presents complete, practical instructions and a wiring diagram for
the home-building of an economical,
professional type of 1000 cycle crossover network.

A full range of specific inductance, capacitance, and resistance values is given, plus complete coil winding information, to adapt the crossover network for use with cone speaker impedances of from 4 to 16 ohms. The steps for the proper installation of crossover networks, wide range twee-



# ORDER

# from ARROW!

# **BC-605 INTERPHONE**

nasily converted to an ideal infercom set for office—home—or factory. Criginal—New Like New \$4,95 3,95

All necessary parts and instructions to convert the above to AC operation with one remote station.

\$8.25 additional



# COMMAND (SCR 274 N)

DC 453	Used	New
BC-453	4.95	\$6.95
BC-455	7.95	2.95
BC-457 BC-458	5.95 5.95	7.95
BC-459 (or T22) 51-696 (or T19) 56C5 Transm 2.1-3MC	9.95 14.95 9.95	24.95
cC-450—3 Receiver Remote Control EC-442	.89	1.95
3 Receiver Rack	1.95	
Complete Command set as removed 3 receivers—2 transmitters—Relay		
boxes mounting racks plugs modulator and dynamotors crated.		

# Miscellaneous SPECIALS

	Used	New
BC 929 Scope		\$17.95
ID 6 APN 4 Scope, Excellent	29.50	******
ID S7 APQ 7 Scope	9.95	
ID 2 APS-SFP7 Assembly		6.95
R 7 APS 2 Receiver Indicator		79.50
R 78 APS-15 Receiver-Indicator		13.00
BC 1287 A Scope		
ASB 7 Indicator Scope	12.95	
ARB Receiver, 200 to 9000 KC		
SCR 522 Transceiver 100 to 150MG		75.00
BC 1206 Receiver, 200 to 400 KC		5.95
MN 26 C or Y Receiver		24.95
RA 10 DA Receives		24.95
T 85 APT 5 Transmitter	81.00	69.50
T 39 APQ 9 Transmitter	7.95	40.00
T 26 APT 2 Transmitter	8.95	
DC 452 T	4.25	
BC 457 Transmitter as in fair condition as they come, some with	3.	
some less tubes and Xtal	1.95	
BC 458 Transmitter as is fair cor		
dition - as they come, some with-		
some less tubes and Xtal		
R 89 Receiver chassis less tuber an	d	
side covers	1.95	-
RT 7 APN 1 Transceiver	7.95	9.95
APN 1 Complete		34.50
BD 71 6 Pos. Switchboard	9.95	12.95
EE 8 Field Phones	7.95	
BC 347 Interphone Amplifier		.95
I-70 Tuning Meter		.09
AM 61 Indicator Amplifier		9.50
SCR 625 Mine Detector		39.50
PE 237 Power Supply		12.95
BC 461 Veeder Root Counter	-	.59
BC 442 Less Condenser	1.49	1.95
BC 306 Antenna TU for BC 375		1.50
A 27 Phantom Antenna		.98
APS 13 UHF Antenna, Pair		.98
Manual for BC 312 & 342 J		1.00
Manual for SCR 269 G		2.50
FL 8 Filter		2.95
BC/939 Loading Unit for BC 610		35.00
I-97 Bian Motor	2.95	
I-97 Bias Meter RM 29 Remote Telephone Control	7.95	9.95
BC 602 Control Box	2.00	.98
BC 639 Receiver with MA 42		. 20
Rectifier	1	
RTA IB Transcoiver		
TA 2J24 Transmitter and MP 10G	Info	mation
Power Pack		prices
SCR 269 Compass Installation R S ARN 7 Compass Installation.		equest
MN 26 Compass Installation	1	-
I. L. S. Installation (R 89-BC 733).	1	
SCR 584 Components	1	

# **BC-604 TRANSMITTER** FM 20-28 MC

11 and 15 meters. Can be operated on 10 meter-10 channel push button crystal. With all tubes and meter but less dynamotor. Excellent Condition. \$12.95 \$12.95 14,95

T. SECTION OF THE PARTY OF THE	-
HS-23 Hi ImpNew	\$2.95
HS-33 Lo ImpNew	2.95
HS-30 Hi Imp New	1.50
Used	.79
T-17D Carbon MikeNew	2.75
T-24 Hi Imp. Carbon Mike New	1.19
T-30 Throat Mike	.98
T-45 (or Navy) Lip Mike New	.98
CD-307 Extension Cord for	
HeadsetsNew	.59
RS-38-Navy hand Mike Carbon	2.75

# MIKES-HEADSETS

BEAM INDICATORS	
1 82-5' New	\$4.95
Transmitter selsyn for above	2.45
both for	7.00
181-3' New	3.45
Transmitter Selsyn for above	2.45

HERMETICALLY	SEALED
CHOKES	

10 H.	100 M.A.	 89 c
59 H.	100 M.A.	 95c
3.7 H.	145 M.A.	 53c
10 H.	20 M.A.	39c

### PP 12A/APS-3 RECTIFIER POWER SUPPLY

110 VAC—800 to 2400 CPS input. Used to supply many voltages for AFS 3 equipment. Contains four VR105: Three SU4G; 2x2; 6AC7: 676-G; VR 150; 6X5GT-G condensers, choice, etc. Parts \$6.95 alone worth more than

# BC 620

27.8 1	Transmitte MC FM-	13 tui	bes M	etered.	Plate	e and
Filame	nt.					
PE 97 P	wer Supp	ply for	above			9.95 brator
type	comple	te				\$6.95
	less tube					
FT 250 M	ount for b	oth BC	620 an	d PE 9	7 New	\$1.50

# BC 223

Brand new Iransmitter with all three	
two tuning unit cases, spare tube	carrying case.
shock Mount and brace, but less tul	bes at new low
price of	\$19.95
Tuning units are available separately	at Ea \$2.50
Cases at	Ea95
PE 125 12-volt Vibrator Pack	New \$12.95
	11 and 8 95

# SURPRISE PACKAGE

20 lbs. Ass't radio parts. A \$25.00 value for only

# RECEIVER

Easily Converted for Use in Citizens Band
Crystel Controlled Local Ceculiator. Broad Band
Pass—20.7 MC 1F's. Complete with 7.6AJS, 1—
12SB7, 2—12SB7 1—28D7 relays, crystals. Used \$7.95 Schemetic furnished

# NEW CATALOG

histing many surplus values, write for your FREE copy TODAY. 

All shipments FOB Chicago 20%, Deposit required on all orders. Minimum order accepted—\$5.00 into residents, please odd regular so as tax to your remittace.

# TUBES Nationally Advertised BrandsAll Brand New

Type Nat Price	Type Net Price	Two Not Price
1A4P \$0.49	6K6G \$0.69	
1A6 .49	6L5G .49	38 50.29 39 44 .24
185 255 .49	6L7G .49	49 39
1822 1,95	6 B 7 TO	50
1 B) 26 2.96	SSFSGT 19	56 29
1829 .69	658GT .69	66 29 67 29
1B32-532A 2.96	6SF7 49	76 .29
106 49	65.17 69	77 39
1CTG 49	6T7G 59	211 Ve4L 39
1 D5GP 49	6U7G 39	260 B
1 D7G49	6Z1G 59	VT166 1.29
16449	6ZY5G 39	316A .39
1F5G	TC4 1203A .29	375B 39
1 H 4 G 39	7E5 1201 .59	7038 1.95
136G 49	10Y VT26A .19	706A98
136G 49 136GT 49	12A6 .39	714AV 5.95
	12A6GT39	7248 4.95
1PSGT 49	12A7 .39	
1V	12ASGT 39	836 96 837 1.95 841 39
2A3	12C8Y 39	637 1.95
2A6	12F5GT 39	841 39
ZA7	12146	
2C26A 19	1235GT .29	DE28 0.29
2V3G	1235GT .29 1237GT .39	954
2 X 2 878 .39		955
387 1291 .39	12Q7GT 39	967
3 D6 1299 .39	12566	1625
3FP7	IZSFSGT 39	1626
4AP10 .98	125F7 39	1629
58P1 1.96	12SH7 .29	1630
58P4 2.96	125 RT 29	1636 2.96
6CP1 2.96	125 R7GT _29	163669
	1223 .29	164269
5021 19.95	168	2050
5GP198	19 69	205159
5J23 7.95	7.522 3.96	719319
5T4	28 07	9002 39
5W4	20SPEC	9000 49
5Z4 59	(V167) .69	9006 29
6B6 69	30 .29	GL4AZ1 29
6C4 .29	32L7GT 59	Amperite
6 D 6 G 59	33	1071 .29
6F5GT .39	34	Jan CRP77 1.49
6146 .29		WE 331A .89
		MEL 36 .69
6.86		VR 150 39
6 JTGT 39	37	VR 105 69
WRITE F	OR QUANTITY	PRICES

CONDENSERS	Esch
2 mfd. 4000 VDC G.E.	\$2.95
4 for	10.00
2 mld, S000 VDC, G.E	. 3.95
3 for	10.00
1 mid 6000 VDC	1.98
28 mtd 15000 VDC	4.95
00025 mid 25000 VDC 4 mtd 1500 VDC	2.95
4 mid 1500 400	2.40
10 fc	2.49

# DVNAMOTORS

DM-28- Filter	e l		3	48	1	wi	11	i	14	04	ad		82	d	_	New	
DY-12- DM-36		R														e New	6.95
BD-77 PE-206																Naw	6.95
PE-101 PE-73	 															Now Now	2.75
DM 53 DM-32										U	ie	d	.9	is		(3 for New	

# **OUTPUT TRANSFORMER**

Hi-Fil used in Scott Manufactured Navy receiver Fully potted. Fri. 500C ohms; output secondary 600 ohms C.T.—Inverse feedback econdary CT-60 ohms. New

# CIRCLE ANTENNA

# CLEAR SHARP PICTURES ON ALL CHANNELS

COMPARE CIRCLE-X

No other antenna combines all the mechanical and electrical features engineered into the Circle-X.

The high gain of the Circle-X is equal to stacked arrays. It is made of light weight carrosion resistant aluminum allays that stand up in all atmospheric conditions.

When you use Circle-X you stock only one type of antenna for all jobs. It has one wire lead-in and weighs only  $2\,V_R$  lbs.

We urge you to compare Circle-X TV Antennas to any other TV antenna on the market.

Use Circle-X on your nest fough TV installation. It may save you a lot of "no profit" call backs.





DEALERS: Air Express or Parcel Post Special Delivery direct from factory to you through your jabber, if he cannot supply you with the Circle-X from his stock.

CIRCLE-X ANTENNA CORP.

# RADIO MINDED???

# **LEARN CODE NOW!!**

A complete code oscillator, plug in and use. AC or DC. Small compact chassis. Variable tone. Operates phones or small speaker. With tube and key. Guaranteed.....\$3.45



SURPLUS GEAR AND PARTS
W.E. OSCILLOSCOPE BC 412B New Crated. \$50.00
Radar Receiver—BC 404D—New Complete. 27.50

Navy UHF Test Receiver CPRAAJ
Navy UHF Test Transmitter CPRAAJ
Navy UHF Test Transmitter CPRAAJ
Dual Range Receiver. Tule lineary, 2—957:s—2—1D8:s.
Dual Range Transmitter 2-HTHRE's: Shipped complete
with Tube. Batteries, Antennas, Schematte, carrying
case. Each unit 1638-8. Shipping weight 33 lbs. New—
for the part—Complete

ARC-S-RC 454—Good condition with tubes
GO-8 Aircraft Transmitter—Yes—Complete
Spery Benthiseght—Yes—In took—Crated
Landing Indicating Meter No. 1205649—2 independent neverments—0-50 microamp.—0-201
microamps. Separate monaries—Yes—Used

persons movements—e-so revenants—e-cofeed by the second of the second

Dynamic Frence Special 1.0 Mfd., 1000 V. 4 for 1. Condenser Special 1.0 Mfd., 1000 V. 4 for 1. XIAI Diodes 1N 21 3 for 1. Midget 1F s-62 Kc.—Q of 20 3 for 1. Midget Variable Condensers APC 28-75 or 1000 Middle Variable Condenser Large worm gear drive such section 500 Mindle with padders

essed, Hammarland
Selenium Rectifier Special 0-18 V A.C. full wave
Iridge, 12 amp. continuous duty

FOB-NY Roted firms 10 days quantity disco

GREENWICH SALES CO.

59 Cortlandt St.

New York City 7

ters, and standard cone speakers are also described in detail.

Of particular interest to the sound technician and the music enthusiast, this booklet is free of charge on request.

### "HI-FI MUSIC GUIDE"

Of interest to both laymen and sound technicians is the new book "High-Fidelity Music Guide" written by David Randolph and distributed by Lafayette Radio of 100 Sixth Avenue, New York City.

This concise, 12-page booklet is written in thoroughly understandable form and contains pertinent data on the selection of proper equipment to reproduce fine music with true fidelity.

In addition, the guide presents parts assemblies, cabinet location data, a glossary of technical terms, a chart of the range of musical sounds, and a technical explanation of the requirements for high fidelity sound reproduction.

# EYELET CATALOGUE

The United Shoe Machinery Corporation of 140 Federal Street, Boston, Massachusetts is offering copies of its catalogue "Eyelets and Eyeleting Machines" to manufacturers and other processors.

This 18-page catalogue contains data on standardized eyelets, telescopic eyelets, canvas eyelets, grommets and washers, tag and calendar eyelets, fancy and special eyelets, and special metal products. In addition, the tools and machines for eyeleting are described in some detail.

Radio and electrical manufacturers are invited to secure their copies of this catalogue by writing to the company at the Boston address.

# RESCO CATALOGUE

The 1950 RESCO catalogue, designed to assist service technicians, dealers, and sound technicians, broadcasters, and industrial firms select radio and electronic equipment, is currently being distributed by Radio Electric Service Co. of 7th and Arch Street, Philadelphia.

This 128-page catalogue has been carefully compiled in order to simplify purchasing problems and serve as a buying guide. Listings include thousands of items needed in radio, television, and electronics.

Copies are free for the asking and may be secured either from the company's Philadelphia store or from any of its eight branch outlets.

# BROWNING EQUIPMENT

Browning Laboratories, Inc. of Winchester, Massachusetts has available a new 4-page flyer describing its line of radio and electronic equipment.

Included are photographs and descriptions of the company's frequency meters, oscillator grid dip meter, WWV standard frequency calibrator, a power supply and square wave

SNAP.
YOUR ANTENNA IS
ASSEMBLED
THE OAK RIDGE 6
FM and TV ANTENNAS

FEATURING THE AMAZING
SNAP-LOCK

\*\*Pat. Pending

\* Revolutionary four-second essembly.
Just snap it out and it's fully assembled.
Estremely rugged—1s inch aluminum elements.

\* Campletely pre-assembled—No loose hardware.

We manufacture a full line of quality FM and TV antennas, including Hi-La's, Conicals, In-lines, Vee's, Stacked Arrays.

\* Ask your local jabber for a demanstration, Inquiries invited.

OAK RIDGE ANTENNAS 239 East 127th Street, New York 35, N. Y. Manufacturing Division at Video Televisian, Inc.

WHITE FOR CATALOG M.

modulator, capacitance relay, signal system, oscillosynchroscope, oscillorecord camera, sweep calibrator, audio amplifier, frequency meter calibrator, two FM-AM tuners, and an FM tuner.

Prices and specifications are included in the bulletin.

# "LANCASTER" BOOKLET

Radio Corporation of America's television distributors are currently circulating a new booklet designed to assist dealers in merchandising the company's new "Lancaster Series" of 16inch television receivers.

This 16-page booklet, which is attractively presented in deep brown, russet and white, cites the advantages of the series' metal-coned 16-inch tubes and the principal features of the "Lancaster Series" instruments.

# MODERNIZING DATA

Modernization data is now available for owners of the earlier types of the Weston Model 798 Tubecheckers, according to information received from Weston Electrical Instrument Corporation, 614 Frelinghuysen Avenue, Newark 5, New Jersey.

All former types may be modified to include the latest tube calibration data. The conversion itself is not too difficult and can be easily made by the user with only simple tools. It is not necessary to return the checker to the factory.

The conversion is advisable for Weston Model 798 Types 3, 3A, 4, 4A, 5, 5A, 6 and 6A Tubecheckers.

# SPRAGUE CALCULATOR

A new capacitor code indicator, just introduced by the *Sprague Products Company*, is designed to facilitate deciphering of molded paper tubular capacitor color codings.

The new capacitor indicator consists of a pocket-size plastic device with retating dials printed in full and accurate colors. When flicked to the proper color bands, the dials instantly indicate capacitance, tolerance, and rated working voltage.

These handy new calculators are available either direct from Sprague Products Company, 51 Marshall Street, North Adams, Massachusetts or through the company's distributors. The units are 8.15 each.

# E-I CATALOGUE

Electrical Industries, Inc. of 44 Summer Avenue, Newark 4, New Jersey is offering a new folder which contains Bulletins 849, 850, and 851 covering sealed leads, multiple headers, and gasket type bushings.

Data and specifications are given on all of these units and in some instances detailed mechanical drawings accompany the descriptive material.

In requesting copies of this new folder ask for "Data & Specifications on E-I Multiple Headers and Sealed Leads."

# **CHELSEA** Presents ANOTHER FIRST!

FOR CUSTOM-BUILT INSTALLATIONS

# JUST PLUG IT IN-IT WORKS!

LIC. RCA CHASSIS FOR 121" OPERATION

with DUMONT

\$13995 PICTURE 1

Completely wired, factory engineered, lested and Guaranteed

SAME CHASSIS FOR 16"
OPERATION, complete with picture tube \$17495

A SET-

NOT A KIT

493 Plus \$1.80 Fed. Tex



# ... Still ANOTHER CHELSEA FIRST! FAMOUS IMPROVED 630-TYPE CHASSIS

WITH VOLTAGE DOUBLER

# For 9 OPERATION

Custom-made, completely wired, factory-engineered, tested and Guaranteed ... with IM-PROVED Automatic Gain Control and IMPROVED High Gain Front End.

FOR 15" & 16" OPERATION, with voltage doubler less CRT 157.95

FOR 1212" OPERATION, less CRT 155.75

Highly-sensitive no drift AM & FM Tuner \$31.50 ea. additional, plus \$1.80 Fed. Tax

# - BRAND NEW TV TUBES AT LOWEST PRICES -

10" CRT...\$19.50 | 12½" CRT..\$26.00 | 16" CRT...\$41.50 | 12" CRT... 20.00 | 15" CRT... 41.50 | 19" CRT... 89.50

# - AUTOMATIC RECORD CHANGERS -

Webster 256-1 Dual Speed 78 & 3313 RPM....\$28.44 incl. tax. Webster 356-1 Three-Speed 78, 45 & 3313 RPM. 29.70 incl. tax.

High and Low Frequency All-Channel Antenna from \$6.71 to \$471.00
WHY PAY MORE ELSEWHERE?

# Write Dept. O for latest literature and prices—and COMPARE!

Phone and mail orders filled on receipt of certified check or money order for \$25 as deposit . . . balance C.O.D., F.O.B., N. Y.

For free demonstrations, visit our street-level showroom.

The House of Bargains

# CHELSEA TELEVISION CENTER, INC.

187 Seventh Ave., New York 11, N. Y. Chelsea 3-4425-6-7

Prices subject to change without notice

# PHOTOFACT BOOKS HELP YOU # WAYS!

1. SAVE TIME 2. SAVE WORK

3. EARN MORE 4. LEARN MORE



# PHOTOFACT TELEVISION COURSE

The book bought and studied by thousands. Gives you a clear understanding of TV principles, operation and practice Complete coverage of all phases. 216 pages; profusely illustrated, studdly bound, 8½ x 11°.

Order TV-1.

Only \$3.00

#### TELEVISION ANTENNAS

All you need to know about TV antennas-describes all types, tells you how to select, how to install, how to solve troubles. Soves time, helps you earn more. 166 puges, illustrated, handy packet size.

Only \$1.25

# THE RECORDING & REPRODUCTION OF SOUND

A complete, authoritative treatment of the entire subject, written by Oliver Read, editor of Radio News Covers all phases of recording and amplification 364 pages 6 x 9", cloth binding Order RE-1" Only \$5.00



# 1948 RECORD CHANGER MANUAL

Covers 45 models made in 1948, including LP and dual speed changers, plus leading wire recorders. Entirely original data based on actual analysis of the equipment. Over 400 pages, de luxe bound, 8½ x 11". Only \$6.75 Order CM-2.

# AUTO RADIO MANUAL

Complete PHOTOFACT Service data on more than 100 past-war auto redia models. Complete, occurate, uniform information Mokes auto radio servicing easier and more profitable. Over 350 pages. Sturdy binding, 812 x 11.

Order AR-1.

# NEW! DIAL CORD STRINGING GUIDE

New Volume 2, covering receivers produced from 1947 through 1949. The only book that shows you the one right way to string a diel cord in thousands of receivers. Handy pocket size.

Only \$1.00

# HOWARD W. SAMS & CO., INC.

DTAG-1 DRA-1 DC-2

Address ...... Zone State

# What's New in Radio

(Continued from page 80)

ments. Each kit contains 11 universal parts. These are combined with a selection of shaft ends and base elements, which are sold separately, to provide maximum coverage of con-



centric dual replacement in home and auto radios as well as television sets.

The base elements, supplied in conjunction with the kits, are complete with no loose parts. The blue molded base has element, collector ring, and terminals installed. Complete step-bystep instructions are included with each kit.

# OUTPUT ADAPTOR

A balanced output adaptor has been developed by the General Electric Company, Syracuse, N. Y., for use with its Model ST-4A sweep generator. The sweep generator has a singleended output, but with the addition of the new adaptor, balanced output is available. The adaptor, Type ST-8A, has been designed to give flat and balanced output when working into a 300 ohm resistive load.

The vernier output control of the sweep generator, normally incorporated in the output cable, is incorporated in the adaptor when using balanced output.

### ORE DETECTOR

Tracerlab Inc. of 130 High Street, Boston 10, Massachusetts is now marketing a professional ore detector, designed for rugged field use in prospecting for all types of radioactive ores, such as uranium, thorium, radium, etc. It is said to be entirely unaffected by humidity or moisture and will even



operate after having been submerged in over ten feet of water, according to the company.

When radiation enters the small

Rensselaer Polytechnic Institute has announced that two members of the teaching staff at the Troy. New York institution have developed an entirely new, all-electronic color television system. Stations transmit color signals which can be picked up by presentlype black and white sets and receivers designed to receive color. An adaptation of the device can be attached to motion picture cameras to permit color pictures to be taken with black and white film. In front of their equipment, used in research, are the scientists. Dr. Victor A. Babits (left) and Frank Hicks. [r.



# EQUIPMENT SALE

RS9/ARN5 Receiver
APN1 Transceiver
APN1 Stransceiver

# S 5.95 5. 5.95 5. 6.95 S FICE ALS OF THE MONTH

Sigma Sens.	Relay SPDT	\$1.69
	Supply Kit	
	TU-25	
_	3" Scope Shield	1.49

# TUBES!! BRAND NEW! STANDARD BRANDS! NO SECONDS! COMPARE! TUBES!!

IUDES DRANG	MEM: 21	ANDAKD	DKWIADZ	INO SECONDS:	COMPARE:	ODES.
0A3/VR75 \$0.89   3D21A \$1.29	371A \$8.69	574 \$0.39	1 G32 . \$4.95	11:7G . \$1.15 6AO6	\$6.59 656\$0.69	1458. \$0.79
0B3/VR9065 3DP1 1.75	3718 69	876 29	FGISTA 3.69	1714G 55 6AR5	.52 6V6CT 57	14117 59
00 3/VR105 .75 31 20 8.97	388A 1.49	878 1.98	FG95 17.95	1H5GT 54 6AT6		143787
0D3/VR150 .48 3FP7 1.75	393A 3.69	NN4 1.34	FG105 9.78	1H6GT 87 6A16		14N7 88
1821 2.87 3GP1 6.75 1822 2.87 4-65A 14.49	3.69 3.69	883 1.54	FG172 13.95 F7210 13.95	20.00		1407 58
1922 2.87 4-65A 14.49 1923 8.75 4-125A 27.48	417A 6.95	902P1 3.69 905 2.95	FT210 13.95 GL146 9.95		AM 5 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2 2	
1824 4.69 4-250A 37.45	450TH 17.95	905 2.95 918 E.49	GL451 97	11.10 90 010	60 66 761 98	245 49
11926 3.95 4AP10 4.75	450TL 44.50	919 1.95			.69 6ZY5G .59	251.6GT .58
	527 5.95	923 79	G1.697 69.50		58 7A4 XXL 49	2525 44
11129 3.49 41120 2.95		997 1.25	HY115 .25	11.C679 618106	.52 TAG .59	25Z6GT43
11032 2.49 0.035 19.38	575A 12.69	93085	HY615 .25	1LD579 6BF6	57 757 58	26
111.10 4.49 41.27 13.95	0.1141 3.75	1931 A 2.49	HYE114833	11.5 69 6BG6G	1.47 7AG7 72	27 42
13011 40 14714 1.05	703A 2.49		KC4 49.50 KD610 9.75	17.114	48 7915 6.9	2819735
IN21A 89 5BP1 1.89	TORKER AR ME		MI.100 49.50	1 1 NOT AND AND ADDRESS.	This 6c	30
IN21B 89 5BP4 2.39	706FY 47.50	957 24		INSGT 59 60%	47 7117 89	32 88
1N23 79 5CP1 1.69	70715 18.95	958A 24	MIL501 69.50		.57 7416 34	32L7GT 89
1N23A 79 5CP7 9.95	708A 3.95	959	M11.702 89.50	1Q5GT 67 6C%G	69 71.5 48	
IN23B 1.95 5C 27/227A 2.69	710A/8011. 85	99124	REL21 1.59	1114 59 6116	. 44 717 50	.54
1N27 79 and 1 24.75	713A	1603 2.85	REL36 .59		79 713 67	35 51
1N34 79 5FP7 1.38	714AY 3.69	161197	JUK21 4.85	184	100	35A5 48
24.95	715C 19.98	1011	RK25 4.19 RK33 27	1774	87 717 89	55415 50
2021 27 5112 9.98	717A 59	1616	RK34 27	TogT 69 SPECT	57 7117 50	3316 53
2(22/7193 17 5314 24.95	7214 2.69	1619 17	RK59 1.98		69 757 89	31.15 4 89
2C26A .28 5J29 12.95	723A/H 7.75	1624 89	R 600 .49	1V	87 71.7 69	49
2C34 .27 5J30 39.50	724A/H. 2.95	1625	RK65 . 24.50	2A3	.69 TNT67	11.23
2C40 3.49 5LP1 13.75	725A 6.95	1626 27	RK7269	2A4G 1.67 6516	39 7:37 59	1574
2C43 8.75 5NP1 1.98 2C44 59 6A86 4.95	726A 4.95 726B 22.95	1629 24	RK73	2A5 69 6:16GT	87 117 69	1107.5
2046 6.95 6021 19.69	720C 49.50	1600	RX120 7.95	and the second second	19 7117 79	
2C51 5.95 61/4 5.59	730A 9.95	1632 69	NS30 89	2V NG .69 6.36CT	20 7.57 29	3- 17
2D21 89 6J4 4.69	730TL 47.50	1633 79	TZ40 2.95	2X2 37 617	67 774 47	30 16 27
21:22 1 19 7BP7 4.49	NIII 1.49	1636 3.69	V701) 6.95		65 724 57	11
21:26 3.39 9GP7 9.98	S01A 29	1638	VH78 29	3A4 .34 GEST	79 124 57	4249
2J21A 7.95 9JP1 6.95	802 4.19	183179	VT127A 2.19	COLUMN TO THE PARTY OF THE PART		4349
2122 7.45 9LP1 19.98 2126 7.95 9LP7 2.25	503 3.49	2050 89	VT158. 9.78	3117/1291 1.59 6167	49 12A7 89 79 12ANOT 49	45 82
2127 12.95 103374 19.69		30.14	W146s 6.95		70 12ANDT 80	452357
2351 8.95 10Y25	807 1.10	8005 4.75	WL530 14.95	3D6-1299 29 6L5GT	1 05 12ATH 44	10 67
2332 12.75 12DP7 14.95	808 1.25	8011 2.75	WL531 7.95		99 12AT7 79	47 69
2J31 18.95 12GP7 12.75	809 2.78	80124 1.39	WIA32 1.98	3Q5GT 67 SLOGA	88 12AUB	49 88
2334 18.95 12HP7 13.95	810 7.95	8013A 1.39	W1.538 3.36	384	79 IZAU7 67	54) I.39
2.137 12.95 15E 1.19	811 2.10	S014A 22.50	W1.578	3V4		10.55
2138 11.95 15R 59 2139 29.50 23104 39	812 2.49 812H 6.98	5016 1.15	W1.616 87.80	5R4GY 1.09 6N7		MOTO
2.140 49.80 30 spec 17	812H 6.98 813 6.85	8020 97	W1.619 18 95 0A2 1.29	23 24 2 4 2 2 2 2	AND 1777 24	SOLEGT S2
2346 39.50 45 spec 26	814 2.49	9001 37	0A4G 89	E31463 600 00000	THE ADDRESS OF THE	50 87
2348 12.95 75TL 3.89	815 1.35	0002 29	0112 1.67		77 12110 37	36
2J49 22.56 100R97	21097	9003	02.6	5X4G 57 68A7	. 44 12J5GT 34	57 45
2J50 22.50 100TH 10.87	K26 39	900425	01A 39		.59 12J7GT	5449
2J53 14.95 100TS 2.25 2J54 22.50 211 42	\$28 12.95 \$29H 7.45	9005 ,89	18344			500
2355 69 50 2170 9.98	830B 7.45	CSB/5C30 6.95	1A4 1.09			701.7
2.161 34.50 24013 2.49	8324 4.89				59 12SA7 57	65
2.162 34.50 2490 1.79	533.4 34.45	COLUMN 3 95		6A4LA 1.09 68117	37 12807	24
2K25 18.75 250R 7.45	536A 97	C100D 98	IATGT 67	6A679 (1837)	47 12885 89	77 43
2K28 14.95 250TH 18.95	837 1.69	CK507AX 1.98		6A7 69 68K7G7		17444
3AP1 4.59 250TL 18.75	535 2.45	1 K 1005		6AN		80
31922 2.49 274A 5.50 31924 1.59 274B 3.49	841 35	CK1006		6AB7		×1 1.25
3R25 4.87 294A 2.95	845 3.95	CK1090 2.95	1B5/258 89	6AD7G 1.69 6807	54 12837 47 45 128K7 57	75
3B26 1.79 304TH 3.75	851 13.95	F123A 12.75		GAFGG .79 GSE7GT	52 1281.7 59	871 69
3027 1.95 304TL 1.39	8609.95	F125A 14.95		6AG5 69 6887	49 125N7 SJ	84 674 56
3BP1 2.49 305A 24.95	801 9.85	1127A 16.50		6AG7 98 6ST7	72 12807	55 69
3C23 2.47 307A 3,75	804 39	1128A 75.00	1107G 89	6AH6 . 1.29 CHL7GT		89Y 38
3C24/24G37 316A25	.865	1000 22.50		6AJ5	.79 122369	1171.7/M7. 1.19
3C30 34 327A 2.75 3C31/C1B 1.95 350A 1.98	866A 1.05			6AK5 85 6176	89 14.41	11787 1.19
3C45 12.95 350B 1.89		FG17 2.85			68 14A7	117P7 1.19
3CP1 98 365A8 2.98	872A 1.19	FG127A 8.95			49 1417 69	11726 69
K. ***	2.57	0.40	2.500.2	and the second	.41 111 .61	11110

	OIL	COND	ENSER	5-0	C R	ATINGS	
Sx.I	mid	600V	\$ .49	15	mfd	2000v	\$4.95
25	mfd	600v	.37	.1	mfd	2500v	1.45
20	mid	8000	.37	.25	mid	2.500v	1.77
1	mfd	600v	.37	.5	min	2500v	1.98
2	mild	500v	.3.7	2	mfd	2500 v	2.89
282	mfd	600v	.77	.01	mist	3000v	1,49
4	gnfd	600v	.57	.05	ant/d	3000v	1.75
15	mid	GOOV	.97	.1	mfd	30009	1 95
%	mfd	500v	1.07	.25	rmfd.	3000r	2.65
10	mfd	600v	1.27	-5	mfd	3000v	2.75
3x.1	mid	1000v	.59	1	res ful	30008	2.98
.25	m fd	10000	.47	2	mid	30000	3.47
.5	mfd	10000x	.57	4	mfd	20008	4.45
1	mfd	1000v	.67	12	DO 5-3	3000v	6.97
2	mfd	1000V	.27	1	mid	3600v	3.45
4	mid	10008	1.37	.5	mfri	4000V	3.75
N	mili	10008	1.97	.25	mfri	40000	2.98
849	mfd	1000v	2.07	1	rm fig	40000v	4.25
15	mfd	10000	2.47	2	sofd.	4000v	4.85
20	mfd	1000v	3.27	3	mfd	4000V	5.45
.5	mfd	1500v	.77	.1	mfd	5000V	2.75
1	mfd	1500v	.97	.25	mfd	50000	3.49
2	mfd	1500v	1.17	1	mfd	5000 v	4.98
4	smfk1	1500v	1.77	1	mifd	7000v	2.97
24	mild	1500v	5.47	1	min	7000v	5.97
1	mfd	2000v	1.07	.01	my fig.	7500v	2.45
.25	mfd	2000v	1.17	.02	mfd	75000	2.75
.5	mfd	2000v	1.27	.03	mfill.	7500v	2.97
1	mfd	2000v	1.07	.05	msfr5	7500v	2.49
2	mid	2000v	1.87	1	mfd	7500v	6.95
4	mild	2000v	3.77	2x.1	per fiel	7500v	7.95
8	mfri	2000v	3.97	0.2	mild	12000v	9.97

		AL	L RATII	NGS D	OC.		
2x3500 2500 3000 650 1000	mfd mfd mfd mfd mfd	25v 3v 25v 80v 15v	\$3.47 .35 2.45 1.29 .98	200 100 4000 4000 2350 10000	mfd mfd mfd mfd mfd mfd	35v 50v 18v 30v 24v 25v	\$ .57 4.5 1.95 3.25 2.25 4.55

# TRANSFORMERS—115 V. 60 Cy. HI-VOLTAGE INSULATION

6350v @ .025 arms, \$12.95, 2500v @ 15 ma,	\$3.95
25000 or 4 ma 6 ly or 1A 2 key or 2A	5.97
700-0-700 & 300 ma. 1600v & 4 ma. 700v CT & 150 ma; 6.3v @ 9A	2.95
1600v @ 4 ms; 700v CT @ 150 ms; 6.3v @ 9A	4.92
1500v @ 7 ma; 2.5v @ 1.75A	4.40
525-0-525v @ 60 ma; 925v @ 10 ma; 2x5v @ 3A;	
6.3v m 3.6A 6.3v m 2A 6.3v m 1A	6.92
500-0-500v # 175 ma 500-0-500v # 25 ma; 262-0-262v # 55 ma; 6.3v	4.95
500-0-500y or 25 ma; 262-0-262y or 55 ma; 6 3y	-
@ 1A: 2x5v @ 2A	4.45
430-0-130V @ 350 mg: 6.3v @ 6A: 5V @ 6A	4.97
425-0-425v @ 75 ma; 5v @ 3A; 6.3v @ 1.5A	3.98
400-315-0-100-315v or 200 mg; 2.5v or 2A; 5v	
6F 3A: 2x6.3v 6F 9A	5.95
@ 3A; 2x6.3v @ DA 385-0-385-550v @ 200 ma; 2.5v @ 2A; 5v @	
3A: 3x6.3v @ 6A-pri 110/220	6.25
385-0-385v @ 70 ma: 2.5v @ 10A: 5v @ 6A: 5v	
IF 3A	4.95
340-0-340V @ 300 ma: 1540V @ 5 ma	4.91
300-0-300 to 100 may 5y to 7A 12 key db 2A	
12 kg v 80 3 A	3. 37
12 kg v m 3A 300-0-300v m 65 ma 2x5v @ 2A 6.3v @ 2kgA;	
	3.4
255-0-255v @ 240 ma; 325-0-325v @ 12 ma	4.91
120-0-120v @ 50 ma	91
80-0-80v @ 225 ma; 5v @ 2A; 5v @ 4 ma.	3.45
36v @ 15A. \$9.95 24v @ 10A.	4.4
18V 07 15A 8.95 13.5V CT 08 3.25A	2.4
12.6v CT @ 10A; 11v CT @ 6.5A	6.9
12v CT @ 10A 2x9v CT @ 10A	7.45
3x10.3v CT @ 7A. \$6.95 Sv CT @ 1A	9
6 3v @ 12A; 6.3v @ 2A; 115v @ .1 amps	3.4
6.3v @ 10A; 6.3v @ .6A.	2.4
6 3v CT @ 3.5A 2x2.5v @ 3A	2.9
6.5v (6) 8A 6.5v (6) 5A 5v (6) 3A 2.5v (6) 1.75A	4. 6
6.3v @ 1A: 2.5v @ 2A \$2.25 6.3v @ 1A	.7
6.3v @ 1A, 2.5v @ 2A \$2.25	1.7
5v @ 3A, 2.5v @ 2A 2.97 2.5 @ 10A	3.9
	-

SEL	ENIUM	RE	CTI	FIERS
-88	145	W-0	A	

	Full	Wave	Bridge	Type	
INPU	T		01	UTPUT	
	AC.	up to	12v TK:	15 Amp.	\$1.47
up to 18v	AC	up to	12v DC	I Amp.	1.97
up to 18v	A.C.	up-to	12v DC	5 Amp.	5.27
up to 18v	AC	up-to	12v DC	10 Amp	
up to 18v	AC	up to	12v DC	15 Amp.	11.57
up to 18v	AC	mp to	12v DC	30 Amp.	22.87
up to 36v	AC	up to	28v DC	1 Amp.	
up to 36v		up to	28v DC	5.Amp.	8,57
up to 36v	AC	up to	28v DC	10 Amp.	14.57
up to 36v		up to	28v DC	15 Amp.	22.27
up to 115v		up to	100v DC	25 Amp.	
up to 115v			100y DC	.6 Amp.	
up to 11av			100v DC	5 Amp.	22.57
up to 115v	AC	up to	100v DC	3 Amp.	17.97

# FILTER CHOKES

HI-VOLT	AGE	INSULATION							
065 by # 2.5A \$	3.95	I by 60 800 ma \$	14.97						
15 by # 70 mg.	6.17	10 by # 250 ms.	2.47						
12 by # 150 ma	5.47	10 by m 200 ma.	1.98						
20 by # 60 ma	1.87	10/20 by # 85 ma.	1.57						
.05 by se 15 amps.	7.97	15 hs of 125 ma.	2.47						
.1 by at a amps	6.97	15 hy & 100 ma.	0.87						
4 by st coo ma	5.97	3 by # 50 ms	.27						
200 hy # 10 mg	8.47	30 by dual or 30 ms.	1.67						
500 by @ 1 ma	3.17	3/30 hy # 250 ma.	8.67						
325 by # 5 ma.		2 by 60 170 ma.	1.49						
3.5/14 by # +0/	6.75	10, 50 hy 61 50/	6.95						
ACMT ROSS SWITTERS		Aller man - wimerings							

# PHONE DIGBY 9-0347

PRICES SUBJECT TO
CHANGE WITHOUT NOTICE
All Marchandise Quaranteed
F. Q. B. New York City, Minimum
Order \$5.00
20% Deposit Required

# for superb HIGH-FIDELITY reproduction MASCO high frequency tweeter unit HFT-100

EXCLUSIVE NEW TWEETER THAT GIVES living hasence HFT-100 Specifications

Frequency range ... 900 to

8 watts

51/4 in.

2% in.

70 degrees

beyond 15,000 cycles

Dispersion, horizontal Capacity

Height, less screen

Impedance

Depth

Power Handling

and vertical Width, less screen with NO distortion

NO cumbersome horns

NO crossover network necessary

NO additional space required

NO narrow dispersion angles

NO need for separating sound sources

Wide range reproduction from the lowest response of the cone speaker to better than 15,000 cycles is obtained by using the HFT-100 Tweeter.

The tweeter is mounted within the cone speaker and connected in series with it.

No filter network is necessary. The HFT-100 has a built-in mechanical filter.


HFT-100 with attached mounting screen for 12" cone speaker..... \$24.50 List Price HFT-100 with attached mounting screen for 15" cone speaker ..... \$26.50 List Price Write to factory for Catalog RN:

MARK SIMPSON MANUFACTURING CO., Inc. 32-28 49th Street, Long Island City 3, N.Y.

SOUND SYSTEMS and ACCESSORIES

MUSIC AMPLIFIER

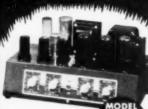the undisputed "Best" or your money refunded



Performance limited only by your input and output components. For any magnetic or crystal pickup, radio. or microphone. Multiple impedance to match any speaker.

Also available in models 50 PG and 200 PG.
Write for literature and name of your neares jabber.

PRECISION ELECTRONICS, I 641-643 MILWAUKEE AVENUE CHICAGO 23, ILLINOIS

SPECIALISTS IN SOUND

BETTER THAN EVER the Model 630-TKTV Kit



Circuit is the exact duplicate of the RCA 630TS, PLUS Voltage Doubler and Keyed Automatic Gain Control. All components mounted, ready to wire over a weekend.

Complete, loss Kinescope \$17950

TECH-MASTER PRODUCTS CO

Geiger tube, which is contained in the probe, a clicking noise can be heard in the earphones, which are supplied with the instrument. A sharp rise in the number of clicks that are heard each minute above the normal "background," indicates the presence of radioactive substances. The tube has a low background rate of only about ten counts per minute at sea level.

The probe, which is mounted at the end of a flexible 30-inch cable, is sufficiently small to permit the exploration of crevices and small bore holes.

A copy of the booklet "Prospecting for Uranium" published by the U.S. Atomic Energy Commission and the S. Geological Survey is supplied with each Model SU-7 ore detector.

#### REGULATED D.C. SUPPLY

Designed for laboratory applica-tions, the new Model EA-50A regulated d.c. power supply, introduced by Chatham Electronics Corp. of Washington Street, Newark 2, New



Jersey, provides continuously variable output voltages from 0 to 500 volts.

Ripple is less than 10 millivolts. In addition, the unit provides 6.3 volts non-regulated a.c. output at 10 amps. and gives 1 per-cent regulation between 30 and 500 volts and 2 per-cent regulation between 10 and 30 volts.

The unit is available in either rack or cabinet mounting.

# SILVER CELL BATTERY

Yardney Electric Corporation of 105 Chambers Street, New York 7, New York has developed and tested a new silver cell storage battery which is said to open new horizons to engineers working in the field of batterypowered electrical equipment.

The new "Silvercel" battery is only 1/3 to 1/5 the weight of common bat-



teries now in use. In bulk, the volume of the battery is only 1/2 to 1/4 that required of other batteries. The am-pere-hour efficiency of the "Silvercel" is said to approach 100 per-cent and the energy efficiency is 85 per-cent.

The unit is said to exhibit great re-

sistance to mechanical shock since there are no plates or separators to be damaged, and shock resistance is limited only by the strength of the case, which can be selected to meet any of a variety of requirements.

Now available are five types of "Silvercel" batteries ranging from 0.5 to 40 ampere-hour capacity. Several other large capacity batteries are now in the development stage.

### NEW TRIPLETT V.O.M.

A new laboratory-type volt-ohm-milliammeter, the Model 630-A, has recently been added to the line of test




instruments manufactured by The Triplett Electrical Instrument Co. of Bluffton, Ohio.

Featuring mirrored, hand-drawn scales and greater accuracy made possible through the use of special 1/2% resistors, the new v.o.m. has six d.c. voltage ranges from 0 to 6000 at 20,000 ohms per volt, six a.c. voltage ranges from 0 to 6000 at 5000 ohms per volt, five d.c. current ranges, decibels, output, and resistance ranges from 0 to 100 megohms.

The instrument is housed in a molded base integral with the switch. It provides direct connections without cabling. One switch permits the selection of both circuit and range. There is a precalibrated rectifier unit.



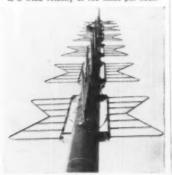Engineer makes final tests atop world's largest heavy-duty low-band television an-tenna installed by station KRLD-TV, Dallas. Built by General Electric at Syracuse, the antenna weighs 10.000 pounds and is 99 feet long. It is designed for 50-pound-persquare-foot wind loading, corresponding to a wind velocity of 150 miles per hour.



# NOW . . . IN KIT FORM! NARROW-BAND, PHASE OR

FREQUENCY MODULATION UNITS

ubes, fabricated chassis, all necessary parts and implies assembly, resting and wiring instructions, sure-fire setupe! M-SR Frequency modulated kit only \$8.45 M-SR Phase modulated kit only \$8.45

# THREE NEW NOISE-LIMITER

THREE NEW NOISE-LIMITER

At lone-last, a completely adjustable noise in
suitable for use on the earphone connection
BC-27-0X and other surplus reviews. (III
EC-45-8, BC-545, BC-548, BC-548, BC-5412,
10se and negative peak limiting, continuously as
able from strong string bester to first cutoff, if
effective, double-doke error to first cutoff, if
effective and in the cutoff of the cuto on from receive particul maintain all signals to a plote tube, all parts, or and wiring instructions.

GR for 6V fit complete \$4.20

"CLIPPER" KIT above except high impedance for inter-i speech amplifiers, (lipping level fully ad-permit higher average percentage without

SP-6E (6V ML) complete \$4.20

# Power Supply for Any 274-N Receiver



# CONDENSER TESTER

socket and bezel. Brilled metal rabinet. Com-instructions and diagrams included with each Only \$4.85.



# HEAVY-DUTY FILTER CHOKE

A hermetically scaled unit, con-tively rated at 1s henries 68 2m that hum bucking tap. Steel of CNLX \$1.98 each.

# HOT SPECIAL ON OIL CAPACITORS

mfd., 1000V, oil filled Made by erroux. Hert case grey fluids, com-bles with mounting brackets. for \$3.95 mfd., 600V, oil-filled. Round case, pright single-hole mounting. With all hardware. \$50 es.; 5 for \$3.75



# LOOK! NO HANDS!

# CHECK THESE C-R TUBE VALUES!

3" C-R tube, Green, med, persist

#### YOUR FONE-PATCH PROBLEM IS SOLVED!

special purchase of 1



exceptionally low for they're hard to

#### HI-LEVEL NEGATIVE PEAK CLIPPER! 836 RECTIFIER TUBES

63.6 RECURENCE of the works are reifler tube for "dispers" on "bash" toubles. Same also used to replace 86% in normal, higher settler applications of the present of the property of the pr

Rectifier Applications.

110V. 60cs. AC. Sec. 2.5V is 10A, 10.000V



#### RCA 8012 VHF TRIODE

TANTALUM plate and grid 35 watte surport, 60 watte plate diss. Use as one, or am, at full raining up to 500 mcl C.T. 6.3V filtered reduces fil lead industance. ALL SHEAND NEW! Normally selfs for \$14.50, large quantity purchase permits our extremely low prices of \$1.50 each, 4 to \$5.50.

#### PROTECT COSTLY TUBES AND EQUIP-MENT AGAINST OVERLOAD!



SCOOP! 6L6 METAL . 90c ea.

.90cea. Four for \$3.40.
.79cea. Faur for \$1.80.
. STANDARD BRANDS 6L6 GLASS . . 79c ea.

# HANDSET HANGER

Approximately sill makes and models, thirdings, W.-E. American etc.) Results for the sill service of the s

TS-10 Sound Powered Handsets Grand New! \$16.95 per RM JA TELEPHONE Brand New \$12.95 ca.

### FL-8 FILTERS AND "FL-8 FILTER FACTS" BOOKLET

FACTS" BOOKLET

A sure bet for better reception, an FL.S. The
low down on the filter is given in "Filter Facts"
booklet See past issues RADIO NEWS for
more camplete dope on this fine during
FL.S Fitter and booklet -combo ofter . \$2.98

Booklet only. (Postpaid in U. S.) .50

INCREASED RECEIVER



# OUTPUT TO HEADPHONES!

FL+ (liter to greatly improved results. Hermetically scaled, plated brass case, good LF response limit ratio appress to 1. An excitent spine at Sperial in ratio for 75A receivers. 95c ca

# **BC-221 FREQUENCY METERS**

Two models available. Metal case, used in good condition. With original crystal and calibration charts.

8C-221 AJ, Brand new with modulation, this POWER SUPPLY KIT FOR BC-221

Contains all parts needed for BC 221 power supply including chassis and diagram only \$5.85

SPECIAL PURCHASE ... BC-624 RECEIVER A few of these well-known UHF receivers from the SCR-522. Complete with tubes. Good. electrical and mechanical condition. \$14.95 cs.

OFFENBACH & REIMUS CO.

373 ELLIS ST. SAN FRANCISCO, CALIF.

# WHY PAY MORE! Save on Surplus Buys

This is the New ALVARADIO! We've reorganized and are before then ever able to serve you and give you bigger and before surplus values. Look to ALVARADIO! NOTE NEW ADDRESS.

### SCR-522 WITH RA-62C

Save \$27.40 on Complete Unit

Everyone is clamoring for this unit Consists of the following units: Traismitter Receiver with plus: Is tubes, voice modulated, output 8-9 watts 18 tubes, voice with the property of the

# BUYING COMPLETE UNIT \$219.95

### SEPARATE PARTS PRICE LIST:

SCR-522 Xmitter Revi	r.														\$49.95
PE-94 Dynamotor															5.95
RA-62C Pwr. Supply		*	*	*	*	۰		*		. ,			,		1.50
SCR-522 Antenna															1.50
														1	\$247.35

# \_\_\_\_

#### BC-929 INDICATOR SCOPE derful deal for cheap test scope. Contain

Wonderful deal for cheap test scope Contains 8 tubes: 1—3BPL, 2—68N7, 2—616, 1—6G6, 1—2X2 and tX3. Full instructions for use with light bulb. Excellent condition \$14.95

# APS-13 TRANSCEIVER

Tailend Charlle-kept the Japs off our tail Now yours at a fraction of original govt evot 5 stages of 30 Mes. IF 16AGS, 2 stages of video single AAGS) which feed into 2-D21 for relay warning. 1646 in transmitter-receiver Just the thing for extreme hand, 420 me han band, or TV, or use for short range radar detection. Worderful possibility for marker and stant alcredit radar Tubes with the control of the second position of the conposition of the control of the control of the control of you. Good condition.

#### BC-906 FREQUENCY METER

A real laboratory instrument at a fraction of original cost. Can be modified for many other uses. Absorption-type. Range. 150-225. MC. Power requirements. 2 batteries. 1.5V and 65V. Uses precision friction-type verifier dial for frequency variation. Bank wirthkelmish metal earlier with door. Complete with tubes and fremency charlet NEW.

# APN-1 ALTIMETER TRANSCEIVER

Here's a real buy! 418-462 MC FM Can be modified for citizens band use. You get \$6.95

# COMMAND RECEIVERS

Used, Good Condition Complete with Tubes 1 190-350 KC (Q-Ser)

# Hattest Value on the Market COMMAND XMITTERS—ARC-5 & ATA

Complete with Tubes & Xtals 1C-450 7-9.1 Mes (Excell cond.) \$12.95 1C-477 4-5.2 Mes (Excell cond.) \$.95 1C-450 3-7 Mes (Excell cond.) \$.95

# BC-221 FREQUENCY METER

From the second state of the second state of the second state of the second sec

DELCO-REMY MARINE CENERATORS, Model 11066; Lev Se ann. Brand new 512,55 EC-1266 RCVR ann. Brand new 522,55 EC-1266 RCVR ann. Brand 1000 to 525 EC-1266 RCVR and 1000 to 500 to 500 EX-1266 RCVR and 1000 to 500 to 500 EX-1266 RCVR and 1000 to 500 to 500 EX-1266 RCVR and 1000 to

# ORDER DIRECT FROM THIS ADI

Cash with order, 25% deposit on all C.O.D. orders, All orders shipped by truck or railroad express callect.

Prices subject to change. All merchandise subject to prior sale.

# ALVARADIO SUPPLY CO.

Dept. A-1, 341 S. Vermont Los Angeles 5, California

# 3-Tube Amplifier

(Continued from page 57)

section is a 20,000 ohm resistor and the variable reluctance pickup is connected across this. The upper section is a 1 megohm resistor and a crystal pickup would be connected across the entire input resistance, or across the two resistors in series. Both the voltage output and the input resistance requirements of a crystal pickup are much higher than those of the VR type. By using a voltage divider of this kind, the shunt resistance across the crystal pickup is kept high, yet the voltage at the first tube grid is reduced to a value comparable to the voltage output of the variable reluctance cartridge

Unless precautions are taken to prevent it, the amplifier will pick up signals from strong nearby broadcast stations since it is quite sensitive. A 100 µµfd. mica condenser is connected from the first grid of the 12SL7GT to ground to bypass the r.f. and eliminate this effect.

The adjustable equalizer is in the plate circuit of the first section of the 12SL7GT. It appears in the photograph as the short shaft with the slotted end, between the two audio tubes and the rectifier. The equalizer consists of a 250,000 ohm potentiometer in series with a .01 µfd. paper condenser, shunted from the first plate of the 12SL7GT to ground, Moving the potentiometer arm toward the plate end of the resistance will increase the treble response and moving it toward the condenser end will increase the bass response. The equalizer may be adjusted for any desired degree of bass and treble response to suit personal preference. Once it is set to the preferred position it does not need to be changed thereafter. The equalizer adjustment affects the over-all gain of the amplifier. With the equalizer set for maximum treble response the gain will be very high and the response much too brilliant for the VR pickup. However, a crystal cartridge may be used with this setting. When the equalizer is adjusted for maximum bass response the amplifier gain is lowest, but there is still enough amplification to drive the application to advice the straightful to adequate room output. In practice, the equalizer is operated at a setting somewhere in the lower half of the resistance.

Although it does not show very well in the photograph, the 12SL7GT is shock-mounted by running the screws which fasten the tube socket to the chassis through small rubber grommets. By means of this simple expedient, the tube is made floating and so insensitive to shock and vibration that no trouble has been experienced from microphonics in this amplifier to date.


The amplifier gain is controlled by a 1 megohm potentiometer in the 35L6GT grid circuit. This is the long shaft extending from the side of the amplifier in the photograph. The a.c. line "on-off" switch is a part of this volume control.

The value of the condenser across the primary of the output transformer was determined by experiment and .02  $\mu$ fd. was found to give the best audio quality. A .002  $\mu$ fd. paper condenser is connected from grid number two of the 12SL7GT to ground to further smooth out the response of the amplifier unit.

Terminal strips of the "tie-point" variety are used for input and output connections.

The power supply filter circuit uses a small filter choke of the a.c.-d.c. type with 20 µfd, of filter capacity on either side. This is adequate filtering for a low hum level from the 35L6GT. Additional filtering for the 12SL7GT is provided by 20,000 ohm resistors and 20 µfd. electrolytic condensers. A 10 ohm resistor is used between the cathode of the rectifier and the filter to limit the peak charging current into the first filter condenser. A line cord resistor of about 220 ohms in value drops the a.c. line voltage for the tube heaters. A 220 ohm, 20 watt wirewound resistor could be used instead of the line cord resistor, or even the heater of another 35 volt tube could be connected in series with the heater string to accomplish the same purpose. The negative side of the

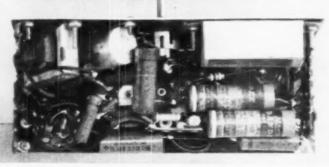Under chassis view of the three-tube amplifier. Parts placement is not critical.





# 70 tell the TRUTH\* you'll find the **GREATEST BUYS at NIAGARA!**

# Famous UTAH 15 and 25 Watt Potentiometers



inals with off pe	ositios.		
Stock No. In	Ohms	25W Stock No.	Resistance In Ohms
Stock No. In  Stock No. In  PW-100  PW-150  PW-200  PW-250  PW-250  PW-300  PW-400  PW-800  PW-800  PW-100  PW-500  PW-100  PW-500  PW-100  PW-500  PW	Ohms 100 150 200 250 300 400 500 800 1000 2000 3006 5000 7500 0,000 0,000 15 watt	Stock No. SW-1 SW-2 SW-3 SW-6 SW-16 SW-15 SW-20 SW-30 SW-50 SW-60 SW-100 SW-200	1 2 3 6 6 10 15 15 15 10 10 10 10 10 10 10 10 10 10 10 10 10
	25 watt. /	ALL SIZES	

# TERRIFIC PRICE SLASH! **BRAND NEW TUBES**

TRANSMITTING	RECEIVING
E1148 8 .34	1H5GT 8 .50
2C26	3A4
58Pt	387
10Y28	306
211	6C4
803 3.63	6AR5
	6D6
	6K7GT
813 Proceeding told	65117
843	655/ 1111/1111 -53
954	7C4
955	12A6
957	1286
958A	12K7GT
1619	128H7
1625	128R7
1626	2807
7193	35L6GT
0000	
9006 18	5015GT 48

All Quantities Limited or additional Tube values see complete Niauara be listing on page 88 this issue.



HEART OF THE BC-221 FREQ. METER

Assembly, used a BC-221 Freq. leter, is ideally

\$6.95

Prices just can't be beat! IMPORTANT NOTICE: Please include 20% deposit with C.O.D. orders, unless rated. Orders recived without nortage will be shipped railway express cellect. Send us your circ. Prices subject to change without notice. All stock subject to price sale. All merchandise F.O.B. New York Ciry. Minimpur ander \$2.00.

agara Radio Supply Corp.

Zun's



# MORE BARGAINS

IN SURPLUS EQUIPMENT

1-2 or 3 of each Check every linel



# MEET THE WINNER!

of last month's

TALL TALES CONTEST

J. C. JACKSON of Portland, Oregon copped this month's \$5 prize with this tall tale—

"One winter in Northern Montana we installed a vertical antenna but because of very cold weather we ran a steam pipe up the center to keep ice from breaking the tower down. After several hours CQ in vain we discovered "standing waves" shivering around the tower trying to keep warm."

\* Honest, this is no tall tale. Niagara's

# NIAGARA'S GOLD-PLATED SPECIAL!



Cat. No. N-257 SPECIAL

\$395

# WAVE TRAPS

# DOES YOUR TV SET DROOP FROM INTERFERENCE BLOOP?



BLEEP BLOOP

# Banish Interference with New Niagara Hi-Pass Filter!

\$1.95 Anywhere in U.S.A. plus 15c sentage and handling

# ATTENTION AMATEURS!



\$4.99

# BARGAINS IN NEW METERS

HILL HILL	West n O-2 RF Ange. Westingtone O-5 A C V Westingtone O-3 RF Ange. G.E. O-10 BC Ange.	4.95
RD,	Asst'd Brands O I KV DC Asst'd Brands O I R F Aliqui W Chester Strong Van Per Sie 1914	1.96
IID.	GE O-M KYD. V	3.95



# Three Good Reasons Why Astatic HOLDS ITS POSITION AS THE NATION'S LEADING MANUFACTURER OF PHONOGRAPH PICKUP CARTRIDGES

. The first Caramic Cartridge with replaceable needle. Takes the special new Astatic "Type G" needle - with either one or three-mil tip radius, precious metal or sapphire - which slips from its rubber chuck with a quarter turn sideways. Resistance to high temperatures and humidity is not the only additional advantage of this cartridge. Output has been increased over that of any ceramic cartridge available. Its light weight and low minimum needle pressure make it ideal for a great variety of modern applications.

• An entirely new Astatic design, featuring miniature size and five-gram weight. Model CQ-I fits standard 1/2" mounting and RCA 45 RPM record changers. Model CQ-11 fits RMA No. 2 Specifications for top mounting .453" mounting centers. Needle pressure five grams. Output 0.7 volts at 1,000 c.p.s. Employs one-mil tip radius, Q-33 needle. Cast aluminum housing.

• The LQD Cartridge — for 45, 33-1/3 and 78 RPM Records is autstanding for excellence of frequency response, particu larly at low frequencies, among all turnover types. A gentle pry with penknife removes ONE needle for replacement . . without disturbing the other needle, without removing cartridge from tone arm. Gentle pressure snaps new needle into place. Model LQD-1, with needle guards, illustrated. Available without. Stamped aluminum housing.

Oth St. Oakland, Calif.
Phone TWineaks 3-9103

405-10th St.

Astatic Crystal Devices manufactured

CHICAGO INDUSTRIAL INSTRUMENT CO.

336 W. Eim Street, Chicago IS, Illinois



power supply is not connected to the chassis, except through a .03 µfd. condenser.

The amplifier, a pickup arm and a dual-speed turntable and motor are mounted in a carrying case of the "suitcase" type. A five inch PM loudspeaker is used, which is somewhat small for best bass response. External speaker terminals are provided and when the amplifier is connected to a ten- or twelve-inch speaker, the bass response is improved and it will be found that the equalizer can be set farther toward the treble end. Despite the small speaker, however, the response on playback of this unit is excellent and the amplifier has proved itself to be just what was desired.

-30-

# Phono Pickup

(Continued from page 41)

on both sides of the beam. A differential or push-pull type of circuit has been devised in this coating. The terminals of the circuit are flat silver areas which make contact with similar areas in the cartridge.1) A single screw in the cartridge may be loosened, and a new element, carrying a new stylus, may be easily put in place. (Fig. 2B)

This pickup is a linear amplitude type of strain sensitive transducer. It is a voltage modulator but not a voltage or current generator. Its total resistance is approximately 250,000 ohms, which does not change with audio frequency. This resistance is higher than that of earlier models. A polarizing voltage of about 45 volts d.c. is applied to the pickup element. This voltage is modulated by the resistance changes in the strain sensitive coating. The a.c. modulation voltage is taken off at the midpoint of the resistance. Although the bending strains on the sides of the pickup change the resistances, the total resistance does not change. The resistance changes in the two sides are equal and of opposite phase. One increases as the other decreases for each half of the stylus motion past its midpoint. Thus the voltages at the two ends of the resistance of the pickup remain the same, but the voltage at the mid- or singletakeoff point varies following the resistance changes in the coating.

A special preamplifier supplying the necessary polarizing voltage and having a unique tone control, incorporated in the preamplifier, provides wide and complete compensation for any type of record. It should be noted that all compensation is accomplished by means of degenerative feedback, not merely attenuating RC networks. (Fig. 3)

Two types of preamplifiers, both with or without an integral power supply, have been developed. One type

<sup>1</sup> For additional description of this pickup refer to "Phonograph Pickup Using Strain Gage," by Germehausen and John, in Electronic Industries. Navember, 1946.

incorporates a one or a two stage gain circuit, made optional by means of a switch. The single 6SJ7 stage has a gain of 45 db. The second 6J5 stage makes a total gain of 70 db. possible.

The output voltage of the single stage preamplifier is .25 volt r.m.s. when using a Clarkstan 102 M sweep frequency L.P. record at 33 r.p.m. With the use of the Clarkstan 1000 A sweep frequency record at 78 r.p.m. the output is .32 volt r.m.s. When the two stages are used the voltage output values are 3.2 and 3.7. records were used because of their convenience and the fact that their over-all level is about the same as that of many records just above the turnover point. The output voltages may be regulated by means of a volume control in the circuit. The tone control is not affected by the choice of one or two stages.

The other type of preamplifier offers a single 6SJ7 stage with a gain of 45 db., and output voltages, obtained as described above, of .22 and .21. By throwing a switch, the circuit adds a 6J5 cathode follower stage. The circuit with the cathode follower output has a gain of 42 db. with corresponding output voltages of .21 and .205. The tone control is completely flexible with either circuit. This second type of preamplifier, because of its lower output voltages, could be used only with a high gain amplifier.

The values of voltage and gain given are for the frequency characteristics described earlier in this article. The voltages are increased if a frequency pattern with more bass is used. In all cases the amount of extra low bass lift is controllable with the tone control knob. None of the preamplifier arrangements show any evidence of distortion when tested with a Hewlett Packard 200 BR oscillator and a DuMont type 208 B oscilloscope. This pickup and preamplifier combination is outstanding for its extended range, high fidelity and the natural quality of the music it helps to reproduce. The linear amplitude type of energy transformation in the pickup plus the level of its output allows complete tone control, with no introduction of distortion for any amount of tone correction. The combination of compensation by means of degenerative feedback, and the fact that the pickup is a modulator, not a generator of energy, appears to be a natural. No evidence of hangover effect, so common to crystal pickups and which contributes to blurring of the tones, is present. The music is as clean as the recording in the record. Microgroove and 45 r.p.m. records can be played with no fuzziness. All the quality that has been engineered into them shows up with crystal clarity and beauty.

The listening tests used in the development of this pickup were made using an H. H. Scott Type 210 A amplifier and an Altec Lansing Type 604 B speaker.

# STOP LOOKING! HERE'S YOUR TV! BEST CUSTOM QUALITY-LOWEST POSSIBLE PRICES



-\$169.50 (Plus \$1.28 Audio Excise Tex)

COMPLETE CUSTOM CHASSIS. FACTORY BUILT, FACTORY ALIGNED: READY FOR ANY INSTALLATION: COMPLETE IN EYERY RESPECT, INCLUDING CR TUBE!

n if you are not a TV expert, cast aside all don worries and don't hesitate in luny, or to sell the to your service customers, because we furn

CLOSE OUT BARGAINS!

CLOSE OUT BARGAINS:
FIRST COME, FIRST SERVED!
ANSCEVER Mfg to Collins 60 to 80 mc.
AN mate. Like NeW 539-95 (1) to the other water like NeW 539-95 (2) to the other water like NeW 539-95 (2) to the other water like New 19-10-10 MC Hery w 19-10-10 MC 19-10-10 MC 539-95 (2) to the other water like New 5295-00 CO 539-95 (2) to the other like New 5295-00 MC 539-95 (2) to the to 145 mr. AM or FM MODULATOR SC-456. Used, less tobes and top cover

AN RF & AF SIGNAL TRACER FOR 79cf

ATTENTION MOBILE MEN!

ATTENTION MOBILE MENT

BC-664 1) orbaturely mark-batton 2.5 W FM Kndr, 20.

27.0 mc. ferred merel less white and dynamotor. 90.00

BC-924 4 chan, 25 W FM sintr, 27.0-36 0 MC model

mark, with 12 V dynamotor. Latest model. \$10.05

14.95

MOBILE POWER SUPPLY UNIT

me, not packed but appear to be new, acre

SPEAKER SPECIALSI

LOOK WHAT \$2.65 WILL BUY! BRAND SPANNING NEW! ONLY
A-27 PHANTON ANTENNA. Use with any 160 mover rig or for marine freqs. 2 to 4.5 MC.

ctal case with spare leads calls chart-

> G. L. ELECTRONICS 1260 S. ALVARADO ST. All prices F.O.B. L. A. Calif. buyers add Sales Tax

GIVE-AWAY PRICES ON C-R TUBES! All Brand New in Original Packing SGP1 SEP1 KKK Standard Test Scope SI.29
SEP4 Name but white acreen. Use for remote TV view but hite barries, extra accelerating energy

COMMAND UNIT SPECIALS

Transmitters 2748 Vype: 2.1-lime (Marine) Heparks, 160 new Y-16 ARC-9: 2.1-lime (Marine) Heparks, 160 \$14.05 town

C. 4571 4.5 line. Like new

C. 4582 5.5 True. Excellent used.

As is Toulities.

C. 4592 Tu time 40 intra Reports. Like new
Fair used, less xtal

As is touddies.

Tu time 40 intra Reports. Like new
Fair used.

ACCESSORIES \$1.50 69: \$2.19 \$1.50

61.69

SC.442 Attenus Briar Unit, with 50 month of the CT-2240. Nichods mount for fit. 442, used for 70.240. It receives rack used. 157.250. 2 Trainmitter rack hard. 157.250. 2 Trainmitter rack hard. 157.250. 2 Trainmitter rack hard. 157.251. (by the country fit of t A Steal at ONLY ST.95 L KfY: 125 all new colle: Contains If cans, tun-A real Deasure choic for

ULTRASONICI Scott Hi-Fi Cutput Francharmer. Ensentially dis 275.05
Scott Hi-Fi Cutput Francharmer. Ensentially dis 275.05
Scotto Providing 150 and 15 done secondaries when

HERE'S YOUR SOO OHM LINE TRANSFORMER! Re, exampledly flot 40-12,500 cycles.

ATTENTION MARINE RADIOMENIS (I) G.L. "MARINER" RECVE., specify 12 or 24 V DC SFO ON-OFF, AVC-MVL. Long wave, fireadrest, Marine Short wave. A beautiful conversion of a doggots pos-Naive surface fear-thing times, all reserves on the coast fear-thing times, all reserves in pluga needed ready to go in pluga needed ready to go (2) BU: Manual Direction Finder, specify 12 o (2) BU: Manual Direction finder, specify 12 o (2) BU: Manual Direction finder, and bearing the serves and bearing to test of 42.1 Mariner or and of 42.1 Mariner or 27.5.00 27.5.00 other receiver of the properties of the second of the seco marine freq. state mike specify freq. (4) 12 V DVNAMOTOR FOR 100 W. Dut 42, to pole. 1030 V or 213 ms. for food, and 315 (4) 12 V. DYNAMOTOR FOR TOR (00 W. DM 42 the eather collision of the colli NEW ASET TRANSMITTER. Light meat airheem rada office 2 tromfore airleines tones on front panel solings condensors, beautiful blower moint and solings condensors, beautiful blower moint and solings.

10 to 10 to

FLASH!
COMPLETE ADF INSTALLATION, SCR-269-G or
AN ARM-7 with MG-149 Exist used \$69.50

BD-71 ARMY TELEPHONE SWITCHBOARD

THE THE PROPERTY OF THE PROPER

POSITION XMTR. MOTOR, LOOP

The with beam position indicates or to be built a vital ing display table, or a team solar Compilete business date foreigned. This as LP 21-A less appoint to the contract of the contract of

# TELEVISION

# SUPERIORITY AT A GLANCE!

The vertical response of this economy TV scope is usable to 5000 kc, not 50 kc. Response is flat to 750 kc, down 3 db at 1000 kc. Amplifier supplies a voltage gain of 20 at 5000 kc.



Check this necessary feature before you buy any scape for TV use.

The R.S.E., AR-3 Scope has been built by Ross Armstrong to our rigid specifications. It's a complete unit that embodies standard horiamplifier and sweep circuits with zontal normal sensitivity.

The case is 8" high x 5" wide x 14" long, attractively finished in "hammered" opalesce blue enamel. Operates on standard 110 volts -60 cycles-40 watts. Tubes, 38PI-6AC7-6SJ7-6X5-5Y3-884. Instructions included.

Complete specifications upon PRICE request. Satisfaction or your \$4995

money back. AVAILABLE TO JOBBERS IN QUANTITY

# Station MARS Station of the Month

# MARS BEAMS WEEKLY BROADCASTS

MARS—Army Headquarters station, WAR, located at the Pentagon Building, Washington, D. C., broadcasts a weekly message each Tuesday at 0.1002 and at 0.4002. (This is Monday at 8 p.m. and 11 p.m., Eastern Standard Time; Monday at 7 p.m. and 10 p.m., Central Standard Time; Monday at 8 p.m. and 9 p.m., Mountain Standard Time; end Monday at 8 p.m. and 8 p.m., Pacific Standard Time; and Monday at 8 p.m. and 8 p.m., Pacific Standard Time;

Fac-fic Standard Time.)
Simultaneous broadcasts are made on frequencies 6997.5 kc., 14405 kc., and 20994 kc. Each message is sent three times, once at 10 words per minute, once at 15 words per minute, and once at 10 words per minute, and once at 10 words per minute.

Designed especially to transmit guast-official traffic and training information to MARS member, the broadcast offers an excellent opportunity to all amateurs in building up their code

bers, the b

COTT Air Force Base Amateur Radio Club station K9FAE has been named the Air Force "MARS Station of the Month" for its allaround participation in amateur activi-

Lt. Maurice Rundquist, W9GPN, present custodian, is the nth of a long line of spiritual guardians of the ham shack and Corporal John A. "Pete" McKowen, W6FNE, is the chief op. The original call W9 Nice Sunny Days was issued early in 1946. The MARS call K9FAE was received 3 August 1949

The scope of operation of K9FAE-AF9FAE just about covers the amateur radio spectrum, beginning with 75 meter phone and c.w. and ending up with 144 mc. phone.

MARS activities consist of meeting the Major Commands' net and acting as NCS for Headquarters Air Training Command nets. In addition to these schedules, which impose a fairly heavy demand on daytime operation, K9FAE is a regular participant in the Illinois Emergency Phone Net, the Illinois Traffic Net, the South Georgia Net, the Missouri Traffic Net and the Marine Corps Net which covers the Pacific and Far East on 10 meters.

While K9FAE does not necessarily point for the Brass Pounders' League, the average traffic totals in the amateur bands totals 300 to 400 messages per month, which if added to the MARS traffic would make an impressive total.

The station's operation in the Amateur Emergency Corps proved a boon to the Military and civilians in the Belleville area last July when the Wood River tornado ripped down power and communications lines in that community. Using a PE 95 power unit and the regular gear in the shack K9FAE stayed on the air almost continuously for 48 hours handling local traffic on the 75-meter emergency phone net and relaying the long haul via 20 meter c.w.

For mobile emergency operation it is only necessary to call the motor pool for a 6 x 6 to nook on the power unit, lift the HT-9 and SX-28 from the shack and the gang is off for on the spot action. It also works out nicely for field day activities.

The shack is located in one corner

# INTERCOM & RADIO

AT A PRICE THAT CAN'T BE BEAT



DETROIT

6 tube superhet-3 tube WHILE THEY LAST intercom permits commu \$2995 nication between radiomaster and up to 4 sub-

stedione Extra Sub-stations \$3.95 each Original cost \$64.50

**PUSHBACK** 



25% BELOW MILL COSTI 1st class, Essex or Lonz, ALL SOLID tinned copper, double coffon serve, waxed finish.


				Production
SIZE	COLORS	lest	feet	Keel
22	BACK-BROWN	34	3.79	3.85M
20	RED-WHITE-BOUE	.49	4.47	3,994


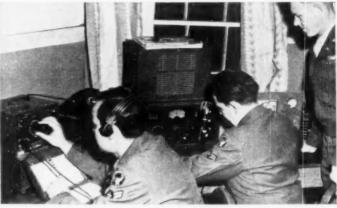
# ORDER INSTRUCTIONS

Quantity and Export Orders Solicited DETROIT 1,

Corp. T. Reed, W9CQK, keeps a frequency check on the sigs at K9FAE while Corp. J. A. McKowen, W6FNE, holds a MARS schedule, Lt. M. Rundquist, W9GPN, custodian, looks on.



90 degree twist, 6 inches long \$8.00 723 AB Mixer-Beacon Dual Oscillator Mount with Crystal holder \$12.00 2 Way Wave Guide directional coupler, type N fining Na & guide 2608 TR-ATR Section, AFS 15 for 1824 with 724 ATR County with 1824 and 724 Faces \$21.00 \$21.00 180° bend with pressurizing nipple 3 cm. 90 bend, 14 long 90 twist with pres \$6.00 ea. \$6.00 ma. 5 FT. SECTIONS choke to cover, Silver Plated SWR MEAS SECTION, & L with 2 type "N" output probes MTD full wave apart. Bell size \$10.00 guide. Silver plated SLUG TUNER/ATTENUATOR, W. E. guide. guide. \$6.50 ROTARY JOINT choke to shoke with \$17.50

"" RIGID COAX .- "" I.C. %" rigid coaxial tuning stubs with vernie rigid coaxial funing stubs with vernier stub doubtment. Gold Parted \$17.50 RIGID COAX ROTARY JOINT. Pressured. press #10613. Gold Parted \$27.50 pole internity. Part of SCR 584 \$25.00 ea. RIGHT ANGLE BEND, with finible cook putput \$8.00 SHORT RIGHT ANGLE BEND, with preus STUB-SUPPORTED RIGID COAX, gold p STUB-SUPPORTED ATOMS

1 lengths Par length \$5,00

RT ANGLES for above \$250

RT ANGLES for above \$150

FLEXIBLE SECTION: 15 L. Male to length \$150

FLEXIBLE SECTION: 15 L. Male to length \$150

MAGNETRON COUPLINGS to 15 rigid case with 18 picket loop, gold blated. \$150

FLEX COAX SECT. Approx. 30 H. \$1650 R. F. EQUIPMENT

R. F. EQUIPMENT

LIGHTHOUSE ASSEMBLY, Part of RT20/APG-5 & APG-15. Receiver and Trans.
Cavities wanter, Tr. Cavity and Type N CPLGTo Rev., User 2C40, 2C43, 1827. Funable APX
2200 2700 MCC. Source named. Sept. Sept.
2010 CPL APC. Source named.
APS-2 10CM RF HEAD COMPLETE WITH HARD
TUBE 1155. Puncer. 718 Abuguerton A174 Misson
TUBE 1155. Puncer. 718 Abuguerton A174.
TUBE 1155. Puncer. 718 Abuguerton A174.
TUBE 1155. PUNCER. TUBE APX
TUBE 1155. PUNCER. TUBE A175.
TUBE 1155.
TUBE

TEST EQUIPMENT

MODEL TS-268/U: Test set designed to provide a means of rapid checking of crystal diddes INZI, INZIA, INZIA, INZIA, INZIA, INZIA, Operates on II/2 volt dry cell battery THERMISTOR BRIDGE: Power meter 1-203-A. 3 cm. Warten Absorption Type 592 50
head. New Absorption Type 592 50
10 cm. Waveneder, W.E. Type 8 435490 Transmission Type Type N Friengs, Verder Root Msion Type Type N Friengs, Verder Root Msonater dial, Gold Park W/Calib. Chart.
299.50

Full Line of UG Connectors in Stock Immediate Delivery AMPHENOL "AN" CONNECTORS

Large Variety Available
At Great Savings Send Us Your Spot. Let us Quote



BC405

\$4.75

150. Ea. Klixon 25A Dual 8 & 25 Amp. De fon 35 Amp. \$1.45

ARC 3 complete Audio Modulation XFMR pkg 7103 carbon Mike to Grid 5.95 7102 615 to PP 616 Grids (Modulation) 1.45 7104 Mod XFMR PP 616 to 832 or 8298 Plates

ARC 5 PARTS EQUIPMENT AND KITS

80 Meter Xmitr Con-xersion Kit \$1.50 Serven Med Trans 807 to Sern of PP or Par 867 1.00 Mrd 1.25 Mrd 25 Cond 05 -01 e5 40 Cond 28 95 49 Cond 28 95 and 40 Mrs 40

5546, all for HF voil ESL out 865 S.T. RF Sections, 6-9.1 Mc.

Trill Control Hex Switch, PL 154 L2 Pnz Female PL 155 IS Pnz Female PL 148A Z Pnz Fe-

PL 148A 2 Pm Fe-male male 9821 8 Pm Fe-male, 5512 7 Pm Male 6578 2 Pm Eemale, 5577 6 Pm Male 6418 8 Pm Male 1837 18 Pm Male Any 4 Plus Den Plus 2 Pm Chassis Plus 2 Pm Chassis Plus Moont 2 Pm .30 .30 .30 .30 .30 .30 .30 .10 .10

on Ind Bulb on Ind Bulb Muf Trimmer iav 24 Dolt 24 Est Sh7 Tube Sh7 Tube 1,98

Fig. 117 2,49 Junction Res. 322 for Tel & Miles 329

Soldering Iron 200W SI SI Cas LEARN



OR TEACH CODE

\$29.50

MOUNTINGS CR 540 BC-701

T.V. Transformer, 7 or 5 vcope, 3000v 5MA, 720 vct 200MA, 4, 54, 5, 1A, 1, 25, 1A, 1, 25 TUN-

ANI 306 Spring Services Street Services Services

XMTR COILS AIR WOUND

80 MTR Sac Prong 100 \$1.19 10 MTR. 5 Prone 50w plug in socket ..... \$1.19 MTR 1 Prong Bar w \$1.19 = C518 2-3.5 MC 300w Fix. Link \$1.19

#1735 7-3.8 MC. 300w Var. Link \$1.45 # C390 5-7 MC. 300w Fix Link \$1.19 160 MTR Bar Type 100w \$1.19

SCR 183 REC. TUNING UNITS

SCR 183 TRANS TUNING UNITS

11 Mr \$1.59 2 10 Mc 1.49 2 4 Ma 1.49 6 2 Mc 1.49 5 Mc w 4195 Kc XTAL 2.95

\$6.95

Birtcher Tube Clomps

13c ea. 100 for \$12.00 1000 for 10c ea

VARIABLE CONDENSERS

190

OIL

CONDENSERS FAMOUS MAKES BEAND NEW

C714 3.2-425mm C713 - 2.8-27Mmm C717 2.8-33Mmm Electric Motor

POWERED

\$37.50 VFO CAPACITOR

100

ROTARY SEAM tak Eastly and Pro-

Hi Gain Dynamic Mike Xfmr ided 49c UNIT IT ald Price Each

FOR BC 223 RE CHOKES TU 18A 3-6.3 MC L'Tior \$2.50 TO 25 8.5-5.2 MC Price \$2.50 1 MHY 12 5MA 1 0-2 MHY 2 5MHY 3 001MA 1 2 MHY 3 0 5MHY 1 0 5MHY 1 2 5MHY 1 2 5MHY 1 5 5MHY 5 001MA 1 5 MHY 10 10 10 SUPER PRO 39 EQUIPT. .98. 10

COLL SALEL ANT INFT 200-400 KC 8A 48-HI THEA OSC 25-5MC COLL SALES ANT OFFT 10-20 MC COLL SALES SALES EACH 65C CERAMICONS M.O. COIL

1800-2250 K.C. BC-929 SCOPE

\$21.50 SCR-522 VHF XMTR-RCVR 10-line, stol controlled re-xontr. Makes ideal 2-meter, bite rig. 100-150 rec. \$34.95

MINE DETECTOR AN PRSI to breating metal, pipes, gold, treasure. \$12.74 

Combination SC-620 and PE-120 No. GIBSON GIRL \$4.95

BC 223 XMITR

MICA CONDERS

RATED CONCERNS SEND P.O. CABLE ADDRESS: COMSUPO
PROME DIGBY 9-4124

131 LIBERTY ST. DEPT. N
NEW YORK 7, N.Y.
C.I.C. MOREY MACE GUMRANTE, 43 w
ROL 8.74.5 SEM MART ROUBLES (RIC., BILLY)



Order NOW

Any Tube Above 32c Each. londling Charge On Orders Under 188 Tubes.

ALL ORDERS SHIPPED C.O.D.

ADIO TUBE COMPAN 32 BEECHER STREET . NEWARK 2, N. J.



# ANTENNA SCOOP!

Outstanding ! "STAR" value Single or double stacked conical for

stocked conical for high-gain reception on all TV channels.
Builds up signals, reduces "snow" and ghosts due to weak reception, all hardware and instructions supplied. Strongly built for lasting service. TV installers don't miss this extra-value deall Supplied less most.

Star Single Canical TV Antenna Star Double Canical TV Antenna

Sec-... 82c Just off the pross . . . BIG BARGAIN BULLETIN ELECTRONIC

DISTRIBUTORS, INC. -7736 S. Halsted, Chicago 20, III.

MAGAZINE LIBRARY

Walter Ashe Exclusivel

An ingenious, custom-built stor-

ORDER YOURS TODAY!

(Plus 15¢ per set for a & pstg. anywhere in U

New low prices on QST CQ Magazine Librari CQ Magazine
Formerly 35c
Now Only 25¢ each
Most 12 issues
(Plus 6¢ ea. to cover pkg
& pstg. anywhere in U.S. of a GI barracks and sticks to support a maze of sky wires are conveniently spotted around the building. The h.f. equipment comprises a BC-610E, for 10 meter and 75 meter operation, a BC 460 for 20 meters, and HT-9 for 40. Receivers are an SX-28 and a "Super-Pro." Antennas are doublets and endfed Zepps cut for each band, plus a four-element, close-spaced beam on 10 meters.

The v.h.f gear is the old familiar BC-639. BC-640 transmitter-receiver combination, rescued from salvage after the State control tower had had the best years of its life. To date only five states have been worked with the best DX being W5JTI but the hours of operation are considerable since K9FAE keeps a daily schedule with the St. Louis 2-meter gang. A 5-element, close-spaced array on top of a 66-foot stick helps the signal on its way

The 6-meter rig is undergoing a complete overhaul from xtal oscillator to a pair of 24G's in the final. A 3-element, close-spaced beam on a 33-foot telephone pole using RG-8U to feed a folded dipole for the driven element has proven satisfactory. So far only three states have been worked on six with the best DX being W1HDQ, but the watchword is now "Sporadic E" with book being made as to who will be the first to snag an LU.

Lt. Lawrence Echelmeyer, W9SII, MARS Director for Headquarters Air Training Command along with 12 other MARS members and a host of SWL's at Scott AFB keep the filaments warm and the plates blushing pink at K9FAE just about 24 hours a day to set a smart pace for other MARS stations to follow.

# -30-Within the Industry

(Continued from page 24)

ment Tube Department. He has been with the Radio Receiving Tube Division of the company for fifteen years. . SAMUEL MORRISON has taken over the presidency of Morrison Steel Products, Inc. while JACOB MORRISON, the former president, assumes the chairmanship of the board. . . . The Magnovox Company has appointed four new district sales managers. BEN CLARK, RICHARD L. HOFFMAN, MARK L. CRUM, and GORDON WRIGHT ... SID-NEY A. JOFFEE is the new vice-president in charge of merchandising for Pathe Television Corporation. LEWIS M. CLEMENT, director of engineering and research for Crosley Division, has been named chairman of the executive committee of the Receiver Section of RMA's Engineering Department. . . . WILLARD H. SAHLOFF is the new manager of the General Electric Company's receiver division. . . . S. M. WEINGAST has been named president and general manager of Precision Apparatus Company. Inc. At the same

# WITH SOVEREI

TELEVISION KIT LESS TUBES

Complete with All Tubes, Incl. C.R. Tube

- - - \$129.50

\$137.50

\$157.50

10" - 121/2" - 16" MONEY BACK GUARANTEE

THE "ALL PURPOSE"

FEATURING

honic ned t.F. for Max. Gain and Ease of Align Tuner Forus and Deflection ized Synchro-Lock Gircuit Holds

SOVEREIGN TELEVISION CO. 5508 New Utrecht Ave. Bklyn 19, N. Y.

10" KIT

ganization. . . R. W. FORDYCE is the new general sales manager for the Television and Broadcast Receiver Division of the Bendix Aviation Corporation. . . . RALSTON H. COFFIN has been appointed director of advertising for the RCA Victor Division of Radio Corporation of America.

BURT G. SCOTT has been added to the sales staff of the Electrical Division of Olin Industries, Inc.



Mr. Scott, who is a sales engineer. will contact manufacturers of hearing aid and radio sets in the eastern states. He has been associated with the electrical field for

several years, having held positions with the MB Manufacturing Co., and International Instruments, Inc., both

During the war he was attached to the Signal Corps, electronics section, as an instructor at Fort Monmouth, New Jersey.

TELEVISION BROADCASTERS ASSOCIA-TION, INC. has announced, through Raymond F. Guy, chairman of the Engineering Committee, that initial steps to effect standardization of TV equipment, as recommended by the TBA, have been taken by the Radio Manufacturers Association and the Institute of Radio Engineers.

Standardization of transmission levels will be undertaken by RMA, while the drafting of the methods of measurement of transmission levels will be

handled by the IRE. RMA will also start work on standardization of patch cords, plugs and jacks camera cables and their associated connectors, and coaxial cable connectors. Work on picture geometry, started some time ago by RMA, will be continued by engineers of the

manufacturers' group

IRE will originate definitions and methods of measurement in the case of missing or obsolete standards upon notification by RMA, the IRE will formulate tentative proposals and forward them to RMA for comments and tentative approval, the RMA will make final suggestions and express approval, and finally the IRE will consider the RMA suggestions, reformulate and issue the standard definitions for test methods.

THE FIFTH ANNUAL TELEVISION INSTI-TUTE and Industry Trade Show held at the Hotel New Yorker in New York City is expected to draw an estimated 50,000 persons February 6th through

In addition to some 1000 industry registrants from all parts of the country, some 50,000 persons are expected to visit the two floors of television receiver and equipment displays which will be open to the public and televi-

Panel speakers will include industry

# **Record-Breaking Values**



2 insulated 6 strand conductors laid paral-lel % mile on a reel. Special for this ad.

All new but \$1495 Weathered. Appr. wt. 1495

# W-130 ASSAULT WIRE

Weatherproof — Durable 2 conductor, twisted, 3 copper and 4 steel strands, tinned, insulated. On original \$5.95 steel reels.

(Appr. wt. 20 lbs.)

### MINE DETECTOR, AN PRS-1

#### GENERAL RADIO VARIACS



Terrific Buy-Limited Suppl 0-135 V.A.C. output- Ea. \$12.95 

#### ELECTRIC MEGAPHONES



# RECTIFIER POWER UNITS

APT 4-115 V. 40H Cy. Input. On ills and Low voltage receiver suppur 836 Tukes and one 115 V. 50 Sec v.-Complete. vs. 48 lbs.: \$5.95

# MICRO-SWITCHES



# LP 21 A LOOP ANTENNAS

Used with BC 433 or R5 ARN 7

DRY CELL BATTERIES -ALL FULLY CHARGED

# COLUMBIA TONG TEST AMMETERS

\$39.95



# ANTENNA RELAY UNITS

is an R.F. Meter, Thermo-couple, sens 50 MMFD, Sprid voilt vacuum ronder excellent condition. Our price.

# SPECIAL DYNAMOTORS

18 V. Input: 450 V. Output. An-2060.



# WILLARD 2 VOLT RADIO BATTERY NEW, Uncharged Appr wt 4 thm Fix \$1.05

### AN/APN4 INDICATOR SCOPES

nd 180 KC, 5CP1 tub ALL BRAND MEW. Our price.

BC 405-INTERPHONE AMPS.



### BENDIX SELSYN MOTORS

IIO V. 60 Cy. AC., somiler to type 5 (Appr. wt. 12 lbs.) fires Heavy Duty, (Appr. wt. 22 lbs.) Pur \$9.05

KC to 550 KC Appr wt. 12 He. to 6 Mc Appr wt. 12 He.

20 TO 28 MC FM RECEIVERS 8C-403

GENERAL ELECTRIC TRANSFORMERS 11 Vait, 65 Amps, 110 V, 60 Cy. Ingsting or High Amp. Fliament Tubes.

MIDGET SELSYNS

ARMY SIGNAL CORPS ELECTRICIANS'
INSULATING RUBBER TAPE TL-192

x 15 ft, per roll. Mfg. by U. 5 flotberry roll infod sympped keeps each roll perfect chattery. Appr. wt. 1 lb for 2: 2 for

FRICTION TAPE

FRICTI

HEINEMANN CIRCUIT BREAKER

ALL NEW (Appr. 1 lb. ca.)

BRAND NEW! KENYON FILAMENT TRANSFORMERS 10. C. T. al. 60 amps. Pri. 115 Volts. 60 spries. Stype. 26 Hs. Never before at \$5.95.

& INCH WATERPROOF SPEAKERS

Used but in excellent condi-15 lbs. Our price on \$4.95 TCS EQUIPMENT

INTERVALOMETER

# MISCELLANEOUS SPECIALS

# G. E. BLOWER-MOTORS



\$11.95

STANDARD SURPLUS 1230 Market St., San Francisco 3, Cal. Telephone HEmlock 1-3106

# INVENTORY SALE ALL PRICES CUT TO BONE

WESTINGHOUSE KUPROX RECTIFIER TURE SALE # 53-247-58-27-014-12 BRAND NEW 10 PHONO RECORDS 1st S1.79
Lass-Pop-Hillbilly-Polkas S1.79 POWER PACK KIT SPECIAL PRICE ... Volta 150 TRANSMITTING FILTER CHOKES Signal Corps Phones 2 M. Ohms (8 M. Ohms Inp.)
1 Ft. Ext. Cord (and Phone) OIL FILLED FILTER CONDENSERS working volts 6 99c 12 51.75 FAMOUS BRAND RECORD CUTTING HEAD TOBE TUBULAR ELECTROLYTICS R WAFER SCRETS-\$1.40 per control to the control to AVFILTER CHORE SMIELDEN 300 SMIELDEN WHE WOUND RES RIT 5-SO W. ASST 450 DOC JOHN WIFE WOUND RESISTANT ST. 1 per dis-RETER WHEE WOUND C.T. VARIABLE 20 OHM RESISTORS SISTORS RECOVER RECOSTATS RECOVER RECOVER RECOVER RECOVER RECOVER WAY TO RECOVER WAY TO RECOVER RECOVE N. ELE. WESTINGHOUSE stc., 60 CYCLE WAYE HOUR METERS, slightly used, perfor condition, asince as used in your home. 110.123 voids. 5 Ampere \$2.93 10 Anne \$3.35 und your own crystals. Pure linguism Quarts, of stree and thirecrees—by his package \$1.00 O-degree disc with 16 push button attachment— \$2 shaft—under by Armeres—Sig Gen. or be 3% RCA Band Switches—
3 gang 3 per 3 hand 30c 6 pang 5 per 4-3 hand 40c
1 gang 4 per 5 hand 50c 6 pang 5 per 4-3 hand 40c
1 C. A 30 MH RF chake 25c
1 frimmer-Padder Asst.—all (solantite singles, dust
1 fripre-100 and, preces reports 100 and pieces

5.—150 data Ari Calonama, \$1.35 Photos cotors 25.

5.—50 dill its a SPLANFII 1.00 tone control 25.

5.—50 dill its a SPLANFII 1.00 tone control 25.

ATTENTION Prospectors, Explorers for Mignos Treasurest construct a U.S. Army Type of Metallic Mine Detector Ampliture until only liess types and batteries with Cables, headplane cond, and jack. Army with Cables, headplane cond, and jack. Army 100.

5.1.35 Army 100.

5.1. FET ELECTROLYTIC CONDENSERS OIO EXPERIMENTER'S SURPRISE PACKAGE CON-LINS BYPASS & FILTER CONDENSES, SHORT AVE TUNING UNITS, FOWER AND AUDIO TRANS-TRUE SOCKETS, RESISTORS, CRASSIS HARD-MRE, DERR 20 LBS OF VALUABLE PARTS & 4.05 O'RILE CODE INTERPERENCE WAVE

MINIMUM ORDER \$2.00-NO C.O.D. SHIPMENTS-PLEASE INCLUDE POSTAGE

456 475 K C. 25c JACKS-OPEN & CLOSED AUTO, 18c Al. 5-15-450 VOLT CAN FILTER CON-

PHONE JACKS-1978 & CLOSE WITH CON-BENSER CONSTRUCTION OF STATE CON-ETT STAKER CONSTRUCTION OF STATE CON-10 - 1 comp - 15c at comp - 20c 11 comp - 40c 10 - 1 comp - 15c at comp - 20c 12 comp - 40c 10 - 1 comp - 15c at comp - 20c 12 comp - 40c 10 - 1 comp - 15c at comp - 20c 12 comp - 40c WESTERN STATE CONTROL OF STATE CONTROL OF STATE TRANSPORTABLE ACT (10) - 20c 12 comp - 20c 12 20c at comp - 20c 12 comp - 20c 12 comp - 20c 12 comp - 20c 12 20c at comp - 20c 12 comp - 20

### STRIPLE STRIPLES | \$5.00 cm

### STRIPLES STRIPLES | \$5.00 cm

### STRIPLES STRIPLES | \$1.00 cm

### STRIPLES STRIPLE

Transmitting Eiller tend, Asst., W.F. Persoli, Bt.A. 6.E. Etc. Cap. | Mills - 1.2 Mills 6 for \$1.00 J.Gang S.W. Variable, No MMPL per sec. Dougle ble spaced 10-20 Meters with Tank Colli-la Ships and Collins | Meters with Tank Collins | M

# NEWARK SURPLUS MATERIALS CO.

Dept. FE 324 Plane Street NEWARK 1, N. J. leaders, station managers, sponsors, agency executives, film and program producers, engineers, and educators, Also taking part in the panel discussions will be representatives of the FCC, the Armed Forces, manufacturers of television equipment, and audience survey groups.

The film industry is expected to be represented by approximately 500 persons including film directors, film producers and distributors, etc. These persons will be present for the Annual Television Film Conference which will be held in conjunction with the Television Institute on February 8th.

CHANNEL MASTER CORPORATION, as assignee of Joseph Y. Resnick, has received a favorable decision in its suit against Video Television, Inc. ownership of U.S. Patent No. 2,465,331 covering a foldable television antenna.

Video Television, Inc. brought the action against Channel Master Corporation and Mr. Resnick, claiming that the invention had been made under circumstances which entitled Video Television, Inc. to the patent.

RADIO PRODUCTS SALES COMPANY of Los Angeles has signed a franchise with Noblitt-Sparks Industries, Inc. to handle the distribution of the Arvin line of radios, TV receivers, and ap-RADIO DISTRIBUTING COMPANY of Indianapolis will handle the Arvin line in Indianapolis and surrounding counties. . . . John Meck Industries, Inc. has appointed JORDAN ELECTRONIC COMPANY of Erie, Pa. as its franchise distributor in that area while OHIO SPECIALTY COMPANY of Cincinnati will handle sales in Cincinnati area. At the same time ROBBINS DISTRIBUTING CORPORATION Was named franchise distributor for the New York City area COLUMBIA DISTRIBUTING CORPORATION of Seattle is the new distributor for Admiral Corporation's line of home radio-phonographs and television receivers in the entire western Washington territory. IRION COMPANY of El Paso will handle the Admiral line in that area. . SAMUEL N. STROUM of Seattle has been named sales representative in the Northwestern States for Insuline Corparation of America. . . . Amperex Electronic Corporation has appointed the ALLEN I. WILLIAMS COMPANY of Denver as their sales representatives in Colorado, New Mexico, Wyoming, Nebraska, Utah, and Kansas. . . . Pyramid Instrument Company has appointed three new sales representatives, DELAVAN ENGINEERING COM-PANY of Des Moines, R. E. MYERS AND SON, St. Louis, and LESTER L. ELSTAD. of Minneapolis. . . . Technical Appliance Corporation has appointed THE BRANUM COMPANY of Dallas to handle its line of TV, FM, and AM antenna systems and accessories. , , , JAMES L. KEARNS of Portland, Oregon has been appointed factory representative for the Cinema Engineering Co. of Burbank. -30-

# ATTENTION ALL ELECTRONIC-TELEVISION **ENGINEERS**

For more than 6 years RADIO-ELECTRONIC ENGINEERING, a special edition of RADIO & TELEVI-SION NEWS, has kept alert engineers dependably and thoroughly informed on all that's really important in electronic engineering.

Selected and exclusive articles and other specialized features of practical and lasting value to electronic engineers are added to the content of the regular edition of RADIO & TELEVISION NEWS.

Subscribers to the regular edition may change to the RADIO-ELECTRONIC EN-GINEERING edition by remitting an extra dollar for each 6 months of the unfulfilled portion of their subscriptions.

New subscribers please use the lower half of order card in this issue.

The RADIO-ELECTRONIC ENGINEERING edition is available only by subscription.



edition of RADIO & TELEVISION NEWS 185 N. Wabash Ave. Chicago I, III.

#### RADIO TUBES AM Largest Tube Stock in the Country FM ORDER TODAY for At LOWEST Prices! TV **Immediate Delivery** 1FSG FREE S20.00 List Value Cornell-Dubillor, Mailtory, Acrevox, Sprague, Solar. Filter Condensers -ten fast moving litters FREE with each 100 tubes. 6C4 6F8GT 6SD7GT 25ZSGT 185 1GAGT 71A 1DSGT 482B SSECT 112A 483 1D7 1H4G 12A 1828 1DIGT 1HGT 184 6A3 39 44 1.860 1AAP 1F4 6K7GT 6K8GT 6PSGT 6SA7GT 6SC7GT 6SG7 6CS 6CBG 6D6 6F5GT 6F6GT 6G6 6H6 6H6GT 6SR7 6U6G 6U6GT 6U7G 6U7GT GALG GAQS GARS GASS GATE GAUG GASG 12SH7GT 12SN7GT 50C5 69° cach 3V4 5U4G 5W4GT 5X4G 5Y3GT 51 VT-52 125 R7GT 35C5 35W4 12BE6 12F5GT 1615 1629 (eye) 24A SEZEGT SEZEGT 56 **EVEGT** 12H6 1B3GT 6G5 12 J5GT 12 J7GT 65G7GT GW4 25L6GT 25X6 SAIGT 35Z6GT 58 76 6U5 5Y4G 6SH7 6X5GT 12K7GT 12K8GT 305 6J5GT 19BG6G 6BA6 6S J7GT SAC4 624 12ASGT 6A7 6BG6G 50A5 185 6BD6 1258GT 125A7GT EACSGT 6.J7G 80 85 **GBEG** 12AT6 32 12SF5 12SF7 6J7GT GE5 807 GAK5 68.16 SKEGT 6SQ7GT 12 AU7 34 SORS 89 1C7G 1LA4 1LE3 1N5GT 1P5GT 287 5V4 5Z3 SZ4 GARS GASS GAVG GB4G GBA7 GB3 6F5 6F8G 6K7G 6R7 6T7Q 6T8 6U7 6W7G 12Q7GT SOLEGI 32L7GT 7B6 7B8 7C4 125 G7 125 J7 GT 53 10Y 12A7 35 51 ISLSGT 125K7GT 75 84 624 658 6SFSGT EYEG EZ7G 12AT7 12SL7 105GT 707 12AV6 12BF6 12507GT 40 11773 7E8 7E7 7F7 6AJS 6557 ASGT LAZGT 6SU7 TAT CSGT 6D8G GAL5 6Q7GT 12.15 STEE 42 XXL 1ABS 1ADS 1H5GT 1LA6 1LB4 1LC5 1LC6 1LH4 1LN5 1S4 2C34 3527 EREG 65UTGT 12A6 14B6 14 K7 2051 83 2V3G 31.F4 63.60 TAR 12BF6 14547 35Y4 SOCE 11776GT 2X2 6B7 701.7GT SEE 7C4 1447 14M7 45 5001 25Z5 GBFG 657G 7CS 14AF7 2050 1407 Loss than 50 tubes, 5c per tube extra Above prices are for 50 tubes or more -may be assorted. Individually boxed-Standard factory guarantee. 50L6, 35Z5, 12SK7, 12SO7, 12SA7, ..., 5 tubes for \$2.19 Miniature tubes 12AT6, 12BA6, \$1.69 12BE6, 35W4, 50B5 ... 5 tubes for \$1.69 1R5, 1S5, 1T4, 3V4 Battery \$1.29 10BP4TV\$17.95 Picture \$17.95 Tube each \$24.95 3S4, 1T4, 1S5, 1R5 50A5, 35Y4, 14A7, 14B6, 7, 14B6, 5 tubes for \$2.95 4 tubes for \$1.29 NEW TEST EQUIPMENT **OUTPUT TRANSFORMERS** All makes, all models. Tell us what you need and we will quote best prices. Best Quality SPEAKERS Ainico 5 PM For Sale, 390 ... 18 or more Price Each Each RF and Antenna Coils. Standard Broadcast Band etc. For 6V6, 6F6, 3Q5, 450 ea. -95c-51.05 VOLUME CONTROLS 10 or more Each VERY BEST BRANDS 19 or more Each 19 mg, or 1 mg, or 1.10 mg, with switch long shaft 2 mg, for battery sets— switch, long shaft 17 mg, .1 mg, .1.20 mg, or 2 16c 214", 3", 4"-95c - \$1.05 \$1.59 UNIVERSAL OUTPUT 35c TRANSFORMER SPECIAL 98c on. 2.95 3.25 35c 10" 4.25 4.50 Up to 12 watte to any speaker (while they last) 12" 4.95 5.95 19c Utah Speaker Baffles—completely enclo for 8' speakers and smaller ea. S Special on No. 47 Pilot Lights Only-BY-PASS CONDENSERS es. \$2.00 S Jobbers: write for quantity prices. 100 Bulbs ... \$3.95 Box of 10 ... 49c 100 Condensers asserted in package IF TRANSFORMERS P PILOT LIGHTS-100 BULBS \$490 .002 E No. 40 6-8 V. 15 Amps. | No. 44 6-8 V. 25 Amps. | No. 41 2.5 V. 50 Amps. | No. 46 6-8 V. 25 Amps. | No. 51 6-8 V. 20 Amps. 600 W Red Hot Vibrator Special. 4-prong, small size Universal, fits 80% of all jobs. ea. 19c Jobbers: Write for quantity price. C Good Rubber with Underwriter proved. 10 for \$1.25 400-VOLT BY-FASS CONDENSERS \$1.69 4 PRONG VIBRATORS-VERY BEST BRANDS .05 mfd. .2 mfd. .25 mfd. TV Antennas: TV PARTS TV Antennas: TV PARTS TV Antennas: 58.75 World's Best Detux Certical with 5-ft. World's Best Detux Certical with 5-ft. World's Best Detux Certical with 5-ft. 100-ahm little 51.55 per 100 ft. \$14.55 per 1000 ft. Merizantal output. RCA Type Ftybach \$1.45 e.e. Discriminator Transferences: 10-12 e.e. 10-12 per 10-1 Standard replace-ment Sensational \$129 ... .5 mfd. 8UFFER CONDENSERS .865 mstd. 1690 WV .60E mstd. 1600 WV .01 mstd. 1600 WV OCTAL SOCKETS 18 for 49c 15c ... CRYSTAL CARTRIDGE Standard replacement crystal \$1.39 VARIABLE CONDENSERS Two gang for superhet Standard 14' shaft 69c 10-20-150 V 10-10-150 V 10-10-150 V 40-20-150 V 40-30-150 V 40-40-150 V 40-40-150 V 40-40-150 V 40-40-150 V 50-50-150 V 50-50-150 V 50-50-150 V 50-50-50 V 50-50 V 30-450 V with 20-20-FILTER 30—450 V with 20-20— 25 V ea. 35c 8-8-450 V -50-50 V ea. 35c 6-8-8-450 V -50-50 V ea. 35c 6-8-8-450 V -50-50 V ea. 35c 20-20-450 V ea. 35c 20-21 V ea. 35c 20-21 V ea. 35c 8-8-8-450 V ea. 35c 8-8-8-450 V ea. 35c 8-8-8-450 V ea. 35c 8-8-8-450 V ea. 35c 8-8-8-8-850 V ea. 35c 8-8-8-850 V ea. 35c 8-8-850 V ea. 35c 8-850 V ea. 35 RESISTORS esistors packed in a box IRC etc. \$1.98 values only-1/2 watt, 1 watt, 2 watt, \$1.98 CONDENSERS SELENIUM RECTIFIERS Standard 100 mml. Very best brands 10 or more asserted 5% discount

OUR NEW ADDRESS

39¢ cath

450 Working Volts

PUSH-BACK WIRE 100-ft, rolls

PREMIER RADIO TUBE COMPANY

551 West Randolph St., Chicago 6, III. Phone: Andover 3-1590 "Your Tube Source Since 1926"

20-26-26 V
150 Working Voits
10-10-150 V
10-155 V
13-156 V
13-156 V
10-135 V
10-156 20-25 V 20-20-25 V 20-20-25 V 20-25 V 25-25 V 36-50 V 100-25 V 450 Working Volts
8-450 V
10-450 V
10-450 V
10-450 V
20-450 V
20-4 Nation accounts—10 days—all eithers 20% digness with order, belonic COD. Minimum order 15.85, All thipments FOB Chicago, Frempt iteration and to force or order, OFDE BY TODAY. One parts and tubes are warranted to be 180% replacements for the protetypes in the listings above. Satisfaction Guaranteed, To speed up defivery, sign your order and your committance with the same name.

16c en.

25-25-150 V-200-10 V c Cathode Condensors

	AN		SAVE	:	
888 mfd 10 mfd 20 mfd 4 mfd 6 mfd 2 mfs 4 mfd 1 mfd 1 mfd	320 vac 600 vdc 600 vdc 600 vdc 600 vdc 600 vdc 600 vdc 600 vdc 1000	\$1.85 .29 .39 .59 .79 .79 1.39 .89 2.15 .95 1.19 1.25 2.25 2.95 5.45	10 mfd :	fd 12KV dc- 12,500	4,95 4,50 2,25 1,95 9,25 5,75 5,50
2" 0-5 ma	ANEL M	ETERS	-BRAND	NEW R.F.	\$2.45 3.50
2" 0-30 an 2" 0-1 ma 2" 0-20 m 2" 0-300 V	Basic Basic a Basic AC	2.45 2.95 1.75 2.95	3" 0-100 o 3" 0-80 mi 3" 0-75 an 3" 0-2 ma 3" 0-20 o 1" 0-20 mi	DC DC DC	3.50 2.45 3.95 3.95 3.95 3.50
110 V 60	FILAME Cy Pri, F	NT TR	ANSFORM and.	ERS	
110 V 60 1 5 Vott 15 2.5 Vott 1 2.5 Vott 2 6.3 Vott 3 5 V CT 2 5 Vott 4A 2.5V CT 2	Amp 0 Amp 17 21 Am 0 Amp 21A, 7.5V 6.3V, 1 0A, 2.5V	6A, 7.5 A CT 20A	V 6A		\$2.75 3.47 4.75 1.89 4.95 2.45 6.95
8 Henry 8	50 ma 22	ohms to ohms	O ma 15 of SF. 820 Vo cycles. Full	3 for 2 for	.99
Migh Ct Mir. Pri. 1	RRENT	TRANS	F. 820 Vo cycles. Full	ts CT a	\$5.95
	COOR	E TRAI	NSFORME termetically 4.5A, 2.5V A, 15Ke In	9.6	\$2.95 4.75 4.95
GEM	Bins, Fi	IRPOS	E TRANSF	ORMERS Stepdown na plus h Now \$1.1	etc
	to I allo Trestant Ma Fi of relay 4	fine to	nd Helry, a al reset. merical re- met 11/1V enedy mad	djustatio	2.95 4.95 7.50 2.50
OHMS 10k-15k	100-15	(60 - 2500	OUND RE	-5k-5300-	1
Maltory V	thropack 00 MA.	Kit. s Fransfor	Volt input mer & Vibr	t. Outpu ator \$3.85 for	1 300
UTC type 6 ohm vo DB	PA 5000 ico coil.	ohm p 10 wa	date to 500 ft. 50 to CLOSE	ohm line 19,900 op OUT AT	and 81.99
01			S BARG	PAINS	
GE 2 med 1	250 Volt	At the	ole notes	n for	\$0.99 .99 .40
Hemenum Erio Cerar oll floor onl floor uno floor Rutherfloor	23 map   nicon por let Pictari To Pictari To Pictari To Pictari	10V Ar nei men I miras nil miras ati maca 11 mm	ChT Breaks	20 tor 10 for 13 for 13 for	1.10 00 90 90 90 40 90
Mc250s Lo.5sio and Lo. meg l	on Polant	ment vi	iriable muh	5 for	.59 .99 .99
heads heads to may it Harmoniche	a 450V or 5 wait fit	C with i	te in can w	4 for	68
O W nord	Must Ob.			nn s for	.69 .99 80
Apparatals nond Western &	Variable Section St	Off Cared Custorine Custorine	table 5 to 3	16	20
G. E. Cresch 20 Aren Objecte Ma	120 V At	40	erpossit Dir	Ole ton	.79
Mornoger Her in M	Smith at Switch at	TOT -	· erer		2.05 1.10 1.75
Power Rise Power Rise Power Rise	Rest 287		F W.		2.98 55 55
Top of an ion also So one of T Member	too Walt from Walt 5 Walt 1	Adr. Ho	mister and Resister	d for	0.00 0.00 0.00 2.00
	Charles		lodel 2524	2 Tor	0.00
Poses line	product 25	oton 61	Walte. w	A for	2 95

# READ CAREFULLY NEW TV PRODUCTS on the Market

#### DU MONT INPUTUNER

The Electronic Parts Division of Allen B. Du Mont Laboratories, Inc. of East Paterson, New Jersey has announced a new four-section Inputuner which incorporates the latest Mallory-Ware spiral-type Inductuner.

According to the company, the foremost advantage is its ability to double the gain and provide increased selectivity over previous models. The tuning range is continuous from 54 to 216 mc., inclusive, covering the TV channels 2 to 13 as well as the FM band. The new Inputuner which requires only 5.9 turns of tuning motion as against 10 turns for previous models provides an improvement in the high-band spread. A new type dial illuminates the TV channel numerals on an outer circle and then automatically switches the illumination to the FM designations on an inner circle when the tuner traverses the FM band.

The unit is completely shielded and is supplied complete with tubes, newtype dial, and escutcheon.

# "UNIMAC" MOUNT

Marvin Radio-Television of 89th at Buckeye Road, Cleveland 4, Ohio, has developed a unique unit which facilitates the erection of TV and FM an-

Known as the "Unimac" chimney antenna mount, the new unit requires only the use of one bolt on each of two units to lock-clamp the steel strapping in place and take up the slack. One wrench and a single operation add to the safety factor of this installation.

Constructed of heavy gauge, weather protected metal, the "Unimac" sets are made of two pre-assembled units.



which come complete with all hardware and two twelve-foot bands for secure installation on even the largest chimneys. Any mast with a diameter of 34 to 134 inches can be accommodated.

# TELEVISION AMPLIFIER

The new Model 212TV amplifier, manufactured by Spencer-Kennedy Laboratories, Inc., 186 Massachusetts Avenue, Cambridge 39, Mass., has been specifically designed for television use.

This single untuned amplifier has a bandwidth of 40 to 240 mc, and a gain of 20 db. into a 72 ohm unbalanced load, and 25 db. into a 300 ohm balanced line.

Capable of replacing up to twelve single channel TV or FM amplifiers, it has a transmission characteristic of



± 2 db, over the bandwidth and an impedance of 200 ohms. In addition to an integral power supply, transformers can be supplied to match 52, 72, and 93 ohm unbalanced and 300 ohm balanced lines.

Owing to the traveling wave circuit used, a tube failure does not mean amplifier failure, but only a loss of 0.7 db. in gain. Compact and simple in construction, the Model 212TV amplifier can be safely left unattended over long periods of time in television distribution systems in hotels, apartment houses, restaurants, sales rooms, and television sets in fringe areas. Full data on this unit is available from Dept. RT at the Cambridge address

# TWO NEW ANTENNAS

Two completely new antenna models, the "Versacone" and the "Jacknife" have been unveiled by Radio Merchandise Sales, Inc., of 550 Westchester Avenue, New York 55.

The "Versacone" is a conical, allchannel antenna which is readily adaptable in various arrays by the simple shifting of rods in the reflector and insulator plates.

The "Jacknife" model was designed to provide a completely pre-assembled, all-channel antenna that has no loose parts and requires no manipulation of the rods, in conical, folded, and straight dipole models.

# ALL-ALUMINUM CONICALS

JFD Manufacturing Co., Inc. of 6101 Sixteenth Avenue, Brooklyn 4, New York is currently in production on a newly-designed, all-aluminum conical antenna which has been named the "Commandair."

The antenna features heavy-duty element brackets with extra-long gripping surfaces for secure anchoring of elements, all-aluminum, corrosion-resistant construction for greater stamina and longer life, elements of heavy-wall aluminum tubing for added

pendous! Gigantic! Colossal

# ren for \$1.00. OROIDAL COIL


Any Network Problem
SHARP CUT-OFF
LOW INSERTION LOSS
HIGHEST "Q"
1000 CYCLE AUDIO FILTERS
1000 CYCLE AUDIO FILTERS
1000 CYCLE AUDIO FILTERS
1000 CYCLE AUDIO FILTERS
1000 CYCLE AUDIO FILTERS to Any Network Problem

\$2.00

# . P.M. SPEAKERS



# HEAT GUN

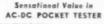



RT 1579 WITH TUBES. DIAGRAM AND PARTS LIST

\$14.95

# THE BUFRAD SECTIONAL TOWER

# "DRILLMASTER" ELECTRIC DRILL

# POWER RHEOSTAT



# SOS EMERGENCY TRANSMITTER

# ANTENNA

SIGNAL GENERATOR

\$9.95

# BARGAINS



\$5.95

T-32 MIKE With desh









# Tuning Turret

\$1.25 each. for \$2.00.

219-221 Genesee St., Dept. RN-2 BUFFALO 3.

# WE WILL PAY CASH

for SCR284, BC654, PEto3, BC348, BC312, BC222, BC324, and BC342 receivers, SCH522 and Rt 610 transmitters. 150 are especially interested any factory, dealer or other outlet submitting a list of surplus electronic equipment for us to bid on.

# DELUXE SUPERHET A.C.-D.C. RADIO KIT



Extra high qualin kil form with complete instruc-

1 n c l u d e 1 12RA6, 12RE6, 50R5 & 25W4. ceives broadcast band from \$50 to

\$12.95 or 2 for

BUFFALO RADIO SUPPLY,

# IN DETROIT IT'S AARON

6 finance 6 L.M. 27 dual tameps 1 set are weenings. Sparse for HC 375 Xmutter contains 8 feeding 2 finance 12 force links 4 weinings 6 pt 128 fal varietish.
--

	FREQUENCY METER 8C 221 Q - with proper map by for
	FREQUENCY METER CAVITY TYPE BC-308-0 \$29.00
l	RADIO COMPASS R.S ARN.7 and MN.76 10 S18 00
l	ARK or BC-966-A IFF RCVR & KMTR with 14 lutes & dynamidar-complete practically resembled from \$5.95
١	idynamidor same as a speed motor lenny advertised for \$5, 35 are give you 14 tubes dynamidor & other medial items for the same proces
l	R. I ARR-I HOMING RCVR Jon. RADIO NEWS Julie how to convert this rese, he history, convertes for use
l	well mill like now, never here mant will, 4 accept
١	have been exposed to unallist-never tierd-out be
	RE-LA ARR-1 Junction box 12 of 24 YDC containing

ADMIRAL TV SET CHASSIS continue plate	Dile
14 pratrot maket & 8 total worket curious	s. More
formerous condenser, after & other to	
rubuits evolved rutcoits front & Just an	
with sub-pasewbly lower charges 7" g3:	
Willie with Benefit of House, chieseste,	
ruttoute for 2 pourout takes & lot where	50.41
Both chassis, less abor., but with hover	6.1 R1

BC-347 INTERPHONE AMPLIFIER contains	SC SE 75
MELNONE REPORTS AND MEDINE YOU'LE L. G. M. P. L. F. L. R. R. L.	
V-100 cy-neatly new	51.91
RC-1141 AMPLIETER this amplifure is used	
BC 623 Mine-Delector-row, with tules I	67.05
SERVO AMPLIFIER Irus lutura conduino	9.8.91
would struct a archete d our makeles	
hisotheds of other seeful parts	6.1.00
G.E. WIEN BRIDGE SERVO AMPLIFIER	
at orne bills 10,000 H choice 2 & 4 Mi	
account no cassent approx 10 lb.	5.9.95
BC 741 A INDICATOR	
deliminate of other busine barries over	5.29.91
and others	519.9
JE: 1806-Pl tunes-surv has scope tobe	59.0
tule	55.9
R 29 APS-2C 37 takes including 1 CTPT-1	
hibra with blower motor etc. over in crafts	5.10.9
RADIO MODULATOR BC ISSA	84.9

		COMMAN				
RC-442				. 3	8 2	
					E	
BC-453	Here				12	. 1
BC 454					6	
		- 1 2 V O	Similar		2	
		out the			6	
NC 457					6.	п
					17	
BC-650						
ET-234	N				1	
					- 1	

RADAR INDICATOR BC 704-A-1-	
ANTO-With I tures less 5" CHT-moles	
scope to be setting word reset Board	Dre Suns
ATB RADIO KMTR CRV-52213	54.45
did byte to from her asset at the	
817	929 95
BC-645-A citie tunit now in Parties	812.95
ALTIMETER BY APPLI - 1 111 111 111 1111	
father-old I may provide well-box-d	
BC 357-BEACON RCVR	53.95
BC-301 RCVR	81.95
BC-733 LOCALIZER RCVR   11 11 MC-1	
	56.95
AN CRW 2 VHF RCVR - contains it lides of	
play in our and recurition return only	55.99
AN ARQ 7 (XA 2) SEARCH REVE & JAMM	NG XNTH
he one post-17 tones including was a	- J   MILT -
Alo VAC or TRUST VIOLE 24 VDC	2407.00
TRANSMITTER BC 410 and with faller	549.23
RECEIVER BC 228 and with biles	
COIL UNIT C-439-A In the Bit All	
STOR BAT A. STORY ATTACK BATT	50.75
STEP DOWN TRANSFORMER to morel to	
martin throat citate-115 V per 11	The state of
or that for 24 h supply	88.05
CONSTANT VOLTAGE TRANSFORMER	99.99
THE COUNTY OF THE CASE OF THE	
	50.05
WILLARD POWER PACK - by butters Ive V	
BIG Table and Pic in him	82.00
VIBRATOR POWER SUPPLY PE 157	half perch
softs 4 light	87.05
TELEPHONE RINGER BOX AMERICAN FOR	
carsonard but good were nord	top armord
EXTENSION CORDS PL 11 4 2	600
EXTENSION CORDS BUT PL 33 & 3	6. 20 ph-se-
1 11 35c 1 11 60c 8 11	75
VT 127 CERAMIC TUBE SOCKETS	97
VT 127 CERAMIC TUBE SOCKETS	For \$1,00

ATTENTION FOREIGN GOVERNMENTS
AND BASED OF THE ACT STABLES MADEST BASES OF THE ACT OF MICH. 1911,1000 Sec.

All items used, unless otherwise stated. Muhigan condents please and 3r ages fax. 25% with order, balance including postage C.O.D.

AARON ELECTRONIC SALES

strength, and dipole insulators made of bakelite for permanently stable anchoring of elements.

Three models of the "Commandair" are available, the Standard Conical, Conical with High-Frequency Element, and Conical with Three-Element Dipole. All are available in either single bay or ½ wavelength stacked arrays.

Literature describing the complete "Commandair" line is available either from the manufacturer, or JFD distributors and dealers.

### ALL-BAND CONICAL

The new "Mighty-X Skyhawk," introduced by Cornell-Dubilier Electric Corp. of South Plainfield, New Jersey, features efficiency on all bands plus only a five-minute assembly and installation job.

The new television antenna is available in two models, the LZX-2, a 2-bay package complete with an 8-foot mast, and the Model LZX, a single-bay package without a mast. Separate wavejumpers for stacking are available as accessories.

### LIGHTNING ARRESTER

A new twin-lead lightning arrester, designed to protect valuable television parts against lightning and static charges, has been introduced by JFD Manufacturing Co., Inc., of 6101 Sixteenth Avenue, Brooklyn 4, as the "safeTVguard."

This new arrester carries the Underwriters' Laboratories approval for both indoor and outdoor use. It can be installed on the mast, on a grounded pipe, wall or window sill, and other flat surfaces. No special tools or experience is required to install the arrester. The twin-lead is merely slipped into the horizontal slot on top of the arrester and tightened in place



by a pair of cap nuts and toothed washers.

The discharge contacts are sealed in rare gas tubes to dissipate charges that might cause damage. The leadin's 300 ohm impedance remains unchanged. Glazed porcelain construction resists temperature and humidity changes. All hardware is solid brass and nickel-plated for greater corrosion-resistance.

# BACE CONSOLE

Bace Television Corporation of South Hackensack, New Jersey has added a new line of 16- and 19-inch home receivers for 1950.

Among the features incorporated in the new line is a built-in antenna. The (Continued on page 159) when you use the **Audax** 

"The Standard by which Others Are Judged and Valued"

POLYPHASE...



ONE single unit plays ALL

your records "10 rager

and at less than the cost of ordinary

only \$11.70 not cost to yourbetieve it or not!

magnetic pick-ups

See it at your local distributor or write us

# AUDAK COMPANY

500 5th Ave., Dope 65. New York 18. Fire Music Reproducers Since 1915

# WONDERING ... ??

• how to adapt the new G.E. triple-play arisable reluctance settings to a Wester 156-27 changer? We agree — that this is the ideal combination no more plagging—in-and-out of lends each time you want to search from LP to standard and hock again, and only 6-8 grams

• But . . . recenting the controloge in a 55-fe bend in a treety ada and unless poor 'we sery hand; with foods, and have you the exist ones, and attention hand to restate the first one which the state of the first of the first of the first such that the property of your boy the castrologe from my 3-8. However, if you have the castrologe from my 3-8. However, if you have the castrologe from my 3-8. However, if you have the castrologe from my 3-8. However, if you have the castrologe from my 3-8. However, if you have the castrologe from my 3-8. However, if you have the castrologe from my 3-8. However, if you have the castrologe from my 3-8. However, if you had been with the changes. If you my a supplies the first the castrology is not been a first from the change of the first of the firs

That's Not All We're Selling . . .

# We've Got DIAMONDS Too!

• Not Jewelly, but payrhood prints for any and every purpling, styline or spline amending frame. Dut you know the flatbooks coloid completes by base limit (is to locard bird one descend country and the land (is to locard bird one descend country and and experience, units empresses and reverse collectors everywhere are being usual most that dimendinate which we have been an advantage of the to one limit of the land of the land of the collection.

 These diamond playlank points are \$15.00 tech, \$25.00 test. These are revalided in my fip radius from 1 mil to 3.5 mils. The microprocas Live require 1 mil radius tip.) Be sure to specify radius neared.

 If your cartridge has a non-removable needlefor example, the first G.F. religitatives, the Picker use 120 and 140 series, Brook PL-20s and PL-50s of -agent in the entire cartridge. With wellh.

 If your cartridge that a removable stylus or alytic assembly, send just the stylus or alytic assembly.

• The new 6.4: Imple-play reliefance cartridge mentioned in the first part of our at is also available with distanced style-on with one dismossi and

# TELEVEX

474 West 238th St. New York 63, N. Y.

# IX ANY RADIO

Simplified RADIO SERVICING By Comparison

Amazing New Invention Find radio faults with a new simplified method. Repair all radios in minutes instead of hours. Revolutionary, different Comparison technique permits you to do expert work almost

immediately. Most repairs can be made without test equipment. Simplified point-to-point, cross-reference, circuit suggestions locate faults quickly and easily.

# NO TESTERS NEEDED

Locate trouble in all sets without test equipment. Make needed tests, measure voltage, clock tubes, trace signal, using only a 5e resistor, con-denser, and crystal detector. Data on all radios, portables, AC-DC, intercoms, FM, P.A., etc. Free trial.



1942 1941 1940 1939 SUPREME Most-Often-Needed RADIO DIAGRAMS Each Manual has an average of 194 pages of diagrams, alignment data, voltage values, parts lists, and service hints: large size, 8½ 111. To order, see coupon→

RADIO

# Supreme Publications

# PICTURES, BLUE-PRINTS, CHARTS, TESTS, HINTS

Learn time-saving trouble-shooting short-cuts, find any radio fault with ease. Follow the tests shown on 24 large circuit blueprints. Over 1,000 practical repair hints. For all types of radios. Hundreds of simplified tests using a 5c resistor and any filter condenser. Introductory material for beginners and to serve as review for experienced radio men. Several chapters on test equipment. Complete plan in manual form, 63 job sheets, 84 pages, data on all tubes, large size: 8½x11 inches. Schematics, pictures, charts. Sold on no-risk trial. Use coupon to order.

# NO-RISK TRIAL ORDER COUPON

# SUPREME PUBLICATIONS, 3727 W. 13th St., Chicago 23, ILL.

Ship Simplified Radio Servicing consister as described at the special piece of only \$1.50, and also the discram manuals cleecked at ruld. You gnarantee complete satisfaction or will refund by money.

I am enclosing \$ send postpaid. Send C.O.D. I are enclosing \$ ... deposit,

Most-Often-Needed Radio Diagram Manuals Mew 1965 Manual, \$2.50

1.1948 PRICED AT ONLY \$2 1942 1941 EACH

11/26-11/38 Manual, \$2.50 SYCAMORE 4-7156

PASADENA 7, CALIF.

# PHOTOCON SALES

FEBRUARY SPECIALS

Please write for our 1950 complete catalog.

TUBE SPECIAL 5CP1—5" CATHODE HAY TIBE. 4 for 84-25. \$1.45 each SCR-522 TRANSMITTER SECSIVER, with takes. Excellent condition PLUGS—Set for SCR-522 NEW 3.75 PLUGS—24 Volt Dynamotor, NEW 4.50 SCR-522 EQUIPMENT with tubes.
PLUGS—Set for
PE-94C—24 V
Used \$2.50
BC-602 Control
BC-631 Jack R
AN-104A Anten
NEW STILL sed \$2.50 SFW 4.50 602 Centrol Bax SFW 95 601 Jack Box SFW 79 1044 Abrema CFW STEEL \$1.95 COPPER 2.95

END POWERED HEAD AND CHEST SET.
Made by Automatic Elec. Co., PAR \$11.00
NEW—EACH 5.95

ner, and batteries 641C AMPLIFTER only

# BASSETT AIRCRAFT RADIOS & ACCESS Two Way Radio Freq. 3105 K.C. ALL NEW EQUIPMENT

MC6-11, Watt Trans-Heer, Tubes, cristal, buttery case, autenna MC4H-sk Watt Trans-Heer, Tubes, cristal, schember, autenna, 12 witts MESA Reserver Range, weather and tower 13.50 MCC1 Aircraft Microphone HEADSET and PLUG MODEL TH 15-Trailing Antenna Wice Set

MELLER, Model 243 for use 250 AUE 224 nagareto. Shred 0-2,000 R.P.M. E4160 211 BILAND NEW \$17.50 RestOn TACHOMETER GENERATOR, Model 224, Tepe C GOOD USER 16.75 (C-64-TARGET RECEIVER—3 Channel 250 AUE 250 AU

remote, butters case, antenna 68-73
MCROTERIOR CONTROL CONTROL

-103 DYNAMOTOR POWER SEPPLY. COMPLETE with dynamotor, filter, re-ies unit, butters cables, and shock mount. Part of SCR-2\*1, BRAND NEW \$19.50 BU-820 Mablie FM Transcriver—P. O. SCR-610. Includes 10 meter band. Excellent condition with tabes. PE-120 Power supply with tabes—Exertient

Combination BC-520 and PE-120 Both for 14.95 FL-8 Range Filter NEW \$1.98 HS-27 HEADSET—BRAND NEW 8,000 5 Rings
27 HEADSIT—HEADS
ohm with ear pads
-30 HEADSIT—With ear pads
-30 HEADSIT—Complete with matching transformer, 6' eard and PL 55
NEW 1.95
98 | 1.95 | 1.95 | 1.95 | 1.95 |

T-17 HAND MIKE. USED \$1.95 ... NEW 3.00 MN-26C-BENDIX RADIO COMPASS, 156-1,500 K.C. Tobes-Excellent cond. ....\$17.50

TRANSFORMETS—c200 V. = 325 ma, accordary—casily C.T. for 3100.0-1100 = 650 ma.—primary 105f 110.15 V. 60 cycles—American Transformer Company — 15, 45 may 15, 50 ma.—15, 6 may 15, 50 ma.—15, 7 may 15, 50 ma.—15 V. A.C. primary accordance of the company of the co

INTERPHENE AMPLIFIES —BC-769—Ideal for Aircraft, booster for telephone system, etc. NEW \$4.50

400 Cycle INVERTER—G.E. SDZINJDA Input 27 V., 05 amps. Output 115 V 135 V.A. single phase 400 Cycle INVERTER—G.E. PK-218 In-27 V., 100 amps. Output 115 V 400 Cycle INVERTIR—G.F. Pr. 218 In-pat 27 V. 100 seaper forlight 115 V. 15.00 V.A. steple phase V. V. V. V. 5.00 Cycle Bloose and Mator—L. V. 800 Cycle Bloose and Mator—L. 15.0 4.700 R.P.M. 120 V. CAV-21772 J. 1.50 24 V. D.C. Bloose and Mator—L. 150 1.700 R.P.M. 120 V. CAV-21773 J. 1.50 1.700 R.P

dist. As excellent hader normal for constructing year own makers. NAV \$1.95 METER RECTIFIED, full wave midget Sciences to value, 20 ma. 29 APS-1 ALTIMETER, Complete. NAV 34.50 LF Transformers—let, 20 m or 3rd, from SCI-522, 12.000 h.t. from Core for rog, can be tuned to relations IF. Sciences and the control of the con-trol of the control of the control of the 2 for \$1.00.

-34\* Mounting Hase -34\* Oxfet Plag -34\* Mounting Rose and Oxfet Plag

### STORY | ST

Perform 52.50

# Make Those Finer Adjustments with

You can quickly adjust to the exact resistance wanted when you are experimenting and designing, or working with apparatus requiring adjustment to meet different line voltages, as well as general radio and television work. Add extra taps if you wish for voltage dividing or use as a multi-tap resistor. But, be sure the adjustable resistor you use carries the name Lectrohm, if you want dependable results. Ask your dealer by name-Lectrohm.

# LECTROHM ADJUSTABLE RESISTORS



EGTROKE

5907 Archer Avenue Chicago 38, Illin Division of National Lock Washer Co., Newark, N. J

# ONLY ONE MAGNETIC TAPE RECORDER . . .

that doubles your playing time and costs you less to operate. Before you buy ANY recorder, send for technical literature!

# AMPLIFIER CORP. OF AMERICA

# TELEVISION . ELECTRONICS

Learn Radio the Northwestern Way

- . BASIC RADIO
- RADIO SERVICE
- COMMUNICATIONS
- . INDUSTRIAL ELECTRONICS
- TELEVISION

Highly Trained Instructors • Modern Equip-ment • Specious Building and Grounds © I. and Reheb. Approved

NORTHWESTERN VOCATIONAL INST.



745 Grand Ave. ST. PAUL S MINN.

# RACON

Here's how you can bring the concert hall right into your own living room! Simply add this Racon tweeter to your present 12 or 15' cone speaker and enjoy to the full the luxurious, life-like brilliance of FM and wide range recordings

Response is clean and uniform to 12,000 cycles, with excellent usable output to 15,000 cycles. High frequency horn logarithmically expanded as two horns wide, uniform distribution pattern. V used with crossover network, will handle amplifiers rated to 25-30 watts. Input im-pedance 4-15 ohms. Dimensions 10% wide, 7 high 812 days high, 81, deep.

Cast aluminum throughout. Cutout template provided for easy flush mounting. Free wiring diagram and instructions to build an economical professional type 1,000cycle crossover network.

Listen to the Racon tweeter at your nearest distributor or write for free Catalog N





ALL RACON PRODUCTS ARE GUARANTEED FOR 18 MONTHS

# Crystal Diode Meter

(Continued from page 35)

which is transformed to a suitable impedance level for driving the detector circuit by the small pickup coil. Le. The detector circuit resembles that of a cascade voltage multiplier, but due to the impedance level at which the diodes operate, this multiplying action takes the form of an effective current gain of approximately 1.5 times, or slightly over 3 db. To assure effective multiplying action, condensers C12 and Ca are made sufficiently large so that the time constant of the diode load circuit is considerably longer than the period of one cycle of the signal voltage, at the lowest frequency to which the instrument will respond,

The indicating meter is a Weston Model 301 50-microampere instrument having a d.c. resistance of 1100 ohms. As the meter itself is of relatively low impedance and constitutes the total load into which the diodes operate the dynamic impedance of the latter at the lowest signal levels encountered may become only slightly less than the effective load resistance, and the rectification efficiency for small signals is impaired. For this reason, the diodes are connected in parallel pairs, with a resulting increase in forward conductance, and a material gain in over-all sensitivity. While pairing of the diodes in this manner may infer that accurate matching of diode units is required, it has been found that virtually any 1N34 units will provide satisfactory operation in this circuit.

The over-all increase in sensitivity over the conventional series diode detector circuit, afforded by the features described above, ranges from 3 db. at half meter scale to slightly over 6 db. at full scale. The actual gain obtained will depend to some extent upon the forward characteristics of the particular diodes used, and the figures given are representative of the performance to be expected with standard 1N34 units. While the dynamic range of the instrument is reduced somewhat by increasing the full scale sensitivity in this manner, it has been found that the range of slightly over 16 db. is adequate for most antenna gain measurements, and as will be pointed out, this dynamic range can be increased by the use of a capacitive voltage divider. With the particular set of diodes used in one model of this instrument, the full scale sensitivity was 150 millivolts. and a useful indication was obtained at a level of 20 millivolts.

In order to increase the versatility of the field strength meter, the over-all dynamic range is extended to 46 db. by including an attenuator network between the coupling circuit and the detector circuit. Because of its freedom from frequency effects and resistive loading of the tuned circuit, a capacitive ladder-type attenuator consisting of condensers  $C_1$  through  $C_{11}$  is used.

The series elements C. C., C. C. and C. C. are semi-variable, and are adjusted to provide a 10 db. change in level for each step of the scale multiplier switch, S.

As a purely precautionary measure, a meter shunting switch is included for use during initial adjustments. Due to the sensitivity of the instrument and the meter itself, it is readily possible to exceed the maximum rated current through the microammeter by several hundred per-cent when the device is used in the presence of a strong r.f. field. The shunting switch allows a full scale current multiplication of five times, and provides a measure of protection against accidental meter damage. It should be noted, however, that the scale calibration with the shunt connected will not be correct, and the instrument should not be relied upon to give direct power ratios under these conditions

# **Construction and Calibration**

Construction of this instrument is simplicity itself. Almost any physical arrangement may be used, but as a matter of convenience, the whole assembly may be built into a standard three-inch, sloping front meter case, The small components, condensers  $C_{\pm}$ and  $C_{ii}$ , resistors  $R_i$  and  $R_2$ , and the four 1N34 germanium diodes are mounted on a 2" x 3" terminal board, which, in turn, is secured to one side of the case near the rear panel. tuned coupling circuit,  $L_0$ ,  $L_0$ , and  $C_1$ , is mounted to the top flat portion of the box near one corner, and the tuning adjustment allowed to protrude from the top. The pin jack for the 2-foot rod antenna is located on the top of the box in the opposite corner. Switches S, and S, are placed on the lower apron in any convenient position. The adjustable calibrating condensers  $C_1$ ,  $C_4$ , and  $C_5$ , together with the remaining attenuator condensers, are mounted on the rear wall on a second terminal board, in such a position that the adjustments are accessible. Insofar as possible, all r.f. grounds are returned to a common point under one of the mounting screws for the coil assembly L. Lz. The underchassis view shows the general layout of the parts in the case.

While the particular instrument described was constructed specifically for the 3.5 to 4.0 megacycle band, other ranges may be substituted, and a possible further refinement might be to include some form of bandswitching integral with the unit. Since the frequency characteristics of the 1N34 diodes allow their use up to about 500 megacycles with little change in rectification efficiency, good performance may be expected from this instrument through the v.h.f. bands, although such operation has not been attempted. Coil winding data for the 3.5, 7, 14, and 28 megacycle bands is given in Table 1.

Calibration of the meter scale is best accomplished at a level of approximately one volt. Full scale (50 microamperes), is arbitrarily designated

# **BC-223 TRANSMITTER**



NEW: \$24.95

TUNING UNITS: TU 18 3 to 4 3 MC TU-25 4 5 to 5 2 MC Fither: NEW \$3.50 USED \$2.50

PE-125 POWER SUPPLY 1/DC-221 NEW \$9.95 | SED \$7.95 CABLE only-Trans

# **NEW TRANSFORMERS** And CHOKES

ALL FOLLOWING TRANSFORMERS-CASED 115 V.A.C. 60 CYCLE INPUT:

to o 750 V.A.C. (600 V.D.C. after at 250 MA.) Includes 6.3 V.A.C. and 5.0 V.A.C. winding at 4 T 625-0-625 V.A.C. (500 V.D.C. aft filter at 250 MA.) Includes 6.3 V.A.C. amps and 5.0 V.A.C. winding at

# TRANSFORMERS

CHOKES-CASED

NH-115-8 Henries at 500 MA, filter choke, 5,000 cent. \$9.95 116-5-20 Henry 500 MA, swinging theb \$9.95 17 S Henries at 700 MA. fliter choke, 7 feet section \$14.95 | S14.95 | NH-118-5-20 | Henries at 700 MA swinging choke. | 7.500 tell insulation | S14.95 | NH-121-15 | Henries at 250 MA | Elter choke | 1.500 | Coll insulation | 1.500 |

# COMMAND RECEIVERS TRANSMITTERS-ACCESSORIES:

	USL1).	51.W
BC-453 Resolver 130-250 K	\$12.95	
BC-155 Receive 6-0.1 MC	6.95	
BC-454 Receiver L- 6 MC	5.95	
Transfermer I (Com. Rev. Sec.	NH-109 above	\$3.00
	USED	NEW
BC-459 Trahonotter-7-9 M	C \$12.95	
BC-457 Transmitter 4 5.3		\$8.95
BC-458 Transmitter-5.3-1	MC 5.95	8.95
BC-456 Trans Medulator		
Transfermer 1.4 om, Trans. Se		
Choke-15 Hy. 250 MA. No. 3	VII 121	4.95

# CONDENSER ASSEMBLIES

Gang Condenser, 25 MMFD in 450 MMFD on. Size: Call a x2 Price.

# GEARED MOTOR

TRANSFORMER



# PM FIELD DYNAMOTORS: POWER SUPPLY

\$5.00

# PM FIELD DYNAMOTORS

#### NEW DYNAMOTORS:

BD-86 14 V 22 A logur suiper	100	y.	200 MA.
Used with BC 315, 191 for loss pers Print			\$7.95
BM-680 12 V input surput esse 6 V input; cuttant ess V, 15s MA	V.	210	SIA. Int.
Price			
Write-tell us your requirements in	Dy	nam	otors, etc.

### WHIP ANTENNA EQUIPMENT



K.	MF-132-1" heavy coil spring, 2" insulat-	irr.
	overall tength: 11%, Wt.: 2% Ba. Price	53.95
3.	MP-22 Spring action direction of brack	ot.
	4" a c" mounting. Price:	2.95
	MP-57-2" beavy cont spring, 5" insulator	3.95
	MP-48-I beart coil spring, I' insulator	
	MP-12-2 brave coil spring, 8" insulator	
	MP-47 T forget roll spring, 9" invalutes	

Tubular steel, copper reseted, painted 3 to screen type. MS-53 can be used to length, with MS-52-51-50-49 for taper, section.	make any
BAG BG-56 f varrying 5 mast sections	
BC-1206 RECEIVER-SETCHELL-CA	RLSON:
5 Tubes, 24-28 VDC 200-400 KC, IF Fre-	
Size 5 x4 xv. Price, LN.	26.95

# BC-645-A TRANSCEIVER-ALSO 110 VOLT TRANSFORMER AND CHOKE

12 Tube Transcriver, ideal for emission in 400 MC. Prequency coverage 425 to 500 MC. With conversion partnersions. \$14.95 Price New and Bloxed. 10 Vol. 100 Cycle in the conversion of the MC of the Cycle in the conversion of the MC of the Cycle in the
ADI 0 V. AC. 6 amps and 5 V. 5 amps. No. NH-045 CHOKE-15 III 150 MA, Order No. NH-686 2.95
SELSYN TRANSMITTER AND INDICATOR SYS-
TEM libral for antenna direction indicator to remote position. Complete with Autom Trans. Taki In- dicator, Transformer, and instructions. \$6,75 Automyn Trans. univ \$2.95. Plus #1-81; \$1.00

# ADDITIONAL "SPECIALS"

SELSYN'S 27 U-TH248-110 V, 60 cycle & Pair	
FT SET MOUNTING DARF CRE-GOA & SON'S & 683 s. Friest NEW . \$9.45 USED.	
Cable-4 Conductor, strictured, 50 Ft. length.	2.00

Cable-4 Conductor, strictured, 70 Ft. Jergth		
PERSONAL CARLEST SEVEN AND PARKS NO. 20 AWILL	700.1	
2 word, especiately alreaded within the outer spice	24 1	
all I conductors Innomated rotate nongetid, I		
	50.0	
CARLS CO., 2007 Conc. S.R. Willer, wholested RC 15 ft.	D.0	9.0
CABLE-2 p in wire, righter covered-get ft.	10.1	
	0.0.1	
R-Londonter Cable-unshielded. Per foot	1	0.0
Cable 1-16-312 w PL-50-61 or 64 Phars. Ex.	30.7	75
Tuning Unit / BC-171 Th-8-7-8-9-10-22-26. Ex-	3.1	
GN-ab benefited	3.1	OΟ
Log & Seat Ass'y, frhand progrators	8	7 %
Crank for hand generators Each		75
BC-357 Marker Beares (used)	25.1	20
Inc364 Market Beacon, Jess tube.	2.4	10.70
BC-047 Accordant Cook less tube		79
THE COST SPORT DOWN FROM THE PERSON		12

# MARK II B-19 TRANSMITTER AND RECEIVING SET

15 TUBES 2-8 MC., 240 MC., AND INTERCOM. IDEAL FOR MOBILE OR STATIONARY USE!



alts and receives 2 to 8 MC. Phone, C.W. and M.C.W. 25 Wa elilator Control. Transmits and receives 240 MC. Phone. At Company and Provinces with 15 Tubes, Heads \$59.50 USED (Tested)

Minimum Order \$2.00 . Prices F.O.B., Lima . 25% Deposit en C.O.D. Orde

# **FACTORY TO YOU** DIRECT!

Ertified



" KIT .. \$5950 \$8050 WITH TURES

This kit can be used with 10' electrostatic tube without any changes This kit includes a 12 channol tuner

Money Back Guarantee-Buy it, Inspect it, it you don't think it's the best buy on the marketreturn unused within five days and your money will be refunded.

B. New York, 20% deposit with order IMMEDIATE DELIVERY



# RADAR, COMMUNICATIONS

# SONAR TECHNICIANS W-A-N-T-E-D

# For Overseas Assignments

Technical Qualifications:

- 1. At least 3 years practical experience in installation and maintenance.
- 2. Navy veterans ETM 1/c or higher.
- 3. Army veterans TECH/SGT or

# Personal Qualifications:

- 1. Age, over 22-must pass physical examination
- 2. Ability to assume responsibility.
- 3. Must stand thorough character investigation.
- 4. Willing to go overseas for 1 vear.

Base pay, Bonus, Living Allowance, Vacation add-up to \$7,000.00 per year. Permanent connection with company possible

> Apply by Writing to D-4, P.O. Box 3575, Philadelphia 22, Pa.

Men qualified in RADAR COMMUNICATIONS or SONAR give complete history. Interview will be arranged for successful applicants.

as zero db. The input level is reduced in one db. steps from that required to produce full scale deflection, and the corresponding current values recorded. It will be found that the resulting db. scale will be approximately linear down to the -10 db. point, or about 5 microamperes, below which the calibration becomes cramped. A scale reading to -16 db. is, however, quite practical. The range multiplier condensers may then be adjusted to produce -10, -20, and -30 db, attenuation by increasing the input level accordingly.

In conclusion, one point in connection with the use of any field strength meter for antenna measurements might be brought out. Inasmuch as a radiating system sets up a strong magnetic field which surrounds the wire for a distance of 14 wavelength and attenuates rapidly beyond, it is advisable for best accuracy to locate a field indicating instrument outside of this 14 wavelength limit. At the lower frequencies, i.e., 4.0 megacycles or so, this means that the field strength meter should be located a minimum of perhaps 75 to 100 feet from the plane of the antenna. The sensitivity of the instrument described is such that, with a pickup antenna slightly over 2-feet long, a usable indication can be obtained at a distance of 150 feet from a 25 watt mobile transmitter on 3.9 megacycles, and it is considered that the measurements taken in this manner are entirely valid. -30-


# SOLDERING TO SHIELDED WIRE

By HUGH LINEBACK Ass't Prof., Oklahoma A. & M.

WHEN a shielded cable is cut, one of the most difficult soldering tasks is to tin the shield, or to solder a ground wire to it without damaging the insulation. Of course, it is usually better to fish the wire out of the shield by spreading the weave several inches back from the end, but when this cannot be done the method shown in Fig. I can be used.

The shield is pushed back a little to loosen the weave, and a cylinder of cardboard inserted around the wires Insulating paper used in motors and transformers is excellent for this. Then when the solder has cooled the cylinder is removed.

Fig. 1.

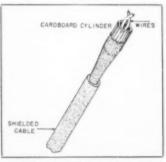

With the If You Don't See Purchase of \$3 What You Want SEND FOR OUR or More BIG 16 PAGE WITH ORDERS BY MAIL BARGAIN BULLETIN HRU-24-28 Volt at 70 Amps. DC Power Supply Gaso \$6995 line Engine Generator with Electric Starter. A thousand uses. This is in Excellent Condition

Cable—6 wire No. 16, glass insul. shielded, plastic covered for beam control. 12c ft. - 100 ft. \$10.00 Wire, shielded No. 20 stranded 100 ft. for \$1.50 Twin Lead 300 ohm Amphenol per C \$1.95 per hund. \$6.95 Twin Lead 75-ohm Amphenol Toggle Switch, center off, - S.P.D.T. 4 for \$1.00 Toggle Switch, SPST & spring return. 4 for 75c Toggle Switch, heavy duty 12 amp. 125V ea. 49c CO-AX Amphenol—Beaded No. 72-20 per ft. 4c 3-SPEED MOTOR - 1/20th H.P. 115V 60-cycle AC motor with integral gear box having three 1/4" drive shafts turning simultaneously at the

following speeds: 4000 RPM Grinders. Buffers, Slow Speed tools, 25 & 5 RPM Sant \$795

1000 USES AROUND THE WORKSHOP DOW TRADING CO. 70 W. Union Street, Pasadena, California
Phones Pasadena SY. 3-8281 - L.A. RY. 1-7944

ANTENNA MASTS 35-foot high with guys. Complete, 7 Sections 5'-6" Long. 11/2 O.D. Steel-Alloy. Painted. Brand New. Bargain. \$19.95 ANTENNA WIRE - 250 ft. 10 gauge 7 strands No. 18 Phosphor Bronze. \$1.95 ANTENNA WIRE - 1000 ft. No. 14 solid Copperweld \$6.96. 2200 ft. coils \$12.95 CO-AX RG34—71 OHM Xmitting - New 50 foot coils - Bargain NEW B & W 500-Watt center tapped ceramic bars, bana

na plugs. 7 types: 15-45 8.0-11.0 45-5.7 11.0-14.0 5.7-8.0 14.0-18.0 Specify frequency oil desired. BARGAIN - Either Type

# International Short-Wave

(Continued from page 96)

nel of 5.960, heard in the United Kingdom 1600-1700.

Ceylon-Colombo, 4.900, heard with BBC news relay 1100. (Pearce, England) Closes 1200 with "God Save the King."

China-"Voice of Free China," Taipeh, Taiwan (Formosa), has moved from 11.725 to 11.800, with schedule of around 0500-1130; since the capital of Nationalist China is now at Taipeh, it is likely that this outlet-announced at BED2 and BED4-will add English to its broadcasts. Most likely times for it to carry English news are 0900, 1100. Balbi, Calif., says the 2300-0100 daily beam to the U.S. on 15.235 has been heard lately at better level; news 2300-2320, commentary 2330; last hour is in Chinese. Here in the East there is QRM from Tokyo on same frequency.

Shanghai; still heard on 5.985 but does not take English 0830. (Dilg.

Former Peiping, 10.260, now announces as Pekin, (Dilf, Calif,) Still heard in East signing on 1800. (Sutton, Ohio) Has terrific CWQRM and other interference.

Curacao-Contrary to widely-circulated reports abroad, PJC-2, Willemstad, was still on 5.010, heard 1840, at the time this was compiled. Could not be found on 7.250 to which channel it had been reported to have moved. (Hankins, Pa.)

Cyprus - Sharq-al-adna, 6.170, Limassol, noted 0000 in Arabic. (Gainer, Maryland) The 9.650 channel noted around same time at weak level. (Far-Ga.) The 6,790 channel heard 1400-1445 in Newfoundland. (Peddle)

Denmark-An official of OZF, 9.520, Copenhagen, informed Worris, N. Y., that arrangements have been made for the last 30 minutes of the daily 2200-2230 transmission to be "fixed" English program. This has been effected. The station asks for reports and comments on the new arrangement. The girl announcer, Marianne, in introducing this last half hour says it will be entirely in English "and not a word in Danish"; at sign-off she concludes with her customary "Glad to have you listen."

Dominican Republic-HI4T, 5.970, and HI2T, 9.735, now sign-off 2300, one hour earlier than formerly. (Balbi,

Finland-Helsinki informs Halvorsen. Norway, its schedule includes 1925-1935 news and press review in English on 17.800 to South America. and Southwestern Europe; 0715-0725 news and press review in English on 6.120, 9.555, 15.190, 17.800, to U.S.A., South America, and Southwestern Europe; these are weekdays only; 1245-1255 news and press review in French on 17.800 to South America and Southwestern Europe, and to same area in French 1700-1715 on 17.800, 6.120. Re-

# KIDDIN'- PLATT'S PALE from PACKING



# **HEADSETS**—Excellent Buys!

with cord and plug, used condition rand New with ear p brand New with ear p brand New with sed and PLSI plus dome with dual place

### CORDS AND PLUGS



with PL 55 and JK

100



# OIL FILLED CONDENSERS

FILLER CHRISTIANS
Framous Makes Tall Society, 24,25
MED. Sono VIN
SAtherally Advertised, 2 MFD, 262
Framous Makes, 4 MFD, 29
Highest Quality 22847, 24
Highest Quality 22847, 22
Highest Quality 23847, 23
Highest Quality 23847, 23847
Highest Quality Highest Mu-f, Highest Mu-f. De 1.95

1 MFD, 400 Velts, Tubu-2.96

# MICROPHONES



therestone, 14 ft cord,

# 274-N COMMAND EQUIPMENT

Sensational Buys! 2.95



# TRANSMITTER-RECEIVER

Navy Model ABA-1 (CG-43AAG) Army Model SCR-515A known as the BC-645

450 MC-15 Tubes RIGINAL 4%. Contains 15 vine. 2-955, 1-WE-115A floor artist. 2-955, 1-WE-115A floor artist.



BC-615 ANTENNA.

BC-645 TRANSMITTER-RECEIVER ONLY, Brand Nov. \$12.95 SELSYN INDICATOR

\$4.95

only 39c

# BEACON RECEIVER BC-1206-C



#### Multitester Foundation BIAS METER 1-97A

of 1, 10, 100, 1500 cott.

COMPLETE BRAND NEW \$3.95 WESTON Model 528. 0 to 7 and 0 to 15 mmp A.C. 20 limit the with leather rane leads and clips WESTON Model 340, if genter, thus miles said said WESTON Model 340, if genter, thus miles said said.



#### FIELD TELEPHONES

\$6.95 LIKE-NEW FIELD TELE-

# DYNAMOTORS



Type 1056 3 A 24 V in 2 INVESTED IT DOG DE V. IN.

# **FILTERS**

FLS Lary Q Radio Pitter Unit, high impedance NLW FLS Prints with Plan and Inc. Co. 1



### TYPE MN-20E ROTATABLE LOOP UNIT

W illameter, used with MN-28 Companies and RA 10DB. Manufactured by Bon-TERRIFIC RUYS \$11.95

# TUBES

# BC-223 TRANSMITTER

to of 2000 to Alex Kit', Complete with all Tun Units. Hereaumended for use of district share from operation. \$27.00 NEW -Uniginal Care \$27.95

BHAND \$22.95 USED. EXCEL- \$14.95

80-71 C Line Postable and speek as \$14.95 ANNOUNCING LUCKY PLATT CONTEST WINNERS

CONGRATULATIONS FROM PLATT!

WRITE FOR OUR FREE CIRCULAR!

Minimum Order \$2.00

PLATT ELECTRONICS CORP. DEPT. A. 489 BROOME ST., NEW YORK 13, N. Y PHONES: RE 2-8177 and WO 4-2915



IMMEDIATE TUBES CARTONED GUARANTEED

SPECIAL QUANTITY DISCOUNT OFFER refer 25 or More Assorted Tubes and Deduct he from a Price of Each Tube.

2034/RK34 IR36 IR36 IR36 IR36 IR36 IR36 IR36 IR36	GSQ7GT 6V6GT 6V6GT 6X4 8X5GT 12AV6 12AV6 12AV6 12AX7 1245GT 1247GT 1247GT 1247GT 125A7	GS578T GVB GVB GVB GVB GVB GVB GVB GVB	6776 7A7 7C8 7C8 1486 50C5 5016 2051 75 576 £cch 0A2 11.A4 11.A4 11.C5 11.C5 11.N5 11.N6 11.N6 11.N6
18-25 6-44 11-140 19-2 Each 19-3 29-3 29-2 29-2 28-2 28-2 28-2 28-2 28-2 28-2	6V6GT 6X4 6X5GT 12AV6 12AV6 12AX7 1245GT 1247GT 1247GT 125A7GT 12	6V60 7A4/XXA 785:1201 7K5:1201 7K7:1201 7K7:1201 12AU7 12BE0 12BE0 12SE0	7CS 7F7 7Q7 7Q7 12CB 14B6 50CS 50CS 50C6 2051 75 9C Each 0A2 0A2 1LA4 1LD5 1LD5 1LD5 1LD5 1LN5 1NGG
1644 E1148 194 Each 199 Koo 29c Each 227 227 6C4 6C4 6C7 6U7G 12A6 12A6 12A6 12A6 12A6 12A6 12A6 12A6	6X4 6X56T 12AV6 12AV6 12AX7 1245GT 1247GT 1247GT 1247GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 135A6 135	7 A4/XXL 786 / 1201 785 / 1201 787 / 1201 787 / 1201 1201 1201 1201 1201 1201 1201 1201	787 797 12CB 14B6 50C5 50L6 2051 75 \$9c Each 0A2 024 1LA4 1LCG 1LD5 1LE3 1LN5 1NGG
198 Each 199 Each 290 Each 27 27 28 28 20 24 20 24 24 26 24 36 36	8X567 12AV6 12AV6 12AV6 12AV7 12I5GT 12IFGT 12IFGT 12XFGT 12SAF0	785 1.201 785 1.201 787 1.2A76 1.2A47 1.2B46 1.2517GT 1.2E3 1.4M7 251.6GY 3.2L7GT 3.4 3.5Z4GT 4.3 4.6 5.3 5.6	797 12CB 14BB 50C5 50L6 2091 75 59C Each 0A2 024 1LA4 1LC6 1LC5 1LE3 1LE3 1LE3 1LE3 1LE3 1T4
19c Each (99 29c Each 2A7 2A7 2K2 6C4 12A6 12A6 12A6 12A6 12A6 12A6 36	12AV6 12AV6 12AX7 1245GT 1247GT 1247GT 1247GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 125A7GT 13A7GT	785 1201 787 1240 1240 1280 1286 1286 12517GT 1223 1407 2516GT 3217GT 3217GT 347 3524GT 43 3524GT 43 56	1406 50C5 50L6 2051 75 59c Egch 0A2 0Z4 1LA4 1LC6 1LD5 1LE3 1LN5 1NGG 1T4
19e Each  199  29c Each  2A7  2212  5C4  5C4  12A6  12A6GT  12P5GT  26	12AV6 12AX7 12J5G7 12J7GT 12K7GT 12K7GT 12SA7GT 12SA7GT 12SA7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SC7G	7 M 7 1 2 A U 7 1 2 B A 6 1 2 B E 6 1 2 5 1 7 G T 1 2 C 3 1 4 M 7 2 5 L 6 G T 3 2 L 7 G T 3 4 4 3 5 2 4 G T 4 3 5 6 5 6 5 6 6 7 6 7 7 6 7 7 7 7 7 8 7 8 7 8 7 8 7 8 7 8 7 8 7 8	1486 SOCS SOL6 2051 75 \$9c Each OA2 OZ4 1LA4 1LC6 1LD5 1LE3 1LN5 1NGC 174
799 29c Each 2A7 2X2 6C4 6S47GT 6S47GT 12A6GT 12A6GT 12PSGT 26	12AX7 12J5G7 12J7G7 12J7G7 12K7GF 12Q7GT 12SA7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SC7	12AT6 12AU7 12BA6 12BE6 12SE7 12517GT 12Z3 14M7 25L6GT 32L7GT 34 35Z4GT 43 46 53 56	SOCS SOL6 2091 75 59c Egch 0A2 1LA4 1LC6 1LD5 1LE3 1LNS 1NGG 1T4
V99 X90 29c Each 2A7 2X2 6C4 65M7GT 6U7G 12A6 12A6 12A6 12A5 12FSGT 26	12J567 12J7GT 12K7GT 12K7GT 12K7GT 12SA7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SQ7GT 12S	12AU7 12BE6 12BE6 12BE6 12S17GT 12Z3 14M7 25L6GY 32L7GT 34 35Z4GT 43 46 53 56	9016 2091 75 59c Egch 0A2 0Z4 1LA4 1LC6 1LD5 1LD5 1LNS 1N6G 174
29c Eoch 2A7 2X2 2X2 6547 GT 6547 GT 12A6 12A6 12A6 12A6 12A6 12A6 13A6 36	12J7GT 12R7GT 12R7GT 12G7GT 12SA7GT 12SK7GT 12SK7GT 12SN7GT 12SQ7GT 12SQ7GT 12SQ2GT 25Z6GT 27 32	128A6 128E6 12517GT 1273 14M7 251.6GY 321.7GT 34 3574 3524GT 43 46 53	2051 75 59c Eqch 022 024 1LA4 1LC5 1LD5 1LE3 1LN5 1NGG
29c Each 2A7 2A7 2X2 5C4 5SH7GT 6U7G 12A6 12A6 12A6GT 12F5GT 26	12K7GT 12G7GT 12SA7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SQ7GT 12SQ7GT 12SQ7GT 19T8 24A 25Z6GT 27 32	1.28E6 1.2517GT 1.273 1.4M7 251.6GT 321.7GT 34 35Y4 35Z4GT 43 46 53 35	75 59c Eqch 0A2 0Z4 1LA4 1LC5 1LD5 1LNS 1NSG 1Y4
29c Each 2A7 2A7 2X2 5C4 5SH7GT 6U7G 12A6 12A6 12A6GT 12F5GT 26	12K7GT 12G7GT 12SA7GT 12SK7GT 12SK7GT 12SK7GT 12SK7GT 12SQ7GT 12SQ7GT 12SQ7GT 19T8 24A 25Z6GT 27 32	1.28E6 1.2517GT 1.273 1.4M7 251.6GT 321.7GT 34 35Y4 35Z4GT 43 46 53 35	75 59c Eqch 0A2 0Z4 1LA4 1LC5 1LD5 1LNS 1NSG 1Y4
29c Each  2A7  2X2  5C4  6SM7GT  6U7G  1 2A6  1 2A6GT  1 2FSGT  36	12Q7GT 12SA7GT 12SM7 12SM7GT 12SM7GT 12SM7GT 12SQ7GT 19T8 24A 25Z6GT 27 32 35/51	1.25J7GT 1.273 1.4M7 25L6GT 32L7GT 34 35Y4 35Z4GT 43 46 53 56	0A2 0Z4 1LA4 1LC6 1LD5 1LE3 1LNS 1NGG 1Y4
2A7 2X2 5C4 6SM7GT 6U7G 12A6 12A6GT 12FSGT 26	12SA7GT 12SM7 12SM7GT 12SK7GT 12SK7GT 12SQ7GT 12SQ7GT 19T8 24A 25Z6GT 27 35/51	12Z3 14M7 25L6GY 32L7GY 34 35Y4 35Y4 46 53 56	0A2 0Z4 1LA4 1LC6 1LD5 1LE3 1LN5 1N6G 1Y4
2A7 2X2 6C4 65H7GT 6U7G 12A6 12A6 12A8GT 12FSGT 26	12SM7GT 12SM7GT 12SL7GT 12SL7GT 12SN7GT 12SQ7GT 19TB 24A 25Z6GT 27 32 35/51	14M7 25L6GY 32L7GT 34 35Y4 35Z4GT 43 46 53	0A2 0Z4 1LA4 1LC6 1LD5 1LE3 1LN5 1N6G 1Y4
2X2 6C4 6SM7GT 6U7G 12A6 12A6GT 12FSGT 26	125K7GT 125E7GT 125K7GT 125K7GT 125K7GT 125K7GT 25K6GT 27 32 35 51	25L6GT 32L7GT 34 35Y4 35Z4GT 43 46 53 56	024 1LA4 1LC6 1LD5 1LE3 1LN5 1N6G
6C4 65M7GT 6U7G 12A6 12A6GT 12F5GT 26	125L7GT 125N7GT 125Q7GT 1978 24A 25Z6GT 27 32 35/51	32L7GT 34 35Y4 35Z4GT 43 46 53 56	024 1LA4 1LC6 1LD5 1LE3 1LN5 1N6G
65M7GT 6U7G 12A6 12A8GT 12FSGT 26	125N7GT 125Q7GT 1978 24A 25Z6GT 27 32	34 35Y4 35Z4GT 43 46 53	ILA4 ILCG ILDS ILE3 ILNS INGG IY4
6U7G 12A6 12A8GT 12FSGT 26	125Q7GT 1978 24A 25Z6GT 27 32 35/51	3574 3524GT 43 46 53 56	1LCG 1LD5 1LE3 1LN5 1NGG 1T4
12A6 12A8GT 12FSGT 26	1978 24A 25Z6GT 27 32 35/51	3524GT 43 46 53 56	1LDS 1LE3 1LNS 1NGG 174
12A6GT 12FSGT 26 36	24A 25Z6GY 27 32 35/51	43 46 53 56	1LDS 1LE3 1LNS 1NGG 174
12FSGT 26 36	25Z6GT 27 32 35/51	46 53 56	1LE3 1LNS 1NGG 1T4
1 2FSGT 26 36	27 32 35/51	53	ILNS INGG IT4
26 36	32 35/51	56	INGG 174
36	35/51		174
	35/51		
			SV4G
	35W4		6AB5G
	3525	50c Each	6AG5
	3526	BOG EGCH	684
	41		6BF6
		1	6BG6G
	5005	1ASGT	6BH6
	57	186	6.16
14	76	1C6G	618G
286	7.6	1676	6W4
486	80		6W6
	85	1D7G	6Y3
5046		108G	
5W4		1E7G	12A
5Y4G	45c Each	154	1.2AT7
GAR4		1F5G	1487
GAMG		1G4G	1407
GATE	185/266	1.G.5	1487
	11.4	LGGGT	22
	185	1H4G	50A5
	154	1H6G	701.7GT
	155	116G	
	ITSGT	304	49c Each
			SAC KOCK
	2A5	354	
	286	3V4	6AC7/1852
	387	5Z3	6AKS
6K6GT	GALS.	5Z4	117Z6GT
6K7GT	6B16	6A6	verrons
	6D7	6AQ5	00- F
	GFSGT	686G	89c Each
	6G6G	688	
	6P5GT	6D6	183GT 6016
	6SL7GT	SERG	6L6G

MINIMUM ORDER \$2.50. Send 25% deposit for all C.O.D. shippornia. Include sufficient postage, excess will be refunded. Orders without postage with he shipped express collect. All extent 1.0 H. way Vers.



# NEW RECEIVING TUBE INTERCHANGEABILITY CHART

Very latest \_\_complete data on direct interchangeability. It's SENCO'S way of greating New Customers and thanking old ones \_ . It's yours for the asking

Nothing to Buy ... Just fill in Coupen ... MAIL TODAY!

NAME

ADDRESS

ZONE STA

Radio Man Who Know SENCO

SENCO RADIO, INC., Dept. R 71 West Broadway, New York 17, N. Y. ports on these transmissions would be appreciated by the Finnish Broadcasting Corporation, Helsinki, Finland.

France—Paris, 6.145, heard in German 0030-0045, 0130-0145, fair level in California. (Balbi)

Paris has replaced 11.700 with 7.280 in parallel with 9.550 to North America (English) 1945-2000. (Parsons, Pa., Arthur. W. Va., others)

French Equatorial Africa-Brazzaville, 17.837, noted 1545 with English.

(Cox. Delaware)

French Indo-China—Saigon, 11.78 heard in Britain from 1815 with news in French (Le Journal parle), recordings; news in English 1845-1900, then program in Chinese or Ammanese. (Pearce) Heard here in West Virginia signing on 1800 with "La Marseillaise"; has bad CWQRM; should have English both at 1845, 1930.

Germany — DTSP, 15.280, Munich, has winter schedule of 1045-1100 point-to-point with the "Voice of America" in New York; radio and press review in English. (Grove, III.) Northwest German Radio, 7.290, Hamburg, is on the air daily 2300-0430, 0600-1900; reports requested, will verify by letter and send photograph of transmitter; QRA is NWDR, Rothenbaumchausse 132, Hamburg 13, Germany. (ISWC, London)

Radio Sweden says the American Forces Network, Munich, is heard on approximately 5.880 from 1215-1330 in parallel with m.w. stations of A.F.N.

This is not confirmed.

Gold Coast—ZOY, 4.915, Accra, heard around 1245 in Britain with weather forecast issued by the Gold Coast Meteorological Survey, followed by news; 1255 has popular melodies; then the announcement, "You have been listening to a broadcast on 61.04 meters from Accra, Gold Coast; good night"; signs with "God Save the King"; QRA is Senior Programmes Officer, Radio Accra, P. O. Box 745, Accra, Gold Coast. (ISWC, London)

Greenland—Godthaab, 5.942, is heard in Norway 1630-1740 but is weak; announcement in Danish is "God Aften. Her er Grenlands Radio." Program consists of news, weather forecast, music. No English, (Halvorsen)

Greece—Athens, 9.607, heard around 0200 with recordings; news in Greek 0225; Home Service. (Pearce, England) A Greek Communist outlet has been heard on 9.455 at 1400 (Bluman, Israel) Larissa, 6.745, heard in Newfoundland signing off 1600. (Peddle)

Guatemala—TGWA, Guatemala Clty, has returned to the air. It appears to run on 15.17 from 0725 to around 1500 or later on weekdays; Sunday sign-off is around 0900. Is using 9.763.6 (measured by Oskay, N. J.) from around 1800 to 2400 or later. Has many programs of beautiful marimba music. I wrote this station for details as soon as it returned to the air, but received (immediately) only a QSL card. The station listed Radio Nacional de Guatemala, "La Voz de Guatemala, "Emisores: TGW-TGWA-TGWB-TGWC.

Haiti-4VRW, Port-au-Prince, after



BROOKLYN SS. N.

broadcasting for years on 10.135 appears to have settled down on 9.790; heard mornings and evenings (EST) with good signal. (Ferguson, N. C.) Signs off 2145. (Grove, Ill.) Widely reported. Recently sent schedule of weekdays 0600-0830, 1200-1500, 1800-2200; Sundays 1200-1700; power listed 1.4 kw., but may have increased it by now. QRA is P. O. Box A-117, Port-au-Prince, Haiti. (Slutter, Pa.)

Honduras-HRA, 9.034, Tegucigalpa, noted evenings (EST) on this channel, usually with QRM from COBZ, 9.026. (Ferguson, N. C.)

Hungary-Widely reported is Budapest, 6.247.4 and 9.834.6 (measured by Oskay, N. J.) with news 1630; runs to 1800.

India - The Overseas transmission 1000-1040 is now on 15.29, 11.85 with news 1030: the 1400-1500 period is announced for 7.240, 9.620, 11.760, 11.850. (Pearce, England) Noted on 9.565 with news 2130, 2230. (Stark, Texas) The 15.19 channel appears to have been brought back into use, noted 2130 with news. (Fargo, Ga.) At long last, AIR, Delhi, is sending out a QSL card instead of verification letter. (Pearce, England) The card is blue and orange with a drawing of a station on (Cox. Delaware) AIR noted on 15.16, 17.78, at 2315 with news, (Balbi, Calif.) AIR, 4.84, Bombay, heard 1115-1125 with talk (English), then Indian program to 1230 closedown with chimes for 2300 IST; Calcutta, 4.880. heard from around 1030 to closedown 1200, mostly native. (Pearce, England)

Indonesia-YDA-2, 6.170, heard after 0530: chimes and station announcement 0630; in native. An Indonesian is heard on 4.85 at 1000-1030, (Balbi, Calif.

Iran-GDX-aren, Sweden, says EQB, 6.155, Teheran, has news 2230-2300.

Israel-At the time this was compiled, Kol-Israel, Tel-Aviv, was using approximately 8 900 afternoons (EST) to 1630 closedown; news 1530. By this time, it is likely that this channel (listed 9.000) will be in use by the World Zionist Organization for beaming overseas broadcasts from Jerusa-lem to World Jewry. Will beam to Europe, to North America, and other areas, and will use several languages including English. I hope to have full details next month. In the meantime, reports may be sent to P. O. Box 17, Hakirya, Israel. Israeli outlets now sign on at 2330, including Tel-Aviv. 6.830, and Haifa, 8.170; news 0700,

Italy-Current schedules of Radio Italiana from Rome are 1930-2055, 0500-0530, 0830-1300 on 11.810, 15.120; 1205-1700 on 9.630, 11.810; 1710-1925 on 11.810, 15.120. (Radio Sweden)

Jamaica-ZQI, 4.950, Kingston, has improved signal 1600-1730; news 1715 and headline news just before closedown; operates on 3.480 at 1930-2200.

Japan-The Japanese Broadcasting Corporation lists these current schedules-Home Service-JKH, 7.257.5, 1525-0900; JKI, 4.910, 1525-1755, 0255-0900; JKI-2, 9.655, 1725-0245; JKJ,

FAN MAIL" for a Star Performer



2653 Int. 1, M. Nativida Manila, Philippines 31 August, 1949

Contleman:

I am a user of a number of Turner Microphones and I know just the right mike for me. My job requires rugged performance because the Philippine climate is very rainy at times, then excessively humid, then hot . . . . If a wrong kind of microphone is used, it is very sure of not lasting long. MODEL 99

The Turner 99 solved for me the problem of the right microphone. I have a mike of this type which was caught several times in sudden showers and believe me, it is still excellent if not perfect. These microphones are the only types I can find suited to my requirements. I recommend Turner microphones for quality and the best performance. Very truly yours,

> TOWAS M. TAGULAO Co-Owner, Sterling "AA" Sound Systems

Ask your dealer to show you the Turner 99 Write for Literature



# THE TURNER COMPANY

900 17th Street N. E., Cedar Rapids, Iowa

TURNER

List Price

\$34.00

IN CANADA: Canadian Marconi Co., Ltd. Montreal, P. Q., and branches

EXPORT: Ad. Auriema

89 Broad Street, New York 4, N. Y.

AUDIO (SOUND) ENGINEERING HOME STUDY TRAINING

HOLLYWOOD TECHNICAL INSTITUTE Giv. R.N. 4925 Santa Manica Blvd. Wolfywood 27, California

radio repairs FREE! Send penny postcard for big 12-page illus-trated FREE MANUAL. No Obligation FEILER ENGINEERING CO., Dept. IRNS



# **Electrical Training**

intensive 32 weeks' residence c in fundamentals of industrial electrical engineering, including radio and electronics. Extensive laboratory, shop work, drafting Prepares for electrical technician and engineering facturing, business machines, sales, service. G. I. approved. 57th year. 5. Catalog. Sept. 7603 TAKOMA AVI. WASHINGTON 12, D. C.

Learn how to simplify

# **COLLINS TUNER for 630TV**



AM and FM tuner, made by Collins Audio Products. Ats front of 630TV chassis, uses audia channel of TV set. Provides full AM range, all FM channels, and phono input. Slide-rule dial. Complete with instructions, connecting leads and set of tubes. \$40.50

# **BC-221 FREQUENCY** METER

These won't last long so order now for one of these famous freq meters. They are just like new, with original calibra-

tion charts. Range 125-20,000 kc, with crystal check points in all ranges. Camplete with crystal and tubes.

# Harvey Special Price \$79.50 PENTRON TAPE RECORDER



Full hour capacity on 1200 ft. reel, 71/2" per second tope speed. Capstan drive with minimum wow and flutter, 80 to 8000 cycles, dual tracking, supersonic erase. Inputs for microphone, FM, external radio or phono, Neon level indicator, Supplied with crystal mike, 5" reel of tape, etc. In sturdy carrying case \$100.34 129.55 With built in radio

NOTE: All prices are Net, F.O.B. N.Y.C. and are subject to change without notice.

LUxemburg 2-1500 Telephone hrd (1) (0) (0) 103 West 43rd St., New York 18, N. Y.

7.285, 1555-2200; JKM, 4.930, 0325-0900; JKM-2, 9.695, 1555-2200. Overseas Service-JBD, 9.505, 0255-0900; JBD-2, 9.560, 0255-0900; JBD-3, 15.225, 1750-0230, and JBD-4, 15,235, 1750-0230. (Pearce, England)

The 6.005 outlet is heard irregularly after 0100. (Balbi, Calif.)

WLKS, 6.105, Kure, opens daily 1530. (DXSA News, South Australia) Kashmir-Srinagar, 4.865, is on the air 2130-2336, 0700-1030; on 7.270, 0100-0230. (Nordh, Sweden) The 4.865 channel heard in England 1030 with relay of AIR news from Delhi; native programs then to 1130, (Pearce)

Kenya Colony-New call for VQ7LO, Nairobi, is VQG1; frequency is 4.850 and BBC news is 1300, local news from the East African Standard 1315, closes

1400. (ISWC, London)

Korea-The North Korean (Communist-controlled) outlet on 4.500 heard from 0230, strong by 0330 on West Coast; 7.778 not heard lately, formerly was in parallel but with much weaker signal. (Balbi, Calif.) Fair signal in Louisiana on 4.500 at 0700. (Locke) Seoul, 2.510, So. Korea, good in California around 0900, (Dilg)

Lebanon Beirut, 8.036V, now appears to have English at 1000-1100 when concludes period with "Knightsbridge March" instead of former "Pack Up Your Troubles." (Pearce, England) Heard in Newfoundland 1340-1600 (Peddle)

Luxembourg - Radio Luxembourg, 6.090, now relays English from its l.w. outlet on Sundays 1615-1900, weekdays 1730-1900. (Short Wave News, London)

Malaya-Red Network of Radio Malaya, 4.780, Singapore, heard in England 0900 with Chinese; signed off 1030 with English and "God Save the King." (Pearce)

Manchuria-Mukden, approximately 3.500, weak but readable in California around 0900; takes relay from Pekin (10.260) at 0730-0830 but does not carry the English 0830. (Dilg)

Martinique - Overseas sources report Radio Martinique on 9.990 at 0100-0118, but this has not been con-

Mauritius - V3USE, 7.340, Forest Side, heard 2200 with news in English, 2235 in French. (NATTUGGLAN, Sweden).

Monaco-Monte Carlo, 6.035, 9.785, noted Sundays 0300-0330 with "Bringing Christ to the Nations" (English). (Cox. Delaware) Full schedule is weekdays 0100-0300, 0600-0800, 1215-1715; Sundays 0100-1715; on Sundays 1600-1700 has English program called "Monte Carlo Calling" (variety presentation by Evelyn Barnard).

Mozambique CR7BE, 9.763, Lourenco Marques, noted in English 1000; leaves this channel around 1105. (Stark, Texas) Has had improved signals here in West Virginia lately on Sundays with request program (English) around 1045. This outlet uses many commercials.

New Zealand-ZL7, 6.080, and ZL4, 15.280, noted with BBC news relay

# SAVE MONEY BRAND NEW GUARANTEED GENERAL ELECTRIC SELSYN .

Type 2JIGI

Will operate from using a resist a condenser ries. Size is 2 in diameter x 4 % "
long I de a l for
beam antenna position indicator

Price \$2.75 per pair - re-moved from new equipment





HAYDEN TIMING MOTORS Type 45629R

110 volts, 60 cycle, 2.2 watts, 1/240 13.00

Price on. net, nev

Type 36938-2 110 volts, 60 cycle, 2.2 watts, % R.P.M. Price

3.00

Type 33669-2 118 volts, 60 cycle, 2 watt, 'eo R.P.M.

3.00

Type 1600

110 volts, 60 cycle, 23 watts, I R.P.M Price

12.70

NEW ADDRESS INSTRUMENT ASSOCIATES 37 EAST BAY VIEW AVE. GREAT NECK, N. Y. IMperial 7-1147



# DYNAURAL

DYNamic noise suppression plus AURAL satisfaction in record and radio reproduction.

DYNAURAL CONVERTER -Model 111-A

adds H. H. Scott Dynamic Noise Suppression to your radio-phonograph using a crystal pickup.

# DYNAURAL PREAMP-Model 112-A

gives you DYNAURAL reproduction PLUS · preamp for magnetic pickup · adjustable turnover frequencies 300, 500, 800 cycles • 20-20,000 cycle range • AM whistle filter . remote controls.

Write TODAY for FREE bulletin 11198.

Two LOW-PRICED models suit your need. Model 111-A \$29.50 net

Model 112-A 47.50 net

Buy NOW from your distributor.



RADIO & TELEVISION NEWS

0600 and signing off around 0628, ZL7 has bad QRM.

Northern Rhodesia—ISWC, London, says ZQP is now using both 7,220 and 9.715 at 1000-1200.

Pakistan—Karachi is currently using 11.770.5 (measured by Oskay, N. J., but may vary as low as 11.768 at times) for news 0700, 1015, but when this was compiled was still on 11.885 for news 2100; Dacca, 15.335, is in parallel at these times. Dilg. Calif., has been hearing a Radio Pakistan outlet on approximately 7.670 with English identification around 0915; heard irregularly and signs off 0930; location unknown.

Fried, Mich., reports Radio Pakistan heard around 1100 on 11.885, 11.770, and 7.225; 11.885 carried separate program while the others were parallel.

Heard on 11.770 announcing use of 25-m. and 31-m. bands; however, could not be located in latter band. (Cushen, N. Z. via Radio Australia)

World Radio Handbook lists call of Karachi, 11.885, as APK-3.

Although Lahore has been widely reported abroad as heard on 11.740, at the time this was compiled I had reliable information that Lahore was as yet operating only on m.w.

Philippines — DZH-3, 9,500, Manila, heard in England from around 1645 with sponsored programs in English; at 1700 gives time as "6 a.m. Philippine Time." (Pearce)

Sanderson, Australia, reports a new Philippine outlet on approximately 4,980 at 0530 with music; she reports a station in Manila on 9.730 noted 0530 with music, may be (new) DZH7? Radio Australia says the 4,980 outlet has been heard closing 0900 giving m.w. call of DYBR, but noise was too high to read s.w. callsign.

Poland—Radio Polskie, 9,530, heard in New York 0000-0300 with strong signal but with QRM from BBC on 9,525. (Schild) Bluman, Israel, lists relay of Home Service on this channel 0100-0400, 0600-0800.

Portuguese West Africa — CR5ST, 9.615. Sao Tome, is testing 1300-1500 with Portuguese recordings; speech poorly modulated; QRA is Radio Clube de Sao Tome e Principe, Sao Tome, Portuguese West Africa. (Bluman, Israel)

Reunion Island—Krafft, Mass., reports he picked up Radio St. Denis on approximately 15.37 at 0030 on a Sunday some weeks ago; had news and identification in English (in which mentioned a resume in French); signal was 100 per-cent readable and fairly well above noise level. May have been test. Not confirmed. Is not listed in 19-m. band.

Roumania—Bucharest, 9.252, has had improved signal lately in East at 1500 when has news; continues to 1600 closedown. Usually has bad CWQRM and other QRM.

Saudi-Arabia New regular schedule of Mecca, 725 kc., 3,960, 5,985, 9,645, 11,760, 11,950, in parallel, is 1200-1800, (Bluman, Israel)

Spain - "La Vox de la Falange,"



# TWIN LEAD TRANSMISSION LINE

for Television Lead-in. 300 ohm. 1,000 ft. to roll. ? roll. \$10.50 ea.; 5 rolls or more, \$9.95 per roll. Order Today!

SUFFOLK TELEVISION AGENCY 41 Suffolk Ave., Central Islip, L. I., N. Y.

# RADIVENGINEERING 27 MONTHS

Intensity, aprecisized routes, haricaltar strong hashin mathematics and obstitud engineering, at harvest Halls Theory and Bosign, Modern taboratory. Less between Self-help operaturities, Also 27-month rotices in Astonautical, Choucal, Cavi, Electrical, and Mechanical Engineering Covil approach to

INDIANA TECHNICAL COLLEGE

# Speaker, Cartridge Buys!

| SPEAKERS: | 100 PM wite. | 4 os. Al. V | 52.59 | 100 PM wite. | 4 os. Al. V | 1.95 | 100 PM | 1.95 | 1.95 | 100 PM | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95 | 1.95

TERMS \_25 DEPOSIT, BALANCE C.O.D.

M. FISHER & SON 2941 N. 5th St. Philu. 33, Po.

# THE FINEST TELEVISION SET EVER DESIGNED

16" RCA Licensed 630 Type chassis Deluxe Model



Improved custom-built 31 tube chassis sold complete—ready to play. Has the new RCA designed Voltage-Debubler circuit which gives bright-clear daylight pictures on 16" picture tube. Sold with the standard RMA guarantee!

Price complete and ready to play — less 15° picture tube.
Plus \$1.80 excise tax

\$159<sup>50</sup>

# **Deluxe Television Cabinets**

Beautifully designed to match the 630 chassis above without any cutting or driling. All cabinets are made like the finest furniture with a satiny plano finish and are complete with a 16" mask and protective class window.

Table Model Cabinet-Mahog- any or Wainut	\$42.95
Blonde	49.95
Console (floor Model) with drop-door panel to conceal	
knobs-Mahogany or	89.50
Walnut	99.50

# ORDER TODAY!

# High-Gain Conical Antenna and Reflector

The most popular antenna used by installation companies throughout the country. Gives high-gain on all television chan-

Complete with most ..... Price \$6.95

300 ohm twin lead line. Price \$1.25 100 ft.

3 by Price .03 each

SPECIAL! Fringe Area Double-Conical Antenna gives exceptionally high-gain for televiaion sets located more than 25 miles from TV station. Covers channels 2-13.

Complete with mast.....Price \$6.95
WRITE FOR FREE CATALOG 82

# EDLIE ELECTRONICS, INC. Telephone Digby 9-3143

154 Greenwich Street New York 6, N. Y.

7.380. Madrid, informed Pearce, England, that it would shortly increase its power and that broadcasts in English would be inaugurated in response to requests from many English-speaking listeners. This expansion should have been effected by the time you read this.

Suez Canal Zone—An unidentified station heard some time ago by Gillett, South Australia, on 7.375 to closing 0830 may be the Forces Broadcasting Service at Kabrit. Was reported earlier to have tested on this channel.

Syria — Damascus, 6.000, 11.750 (moved from 12.000), has news 0530, 1400. (GDX-aren, Sweden)

Tahiti—Papeete has recently been using its old 6.982V channel in parallel with the new 12.080 frequency at 2315-2400. (Dilg, Calif.) The 6.982 outlet at times is the better of the two here in West Virginia. Has some English at times now.

Thailand—More recently, Bangkok appears to be using 6,240 instead of 6,010 for its native transmission around 0700-1030 (sign-off varies); 9.796 is in parallel. (Dilg. Calif.) At the time this was compiled, Bangkok was using 9,796 and 6,010 for news 0515, 0615.

Trans-Jordan—The Hashemite Jordan Broadcasting Station (self-styled "Hashemite Kingdom of the Jordan") at Jerusalem over s.w. outlet Ramallah on 7.075 is on the air daily 0045-0130, 0645-0730, 1100-1215 in Arabic and 1215-1300 in English (Bluman, Israel)

Turkey—Ankara is using TAP, 9.465, daily with news 1445; English program on Thursdays 1630; and Mailbag on Sundays 1630. Good signal here in West Virginia. According to announcements from Radio Ankara, its new 100 kw. s.w. outlet should be on the air early this year.

USSR—The Soviet outlet on 6.055 is used to China; signs on 0230; uses Chinese exclusively: others in parallel are 6.11, 9.545, 9.565 from 0230 to around 0430 when these are heard in Russian in parallel with 6.075, (Balbi, Calif.) Location is Komsomolsk for the 6.055 channel which relays Moscow to the Far East.

Schwartz, Vienna, reports Stalinabad on 7.440 with good signal after 1945, best 2030. (NATTUGGLAN, Sweden)

Vatican City — HVJ, 15.095, noted fairly good level with news 1000, but has bad sideband QRM from Montreal, 15.090, (Fargo, Ga.) Radio Sweden reports that HVJ is now operating on 7.280 in parallel with 5.968 and 6.190; after 1530 the new outlet is badly jammed by Paris on same channel.

It is reported by Patrick, England, that money subscribed by Catholics all over Holland is being used to build a new 100 kw. Philips s.w. transmitter for the Vatican; it will be completed in 1950 and will be presented to His Holiness Pope XII on behalf of Dutch Catholics to commemorate the Holy Year that began Christmas Day, 1949. Yugoslavia — Belgrade, 9,505, is

One of the high-powered tubes used in the new short-wave transmitters of "Radio New Zealand" at Titahi Bay, New Zealand.

widely reported 0115-0130 with news. In the Eastern U. S. has some QRM from GSB, 9.510.

### Press Time Flashes

At press time I was hearing Radio Pakistan, Dacca, on 7.670 at 0700 with news, in parallel with Karachi, 11.770.5; since I could not find Dacca on 15.335, it is assumed it may have moved to the 7.670 spot. If this is the case, the 7.670 outlet likely is in use as late as 1130.

J. M. Hill, production manager of CKRC, Winnipeg, Manitoba, Canada, informs me that the s.w. outlet which has been off the air will return early in 1950 on 11.720, with news at 1300, 1330, 1400, 1500, 1600, 1700, and 1800.

Radio Sweden has just issued an attractive new QSL card which is entirely in the English language. Sweden now has an English news review daily at 1345 on 6.065, 10.780.

The Radio Club of Sweden (SRK) has started a novel service for its English-speaking members; each month such members will be sent an English translation via airmail, giving most important DX items, while the club's regular bulletin in Swedish will follow via surface mail. This club reports Radio Malaya, 7.200, 9.712, Singapore, closing 1030 (Saturdays 1100). opens 0530; DZH-3, 9.500, Manila, Radio Philippines, closing 0900; that CR7BJ, 9.635, Lourenco Marques, is looking for a new channel and has been heard on 9.635, 9.640, and 9.670 at times; Lisbon, 11.027 and 15.165, noted parallel 1600-1615.

A more recent measurement of Budapest's 31-m. outlet was 9.831.5 instead of 9.834.6. (Oskay, N. J.) English now seems to vary at 1615 or 1630.

Radio Addis Ababa, Ethiopia, again seems to be using approximately 15.075 irregularly; noted on a Sunday in Sweden and in England around 1010-1100 sign-off with English religious broadcast.

Radio Sweden reports the clandestine Greek Liberty Station on 9.455 in Greek at 0700-0730, 1115-1145, and 1215-1245; in French 1330-1415

At press time I was hearing the Forces Broadcasting Station Middle East, on 4.965 from 2330 opening.

Revised AIR winter schedules received via airmail are: Delhi-VUD2, 6.190, 2130-2330; 9.660, 0200-0400; 7,290, 0630-0800; 3.495, 0815-1230. VUD3, 15.290, 2030-2145; 9.680, 2200-2230; 11.810, 0200-0240; 17.760, 0300-0400; 11.830, 0730-0750; 15.29, 0830-0915; 6.010, 0930-1230, VUD4, 9.630, 2030-2230, 0200-0400, 0700-0750, 0830-1100, 1130-1230, VUD5, 15.190, 2030-2200; 15.160, 2300-2330; 21.510, 0230-0330; 17.840, 0600-0815, 0830-0915; 15.190, 1000-1040; 15.290, 1100-1230; 9.620, 1400-1500; 15.160, 1930-2015, VUD7, 9.565, 2030-2115, 2130-2200, 2215-2310; 17.830, 0230-0330; 15.160, 0430-0530, 0615-0730; 6.190, 0745-1045; 11.790, 1100-1330; 11.760, 1400-1500; 11.830, 1845-1900, 1945-2000, VUD8, 7.275 2030-2230: 15.350, 0220-0250: 7.290, 0310-0320, 0340-0350: 7.275, 0700-0750, 0830-1330, VUD9, 11,790, 2030-2230; 9.680, 0220-0240; 15.290, 0300-0400, 0730-0750; 11.790, 0830-1100; 9 680, 1130-1230. VUD10, 7.225, 2030-2115, 2130-2200, 2215-2310; 17.780, 0230-0330, 0430-0530, 0615-0730; 7.225, 0745-1045; 9.660, 1100-1330; 7.240, 1400-1500; 9.630, 1845-1900, VUD11, 11.856, 2030-2200; 17.780, 2300-2330; 15.190, 0230-0330, 0600-0815, 0830-0915; 11.850, 1000-1040, 1100-1230, 1400-1500, 1930-2015,

Bombay-VUB2, 6.150, 2100-2230; 9.550, 0215-0400; 7.240, 0630-0845; 4.840, 0900-1230, VUB3, 7.240, 2100-2230, 0215-

0400; 9.550, 0630-0845; 7.240, 0900-1230.

Calcutta-VUC2, 6.010, 2030-2230; 9.530, 0200-0430; 7.210, 0600-0800; 3.305, 0815-1200. VUC3, 7.210, 2030-2230, 0200-0430; 9.530, 0600-0800; 4.880, 0815-1200.

Madras-VUM2, 6.085, 2030-2230; 9.590, 0200-0430, 0530-0630: 4.920, 0700-1200. VUM3, 7.260, 2030-2230, 0200-0430, 0530-0630, 0700-1200.

Acknowledgement
Many thanks for the usual FB cooperation; keep reports coming to Ken Boord, 948 Stewartstown Road, Morgantown, West Virginia, U. S. A. . . . . K. R. B.

# WANTED

GOOD LOOKING OLD CONSOLES THAT NEED A NEW "HEART"

install an

# ESPEY AM/FM CHASSIS

and your favorite console is "right-up-to-date"




trument by Ameritranic angineers. Fultranic engineers, Fuly licensed under Repatents. The photo
shows the Espey
Model 511, supplied ready to play.
Equipped with tubes,
antenna, speaker
and all necessery hardware for m

ATTENTION SERVICEMEN-Did you know there are over 19 million consoles waiting to have a modern AM FM chassis installed? Here is a gigantic sales market just waiting for you to develop. Send for Espey Bulletin "19 million customers". It will tell you how to make real money!

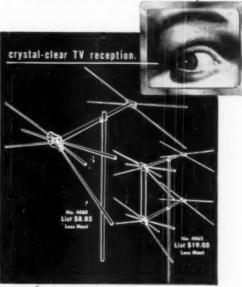Write for literature RN cations on Model 511







# amazing antenna out-sells all others/

WALSCO features a silicone-treated styron molded insulator to assure crystal-clear TV reception.

WALSCO uses marine type high tensile dural for elements . . . with a "yield point" 94% higher than ordinary aluminum.

WALSCO uses a butt-seamed tubing for elements to assure the highest elasticity.

WRITE FOR FREE ILLUSTRATED CATALOG 49-T

WALSCO New TV Alignment Tools are used everywhere. Available at your local jobber.

# WALTER L. SCHOTT CO.

Beverly Hills, California Chicago S. Illinois

## Just Out! New 10th Edition! RADIO OPERATING

QUESTIONS and ANSWERS

-to help you meet NEW F.C.C. Study Guide Requirements



539 pages \* \$5.00

HERE is the information pass any class of comme amination; the correct answ need to help and Just Published!

BASIC TELEVISION By Bernard Grob

An A-to-Z manual for everyone concerned with TV receiver in-stallation and servic-ing. Elaborate trouble-shouting charts show symptoms, and cures for ever 50 common

1500 new examination questions listed in the FCC Study Guide. Elsents 1,2,4,4,5, and 5, revised July 1, 1948, and 5, 1950 . PLIS the answers to the FCC supplementable he new element for aircraft radional for aircraft radional population of the FCC supplementable he new element for aircraft radional for aircraft radional population of the FCC supplementable for aircraft radional for aircraft ra \_\_\_ CONTENTS \_\_\_

Basic Radio Laws Basic Theory and Practice • Radiotele-phage • Advanced phone • Advanced Radiotelephony • Radio Telegraph • Advanced Radiotelegraphy · Aircraft Radiotelegraphy

AMPLIFIER GUARANTEED FOR LIFE AGAINST **OBSOLESCENCE** 



NEVER become obsolute ment in amplifier design by R. C. Shaney guarantee ideal operation-regardless of what kind of input device becames available, whether it he a new type phone pickup, tape, film or wire recorder, photocell input, or what have you! plus --

- · the highest fidelity circuit over built into any super-fidelity amplifier,
- · exclusive non-frequency discriminating scratch and noise suppressor.
- · exclusive path-pall triade volume axpander.

Write today, and get your name on our mailing list to receive literature on the revolutionary new ACA 100 VV (Double W for Very Versatile)

AMPLITIER CORP. OF AMERICA 398-2 Broadway

New York 13, N.Y.

#### FOR SALE!

2 mfd .5 .3 at 200v. D.C.	5 for \$1.
G.E. Transformer cat. #7167172	
60 cycles 9 taps	\$20 each
Condensers 100 mfd at 50 volts	% for \$1
Throat Mikes T30 Q W.E. (new)	5.0c each
Headset R14 (new) with PL 54 plug.	98c each
Handsets TS-13, TS9	
(guaranteed like new)	\$3.95 m
W.E. Carbon Mike tiess housing)	
D96554	.98e each
AA-Variator	75c each
New PLQ-103	4 for \$4
Induction Cods CIAS	4 for \$1.
Cord—CD501	75c each
EES-Field Phones	. F ac chica
(with new handles)	68 50
(With new mindless)	200.000 011.

Cash with order or C.O.O. All Ships EASTERN TELEPHONE CO.

#### SEE THEM 10 DAYS FREE

McGraw-Hill Book Co., 330 W. 42d St., NYC 18, N.Y. Send use book fall checked helow for 10 days' ex-amination on approval. In 10 days I will send regul-

Hornung's RADIO OPERATING Q & A-\$5.00 Grob's BASIC TELEVISION-\$6.50

Position This offer applies to U. S. only

SENSITIVE - ideal for rad and audio measurements of AVC AFC and FM discriminator volt

FULLY SHIELDED - in motal case with enclosed battery power sup-ply – ideal for accurate measure-ments in the powerful R.F. fields of transmitters! VERSATILE – has polarity revers-

ing switch, measures D.C. and A.C. volts, D.C. current and resist-

ACCURATE — incorporates 1% tolerance precision resistors and 2% accuracy 4½" meter in self-regulating, stable push-pull VTVM

bridge circuit

SELF-CONTAINED — completely
independent of power line — use
it anywhere! LONG-LIFE BATTERIES — last up to one year with

RUGGED - toughly made to withstand abnormal abuse, with electronic circuit-meter protected against burnout; unbreakable meter facel

meter race:

COMPACT — size 91/2" high,
614" wide, 51/2" deep. Weighs
9 lbs., including batteries.



It's Sensational! RCA Battery Voltohmyst-vacuum tube voltmeter and volt-ahm-mil-liammeter combined — featuring self-contained long-life battery ower supply!

The RCA WV-65A Voltohmyst is a highly accurate electronic voltements is a highly accurate electronic voltement another-obmeter for laboratery and on-the-job testing! Supplied with 1-Meg. isolating shielded signal-tracing probe for measuring D.C. in presence of R.F.!

RANGES

D.C. VOLTS - 0-3 /10 /30/100 /300-/1000 volts, input resistance 11 meg-chms constant for all ranges A.C. VOLTS - 0 10 30 100 300 1000 volts // 1000 ahms per volt

RESISTANCE - 0-1K/10K/100K/1 meg 10 meg 1000 megohmi D.C. CURRENT - 0-3 10 30 100 300 milliamperes, 0-10 amperes RCA WV-65A Valtohymst camplete with 1-Meg. D.C. 3950 dynamic test probe and test leads, less batteries

BATTERY KIT - Two 45V and four 11/2V, factory-fresh! 2.58 WG-263 — RCA Crystal Probe, read R.F. voltages flat 8.95

WG-284 - RCA high-voltage probe, read D.C. volts 15.95 to 30,000 volts

RADIO CORPORATION

Distributors of Radio & Electronic Equipment 85 CORTLANDT STREET, NEW YORK 7, I WOrth 4-3311 • Cable: TERMRADIO

#### Speaker Cabinet


(Continued from page 47)

sion of some of the problems and characteristics of the various types of baffles may be of value to the experimenter.

One common problem encountered where low frequencies are reproduced at fairly high level is that of cabinet In the most objectionable rattles. form, these are usually high-frequency resonances excited by the sudden contact of two loosely separated portions of the baffle. The high audibility and nonharmonic character of these sounds make them a very undesirable accompaniment to bass passages. Firm contact or adequate damping is usually the solution to this problem. The first method is usually employed in conventional baffles where heavy construction and glued joints are commonly used. A combination of the two methods is desirable in a collapsible structure. The hinges or other means of connecting the various sections should provide a firm contact without any play, while sections that come in contact with each other may be lined with felt or other material to damp transient vibrations.

A related, but seldom mentioned, characteristic is the tendency of the baffle itself to act as a radiator or series of radiators. This often results in very uneven frequency response and the production of unpleasing standing wave patterns as well as related transient distortions. One of the causes of this appears to be the practice of coupling the loudspeaker rigidly to the baffle; as a result, the mechanical reaction of the moving speaker cone will cause the entire baffle to vibrate in different phases and amplitudes, resulting in the previously mentioned distortions. Although the mass of the speaker cone is small in comparison to the mass of the cabinet it should be realized that a fair sized enclosure has a much greater radiating surface than the speaker. In the enclosure shown, the effective radiating area of the cabinet is about twenty-five times as great as that of the speaker cone. Similarly, the coupling that often

Fig. 2. Top layout of the collapsible baffle.

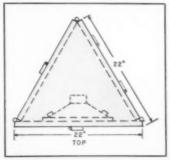

BADIO & TELEVISION NEWS

exists through the floor of the room may be of considerable importance as loose flooring constitutes a source of possible low-frequency radiation. Under some conditions this effect is very noticeable and the operator may find it desirable to use some form of mechanical isolation, such as sponge rubber "feet" under the speaker enclosure in order to preserve greater uniformity of characteristics in different locations.

The photograph shows the speaker mounting method used with the collapsible baffle. A sponge rubber gasket is used to separate the speaker frame from the front of the enclosure while small isolating pads are used between the mounting nuts and washers and the rear of the speaker. Although not providing perfect separation between the speaker and the baffle, this arrangement appears to be of definite value in damping out sharp transients that would otherwise tend to shockexcite various cabinet resonances and rattles and a definite improvement in the smoothness of the low-frequency response appears to result.

Similarly, a common practice is to line the interior of the speaker baffle with sound absorbent material to reduce the effect of internal resonances. It is important to note that in speaker enclosures utilizing the back radiation from the speaker, such as the bass reflex, the acoustic phase inversion is usually effective only in regions where the wavelength of the sound is somewhat greater than that of the return path. Above a few hundred cycles the phase of the radiation from the return path tends to change greatly, producing alternate cancellation or reinforcement which, in turn, results in uneven response. By lining the interior of the enclosure with sound absorbent material the high frequencies in the back radiation tend to be attenuated and thereby produce smoother mid- and high-frequency response.

A number of modifications are possible with the baffle described. If anpropriate locations are available, the rear of the cabinet may be left open to provide a modified form of corner radiator system. Although the triangular shape of the baffle was chosen for reasons of simplicity and mechanical rigidity, using another piece of wood for the back of the enclosure to make a four-sided unit will approximately double the internal area. Likewise, it is interesting to note that use of multiple speakers of similar characteristics in the same cabinet, as suggested by Goodell, tends to give a higher ratio of speaker cone surface to cabinet surface and tends to reduce the effects of cabinet vibration.

Total cost of the materials in the unfinished cabinet illustrated was slightly less than ten dollars including the cost of having the sides cut to dimensions at a local cabinet shop, thus making this an inexpensive addition to the soundman's equipment.

# greylock presents -SPECTACULAR SAVINGS ON Radio Jubes!

Your Corl		Type Cost	Fach	Type Co.	ur Net	Type Cost	Esch	Type Cost		Type Cost 6		Type Cost Ex	
Type Cost I DY4	.89	287	.69	EASGT	.69	61.5G	.49	6X5GT	.39	32	.59		65
0Z4M	.59	2V3G	.99	684G	1.19	61.6G	.79	6Y6G	69	33	49		79
1A3	49	2X2A	.89	685	99	6L6GA	79	627	49	34	49		65
1A4P	39	2X2 879	59	686G	.69	61.650	1.19	6ZY5	49	35/51	40		65
1A5GT	.49	3A4	39	687	99	61.7G	49	104	49	3585	39		59
1A6	39	3A5	.69	688G	49	6N6G	.89	12A6	39	3505	39	747	59
1A7GT	69	304	.39	6BA6	.39	6N7GY	.89	12A7	59	351.6GT	49		65
183 8016		305GT	79	68A7	.39	6N7M	.89	12ASGT	.39	35W4	39		59
104	49	354	39	6BE6	.39	6P5GT	49	12487	.59	35Z4GY	49	TAGE	59
185 255	49	3V4	.39	6856	.49	607GT	.59	12AT6	.39	35Z5GT	39		59
1C5GT	59	ST4M	.69	6BH6	39	687G	.49	128.17	.39	35260	.79		65
106	39	5U4G	49	68G6G	49	SR7GY	.49	12AU6	.39	36	49	786	65
1C7G	.49	5V4G	99	6816	49	6S7G	49	12AU7	39	37	49	787	65
105GP	.49	5W4M	59	6806GT		6S8GT	49	12AX7	49	38	49	788	79
107G	49	5W4GT	39	6C4	39	6SA7GT	.39	12BA6	.39	39.44	39		65
108	.69	5X4G	.59	6C5GY	39	6SC7M	.69	128A7	49	41	.49		65
154	.39	5Y3GT	39	6C6	49	6SD7GT	35	128D6	49	4.2	59	706	65
1F5G	49	5Y4G	49	6C8G	.99	6SF5GT	49	12BE6	39	43	.59	707	65
IGAGT	.69	5Z3	59	6CB6	49	6SF7M	69	128F6	.39	45	49	764	65
1G6G	59	524	.59	606	49	6SG7M	.69	12C8	89	4523	.69	765	65
1H4G	.69	6AB4	49	6D7	49	6SH7GY	39	12F5GY	49	45Z5GY	59	766	59
1H5GT	59	6AC5GT	49	6D8G	49	6SJ7GT	49	12J5GT	39	46	49	76.7	59
116G	49	6AC7M	.79	6E5	79	65K7GT	39	12J7GT	39	4.7	69	767	79
11.4	.39	6AG5	39	6F5GT	49	6SL7GT	49	1287GT	39	49	59	768	89
INSGT	59	6AG7	99	65667	49	6SN7GT	49	12K8Y	49	5085	39	7G7	39
1P5GT	49	6AH6	59	697	79	6S07GT	.39	1207GT	39	501.6GT	49	767	.79
105GT	69	6A15	59	6F8G	79	6SR7M	49	12SA7GT	39	53	39	717	79
185	.39	6AK5	49	5G5G	49	6SS7GT	49	12SC7	:69	56	39	787	.79
154	89	6AK6	.59	6G7	59	6557M	.69	12SF5GT	49	57	39	71.7	65
155	39	6AL5	.49	CHECT	49	677G	49	12SF7GT	49	58	49	787	79
114	39	6AN5	.69	6H6M	49	6T8	.49	125G7M	69	70£7GT	49	707	59
ITSGT	69	6AQ5	39	6.15GT	39	6SU7GT	49	12SH7M	49	71A	.59	787	35
1114	39	6A06	49	6.16	.39	6U5 6G	5 .79	12S17GT	.39	75	49	757	65
105	39	6AR5	49	617GT	49	6U6GT	39	12SK7GT	39	76.	49	7V7	79
iv	49	6AS5	.59	638G	99	6U7G	39	12St 7GT	49	22	39	7W7	79
1×2	79	6A16	.39	6K5GT	49	6V6GT	39	125N7GT	.20	78	49	7X7 XXEM	
2A3	.99	6AU6	.39	6K6GT	39	6W4GT	39	12S07GT	39	80	.19	784	49
2A4	1.29	6A1	.99	687GT	49	6X4	39	1258GT	49	81	6.9	724	65
2A5	.69	6A6	.99	6MSGT	79	-		12SR7GT	39	8.7	.89	1484	.65
2A6	49	6A7	.69	oneu.				1223	49	RIV	.79	14A7	.59
2A7	.49	9119			-			19	49	84 624	.89	14877	79
APT			-				1	198G6G	49	85	49	1486	59
					10		1	1918	39	89	49	1405	.59
		-		OFFE	K		١.	22	99	11717 50			.79
		DECV	AL	O	- 1'd		1	24A	49	117P7GT	99	1407	65
1	2	PECI/	- Mar	ndred a	221 0	6501	1	25AC5GT	.69	11723	39	1467	69
1		\$32.95 P	61					25A7GT	49	11776GT	59	1468	79
4					120	No. 1 19 6	0	25806	49	11.84	69	1467	79
	. Y.I.	5 68A6	8/13/71	1780		5061	1	25L6GT	39	11.A6	69	1417	.79
LAAF	3.8	to see o	6V9	G1 178A	16 251	861	1	25W4	49	11.84	89		.19
100		0.00 G.B.MG	6 X 8	1286	0 25	1661 11	1	2525	49	11.05	69	1607	.59
154		AGS 6CSG	1 95	ASGT 178	30	11	23	2526GT	.19	11.06	.69	14K7	.89
185		635	1.3	Att. 171		28xx 60	4	26	.39		65	35A5	79
153	5	SATE END		AT6 123		100 assorted	. at	27	.39	11.53	69	3584	.65
17		CAUG SAN	1 44			100 associate of	STATE OF	30	.39	11.65	69	1 3316	.00

# GREYLOCK ELECTRONICS SUPPLY CO.

NEW YORK 7, N. Y.

#### TELEVISION RECEIVER-\$1.00

#### AUDIO ENGINEERING SCHOOL

Placin training abraiable Broadcast, Motion Picture, Travition, and Commercial Beneding work.

Approved for Veterans

#### HOLLYWOOD SOUND INSTITUTE, Inc.

#### Television Close-Out Sale

various true and va at	or rue free	rement
	List S	ale Price
8 sets 120 sq. in. picture \$	1495.00	\$189.00
2-12" Tube Sets	450.00	189.00
1-1212 Custom Built	475.00	229.00
1-15" Custom Built	995.00	519.00
1-15" Remote Control	750,00	419.00
1-10" G.E. Table Model.	325.00	209.00
1-10" G.E. Consolette	359.00	254.00
2-Field Strength Meters	99.00	59.00
2 - Sweep Signal Genera-		
tors	99.00	59.00
1—Boosters	39.00	22.00

Special prices on entire lot

All sets are new, built for fringe areas. We carry a complete line of antennas, rutators, bardware, installation accessories, etc. Terms. Net Cash. F.O.B. Columbia, N. J.

COLUMBIA DISTRIBUTORS, INC.



NOW a full line of Titone's amazing ceramic pick upp-made by Jamous someones. All with these great basic features: Full frequency (response from 50 to 10,000 cycles.) Hell-like supertone makes new or old players trilling. Climate-proof, mingus-proof! Lightest pressure avea needle wear, review worn records. NO needle talk! NO crystals, magnets, filaments to fail. NO pre-amplifiers. Performs perfectly for years!



Call your Jobber or write to

SONOTONE, Box 5, Elmsford, N. Y.

#### Ultra-Modern WOR-TV

(Continued from page 37)

Theater. One studio is arranged for audience attendance and participation. The existing theater facilities in the New Amsterdam were adapted for television purposes as follows: one control booth was built under the orchestra in a space formerly used for storage, and the other was set up in a former projection booth.

The stage itself was adapted for television purposes by the addition of three ramps and the extension of the apron. The ramps extend radially from the stage at either end and from the middle. They allow the cameras great flexibility and freedom to dolly in and back.

A second studio, comprising three basic sets, was constructed in a portion. of the theater's original balcony. The control room for these sets is located in the former projection booth.

Each studio is planned for threecamera operation, and each studio control room equipped accordingly. The cameras are RCA TK-10A models using the type 5820 image orthicon tubes.

Control room monitors, the synchronizing generators, and the stabilizing and distribution amplifiers are of the latest RCA design.

At the time of writing the larger of the two control rooms is also being used as a master control point until the permanent master control can be completed in WOR-TV's new studios in the Television Center" on 67th Street, New York.

Facilities there include a master control room, a projection room, three studio control rooms, two large studies, and two announcing studies. Each of the three studio control rooms are identical, as regards facilities. Two of these control rooms face on corresponding studios.

Among the novel features incorporated in the 67th Street setup is the removal of all video operating personnel from the studio control rooms. This is done in order to minimize the number of people present in the control room during the actual production of programs. Located here is a program console, in which are mounted seven picture monitor tubes. Four of these monitors are used on the individual cameras for that studio.

Two may be switched for previewing incoming remote signals or film inserts, which may be a part of the studio show, and the seventh monitor is used as an outgoing line monitor for that particular studio.

The production man and a video switching engineer are seated at the control desk in front of the monitors. To the right of the video console is located an audio control console at which one audio man operates. Thus, the total personnel in the control room is reduced to three for producing a television show.



**Lightning Arrester** Protects Television Sets Against

Lightning and Static Charges UL

LIST The ONLY Twin Load Lightning Arrester Approved by UL for Outdoor-Indoor Installation.

SIMPLE TO INSTALL . . . attaches to any grounded object-pipe, radiator, roof, wall-at any position between antenna and the set, indoor or outdoor.

NO WIRE STRIPPING OF CUTTING OF SPREADING OF lines necessary. 300 ohm impedance . . . does not unbalance line.

One Dozen To Pack-age with FREE Self-Selling Display Card. Selling Display Card. No. AT102-12

Advertised in Con-To Help Your Sales @1950, JFB MFG. CO., Inc.



MANUFACTURING CO., Inc. 6105 16th Avenue

Brooklyn 4, N. Y. PIRST IN TELEVISION ANTENNAS AND ACCESSORIES



# SURPLUS

RADIO PARTS

Clesing Out Entire Stock OFFERS WANTED

All new Nationally Advertised Brands

CONDENSERS-Metal encased tubular. I Filled Filter and Bath Tub type. sistors and miscellaneous radio parts. Write for descriptive list and approxiate quantity available.

ERIE SUPPLY CO. Rochester 3, N. Y. 0. Box 907

The video operators who set video and background levels on the individual cameras for all studios are located in what is called the "camera control center," a part of the master control room. Here, all of the camera control units with their picture monitors and oscillographs are centrally located for all studies in one console unit. The video operators at this point are in communication by wire with the directors and camera operators themselves. Their only function is to see that the cameras are electrically focused, and that the levels on the oscillographs are properly held. This system has a further advantage in that a video operator operating in one studio can quickly switch over to the control units of another studio, thus further minimizing the personnel requirements for the station.

Another feature of this system is a camera cable patch panel, located in the camera control center, which enables the quick patching of any one of the eight studio cameras' camera controls into any of 15 camera outlets in the two studios or "announce" booths

when required.

For example, if it were desired to augment the four cameras in Studio A for a particular show with a fifth camera from Studio B, it is merely necessary to plug in the fifth camera control in the camera control center into the cable leading to Studio A, and the same video operator in the camera control center will have this control unit at his fingertips.

The two large "announce" studios are equipped with camera cable feeds to the camera control center, so that if a single camera shot of an interview or a news program is desired, it is merely necessary to patch in one of the eight camera controls to the "an-

nounce" booth cable. The projection room adjacent to the master control room is equipped with four TK-20A film camera chains. Each film camera is fed by means of a multiplexer with several sources of slides or film. Included in these facilities are 35 mm. projectors, 16 mm. projectors, 2 x 2 slide projectors, and opaque projectors.

The film camera control units, with their monitors and oscillographs, are centrally located with the studio camera units in the camera control center. This further simplifies the operation in

several ways.

The program control for the film equipment is located in the Studio C control room and is identical with each of the two live-talent studio control rooms. This control room enables the production personnel to put on an allfilm program or to handle film inserts in a remote show.

The video switching system for each studio control room handles a total of twelve inputs. The switching is actually done by relays in the master control room, but controlled from the individual studio control rooms. This gives considerable flexibility to the switching of cameras between studios



The ideal all-purpose television receiver. Carries easily from place to place, operates from its own entenne—no connections required except plugging in power cord. Antenna is adjustable for largeth and direction for maximum picture brightness. Brings in crystal clear pictures even under variable conditions of lighting and signal strength. ength. Tubes plus Picture Tube and 4 Recti-rs, 23 sq. in. rectangular picture on face

sq. in. rectangular picture on face 7-inch tube. Push-button tuning

7-IN. PORTABLE TELEVISION SET REGULAR S119.50 VALUE

WE AGREED NOT TO MEN. TION THE NAME-BUTWE GUARANTEE YOU'LL BE PLEASED!

- You can get 10-in picture with this set, order Glenwood unbreakable entarging fens (our stock No. 35833) at only \$8.79.
- · Get maximum low cost TV en-

provides instant station selection on any of the 12 tuning channels. Sturdy wood cabinet covered with lan leathereste. Cover with corrying handle hinges and snaps to side of set, fully protecting picture tube and controls. Matched antenne astends from top of cabinet. Size overall 20 in, wide, 10½ in, high by 18½, for 105-125 volt 60 cycle AC only.

No. 39A20

No. 39A20 EACH \$89.97



A real "Triple-Threat" disc recorder

that makes recordings from micro-phone or from its own radio, plays

phonograph records, and contains an

excellent superheterodyne receiver.

Uses only one tone arm for both cut-

ting and playback, making this unit

exceptionally easy to operate. Cuts and plays records up to 12". Constant-speed 78 RPM motor

IT'S A RECORDER, A RADIO AND A PHONOGRAPH

### THE WILCOX-GAY Recordette

· The Recordette is compact in design, and easily portable, weighing less than 18 lbs.

 Has four-position switch, "Listen-Phono", Listen-Radio", "Record-Phono", Listen-Radio", "Record-Radio", "Record-Mike"-plus volume level indicator.

chassis has low impedance loop antenna. Quality PM speaker, Crystal pickup and recording cartridge. Crys tal microphone is carried in special holder on inside cover. Tan-andbrown leatherette-covered case, 121/2 x 6". With tubes, mike, cutting needle, pack of steel playback needles. For 110-120 volts, 60 cycles AC. Shpg. wt. 20 lbs.

No. 318229 SPECIAL EACH

\$49.95

four pole recording type. Has 10 turntable with rim drive. AC superhet

# PEN-OSCIL-LITE

Extremely convenient test oscillator for all radio servicing; alignment • Small as a pen • Self-powered • Range from 700 cycles and it to self-e 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Leed by Signai Corps • Writts for information.

GENERAL TEST EQUIPMENT Buffalo 9, N. Y. 38 Argyle

# ENGINEERIN

TRI-STATE COLLEGE

1620 Callene Ave

#### STOP! LOOK! BUY!

3.99

#### POLY-TECH

519 Damon Street New York 58, New York 25%, Decord with Orders, Balance C to 0.



A MESSAGE TO

Service-Dealers: WORRIED ABOUT COMPETITION?

Become the

# TV SALES and SERVICE CENTER

IN YOUR COMMUNITY

- Beat competition at a profit.
   Stop being undersold by
- Stop being undersold by anybody!

Here's a real opportunity to MAKE MONEY in Television. If you can qualify, you can become the Transvision Television Center in your community—and BUY TV and RADIO PARTS AT JOBBER PRICES. Practically no investment required. This offer is open only to service-dealers in territories where we do not have an authorized distributor. CONTACT US today!

# Now . . . 16" WIRED

Completely wired and aligned by TRANSVI-SION. Specify: MODEL WIGRS TV CHASSIS. List price, less C.R. Tube

Also available as a KIT which

Also available us
can be completed in ONE DAY. Specify
Model Wi6R5 TV Kit.
List price, less C.R. Tube. \$119

FILL OUT AND MAIL THIS COUPON NOW!

# TRANSVISION, INC.

Please ship THRO LOCAL OUTLET:	DUGH	YOUR N	EAREST RN 2-50
I am enclosing	10%	DEPOSIT	in the
amount of \$ ( ) Send details			

Name (please print)
Address

City & State

and the handling of remotes in individual studio control rooms. Five banks of video switching relays are used with each studio switching system. One of these gives an output for the main program to the master control. Two other relays are used to switch the two preview monitors to any of the twelve inputs, as desired. Two other outputs are provided to feed a mixer amplifier for "super positions," "lap dissolves," and any other special effects which may be required in the future.

The twelve inputs are set up normally so that eight inputs are camera signals, that is, video and blanking only, three for composite signals, such as incoming remotes, and one the "effects" input to the program output.

The master control switching facilities also present a novel system, at this time. The system is designed for six composite video inputs and six audio inputs, with four outgoing channels. The system provides for presetting on both audio and video signals with either simultaneous audio-video switching or separate audio and video switching. Two of the standard RCA console sections are used for each outgoing channel. One of these sections houses a TM-5A master monitor with picture tube and oscillograph, while the adjacent section houses the preset control buttons and tally lights. A master "trip" button appears on each of the four channel sections, enabling the operator to trip all four outgoing channels when required. A "local" or "master" control switch on each of the sections also enables the operator to set up an individual channel for separate control when so desired. The system is extremely flexible, and it is anticipated that it will fulfill all of the requirements for television master control switching in the near future.

#### Mobile Units

Approximately half of all WOR-TV programming is remote, and fed to the transmitter from WOR-TV mobile units. These were made to order according to WOR-TV engineering specifications. Each unit contains a three-camera setup with associated sync generators and monitors.

Maintenance of these mobile units and their equipment is especially important since so much of the station's program schedule depends on their smooth and accurate functioning.

The signal from any remote pick-up can be beamed to the 550-foot level of WOR-TV's New Jersey transmitter. A microwave relay house at that level picks up the signal and feeds it directly to the transmitting equipment below. When required, it can be routed to the master control in the city for switching.

In the over-all planning of WOR-TV's technical facilities, the emphasis has been placed on obtaining flexibility and ease of operation to insure smoother and better programming on the air.

-30

# FACTORY SPEAKER Lontono FACTORY SPEAKER SERVICERS' BARGAIN KITS MOULDED BAKELITE CONDENSERS MILE 50 asati. DIAL SCALES Airplane & slide rule. Acetate & SPEANER CONES Asatd, popular sizes 4" SPEAKER REPAIR KIT-EVERYTHING FOR SPECIAL OFFER! HOTH CONE & RE \$3.95 OUNCER INPUT TRANSFORMER Low imped mike of P U. to grid 7s 11s 750 S.P.D.T. SLIDE SWITCH Bakelite lever, \$44, 1254 6 VOLT TELEGRAPH KEY & BUZZER (W.E.) 21.25 ALUMINUM PANELS (0.31 - 7 x10 - 39c; 7 x12 49c; 7 x14 - 55c; 7 x15 - 6 ce O-100 DC AMMETER - 212 eq. panel with 980 abunt MIGH FIGELITY CRYSTAL MICROPHONE—so diaphragm, hi-imped, 118, 0.D., 1, d deep ber abuck-mtd. Less housing. mitted Eadio & Electronic of OffMeles, SPEAKER ACRESISTORS, FTC. FTC. 21 Ibn., AND ONLY \$2.95 WIRE-WOUND RESISTORS 5 50 20 WHILE KIL SO.98 OLUME 6 TONE CONTROLS incl. wire would

# FIELD TELEPHONE Army Signal Corps

67 Dey Street, New York 7, N. Y

Complete with New Handset, Excellent Used Condition, Factory, Tested and completely reconditioned in our own shop.

Price per pair \$12.95
In lets of 100—Price \$5.65 each
25% with order, Balance C.O.D.

MASPETH TELEPHONE & RADIO CORPORATION 142 Ashland Place Brooklyn 1, N. Y. Tel.: MAIn 4-2982



veloci high speed and profiteiency. Learn code for Amateur or Commercial Badiatelegraph Licence, or immove your sending and receiving with the Landler code Chamberra.

CANDLER SYSTEM

Ban 938, Dect 2-8

CASIDERIA.

BADIO & TELEVISION NEWS

# Technical BOOKS

"THE TECHNIQUE OF RADIO DE-SIGN" by E. E. Zepler. Published by John Wiley & Sons, Inc., New York, 388 pages. Prices \$5.00. Second edition.

This book is based primarily on the experiences of a radio designer encountered over a period of years. In contrast to many technical books it deals with the problems which occur most frequently rather than the abstract problems which are seldom encountered in engineering practice.

The author believes that the real technique of experimental work starts when unexpected complications occur while following a design, while the technique of design calls for foreseeing complications that may arise and overcoming them before serious trouble develops. With this in mind the author has tried to instill in the reader a feeling for the right order of magnitude, a quick grasp of essential facts, and the use of common sense in approaching design problems.

In developing his theory the author has devoted considerable space to a discussion of fundamentals without slighting his material on practical applications. This new edition includes a rewritten and expanded chapter on receiver noise and much more space has been devoted to negative feedback.

The author has avoided complicated mathematics and has stressed practical applications. Design engineers should find this book of value in coping with everyday design problems.

"FACSIMILE" by Lee Hills & Timothy J. Sullivan. Published by McGraw-Hill Book Company, Inc., New York, 311 pages. Price \$3.50.

Written in layman's language, this book is the story of facsimile from its earliest beginnings in 1842 to present-day methods and equipment.

Since the authors are managing editor and faesimile editor, respectively, of *The Minami Herald*, one of the pioneers in the faesimile transmission of newspapers, their material is both interesting and practical.

The early chapters of the book are devoted to a discussion of the medium, a history of facsimile, and the present and future applications of the art. They then go on to discuss "Colorfax" and "Ultrafax," two of the recently developed facsimile systems. There is plenty of down-to-earth data on applying for a facsimile broadcasting license, facsimile programming, and the various techniques for presenting copy for facsimile transmissions. Several chapters cover some of the technical aspects of how facsimile works but the discussion is non-technical and need not tax the comprehension of the veriest layman. A chapter which will be of particular interest to the faculties of journalism schools is one entitled "Teaching Facsimile" and covers




#### 

Include postage—we refund excess
LONG ISLAND RADIO CO.,
164-21 Northern Blvd., Flushing, N. Y.
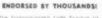
### EASY TO LEARN CODE

H is many to least or increase speed with an intertwining the Vide Twentier Affords the quickent and most practical control yet developed. For backets of the option of state of the property of advanced state of the Arabica for typical consumption on all subjects speed concerns to the WPM. Always residue QUM.



with to taken the black of an operator indirector and manifes anyone is been early and manifes relie without further desiration. These and of early acquired that calls with the b



INSTRUCTOGRAPH COMPANY

Write for Our Monthly Bulletin



HOYT MODEL-515 O-15 AMPERES DC METER

MIRROR SCALE



Includes test leads and steel carrying case. Meter size 4"x5". Basic movement approx. 12 ma.

Special .....\$3.33

10 FOR \$30.00

**Build Your Own Geiger Counter** (See Radio & Television News-July, 1949) 1898 Gamma Counter Tubes Only \$9.87

SURPLUS EQUIPMENT TROUBLE SHOOTING MANUALS BC-348-J N G BC-779 SCR-522 BC-610 \$1.00 \*\*

COMMAND RECEIVERS

SPECIAL!! FL-8A FILTERS . . . . \$1.37

TUBE SPECIALS

1A3		6366 C	FO 88	CHOL	62 25
183	\$0.40	2400	30.00	1824	.29
183GT	1,18	7.50	.19	2055	
2A3	.89	785	.29	2001	.49
2 X 2	.49	10Y	.13	2022	.22
5V4G -	.84	12A6	.24	2C26	13:
SY4G	.38	12AT6	59	PH - 34	.28
SY4GT	.46	12AT7	.99	24 G	.44
523 6AC7	,69	12AU6	.72	211	62
6AC7	.79	12AU7	.86	304 T.L	1.25
6AG5	.89	12A X 7	.86	316A	.66
6AK5	.89	12BA6	.64	445 A	.79
GAK6	.82	12BA7	.86	807	1.15
GALS	.69	12BE6 .	.64	810	6.55
6AQ5	-72	125A7GT	.59	811	5.95
GATG	.64	125 K7	.59	813	6.95
6AU6	.72	125LTGT	69	815	1.72
GBA6	. 65	125 N7 G.T	.79	829	4.91
6BE6	-65	125Q7GT	.59	832	3.95
6.B.G.6.G.	1.72	19T8 25Z5 25Z6GT	1.04	832A	4.91
68H6	.72	25Z5	.55	837	1.38
eB16	.72	25Z6GT	.49	838	2.93
6C4	.21	35L6GT	.59	866A	.95
616	49	35L6GT 35W4	45	1613	.61
616	.89	352564	.44	1619	.13
616 6K6GT	.52	5085	.69	1624	.69
6L6GA	.87	50L6GT	.5.7	1625	.19
6SL7GT	6.9	ZAPI	3 65	1626	.29
65N7GT	.64	3API	4.63	1629	.29
GTS	1.04	3881	2.69	9001	.42
6V6GT 6W4GT	.59	SBP1	2.40	9002	.39
6W4GT	.65	SCPT	2.87	9003	3.9
6X4 6X5GT	.59	5CP7	3.76	9004	.39
6X5GT	.69	SERT	5.7	9006	29

#### COAXIAL CONNECTORS

83-1AP	\$0.09	UG-21 U	\$0.67
83-1F	1.12	UG-22 U	.86
83-1H	.10	UG-23 U	63
83-1J		UG-24 U	67
83-1 R			
83-1 RTY	45		
83-15P	.28		94
83-15PN	28		
83-17	1.12	110 00 11	
83-22AP	.85		
83-22F	.88		1.22
83-22 R	.48	UG-87 U	.68
83-22SP	48	UG-175 U	.15
UG-12 U	.63	UG-176 U	.15
Full Line	of Coasial	Connectors	in Stock.

ADN I Ratio Altimeter complete with tables Excellent used count tenry 400MA Peller Choke 902 DC re-remetrally sealed; high voltage moulation control of the tor making connections to 2JIG1 layrs. \$3.95 lsyne ra 39
Yag) Antenna, 5 element, rotatable array 7.00 Power Unit. Use as Mike of Re-\$1.11 co., \$2.22 pr.

Include Postage with Orders

LECTRONIC RESEARCH LABS. 1021-R Cellowhill St. Phila. 23, Pa.

the editing, make-up, equipment operation, campus editions, and lecturers' observations

A concluding chapter summarizes the future which is in store for the medium.

The book is interestingly and entertainingly written and should answer many of the questions about facsimile that have heretofore gone unanswered.

"MAINTENANCE MANUAL OF ELECTRONIC CONTROL" edited by Robert E. Miller. Published by McGraw-Hill Book Company, Inc., New York. 296 pages. Price \$4.50.

This book is a compilation of a series of articles on the subject of electronic control maintenance which originally appeared in Electrical Construction and Maintenance.

Each chapter has been written for the electrical and electronic technician by a specialist in his field. It is, simply, a practical installation, maintenance, and service manual written for the men whose job it is to see that industrial equipment using electronic controls is kept in top working condition.

The first chapter is introductory and discusses the various circuits encountered in the electronic control field. It is written in non-technical and easy-to-understand form and serves as background material for subsequent chapters.

The text then covers such subjects as general considerations in installing and maintaining electronic control; the cathode-ray oscilloscope, what it is and how to use it; installing, maintaining, and servicing electronic relays and timing relays; installing, maintaining, and servicing photoelectric relays; installing, maintaining, and servicing electronic motor control; and installing, maintaining, and servicing electronic resistance-welding controls, electronic temperature-control systems, and sealed-ignition rectifiers.

All of the contributors are electronic specialists with General Electric Company and they have illustrated their articles with excellent photographs and complete diagrams. Sixteen reference charts covering troubleshooting, inspection schedules, cable sizes, water flow and temperature, tube and circuit connections, and abnormal conditions and protection data add considerably to the practical value of this book

"INTERNATIONAL RADIO TUBE ENCYCLOPAEDIA" edited by Bernard B. Babani. Published by Bernards (Publishers), Limited, London. 410 pages. Price 42 shillings.

This is a comprehensive work covering tube types used by the Armed Services of the British Commonwealth, the United States, and Europe in addition to the C.V. and normal civilian types. Nearly 15,000 tubes are listed in tabular form with such information as base, pin connections, top or side caps, and manufacturers. This tabular data is all coded and related to

#### RADIO Surplus Buys

#### COMMAND RECEIVERS Used, Good

BC 453 1.9-556 ... 8 1.00 command sets



#### LIKE NEW

R-5/ARN	-7	COMPASS RECEIVER \$14.98	5
BC-433G	C	MPASS RECEIVER \$14.98	ŝ
BC-603	FM	RECEIVER \$12.95	S
BC-604	FM	TRANSMITTER \$ 05.98	š

#### ARC-4 VHF TRANSMITTING RECEIVER

140 to 144 MC Crystal controlled 10 watt output. 13-tube receiver, containing 2 in-dividual RF sections and A10 MC. If am-plifier. Both RF sections may be operated simultaneously or individually. Less crys-\$5.95 tor and tubes. USED GOOD CONVERSION TO 144-148 MC. .....\$1.00

12 & 24V DYNAMOTOR FOR ARC-4.84.95 

SEND 10: FOR COMPLETE SURPLUS CATALOG!

Enclose full amount All Equipment with order. • F.O.B. Pasadena

#### C & H SALES CO.

2176 RO-1 East Colorado . Pasadena 8, Calif.

#### Yours for 7 Days FREE TRIAL

COMPLETE SECTION IN FULL COLOR ON COLOR TELEVISION



FREE TRIAL OFFER!

#### THIS BOOK FREE!



	MAIL THIS FREE BOOK COUPON NOW
	Educational Sock Publishing Division COVMS ELECTRICAL & RADIO SCHOOL 500 S. Paulina St. Dool. 20-T3. Chicago 12, 611. 0 K. Rush Apptied Tractical Radio Television post paid for FIGE. 7-day trial per your offer, income FRE. Rook of "130 Mantia Television Diagrams.
ļ	Name Age
	Address
į	Town State State
í	Wasse Woodwood

standardized instructions which have been given in fourteen languages. Included are instructions in English, French. Italian, Spanish, Portuguese, German, Dutch, Swedish, Norwegian, Danish, Russian, Polish, Czech, Hebrew, and Turkish so that practically any potential user can apply this material.

There are ten main sections covering receiving tubes, triode transmitting tubes, transmitting tubes, and other transmitting tubes having more than five elements, rectifiers, thyratrons, regulator and control tubes, tuning indicators, cathode-ray tubes, photo tubes, and rare tubes and their equivalents.

There are six pages of tube base diagrams and a comprehensive listing of manufacturers and their addresses.

One valuable feature of this encyclopedia is the fact that the publishers are planning to issue an annual supplement which will give information on tube types not included in the original text and data on new tubes in production. In this way the book will not become dated.

For those whose work involves radio tubes of all types and makes, this encyclopedia is an important contribution to the literature.

#### "TELEVISION FOR RADIOMEN"

by Edward M. Noll. Published by *The Macmillan Company*, New York. 588 pages. Price \$7.00.

The author, who is well-known to readers of Radio & Television News as a contributor of television articles, has prepared this comprehensive instruction manual for the radio technician, electronic technician, radio amateur, experimenter, and the technical school student.

Although it is assumed that the reader of this book will be thoroughly familiar with radio theory and circuits before tackling television, the author takes it for granted that the student is a tyro in the television field and proceeds accordingly.

The book is divided into fourteen chapters, the first of which is devoted to an introduction to television and the last to a discussion of practical television mathematics. Although mathematics appears throughout the text where needed to present a complete treatment of the subject, the practical television technician can safely ignore the formulas, interpretations, and derivations without losing any of fundamentals.

The balance of the book is devoted to a discussion of the composite television signal, the general operation of the television system, r.f. and i.f. systems, video amplifier systems, television picture tubes, sync and inter-sync systems, sweep systems, FM sound system, large screen and projection television, television receiver antennas, installation, adjustment, and operation of television receivers and antennas, and alignment and trouble-shooting.

Since this book is intended to be



# hallicrafters HEADQUARTERS!

#### POPULAR HALLICRAFTERS MODEL SX-43



All essential ham frequencies from 540 kc to 108 Mc. In the band of 44 to 55 Mc, wide band FM or narrow band AM, just right for narrow band FM reception is provided. 115 V. AC. 10 tubes plus rectifier. Only \$159.50, less speaker.

# GI.

#### MEDIUM PRICED HALLICRAFTERS MODEL S-40A

540 kc. to 43 Mc. Temperature compensated, One RF, 2 IF. 3-watt output, 4 bands, 115 V, AC. 8 tubes plus rectifier. Internal speaker, Only \$79.95.

I have a complete stock of Hallicrafters receivers and transmitters and Television equipment. I'll make you the best deal on a trade-in of your communications receiver for a television receiver. I give you immediate delivery, 10-day FREE trial, and 90-day FREE service. Nobody can beat Bob Henry on a trade-in, and I offer you the world's lowest credit terms. Write, wire, phone, or visit either store today for the best deal.

# HENRY RADIO STORES 100 ANGLES 10 ANGLES 10 CALIF.



Me's doing feat, profitable business with the complete Phoenix line of television mounts and accessories. Are you one?







BC-429, or BC-430, USED, \$5.95 each, both for \$5.95 PE-94C, 24 volt SCR-522 dynamotor, two for \$4.01 PE-101C, 12 or 24 volt dynamot BC-645, two for DM-32A, 24 volt dynamotor for 274-N receivers, USED, two for..... 76c 10 MA, 2340 volt DC, Heinamann cuit breakers, two for MS-51, three foot antenna mast section two for 51c Sensitive relay, SPDT, 3 MA, 7500 s SIGMA, two for ..... \$2.51 F-10A, antenna fairleads, 3 foot bakelite, two for..... \$1.01 46c 51.01 CD-604, transformers for HS-30, two Much more is included in this SALE, such as transformers, chokes, oil filled condensars, and other items of inferest to the amateur and the experimenter, Be sire to get our FREE CIRCULAR, Chock FULL of MOKE RED HOT BARGAINS. This sale ends on Saturday, April 1, 1950, and no orders received after that date will be shipped. All prices are NET, FOB our warehouse, all merchandise is subject to prior sale, 20% minimum deposit with order, balance COD.

Quad ELECTRICAL SUPPLY, INC. 1650 N. Damen Ave., Chicago 47, III.



We have more than 30 exciting models. 2-speed recorders, 24-hr. recorders, conference recorders and many others. Get the facts in our new 16-page catalog. Complete specifications given. Write today for your copy.

### AMPLIFIER CORP. OF AMERICA

298-2 Breadway

used for self-instruction or as a classroom text, each chapter is followed by a list of questions by which the student can check his grasp of the subject matter covered in that chapter. A bibliography listing other books and articles on the same subject is also included at the end of each chapter

Typical circuit diagrams, block diagrams, and photographs are liberally used throughout the text and assist materially in clarifying the subiect matter.

This book should find a vast audience among the thousands of radio service technicians who are seeking a practical and authoritative text on the subject of television.

"PRACTICAL TELEVISION SERV-ICING AND TROUBLE SHOOT-ING MANUAL" by The Coyne Staff. Published by Coyne Electrical & Radio-Television School, Chicago. pages. Price \$4.25.


Especially compiled for the radio technician, this newest Coyne text covers such subjects as television servicing methods, tuners, television sound problems, alignment methods, video i.f. amplifiers, traps for interference, picture tubes, video detector and amplifiers, deflection methods, the sync section, sweep oscillators and generators, sweep frequency auto controls, sweep outputs, high voltage power supplies, low voltage power supplies, trouble location with test patterns, television antennas, and u.h.f. and color television.

One particularly valuable section deals with the test instruments needed in television servicing, their use, and method of employing them in test procedures.

The text is liberally illustrated with diagrams, graphs, and photographs. The photographs have been taken of the various receiver sections just as they would appear to the service technician working on the set.

An unusual feature in the makeup of the book is that the chapter dealing with u.h.f. and color television has the illustrations printed in colors as they would appear on the screen of a color TV receiver.

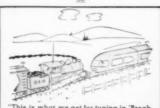The experienced radio technician should experience no difficulty in grasping the material as presented in this book, as the text is clearly and concisely written. The book would also be suitable for the student studying television by self-instruction. -30-











oding on tubular molded capacitors in new IV and Radio sets? There's no need to con-ult complicated wall charts or tables!

The Sprague Capacitor Indicator gives you the needed data in a 1iffy. Just flick the dials to the color bands and read the capacitance, tolerance, and voltage directly.

This slick plastic service help fits your pocket. Always on hand, it saves time and avoids mistakes... and it's only 15c. Ask for one at your Sprague distributor today!

SPRAGUE PRODUCTS COMPANY

#### Spot Radio News

(Continued from page 18)

commercial operation of the station was discontinued and the Navy assumed control. Control was maintained by the government until 1919, when the newly-formed RCA became the operator and a chain of historic events followed. The Commissioner revealed how for the first two years, Chatham, the receiving site of the system erected by Marconi, was a point-to-point station, exchanging messages with Germany, Norway, and Sweden. In 1921, as plans were set up to transfer all point-to-point activities to the then newly-built Radio Central on Long Island, a 500 kc. transmitter with the famous call letters WCC was installed at Chathamport to serve as a ship-to-shore link. A year later, a second WCC transmitter was installed to operate at what was then considered to be an ideal frequency, 2200 meters. The 500 kc. transmitter assumed the call letters

"However," continued the Commissioner, "with the addition of the 2200meter equipment, interference prob-lems increased. To eliminate transmitter interference at the increasingly busy receiving positions meant the removal of the transmitting equipment a considerable distance from the receiving antennas. And thus WCC's transmitters were moved to Marion."

Marion and Chatham became the scene of many record-book events, the Commissioner revealed, recalling the incident which has become a legend in brass-pounding history. In 1927, when the Prince of Wales was on his way to this country aboard the SS Berengaria, a severe windstorm broke contact at several points between Chatham and Marion. The break, coming at an hour when message traffic to and from the British liner was at its peak, caused a near panic.

"With 300 messages waiting to be radioed to the vessel," reminisced the Commissioner, "one of the crack operators, carrying his telegraph key, set out through the gusty night, feeling his way in the dark from pole to pole until he spotted the break nearest Marion. He connected his telegraph key into the line, and in this unorthodox manner, proceeded to operate the Marion station transmitter, until the last of the messages had reached the Berengaria."

THE TAXICAR report, delivered by Commissioner George E. Sterling during the annual meeting of the National Association of Taxicab Owners in Buffalo, disclosed that today there are approximately 2700 radio cab systems, with a total of 55,000 cabs authorized. An investment of nearly \$30,000,000 is involved in radio-cabs now in operation, said the FCC spokesman.

There's a BIG Future for YOU in TELEVISION RADIO-ELECTRONICS

### **Builds Your Career in a Minimum of Time** Industry Needs More Trained Men Now Day and Evening Classes Now Forming

GRADUATES of CREI Residence School are pre-ferred by industry because of their training and ability. This recognition is the reason that CREI neaching experience in these highly technical fields. CREI offers an outstanding faculty, modern and com-plete laboratories, shope and equipment.

New students are accepted twice monthly and each my advance as rapidly as he is capable.

CREI is recognized as one of the country's leading schnical institutes, offering college-calibre education for the young man who wants a practical career education roung man who wants a practical career education leads to a good-paying job in a minimum of time



Approved for Veterans' Training

Mail Coupon for FREE Catalogue

#### CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 132 B, 16th & Park Rd., N.W. Washington 10, D. C.

Please send me your illustrated catalog and complete details about the CREI Residence School.

NAME STREET ZONE STATE I am entitled to training under G.I. Bitt

# The PENN Teletower... NEW 3-WAYS!

(1) NEW Low Price

(2) NEW Ease of Erection (3) NEW Extended Field of Reception

RETAILERS Grab at Low Price of Less Than Dollar per foot!

Everyone's known for a long time that a tripod-type tower provides the best support for antenna. But until now, "only the rich could afford it." Today, Penn prices the tripod within reach of the solid bulk not just the thin cream of television's market.

INSTALLERS Go for Ease of Erection!

So foolproof - so safe - is the Penn Teletower that just two men zip it up fast without use of rigging hoists. Exclusive pilot hole provides automatic alignment.

#### HAMS **Enthusiastic About Reception!**


Ingenious Teletower sectional construction makes it easy to gain height . . . rise above interference.

WHOLESALERS: Write for details about Penn's profitable line distributed entirely through jobbers.

# Teletower...

Manufactured by PENN BOILER and BURNER MFG. CORP. Makers of Penn Packaged Heat ESTABLISHED SINCE 1932 LANCASTER, PA

## ISOLATION BENCH TRANSFORMER

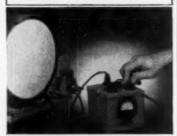

### REGULATE YOUR LINE VOLTAGE TO FIT YOUR REQUIREMENTS

#### N-303 VARI-VOLT JUNIOR \$15.00 DEALER NET

A voltage regulating isolation transformer to make your bench test voltage exactly what you want ... on 117V line, variable from 95 to 145 volts... if line drops to 90, variable from 75 to 115V....output adjustable in 11/2 volt steps...metered output voltage ... capacity up to 250 Watts inter mittant, 50-60 cycles...for radio and television receiver testing at under or over voltage...to isolate "hash" and live ground from AC-DC equipment .. controled voltage for meter calibration...speed up or retard heating of light soldering iron ... and for many other similar uses.

See your local Halldorson distributor for complete line of replacement transformers...exact duplicates television and auto Vibrator transformer replacements, or write direct to us for complete information. THE HALL-DORSON COMPANY, 4500 Ravenswood Avenue, Chicago 40, Ill.



# WANTED TO BUY

Large and small quantities of new or used electronic government or manufacturers' surplus tubes and equipment. Highest prices paid. State quantity, condition and best price in first letter.

Box 496, % RADIO & TELEVISION NEWS 185 N. Wabash Ave., Chicago 1, Illinois According to the Commissioner, within three to five years, 90 per-cent of all cabs will be radio equipped.

"The radio-less cab will be as much of a rarity as the surrey with the fringe on the top," he declared.

Describing the advantages radio offers to the cab, the Commissioner said: "Radio means greater safety for the passenger and for the driver, as the driver is always in ready communication with the dispatcher who can send police aid or other assistance. . . The radio-equipped cab, ranging far and wide over the city streets at all hours of the day and night, is also proving a valuable ally to the local authorities in the reporting of fires and accidents, and in facilitating rescue work in floods and other disasters.

... Even the emergency delivery of babies which occurs from time to time in cabs has been facilitated by the cabbie's ability to summon assistance to supplement his own versatile talents. . . . So rapidly has two-way radio proved itself that today, only four years after it was introduced on an experimental basis, it has been authorized by the FCC for two-thirds of all the taxicabs in the country."

FREEDOM OF THE AIR, as viewed by the FCC, served as the focal topic of an engaging talk by FCC Headman Wayne Coy, delivered at Amherst College.

Admitting that some of the Commission's actions do restrict a licensee's freedom, Coy explained that the control is actually of a friendly and helpful nature to the operator and public too.

Expounding this view, he declared that the rulings . . . "restrict the freedom to be unfair . . . use a publicly-owned frequency for whims and caprices . . . use a scarce frequency out of the public domain that belongs to all the people to dole out time to bets or use it for his own interests and withhold it from those groups with whom he happens to differ. . Abridge his freedom to dodge his responsibility to operate his station as an open forum for all the conflicting interest of the community instead of as private chattel to do with as he will. Abridge his freedom to evade responsibilities as a trustee. . . . For my part. I conceive it my duty to make every effort to curtail the freedom of radio station licensees to be unfair or to use their licenses solely for their own private benefit rather than for the public interest."

AN EIGHT-YEAR program to extend the use of radio throughout India is now under way, according to a report from the International Broadcasting Union, Geneva. When the plan is completed, broadcasting stations in India will serve ten times their former areas, or about 80,000 villages, as compared to some 5000 at present.

Reporting on the increase in receivers in Japan, the Civil Communications Section of General Mac-



#### Mass. Radio School

273 Huntington Ave., Boston 15, Mass.
Offers Training Courses for Radio Technican (Pre-Television) and Licensed Radio
Operator (All Types) including maintenance and operation of General Electronic
Equipment. Over 20,000 Alumni and 30
years' radio-training EXPERIENCE.
Courses approved for Training for Veterans.

Send for Catalog
Licensed by Commonwealth of Mass.
Department of Education

# WILL BUY

Any quantities of new or used Electronic Surplus Equipment: APN-9, RTA-1B, TS-67, TS-170, ARC-1, ARC-3, ART-13, BC-221, BC-348, SCR-522, etc.

State Condition and Best Price.

BOX 491, c/o RADIO & TELEVISION NEWS 185 N. Wohash Ave. Chicago 1, III.



"RADIO-TELEVISION Questions and Answers"

A separate book for each element of the shady-guide questions performing the various closes of comercial U.S. A radio operator licenses. You need buy only those elements required for the license you want.

Beneral 2, but 12 and 2, but 2.

Blement 2: Basic Theory and Proctice
Blement 3: Sudiscourant and Proctice
Blement 4: Sudiscourant sudiscrephony
AT YOUR DEALER - On moil orders from us, \$1
postpoid for one, or 90c each for two or more.

EDITORS AND ENGINEERS, Ltd.

### LEARN RADIO!

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
COMMERCIAL OPERATOR (CODE)
RADIO SERVICEMAN

Television Servicing

(Approved for Veterana)
SEND FOR FREE LITERATURE
BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALT. 17, MD.

#### SCHEMATICS-CONVERSIONS FOR SURPLUS GEAR

BC-375-E original schematic, tuning complete parts list, values, character BC-224-F, K, BC-348-H, K, L, R original BC-ZZ4-F, N. Conversion. 52.00 schematic parts list. AC conversion. 52.00 BC-348-J, N. Q original schematic with parts \$1.00 BC-224-F, K, BC-348-J, N, Q, H, K, L, R

and complete alignment, voltages, etc. \$2.00 Anchor \$2.00 for 2-meter AC conversion with all speec, turn-up representations of the speech and the speech and alignment the schematics and alignment therat. \$3.00 for AC conversion with added AF, and broad-sharp, see even, example of gain, and gain with en-off, phone fack, all on front tangle.

front narel
ASS chematics, parts values, voltages; specily: Indicators (279.55.4Z, 55.54E; rec(791.45.4Z, 3.000 C.97.55.4Z, 55.54E; rec(791.45.4Z, 3.000 C.97.55.4Z, 5.5.54E; sec(791.45.4Z, 3.000 C.97.55.4Z, 3.000 C.97.55 DCR-DZC-R, AM, and C schematics, parts lites with recent functions, explanation of differences, chart for stal selection. \$2.00 BC-659 & PE-II-9 schematics, voltages \$1.00 APT-5 schematics with circuit operation, values, reprint of manual. \$2.00 APT-5 schematic. AC power, complete sch-up and tuning instructions. \$1.00 SCR-Z73M PCR-BZ-553 tt. SCR-274M revrs. BC-453, etc., all sebematles. AC concesion, local control adapter, alignment, parts locations, voltages. \$2.00 BC-9468 best AC home-revi conversion \$2.00 PE-103 schematic, circuit explanation \$1.00

The fellowing schematics are \$1.00 each:
APN-1; APN-9; APT-2; ARN-1; ART-13A;
System horkup for BC-603, 504, 683, 684,
GP-6, GP-7, TCE-2; MN-20; No. 19 Mark
II; R-89/ARN-5A; RA-10; BC-733B; BC-433G; CR-625,

The following schematics are \$2.00 each: BC-654; RC-603, 604, 683, 684; BC-923, 924; 1D-6A, 1D-6B, R-9A, R-9R/AFN-4 (specify which); RU-16/GF-11; RU-17/GF-12; SCR-(-)-183, 283; SCR-625.

R. E. DAS 1/2 N. PALM DRIVE GOODHEART BEVERLY HILLS, CALIF.



RADIO REPAIRS! Free Manual

Nothing complex to o Calburature,
beginners and
Send for FREE manual, "TME INSIDE
'today, 32 pages—illustrated—easy to read'
ow obsolete methods present full use of your
ty. Explains use of New techniques. You
o yourself and your future to "jest out in

SEND COUPON OR PENNY POSTCARD FOR FREE MANUAL TODAY!

RUSH my FREE copy of The Inside Stor

Arthur's command in Tokyo stated that there are now 3,000,000 more sets in operation since '45, or about 8,000,-000 receivers in approximately half the homes in the land.

There has been quite a rise in receiver use in Great Britain. According to Geneva reports, there are over 12,000,000 sets now licensed, of which about 170,000 are television models.

The Bonn transmitter, in the British zone of Germany, now operating on 400 watts, will soon have its power increased to 5 kw., according to the International Broadcasting Union. The transmitter, now located in a wooden hut, and placed into operation a few days before the German Confederation went into effect, will be housed in a streamlined stone building, now being erected. This transmitter forms part of a group of synchronized stations located in Hanover, Flensburg, Osnabrück and Berlin, all operating on 1350 kc.

ALL OF INDUSTRY was shocked to hear of the death of that distinguished leader in scientific and industrial research, Dr. Frank B. Jewett. A former president of the National Academy of Sciences, and the Bell Telephone Laboratories, his work in radio and allied fields had been applauded throughout the world, with such awards as the Edison Medal, the Faraday Medal of the Institute of Electrical Engineers, the Franklin Medal, and the John Fritz Gold Medal, highest American engineering honor.

He was recently awarded the Hoover Medal for 1949 for . "distinguished public service," and the presentation was to have been made during the winter meeting of the American Institute of Electrical Engineers.

Under his leadership at the Bell Laboratories, many significant advancements were recorded. His engineering research, which made possible the transmission of speech by telephone lines across the continent, and the all-important network operation, was an epic achievement which will never be forgotten . . . L. W



Slugger has the fight in the bag Kidd's punches are all going wild!"

### WHERE TO BUY IT . . .

#### WHOLESALE RADIO of Baltimore

**Boosts TV Signals 10 Times** For Brighter Sharper Pictures!

#### STANDARD TV BOOSTER



	DOZIEN ANTRES P	num
	"WHOLESALE"	
ANCHOR (AR	(C (01-50)	\$22.50
RMS (SP-4)		22.50
JERROLD TV		
With Built-	in Match-n-Trans	22.50

#### Get Perfect COAX-RECEIVER Match! 72 to 300 OHM

MATCHING TRANSFORMER

TV ANTENNA ACCESSORIES

di. Weather treated, Crimped for easy	
stacking	.95
ARTERNA SWIVEL BASE	. 19
GUYWIRE. 6 stranded No. 50; per hit ft	-29
24 reels, 50 ft. ex. intercornected	6.00
TZ OHM CORNIAL CABLE RUSSU.	
(4c per ft.), per 100 ft.	3.7%
300 OKIN TWEEK LEAD.	
(\$1.45 per 100 ft., 1000 ft.	EL.FS
CHIMNEY MOUNT BRACKETS.	
Set of 2. Complete with strap	1.59
HI-BAND ADAPTER. Folded disple and re-	
flector. Clamps on existing pole.	5 THE
31 - 100 OHM STAND-OFF INSULATORS	
Wood screw-in Type (Re ex.), per 100	21.75
SAMS TV ANTENNA MANUAL	1.25

#### STOPS PICTURE JUMPING! NEW! AGC for 630 type TV CHASSIS Techmaster Keyed AGC Kit

Install It In 15 Minutes! \$4.45

#### Add Thrilling Hi-Fidelity FM to any AM Sett MEISSNER Model 8C FM TUNER



\$39.66

WRITE FOR FREE "FYI" BULLETIN Address all orders to Dept. QR 106

HOLESAL BALTIMORE 1, MD.



Directional Indicator **Electrical Stops** Easy Installation Life-Time Lubrication One-Year Guarantee Electrically Safe Non-Warp Castings Ball Bearing Equipped Machine Cut Gears



Write for details CROWN CONTROLS CO., Inc. New Bremen, Ohio



Rate 20c per word. Minimum 10 words

#### RADIO ENGINEERING

PANEL engraving, machining, painting. Complete service. Circular upon request. Gilpin Instrument Works, Box 517R4, Mt. Clemens, Mich.

RADIO Engineering Broadcasting, Aviation and Police Radio, Servicing Marine Operating and Electronics taught thoroughly Expenses low Write for catalog. Valparaiso Technical Institute Deptt N. Valparaiso, Ind

CONVERSION of 10-meter Gonset to 75 meters, \$6. Robert Lewis, WSMQU, 3806 LeErda St., Flint, Mich.

#### SALE

FOR Sale 3 Webster No. 156, 78 RPM automatic Record Changers equal to new condition, price \$15 each, Foff, New York. Norman Bayls, 395 Ocean Ave., Brooklyn 26, N. Y.

PRACTICALLY new Eiror Tape Recorder, Roll of Tape with code up to 15 W.P.M. \$95.00. Gardner Tape Machine, 19 rolls of tape \$12.20. Phono & Key oscillator mounted on one panel \$8.50. F. H. Royd, Ashton, III

Royd, Ashton, III.
CODE Practice Tapes, Radiotelegraph, For school
and individual use. Fit standard phototube keyers,
\$2.50 each, postpald. For list write: Citradyne
Electronics, George, Ore.

PROJECTION Television sets 16"x21" picture, UST, used, with AM-FM Short wave: Cabinet 5½ x3½ x19" complete \$150.90 Murray Barlowe, 880 59th St. Brooklyn 20, N. Y.

FRANK Cotton, Omak, Wash, has ver Test Instruments for Sale. Reas has McMurdo Sil-

ANTI SLIPSTIK for dial cords and belts. An economical hard crayon that licks the most britating jobs when applied according to directions. Actually preserves and strengthens old and new cords. Money back guarantee. Send dollar bill and this ad to Walcor, 593 Sherman Ave., Peoria 5, III.

WEBSTER Chicago record changer and wire re-corder replacement parts. We ship everywhere! Friend's Wholesale Distributors, 106 N. 6th St., Philadelphia 6, Pa.

NATIONAL TVTW television rec. with lens, 3 months old, and Halli-rafter SX16 receiver. Make offer Alvin Olberg, Clearbrook, Minn.

offer Alvin (heefg, Clearmook, Minh SURPLUS: BC157, 8-95, BC458, 85-95, ARCs 722, 89-95. Used, good condition. Other Surplus and Amateur items. Write for complete list. Albert J. Arnold, Box 796, Amarillo, Tex.

CABLES & Wire. Multi-conductor #18 to 36 AWG solid or atranded copper. Cotton, shielded, or weatherproof plastic covering. Single conductors or twisted pairs. Write for quotations. Tel-Rad Company, 61 Allyn St., Hartford, Conn.

RECORD Changer Parts for leading makes. We ship everywhere—Friend's Wholesale Distributors, 196 N. 6th St., Philadelphia 6, Pa.

regular \$15.00. Park, N. J.

NOTICE: Surplus Radio Equipment, parts supplies. Write John R. Aab, Radio Divi Spartan Aero Repair, Municipal Airport, T

RADIO Diagrams under seven tubes, 30c; over six tubes, 60c. Record Changers, 60c; Television Diagrams with service data. \$1.00 m. State manu-facturer and model number Kramer's Radio Ser-vice, 35 Columbus & E., New York, 23, N. Y.

BARGAINS New and reconditioned Hallicrafters, National, Collins, Hammarlind, RME, Meissber, other receivers, tuners, tear-rangement, mitters, amplifiers, speakers, etc. Lowest whole-sale prices. Terms Shipped on trial Liberat trade in allowances. Write Henry Rodin Brider, Mo, and I 124 W. Olympic, Lox Argeles, Calif.

BARGAIN Hunting? Radio Servicemen write Sensational catalog. Henduw Radio Supply, 3619 Troost, Kansas City 3, Mo

LOWEST Prices Radio Tubes, parts. Bargain lists, Sc. Potter, 1314 McGee, Kansas City 6, Mo HOTTEST surplus list in the country. Electronics-Hydraulies, Aircraft-Gasigets, Dick Rose, Everett, Wash.

PARTS for articles described in this magazine Reasonable Leo 3. Vincy. WSFYA, 2805 E. 117th St., Cleveland 20, Ohio.

FIVE Element TV Yagi Beams, High Band, 86.75; Low Band, 88.50. Aluminium Tubing, etc. Wil-lard Badeliff, Fostoria, Ohio.

CARBON Tetrachloride, cleaner, solvent, 27 oz., \$1.50. Polystyrene high frequency coil and splice dope, \$1.60 pint. Special thinner, 65c pint. Craft Chemical Lab., 453½ E. Exchange St., Akron 4,

COANIAL Cable, 100 feet \$3.00; Sample 10c Harry H. Van Dick, Box 236, Little Falls, N. J.

marry n. van Bick, flox 23b, Lattie Falls, N. I.
TURES, parts. Bargain sheet Sonoret Radio Co.,
36 Woodbury St., Wilkos Barre, Pa.
ALL, Steel T. V. Towers which can be creeted to
76' or more. Ruild to climb. Shipped direct from
the factory at 88 56 F.0. R. per 10' section. Weight
29 nounts per section. Wifte for more details. The
Youngstown Steel Towers, 1316 Wilson Avente,
Youngstown S., Ohio.

#### WANTED

SNIPERSCOPE & Snooperscopes wanted. Any type, any condition, Needed immediately. Box 495, §, Radio & Television News, 185 N. Wabash Ave., Chicago I, Ill.

WANT to buy BC447, APS-6, ARC-5 interested in substantial quantity for parts requirements new or used condition acceptable. Rarry O. Eyrse, P. O. Box 218, Grand Frairie, Parts

#### HELP WANTED

INSTRUCTORS in Electronics and Radio. Prefer former Navy Radio Technician instructors willing to locate in the Detroit, Mich., area. Write to Bux 432, c/o Radio & Television News, 185 N. Wabash Ave., Chicago, Ill.

#### PATENT ATTORNEYS

LANCASTER, Allwine & Rommel Registered Patent Attorneys. Patent practice before U.S. Patent office Validity and Infringement investi-gations and opinions. Bookler and form "Evi-dence of Conception" forwarded upon request. Suite 414, 815 15th St., N.W. Washington 5, D.C. HERMAN Lewis Gordon, Registered Palent Attorney. Patent Investigations and Opinions. Warner Building, Washington, D. C.

#### CORRESPONDENCE COURSE

AMATEUR radio licenses. Complete code and the-ory preparation for passing amateur radio examinations. Home study courses. American Ra Institute, 101 West 63rd St., New York 23, N. USEB Carrespondence Courses and Rooks, hought, sold, rented, and exchanged Catalog free. Lee Mountain, Pisgah, Ala.

USED Correspondence Courses and Educational Books bought, sold rented catalog free. Educa-tional Exchange, Summerville, Ga.

#### MISCELLANEOUS

"RADIOBUILDER" for Crystal, tube Experimenters, 3 issues 25c. Catalog. Laboratories, 578-H

WANTED Sales Agent. Important nationally known WANTED Sales Agent Important nationally known manufacturer has developed lowest evis paging and alarm system now produced. Suitable for all medium sized factories, offices, hospitals, retail stores, restaurants, banks, etc. Our own salesmen cannot handle this product because they cover different trade. Exclusive agent appointments will be made at ence, prefer man with small sales organizations now covering above mentioned outlets. Liberal commission and special discounts on samples. Write fullest qualifications to President, Chimes & Signals, Inc., Dept SA-S, Madison & Rednank Roads, Cincinnati 27, Ohio.

QSL's! SWL's! Free Samples. W1fGI, Box 32C, Manchester, N. H.

EMHOSSED Business Cards 1,000, \$3 45 postpain Spada Enterprises, 10D Lexington, Wethersfield 9

MAGAZINES, radio, electronic, etc., sold and bought, Landa, 157a Leverett, Boston 14, Mass. WOLLD you pay 3%, first \$150 made! Book "505 Odd Successful Enterprises" free! Work home. Expect something odd! Pacific, 8K, Oceanside,

JOR Printing, QSL rards, stationery, business and personal, greeting and all occasion cards. Print-ing, 21 Barclay Ave., Portsmouth, Va.

PHONOGRAPH Records, Lie Catalogue free Par-amount, VE 313 East Market Wilkes-Barre, Pa RADIOMEN, Servicemen, Beginners, Make more maney, easily, quickly, 8256 weekly possible We show you flow Information free Merit Predicts, 216-32R 132 Ave. Springfield Gardens 13, N. Y. CIRCULAR Saw Blades: 8° diameter: Sample 82 m Van Bick, Lutte Falls, N. J.

#### New TV Products

(Continued from page 134)

phasing control, selective directivity without mechanical rotation, substantial reduction or elimination of and nuisance interference, 'ghosts" and high gain throughout the video band have been achieved with this new type of built-in antenna, according to the company.

The chassis carries 26 tubes plus 4 rectifier tubes. The sets use all-glass picture tubes.

#### DU MONT'S 15-INCH CONSOLE

The new 15-inch television console recently introduced by Allen B. Du Mont Laboratories, Inc., Passaic, New



Jersey has been designated the "Wel-

This receiver provides a 132 square inch direct-view picture and has the new improved Du Mont high-performance chassis. In addition to television reception, the new set provides both AM and FM radio coverage, and threeway record reproduction.

The "Wellington" also includes such features as the Inputuner, a Local-Distant Switch, and the company's square station selector dials, for both AM and FM reception. The combination is housed in a traditional Georgian cabinet of mahogany veneers. The set uses 29 tubes, plus 6 rectifiers, and the 15-inch cathode-ray tube.

#### "FAMILY THEATER SERIES"

The Crosley Division of Avco Manufacturing Corporation, Cincinnati, is presenting a new series of television receivers which incorporate an exclusive theater-type direct viewing screen.

Designed to give observers the effect of actually being in the theater, the new receivers are housed in mahogany console and table model cabinets with 1212 and 16-inch direct-view picture tubes that are prominently mounted and shielded against conflicting reflections by a projecting stage formed by the top, sides, and bottom of the cabinets.

Three models in the "Family Theater Series" are currently available, including two consoles and one table model.

#### NATIONALLY ADVERTISED BRANDS -Tung-Sel-National Union-G. E.-Philo 100° guaranteed. Individually boxed. All new tubes. PRICE TYPE PRICE \$0.80 .72 .96 .96 \$0.54 SPECIAL 5 W 4 5 X 4 Q 5 Y 3 G Y 5 Y 4 G 6 A 3 6 A 4 / L A 6 A 6 6 A "ALL AMERICAN" 7GT PACKAGE DEAL 10 each of the following tubes 12SA7GT-12SK7GT 12507GT 6AC5 6AC7 5AD7G 6AE6 6AG5 6AK5 6AK5 6AK5 6AK5 6AK5 6AK5 6AK5 35Z5GT-50L6GT \$2495 50 Tubes for units All Nationally Advertised Brands Package Connet Be Split 6S8GT 6SA7GT \$0.65 .60 .72 1.15 .72 .72 .72 .80 .60 .85 .80 .65 .65 .65 .98 68C7 68D7GT 684G 687 688G 6C4 6C5 6C8 8C6 6C8 8D8 6E5 6F5GY 6F6 6F8G 125 M 7 128 L 7 G Y 128 M 7 G Y 128 M 7 G Y 128 M 7 G Y 14 M 8 14 M 7 58 70L7GY 71A 75 76 77 78 78 86 81 82 63V 84 63V 84 624 .80 .60 .72 1.15 1.15 .96 .60 .54 .96 .72 .54 .60 EGEG EMEGT EJSGT EJS 6US ..... 6U6 ... .65 .65 1.15 .72 76.7 SVSOT 61.6 GLEGA TERMS: 25% with Order —Balance C.O.D.—F.O.B. Balance C.O.D.— Balance C.O.D.

ARB APS-13 Sensational WARNING Buy of BADAR

CO.

and 30 Mc. With instruct



\$1,30

#### BC-906 Absorption-Type FREQ. METER

eq range 150-225 Me es 0-500 DC microam

150 710 MC, input 115 VAC 60 c for 85 ant. dector 6 OSC Mas conversions. Makes good 2 meter receiver. With 14 Tubes. Used

COMMAND RECEIVERS

Dept. RN-2A

COLLINS AUTO-TUNE XMITTER

2-18 megs 100 W output. Uses 813 final, 811's mod with tubes and stat Excel cond Complete with tobes, can bestion cheef and set of fresh bat-tevins, Upod. \$14.95 ART 13 195.00

BC-1068 or BC-1161 RCVR

\$22,50

AN-29 Collapsible Antonna. \$2.95 COMMAND EMITTEES

1313 West Randolph Street

Chicago 7, Illinois

\$23,95

LAZY Q-Ser

1080 eye Lazy Quanto that QRM for

95c



\$5.00 MINIMUM ORDER, PLEASE

& ELECTRONICS

# SPOT SURPLUS!

MODULATION TRANSFORMER 1 KW
Thermador or SOLA, Sig. Corp. 225639, 29
Fr. Inn. 6600 OHM, CT. 500 MA. See. 4900
NEW!
OHM 400 MA. See., 2000 OHM 800 MA. 518.95

6 OR 12 VOLT. Input-dutput 500 V. 169 MA. \$17.95 w/all cables & filter box. LIKE NEW? \$17.95 AMERITAN TRANSFORMER 5 VOLT, 100 Amp. Ph. 105-125 V. 25 KV \$15.95 Ins. Siz. Corp. 2639SAJ. 13

SELSYN MOTORS 110 V. 60 CYCLE Heavy brass jobs. Weight, 17% lbs. per pr. USED: \$9.95 pair. NEW: \$19.95 pc.

PE-103-A DYNAMOTOR

COMPLETE KITS • ALL NEW • SPECIAL!
100 INSULATED RESISTORS
RIMA color coded, § § \$ 5, \$ 5, \$ 1, 2 wasts. Com\$1.75
tains over 50 values. Complete Kit.

50 RF CHOKE COILS
All sizes for plate, grid, filament circuits, Includes popular 2.8 MH chokes. For Trans., T.V. osc., etc. \$1.45
50 MICA CONDENSERS
Over 20 values, inc. ciliver mica types.
Complete Kit.
\$1.75

25 PRECISION WIRE WOUND RESISTORS
Well known brands, Inc. over 20 values. \$1.95
VOLUME CONTROL KIT

VOLUME CONTROL KIT
15 types, ine. carbon and wire wound S.D. and shaft
types, some wivestch.
Complete Kit
50 CERAMIC CONDENSERS
Over 30 values.
CODED \$1.95

50 BY-PASS CONDENSERS
Tubular, Bakelite molded, etc. Popular values.
For all purposes, GUARANTEED \$1.75

Tubular with leads, FP types, upright mount.
All popular numbers.
\$2.25
Check this terrific buy!

Prices F.O.B. Phila.—Check or M.O., no C.O.D.'S.

20 ELECTROLYTIC CONDENSERS

Please incl. postage. Balance promptly refunded.

THE ELECTRIC SPOT
132 S. 11th St. PE S-9146 Philip. 7, Pg.

RADIO COURSES

RADIO PERIATING • CODE
RADIO SERVICING
• F.M. TELEVISION
• REFRIGERATION SERVICING
Write for Catalog T.G., and Picture
Brochare

TRADE & TECH. 229 W. 46 51, N. J. T.S.
SCHOOL



# of Advertisers

While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission is the preparation of this index.

ADVERTISERS	PAGE	ADVERTISERS	PAGE
Aaron Electronic Sales	134	Heath Company, The	24 24 22 24
Acorn Electronics Corp.	29	Henry Radio Stores	153
Alliance Manufacturing Company	19 97	Henshaw Radio Supply	
Altied Radio Corp. 9, Alvaradio Supply Co	122	Hickok Electrical Instrument (	Co., The 21
American Radio Institute	156	Hollywood Sound Institute, In	e
American Phenolic Corporation	87	Hollywood Technical Institute.	
Amperite Company, Inc	153	Hytron Radio	3rd Cover
Amplifier Corp. of America 136, 1	46, 154		
Approved Electronic Inst., Corp	154	Indiana Technical College	143
Arrow Sales, Inc.	115	Instructograph Company	151
Ashe Radio Co., Walter	01, 128	Instrument Associates	
Astatic Corporation, The	124	Insuline Corporation of America	ra 112
Audale Company	134	JFD Manufacturing Co., Inc.	,100, 118
Baltimore Technical Institute	156		
Bell Telephone Laboratoriès	90	Lafayette Radio	20
Bliss Electrical School		Lectronm, Incorporated	150
Bayce-Rache Book Co	93	Lectronic Research Labs	
Brook Electronies, Inc.	112	Leotone Radio Co	151
Browning Laboratories, Inc	100	Earlie Handle Co	
Ruffalo Radio Supply		Mallory & Co., Inc., P. R.	4th Course
Burstein-Applebee Co	02, 140	MacMillan Co., The	84
C & W Salar Co	150	Maspeth Telephone & Radio Co	rperation 150
Cardian System 0	150	Mass. Radio School	156
C & H Sales Co. Candler System Cannon Electric Development Co	98	Merit Transformer Corp	
Capitol Radio Engineering Institute	23, 155	Midwest Radio & Television Co	arp 21
Centralab, Division of Globe-Union, Inc.		Milwaukee School of Engineer	ring109
Certified Television Laboratories !		Murray Hill Books, Inc	26, 27
Chelsea Television Center, Inc	117		
Chicago Industrial Instrument Co	124	McGee Radio Company	
Cinex, Inc	92	McGraw-Hill Book Co	146
Circle-X Antenna Corp	I16		
Cleveland Institute of Radio Electroni	cs., S	National Radio Institute	3
Columbia Distributors, Inc.	147	National Schools	11
Columbia Electronic Sales	101	Newark Surplus Materials Co. Newcomb Audio Products Co.	0.1
Comet Electronic Sales Co	113	Nineara Radio Supply Corn.	80 123
Commonwealth Sales Co.	1.00	Ningara Radio Supply Corp Northwestern Vocational Inst.	136
Communications Equipment Company	122	Action of the Action of the Print,	
Coyne Electrical, Radio & Television School Crown Controls Co., Inc.	79, 150	Ouk Ridge Antennas	
Crown Controls Co., Inc	1.58	Offenbach & Reimus Co	
		Ohmite Manufacturing Co	
DeForest's Training, Inc	7	Onan & Sons, Inc., D. W	
Dow Trading Co	138	Opad-Green Company	
		Owl Radio Tube Company	
Eastern Telephone Co	146		
Editors and Engineers, Limited 92,	105, 156	Peak Electronics Co.	
Edlie Electronics, Inc	144	Penn Boiler and Burner Mfg.	Corp 155
Electric Spot, The	160	Phoenix Electronics, Inc	153
Electro Products Laboratories, Inc.	96	Photocon Sales	L35
Electro-Technical Industries	88	Plastics & Electronics Compa	my 80
Electron Age Co	161	Platt Electronics Corp.	1139
Electronic Indicator Corp.	140	Poly-Tech Precision Electronics, Inc	
Electronic Instrument Co., Inc	86	Premier Radio Tube Company	130
Electronics Institute, Inc	108	Progressive Electronics Co.	542.5
Emmoos Radio Supply	146	Pyramid Electric Company	99
Espey Manufacturing Company, Inc.	145	agricultural annihilation of the state of th	
		Quad Electrical Supply, Inc.	
Fair Radio Sales	137	RCA Institutes, Inc.	-
Federated Purchaser Incorporated	108	R & M Radio Company	174
Fetler Engineering Co	141, 157	Escon Electric Co., Inc.	126
Fisher & Son, M	E-635	Radio Corporation of America	
Franklin-Ellis Co.	159	Radio Corporation of America Radio Craftsmen Incorporate	7, 91, 2nd Cover
G. L. Electronics	125	Radio Ham Shack Inc	F10
General Electric Company	. 14. 69	Radio Supply & Engineering (	a. Inc. 120
General Electronic Distributing Co.	102	Radionic Equipment Corporat	ion 100
General Test Equipment	1.19	Rauland Corporation, The	14
Goodheart, R. E.	157	Baytheon Manufacturing Con	npany 96
Gould Green	92	Rider, John F., Publisher, In	ie 113
Gould Green Greenlee Tool Co.	90		
Greenwich Sales Co.		Sams & Co., Inc., Howard W.	
Greylock Electronics Supply Co	147	Sansama Electric Company	9.5
		Schott Co., Walter L	
Hallderson Company	156	Schatt Co., Walter L. Scott, Inc. Senca Radio, Inc.	
Hallderson Company Hallierafters Co., Inc.	30	Senco Radio, Inc.	
Harvey Radio Company, Inc	112	Simpson Manufacturing Co.,	Inc., Mark 120

ADVERTISERS	PAGE
Sonotone Sovereign Television Co., Inc. Spellman Television Co., Inc. Spellman Television Co., Inc. Spellman Television Co., Inc. Spraxue Products Company Sprayberry Academy of Kadio Stahi, Inc., Michael Standard Coll & Transformer Standard Transformer Standard Transformer Corporation Standard Transformer Surface Company Surfac	128 90 16, 154 19 102 6 129 80 128 143 86 135
TAR Tech-Master Products Co. Televe Televes Terminal Radio Corporation Transvision, Inc. Tri-State College Turner Company, The	90, 120 101 134 146 150
University Loudspeakers Inc.	70
V & H Radio & Electronics Supply Valparaiso Technical Institute	159
Weller Manufacturing Company Wells Sales, Inc. Wholesale Radio Parts Co., Inc. Workshop Associates, Inc., The World Radio Laboratories	157
VMCA Trade & Tech. School	160
Ziff-Davis Publishing Company	87, 130

# PHOTO CREDITS 40 55 144

#### ERRATA

In the article "Unity Returns to Ham Radio" appearing on page 55 of the December 1943 issue, the figures on the results of the 50.0 mc. poil should show that the vote was 65% adjust the assignment of exclusive c.w. trequencies in the 50.050.1 mc. portion of the best . . .

bond.

There are several corrections which must be made in the article "A Hern-Type Trensducer of Minimur, assistant by 1. Doby and G. Augspurger. Ir., appearing in the November issue, according to the authors.

On longe 55, the dimensions of Fig. A.1 should be 17" x 81", x 24" instead of 16" x 3" x 20". For Fig. E.5, chance 2315" to 24" and 1414, "to 17" taken at midpoint. In Fig. 13 change 2315" to 24". On Fig. G.5 change 12" to 13" and 3" to 38". On Fig. G.5 change 12" to 13" and 3" to 38". On Fig. G.5 change 12" to 13" and 13" to 38". Change 37" to 25".

The location of the relief ports as well as their design is optional. Locating them on Fig. G.8 conceals them from the front of the unit.

Fig. H-7 should not be laid out until the re-mainder of the cabinet is constructed and then its dimensions should be made by actual measurement from the individual transducer

Mr. George Augspurger, Jr., has kindly con-ented to answer readers' questions if they re-addressed to him at 4618 North 6th Street hoenix, Arizona.



"Always at the television set, he's such a baseball fan. Turn the volume up. dear, so we can find out what the score is!"

# 1950 PROGRESSIVE RADIO "EDU-KIT"

ABSOLUTELY NO KNOWLEDGE OF RADIO NECESSARY. YOU NEED NO ADDITIONAL PARTS. EXCELLENT FOR BACKGROUND IN TELEVISION. BUILD 15 RADIOS. . . .

The PROGRESSIVE RADIO "EDU-KIT" will help you, if you want an EDU-CATIONAL AND INTERESTING HOBBY, or if you want to get into a WELL-PAYING BUSINESS, or if you want to INCREASE YOUR KNOWLEDGE OF RADIO.

Absolutely no knowledge of radio is necessary. The PROGRESSIVE RADIO EDU-KIT" is the product of many years of teaching and engineering experience. "EDU-KIT" is the product of many years of teaching and engineering experience.

The detailed instructions and quizzes are clearly written and illustrated, so that they can be understood by anyone between the ages of 12 and 5.

can be understood by anyone between the ages of 12 and 80.

The PROGRESSIVE RADIO "EDU-KIT" is not merely a collection of radio parts accompanied by a radio diagram. IT Is PRACTICALLY A RADIO COURSE, offered at a mere fraction of its real value. You will be taught to build radios in a progressive manner. First, you will, build a very simple 1-tube receiver. The next sit is a little more advanced. Gradually you will find yourself constructing elaborate radio sets, and doing work like a professional radio technician. Every part is illustrated. EVERY STEP INVOLVED IN BUILDING THESE SETS HAS BEEN CARE-FULLY PLANNED, YOU CANNOT MAKE A MISTAKE.

Each of the 15 radios you will build operates on 110-120 volts, AC or DC. These sets have been designed to teach you the PRINCIPLES OF RADIO. Therefore, you will build a variety of circuits. The PROGRESSIVE RADIO "EIN" KIT" is EXCELLENT FOR LEARNING THE PRINCIPLES OF RECEIVER, TRANSMITTER, AND AMPLIFIER DESIGN, It is used in many Radio Schools and Colleges in U.S.A. and abroad. It is used by the Veterans Administration for veteran training.

Quizzes are provided as part of the PROGRESSIVE RADIO "EDU-KIT." They will be corrected by our staff at no extra cost

FREE 1950 EXTRAS:

. . . . . . . . . . Electrical and Radio Tester Electrical Soldering Iron Screwdriver Book on Television Generous Hank of Wire Alignment Tool Spool of Rosin Core Solder Membership in Radio-TV Club

ORDER YOUR PROGRESSIVE RADIO "EDU-KIT" TODAY, OR SEND FOR FREE "KIT-KATALOG," POSTAGE PREPAID ON CASH ORDERS. COD ORDERS ACCEPTED IN U.S.A.

PROGRESSIVE ELECTRONICS CO. 497 Union Ave., Dept. RN-30
Brooklyn 11. N. Y. Brooklyn 11, N. Y.



# BUY AT'S A

HiPower Variable Antenna Network -I KW HF RF

TOU TIMES THE \$7.98 SNOOPERSCOPE INFRARED

complete data & Tute. "Talt" HPECIAL \$7.00 2 for \$14.50 Write for quantity prices Volt CARTER "MAGMOTORS"

UNBURPASSED BARGAIN: Perm Magnet. Extremely Hi-Eff. Abgaldagaging Low-Temp Fransmitting Magmoter 130 5 3 vde Outpl. 434 58.98

Receiving Magmater Outpt: 250V/150Ma. \$4.98 UHF ANTENNA

onto Ditario New 34-on First 100 Ft 250 for above 28-ANT AN 1318 Spring Switzeled West ANT AN 131A, 11 ft. Compr. Spring 8 ANT ANISIA 11 ft. Compr. Spring. And ANISIA 11 ft. Compr. Spring. Spri

TELEVISION PWR SUPPLY XFORMER

City WDGS ON DE ST.98 1800 VOLT SCOPE POWER SUPPLY KIT et akV ins Sigt Sper, Hermald, tubes & Ald, Flir Parts & \$5.98

**RCA Univ Output Xformer** LOW a Ideal Lary Q-CW or Phone Get ONL You Want to Hear \$1.39

Dyn Mike & Xfmr Special! \$1.49

VARIABLE CONDENSERS LSOMMER ROOM CORP.
BY MILLEN OF CARDWELL \$1.00 DEAL ISMMER ROOM VOIL 179c CAP RE \$1.49 CAP RE \$1.49 COUNSON TOHOU 74 ET 12MMF DOUGT T ET IZMME W into Split Stator, ND MCISS Sommel LIST es. 79c; 3 for \$2.00 Tank & Christ . 696; 2 for \$1.00

POWER PACK KITS 250V DC / 60 Ma & Filter 350V DC / 125 Ma & Filtan a 550V DC / 200 Ma & Filtan a 1260V DC / 300 Ma & Filtan a 1500 V Dtfr / 25 Ma & Filtr 9.98 21.95 UNCONDITIONALLY GUARANTEED

Each Tube INDIVIDUALLY TESTED—BRAND NEW!

Standard RMA Guarantee

Smaller Quantities, 39c Each 65NTGT 6T8 6X4 6X5 7C4 1203A 12A6 12AL6 12AT7 12AU6 12AU7 1U4 1U5 3A4 3G4 3S4 3V4 5Y3GT 53 117Z3 9001

TUBES AT GIVE-AWAY PRICES! \$.49 1629 .27 9002 .42 9003 .18 9004 .28 9006 .37 Min. .35 R'Ex

SOCKETS FOR Slide Rule CRYSTAL HOLDERS for \$4.8 to spacing.

for \$4.8 to spacing.

10c 12 \$1.00

Hisrey Dun Xtal holder

\$7247 | 10c 12 \$1.00 C. HF Xtsi Holder 12 apa 986; 6 for \$5.00 D. Johnson Myrales if pin HENDIX & 45c. PARALLEL RULES BUILD A BANTAM

CIRCIII AR

SOUND POWERED

ead and Chest Set Wif Plup Adjustable Units. Touted Land Fac found Each \$5.49, Pair \$9.98. Hitable NEW RCA UNITS. Jack \$7.98, Pair \$13.98. Actionatic E. Sozial per & Lock \$3.98, Pair \$16.98. MERCURY THERMO

REGULATOR 980

PROFESSIONAL SHARPENING STONE

Hayden Clock Meter Sync Stollwas Sincys SYNC 1rpm /116 \$2.49

RF CHOKES

4.98 Silve SOA (Similar 4MH H. Hoch Library 250.8 No. 1 S. C. 1 S.

Aur

I G N A L GENERAT \$13.94 CONTROL UNIT RM29A D NEW \$8.49

I-WATT XMITTER

4-Year FLASHER

FUSES-HOLDERS

### FUSE S — HOLDERS

### SAGE No. 16 100 for \$1.76

### SAGE No. 16 100 for \$1.76

### SAGE No. 16 10 for \$1.76

### SAGE NO.

FREQ. METER, WAVE METER

dispensable for ar orbeat, son Bulb Flashes Brilliantly Dark, Four Yr Life, Na stricing, Including \$1.96 stery.

& CONTROL UNIT

\$19.95

BUY

**VIBRAPACKS** Ovis. 425V 110ma Out. \$10.96 Pr. 157 Park & Hat ther & Spike will 503. 58.95 (2Vist light 190V 85ms Unity) \$3.49 DYNAMOTORS Voit times 1.N \$2.50 220V 100ms & 440V/ Same Above NEW w nitre &

BOXES, CABINETS

USN Spare Parts Box, 514"

Hx10"Lx1412"W N1 e e 1/
Grey NEW \$1.39

MOTOR-115V/60CYC GE - Delen - Diehl W Codst ContDity Se shaft \$3.49

GIBSON GIRL GIRL COMPONENTS Signal Lampenia, 89c; Waterproof Haversack; St. Oktober 12 feet 81.98 BUZZER TYPE

FOGHORN \$1,49

External Pwr Sup. Cord CD277 & Plug PL114. Fite Skt NO 4 Revr BC312 314.342, 344 BRAND NEW \$1.49 O'Reas Pkgd. \$1.49

ALIGNMENT TOOLS

STORAGE BATTERIES re. Models. Willard Htt 18 Hets. 3-11 [0x1-7/16x29 32" 81c APECTAL 2V 11 AR Williard BRIDGEU 2V 27 MR Williard BRIGGE 3V 6AH Williard FRESE 3V 6AH Williard FRESE BRIACH W'ExpOnly) | pt. 59c; 2 pts.

HOOKUP WIRE SPECIALS!!

HEADSETS

\$13.75

\$29.75 OIL CONDENSERS

Lowest Prices Everl mid. 4 for \$1 mid. 3 for \$

SENSATIONAL AC/DC 2-SPEED PHONO-AMPLIFIER COMBINATIONS \$12.49

Write for Your FREE


TATOGRAM

33 Min. Order,
F.O.B. N.Y.C.

Add. Shpg. Charges
and 25° Deposit
PHONE: WOrth 2-7230

DEPT. 2RN SIX CHURCH ST. NEW YORK 6, N.Y., U.S.A. - CORNER CHURCH & LIBERTY STS

# THE EYE IS QUICKER THAN THE EAR

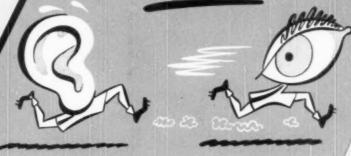

IF you service TV, you know this. Customers are quick to see imperfections. Much slower to hear them. Therefore premium-quality Hytron receiving tubes for the tougher TV jobs. At no extra cost! You gain also: Through fewer expensive service call-backs. Better customer satisfaction and confidence. More profits.

How does Hytron do it? By working closely with leading TV set manufacturers. By endless striving to better already superior performance. By improved design ... processing ... inspection ... testing.

Try Hytron TV receiving tubes: 1X2, 6AG5, 6AL5, 6AU6, 6BG6G, 6BQ6GT, 6J6, 6SN7GT, 12SN7GT, etc. You pay no more for Hytron. But see the difference yourself...on the TV screen...on your cash register.

OLDEST MANUFACTURER SPECIALIZING IN RECEIVING TUBES



RADIO MND ELECTRONICS CORP.

HYTRON SOLDERING AID



49¢ net

OUR APOLOGIES! We knew these Hytron shop tools would be popular . . .

because they are designed "by servicemen, for servicemen." But we didn't dream they would be so popular. That you needed them so badly. First production runs of both Soldering Aids and Tube Lifters melted away like snow in the red hot demand. New, more adequate production facilities had to be rushed into action. NOW YOU CAN

Sorry, II you twee one of the unlacky ones who had be wall. Your Hytren jubber should now have both Soldering Aids and Tube Lifers in stack. If he hasn't,

HYTRON TUBE LIFTER

15c m

ALSO AT YOUR HYTRON JOBBER'S ..

C net

TUBE TAPER 5C net





7-PIN MINIATURE STRAIGHTENER . . 55

P. PIN MINIATURE STRAIGHTENER SSC ...

AUTO RADIO TOOL 240



Mallory FP Capacitors are built to withstand continuous high temperatures. Tests show they perform consistently during 2000 hours of operation at a temperature of 185°F. At lower temperatures, even longer!

Proof of this performance is found in the experience of one television manufacturer, who kept records of field failures for six months. Of 385,000 Mallory FP Capacitors in service only six failed! Special design and meticulous production care make such records possible . . . by eliminating the major source of internal corrosion.

Mallory Capacitors have set new long-life standards for the industry, yet cost no more. You will find it pays to rely on the complete Mallory Capacitor line—paper—ceramics—FP Electrolytics.

See Your Distributor for Mallory Precision Quality Parts at Regular Prices



